

Nuts & Volts

Exploring Electronics And Technology For The Hobbyist And Professional

www.nutsvolts.com

September 1999 Vol. 20 No. 9

OUTFITTING YOUR "MAD" SCIENTIST'S LAIR

This Halloween is your time to cackle, throw back the curtains, and reveal wild arcs of electricity surging through your house with your very own Tesla coil!



ION PROPULSION IS A REALITY!

Build your own ion propulsion motor that works on the same basic principles as NASA's Deep Space 1 craft.

PLUS
SERVOS, STEPPERS, AND OPTICAL ENCODERS
BUILD A PHOTO-ELECTRIC COUNTER
PUT THE OPERATION BACK IN OP-AMPS


And More!

U.S. \$3.50 CANADA \$5.00

09>



0 74470 89295 3

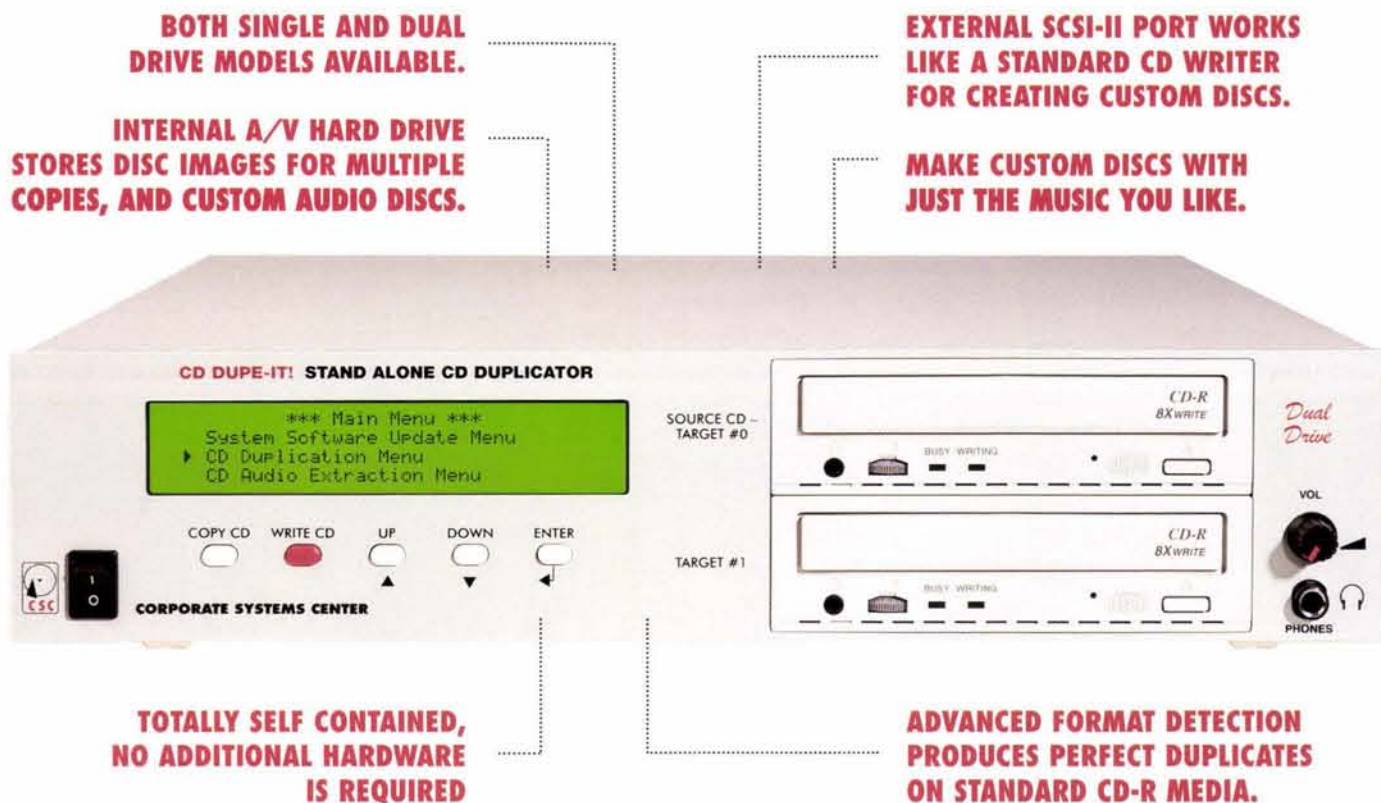

COPY ANY CD NOW. NO PC REQUIRED.

DUPE-IT!

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce compact discs quickly and economically. No mastering or multimedia experience is required.

Insert your original CD and press "start." The multimedia processor quickly copies any disc to the internal A/V hard drive. Insert blank CDs and make as many copies as you like. You'll produce perfect duplicates. The system is totally self contained — no additional hardware is required.

FROM \$595!

100 BLANK CDs \$169!
408 330-5524

Just plug in the power cord and press "start"—it's that easy.

You can even make your own custom music CD without a PC! Insert your original CD's, select the tracks you want, and Dupe-It will copy them to the internal hard drive. Built in amplified stereo speakers allow you to preview the music before recording a CD. Then insert a blank CD, and you'll have a custom music CD with just the songs you want.

With the included CD mastering software, Dupe-It will work overtime as your personal CD design system. Just attach a SCSI cable to your PC or Mac, and you're ready to design and create your own original CD's. Similar systems used in duplication houses cost over \$5,000. Now you can easily copy CDs yourself for a fraction of the price.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE, SANTA CLARA, CA 95054
WWW.DUPEIT.COM

Musicians—ask about our pro-audio CD recorders. Software publishers—ask about our high-volume multi-drive duplication systems. Dupe-It is sold and intended for backup and in-house design purposes only. Copyright laws must be observed. Dual 8x20 model is pictured above.

HSC**Electronic
Supply**Serving
Silicon Valley
since 1964!...brings you a potpourri of high-tech goodies for the techno-tinkerer!
For thirty years we have been your source for Silicon Valley exotica!**Pentium II/Celeron 440 LX
Motherboard!**

- ◆ Part Number: HOT367
- ◆ Intel 440 LX chipset
- ◆ Supports 266-400 (at 66 MHz bus) Celeron CPUs
- ◆ Supports Pentium II processors from 233-333 MHz
- ◆ Award BIOS, ATX Form Factor
- ◆ 1 AGP, 4 PCI & 3 ISA slots, 4 DIMM skts.
- ◆ Integrated EIDE/Floppy cont, 2 USB, 1 PIO, 2 SIO, 1 PS/2 mouse, and 1 PS/2 keyboard
- ◆ Supports up to 512 MB EDO OR SDRAM
- ◆ Modern Ring Power-on
- ◆ Includes CPU retention bracket, IDE cable, Floppy cable, CD-Rom driver and manual
- ◆ New in box, 90-day warranty

HSC#18016 \$47.50**Power Supply**

- ◆ "LITEON" 145W fan-cooled supply
- ◆ Perfect for bench use or motherboard test/development!
- ◆ Note: this is not standard tower-case form-factor.
- ◆ Input: 100-127VAC ~ 5A/200-240V ~ 2.5A, 50-60Hz
- ◆ Output: +5VDC/18.5A, -5VDC/0.3A, +5Vs/0.02A, +12VDC/4A, -12VDC/0.3A, +3.3VDC/7A
- ◆ Standard ATX-motherboard, disk drive power connectors
- ◆ Measures 2.75" x 4.125" x 6"
- ◆ New, 90-day warranty

**HSC#17973 \$12.50****Tiny Color CCD Camera!**

- ◆ Last batch of these popular cameras found in warehouse!
- ◆ Camera-on-a-board measures 1.87" x 1.3", 1" thick!
- ◆ Has glass micro-lens element, not pinhole lens
- ◆ DSP on board for auto white-balance, shutter
- ◆ Standard NTSC composite video output
- ◆ 350 lines horiz. resolution, good low-light sensitivity
- ◆ Uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
- ◆ New in OEM pkg. (no box), 90-day HSC warranty


**HSC#17736 \$89.95****Infrared Connections!**

- ◆ IBM "Options" series ISA-Bus and PCMCIA card adaptors will add industry standard infrared communications capability to your desktop PC (with ISA slots) or notebook computer! (Win95 instructions available on our website)
- ◆ Allows wireless connection to compatible notebooks, workstations, printers, and other peripherals supporting the Infrared Data Association (IrDA) standard.
- ◆ Also will emulate a COM port for cable-less hook-ups
- ◆ Communicates up to 115KBps, or up to 1.152MBps with the included TranXit Software.
- ◆ Operates over distances up to 3 meters (10 ft.)
- ◆ Includes Card, transceiver module, driver disk & book
- ◆ Both styles new in box, 90-day warranty

HSC#16483 PCMCIA Version \$19.95**HSC#16813 ISA-Bus Version \$19.95****Rechargeable Battery Buy!**

Three types of rechargeable battery for a variety of uses!

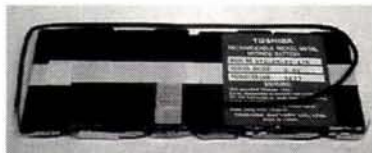Amazing power in a small package! Nickel-Metal Hydride (Ni-MH) batteries have the capacity of Nicads without the "memory" effect. These are factory-new, not pulls!



- ◆ Toshiba 8TH-F5-F1-AIR, 9.6VDC at 600 mAh, measures 4.5" x 1.875" x .25" thick (8 cells in series)
- ◆ Appears to have a thermal fuse for over-current protection

HSC#17871 \$17.50

...Or you can choose a NiCad battery pack in a similar form-factor. These are a flat array of cells, like the battery above, with handy solder tabs for connection.

- ◆ Thin NiCad pack, 8.4VDC at 450 mAh, measures 4.5 x 1.875 x .25" thick (7 cells in series)

HSC#17872 \$12.50

...Or you may need the power of a lead-acid battery. These are all new batteries with tab terminals. Perfect for hobbies, security systems, battery back-up, garden equipment, etc.

- ◆ TR1.2-12, 12VDC at 1.2 AH, measures 3.75 x 1.875 x 2"

HSC#17197 \$4.95

- ◆ TR4-6, 6VDC at 4 AH, measures 2.75 x 1.75 x 4"

HSC#17588 \$4.95

- ◆ BAT-0063 (x2), 12VDC at 10AH, 4" x 6" x 4", this is two 6-volt batteries packaged in series by Best Power

HSC#17810 \$17.50**Video-hack is back!**

- ◆ Logitech Videoman Video-conference camera & interface
- ◆ These units were sold with Hewlett Packard S-700 workstations for videoconference capability
- ◆ We have collected some data, check on our website at <http://www.halted.com/online/index.htm>
- ◆ All we have is cameras with stand, and SCSI-II interface
- ◆ The camera is on a weighted stand that extends from 13" tall to over 20" tall, and has a electret microphone
- ◆ Color camera is digital output, but some delicate SMT surgery will provide NTSC signals (not for amateurs!)
- ◆ Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic. out jack, composite video input (BNC), and the connector for the camera cable.

**HSC#17503 Now -- Lower Price! \$29.95****Laptop Carrying Cases**

- ◆ Measures 12.5" x 10" x 2" inside dim.
- ◆ Velcro-sealed outer pouch, padded shoulder strap with heavy-duty swivel hooks, zipper closure
- ◆ Handsome black vinyl "leather-grain" exterior
- ◆ Cushiony plush interior protects your laptop's case
- ◆ Quantity discounts available

**HSC#17662 \$17.50****Price Breakthrough on
Variable Transformers!**

You say you've wanted one of these in the past, but the price kept you away? Now you can afford a brand-new variable AC supply for your workbench! All have enclosed cases, knob and dial.

- ◆ Model AICVR-500W, 120 VAC input
- ◆ 0 - 120 VAC output, 500 watts
- ◆ Measures 5" dia., 6" tall
- ◆ Features meter, binding post terminals for input, output
- ◆ New in box, made in China

**HSC#80474 \$50.00**

- ◆ Model AEEC-1090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 1 KVA
- ◆ Measures 6.5" dia., 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China

**HSC#80481 \$85.00**

- ◆ Model AEEC-2090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 2 KVA
- ◆ Measures 8" x 10" x 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China

**HSC#80461 \$125.00****ISA to SCSI Adapter**


- ◆ Adaptech model AVA-1505AI -- Brand Name Quality!
- ◆ Single, complete PC connection
- ◆ For single non-bootable SCSI2 peripheral
- ◆ New, OEM pack, with install diskette & manual

**HSC#17995 \$17.50****Special! ...w/DB25 adapter & cable \$19.95****Sidewinder Slashed!**

- ◆ Microsoft "Sidewinder" game controller ... Wow!
- ◆ New OEM package, high quality for fast action!
- ◆ Download drivers from Microsoft.com
- ◆ Eight programmable action buttons, two fire buttons

**HSC#80486 \$17.50****S-3 Aurora Video!**

- ◆ 64-bit DRAM base graphic engine MPEG accelerator!
- ◆ Smooth video playback up to 30 frames per second
- ◆ Integrated 24-bit RAMDAC w/135 MHz output rate
- ◆ Glueless PCI 2.1 compliant, VESA DDC 2.0B support
- ◆ New, W3.x & W95 comp., CD install, 90-day warranty.

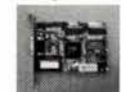**HSC#80458 \$17.50****Chiantech ATX Socket 7
Motherboard
with Intel TX Chipset!**

- ◆ Part Number: 5TTM-M201
- ◆ Original Intel TX Chipset
- ◆ General Specifications:
 - Standard ATX Form Factor - single rack
 - 512K Cache on board
 - Supports EDO/FPM DRAM, 256 MB max
 - Standard IDE I/O on board
 - 4-16 bit ISA and 4 PCI slots
 - 4-5V, 72-pin SIMM sockets, 3-3.3V 168-pin DIMM sockets
- ◆ CPU Compatibility List:
 - Intel MMX 200 to 233 MHz
 - Cyrix/IBM 6x86 (rev 2.7+), 6x86L, PR120+ to PR166+ and 6x86 MMX, PR166+ to PR200+
 - AMD-K5 PR75 to PR166 and up to 233 MHz AMD K6 CPUs
 - Supports 55/60/66/75 MHz system clock speeds
 - ZIP Socket7, 321-pin
- ◆ Comes with cables, drivers, utility CD -- 90-day warranty

HSC#18015 \$37.50**ATX-Style Mid-Tower!**


- ◆ Need a case for your motherboard?
- ◆ ATX-style mid-tower cabinet
- ◆ ATX power supply included
- ◆ Three 5.25" and two 3.5" front bays
- ◆ 16.5" H x 8.25" W x 16.5" D
- ◆ Brand new in box, 90-day warranty

**HSC# 80459 \$47.50****Noise-Cancelling Headset!**

- ◆ Andrea Electronics NC-50 headset with microphone
- ◆ Features passive Noise Cancellation technology
- ◆ Mono speaker & mic., use with your sound card, etc.
- ◆ New in bag, 90-day warranty

**HSC#17445 \$4.95****PCI-Bus 56K Modem!**

- ◆ Genica PCI-Bus 56K Modem at unheard-of price!
- ◆ Data, FAX, voice, full V.90 compatibility
- ◆ Voice from handset
- ◆ Windows 95/98 or NT only (Not Win 3.1 compatible)
- ◆ Uses latest Lucent chipset, comes with Lucent drivers
- ◆ New retail box, with expanded application software on CD
- ◆ 90-Day Warranty

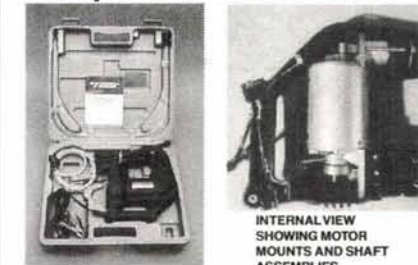**HSC#17532 \$39.95****Topside Oil Extractor!**

- ◆ **SAVE MONEY! Quit crawling under your car!**
- ◆ For autos, yachts, forklifts, tractors, textile machines, lawn mowers...any large or small engine!
- ◆ Pumps 4 liters in 3 minutes
- ◆ Model R602A, 12VDC powered!
- ◆ Air compressor option NOT included or available
- ◆ Many uses...wherever you need a small, portable pump!
- ◆ New...includes manual, hoses and molded carrying case

HSC# 17999 \$19.95**Halted
specialties co.****HSC****Electronic
Supply**

Toll Free (Orders Only) 1-800-4 HALTED

Internet World Wide Web:

3500 Ryder St., Santa Clara, CA 95051

4837 Amber Ln., Sacramento, CA 95841

5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)

<http://www.halted.com>

(408) 732-1573

(916) 338-2545

(707) 585-7344

-or-
FAX your orders to:
(408) 732-6428**Visit HSC's Website!**

- ◆ Pay us a virtual visit on the World Wide Web!
- ◆ Simply point your browser to <http://www.halted.com>
- ◆ Site is constantly being revised, please visit often!
- ◆ Or, you can email your order to hscmail@halted.com

HSC Catalog online!

- ◆ That's right, get HSC's catalog on the World-Wide Web!
- ◆ Simply go to www.halted.com and follow the big red link.
- ◆ Adobe .PDF files are available for download and viewing.
- ◆ Or drop on by and pick one up...we'd love to see you!

Terms: Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight!) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.

THE ALL NEW MULTICOUNTER

\$399



TA100S Antenna Included
U.S. Pat. No. 5,471,402

Optoelectronics presents the **NEW Multicounter** CD100 Counter / Decoder.

The **Multicounter** combines a frequency counter and tone decoder in one handheld package. As the **Multicounter** locks onto a nearby RF signal, the frequency along with either **CTCSS**, **DCS**, **LTR**, or **DTMF** is instantly shown on the two-line LCD display.

Like the popular Optoelectronics Scout, the **Multicounter** also **Reaction Tunes** many radios for instant monitoring of the frequency captured.

ORDER NOW

The **Multicounter** is so easy to operate that it is ideal for quick radio checks by a two-way radio technician or the hobbyist looking for unknown frequencies and tones.

FEATURES

- 10MHz - 1GHz Frequency Range
- Measures frequency and tone in < 1 second
- Decodes CTCSS, DCS, LTR, and DTMF
- LTR displays Area code, Go to Repeater, Home Repeater, ID, and Free repeater
- Built-in .5ppm TCXO for accurate frequency measurement
- Reaction Tune the ICOM R10, R7000, R7100, R8500, R9000, AOR AR8000, AR8200, OS456/Lite, OS535, Optoelectronics R11, and Optocom.
- Two Line LCD Display with EL backlight
- Internal memory for frequency / tone measurement
- Download memory to PC with optional Optolinx PC interface
- Patented Digital Auto Filter



Reaction Tune
Scanner Not Included

OPTODIRECT 800-327-5912

OPTOELECTRONICS

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334 • Visa • MasterCard • C.O.D. •
Prices and Specifications are subject to change without notice or obligation

Tel: 954-771-2050 Fax: 954-771-2052 Email: sales@optoelectronics.com Internet: www.optoelectronics.com

10. Ham Gear for Sale	32	120. Components	41
20. Ham Gear Wanted	0	125. Microcontrollers	42
30. CB/Scanners	32	130. Antique Electronics	42
40. Music & Accessories	0	135. Aviation Electronics	42
50. Computer Hardware	32	140. Publications	42
60. Computer Software	33	145. Robotics	42
70. Computer Equip. Wanted	34	150. Plans/Kits/Schematics	55
80. Test Equipment	34	155. Manuals/Schematics Wanted	56
85. Security	37	160. Misc. Electronics For Sale	56
90. Satellite Equipment	38	170. Misc. Electronics Wanted	56
95. Military Surplus Electronics	38	175. BBS & Online Services	0
100. Audio/Video/Laser	38	180. Education	57
110. Cable TV	39	190. Business Opportunities	57
115. Telephone/Fax	41	200. Repairs/Services	57

About the Cover

The lab on the cover is a 3D re-creation of the labs and sets used in the original 1931 version of *Frankenstein* with Boris Karloff and Lon Chaney. Of course, there are a few modern features added to this lab, and a couple hidden surprises. (Can you find the photo of the artist and the author of the Tesla coil article?) The Tesla coil seen is an exact replica of the one designed and built by Walt Noon. Matthew Roddy is a video producer and 3D artist in Southern California. For the cover, he used Imagine for Windows 2.0 (by Impulse/www.coolfun.com) and Corel Photo 8 (www.corel.com).



VOLUME 20 • NO. 9 • SEPTEMBER 1999

Published Monthly By
T & L Publications, Inc.
 430 Princland Court
 Corona, CA 92879-1300
 (909) 371-8497
 FAX (909) 371-3052

E-Mail — editor@nutsvolts.com
 URL — http://www.nutsvolts.com

Subscription
 Order ONLY Line
 1-800-783-4624

PUBLISHER
 Jack Lemieux N6ZTD

EDITOR
 Larry Lemieux KD6UWV

MANAGING EDITOR
 Robin Lemieux KD6UWS

ON-THE-ROAD EXHIBIT
 COORDINATOR
 Audrey Lemieux N6VXW

SUBSCRIPTIONS
 Abby Madain

CLASSIFIED ADS
 Natalie Sigafus

DISPLAY ADS
 Mary Gamar

Copyright 1999
 by
T & L Publications, Inc.
 All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princland Court, Corona, CA 92879.

ION PROPULSION IS A REALITY

Build your own ion propulsion motor that works on the same basic principles as NASA's Deep Space 1 craft. *David Williams*

6

PUT THE OPERATION BACK IN OP-AMPS

Almost every project today uses an op-amp to amplify analog signals. However, operational amplifiers were originally designed to perform mathematical operations in analog computers. Check out these sample circuits that can do much more than just amplify. *Richard Panosh*

23

HAMS HAPPY IN HOLDING PATTERN

Ham radio operators are getting the royal treatment from equipment manufacturers and dealers in preparation for the long-awaited amateur radio service restructuring rules. *Gordon West*

43

POWERPOINTING YOUR PROJECTS — PART 1

Learn how to use Microsoft's PowerPoint for creating a personalized "palette" of schematic symbols and a "toolkit" for creating PC board drawings. *Steve Daniels*

49

BUILD A PHOTO-ELECTRIC COUNTER

You can "count" on this construction project to give you the numbers that you need for myriad applications. *Fred Blechman*

62

SERVOS, STEPPERS, AND OPTICAL ENCODERS — PART 2

Which one works best in your robotic or R/C project? This month: bipolar stepper motors. *TJ Byers*

69

OUTFITTING YOUR "MAD" SCIENTIST'S LAIR

This Halloween is your time to cackle, throw back the curtains, and reveal wild arcs of electricity surging through your house with your very own Tesla coil! *Walt Noon*

Cover Story

87

Columns

Advertiser's Index ...	72
Classified Ad Info ...	72
Dealer Directory ...	21
Events Calendar ...	18
New Product News ...	92
News Bytes ...	16
NV AdMart ...	66-68
NV Bookstore ...	48
Prize Drawing ...	92
Reader Feedback ...	10
Tech Forum ...	28

Departments

AMATEUR ROBOTICS NOTEBOOK

Why use a multimaster I2C network? Read on ... *Robert Nansel*

78

ELECTRONICS Q & A

TJ Byers

58

OPEN CHANNEL

Dealing with instrument problems. *Joe Carr*

74

STAMP APPLICATIONS

Protecting your Stamp from the cold, cruel world through de-coupling capacitors. *Lon Glazner*

12

NUTS & VOLTS MAGAZINE IS PUBLISHED MONTHLY FOR \$19.00 PER YEAR BY T&L PUBLICATIONS, INC., 430 PRINCLAND COURT, CORONA, CA. APPLICATION TO MAIL AT PERIODICALS POSTAGE RATES IS PENDING AT CORONA, CA AND AT ADDITIONAL MAILING OFFICES. POSTMASTER: SEND ADDRESS CHANGES TO NUTS & VOLTS MAGAZINE, 430 PRINCLAND COURT, CORONA, CA 92879-1300.

ION PROPULSION IS A REALITY!

On October 24, 1998, NASA launched the spacecraft Deep Space 1 with a remarkable new ion drive. The Deep Space 1 mission was the first launch of NASA's New Millenium program. This is the first time that ion propulsion has been used as the primary means of propelling a spacecraft.

In a spacecraft, ion propulsion has advantages over conventional chemical propulsion systems. It can operate on a small amount of fuel for extended periods of time.

The limitations of ion propulsion are that it produces very low thrust and uses a lot of electricity. The engine on Deep Space 1 consumes 2,500 watts of electrical power at full throttle, but only exerts 1/50th of a pound of thrust. However, given extremely long periods of time, an ion thruster can allow a spacecraft to achieve theoretical velocities over 60,000 miles per hour.

Since NASA's ion engine works in the vacuum of space, it uses xenon gas as a fuel. Solar panels on the spacecraft generate the electricity needed to ionize the gas and to charge a grid in the engine's chamber to a 1,200 volt potential. The charged grid exerts a strong electrostatic pull on the xenon ions. The electrostatic force is powerful enough to cause the xenon ions to reach an exhaust velocity over 30 kilometers per second.

BUILD YOUR OWN ION PROPULSION MOTOR

Now you can build your own ion propulsion motor that works

on the same basic principles as NASA's Deep Space 1 craft. This project uses a high-voltage potential that generates four streams of "ion wind." The ion streams exert enough force to spin a rotor at a remarkable speed. This high-tech device makes a great science project or an interesting desktop toy. The ion motor also generates negative ions, which can reduce pollen and pollution in the air to produce a healthier environment.

The ion motor in this project doesn't need exotic gases for fuel, because it ionizes regular air. Figure 1 is a block diagram that demonstrates the motor's principles.

A wall transformer provides nine volts DC to a step-up voltage converter. The DC-to-DC converter boosts the nine volts to a negative potential of over 10KV. The output current of the converter is limited to a safe level of less than 0.5 milliamps. The high-voltage is connected to a metal pivot pin and a PC board rotor is balanced on the point of the pin. The rotor has four ion discharge points made from four bent pieces of solid wire.

During operation, the four wire tips on the rotor get charged to 10,000 volts and the strong negative potential affects the surrounding air. Any air molecules that come near the wire tips become negatively charged "ions."

Since opposite charges attract

and similar charges repel each other, the negative air molecules are repelled from the negative wire tips. As the air moves quickly away, it creates an "ion wind." It also generates a reactive force on the wire tips that causes the rotor to spin on the pivot pin.

The neutral side of the DC-to-DC converter is connected to an aluminum plate on the bottom of the ion motor's enclosure. This metal plate is at a higher voltage potential than the negatively charged air ions. Therefore, it attracts some of the ions and gives the rotor additional speed.

CONSTRUCTION

All the parts for the ion motor are shown in the Parts List. The rotor is made from a small printed

circuit board. The foil layout for the PC board is shown in Figure 2.

Begin by inserting one of the pin sockets in the center of the PC board rotor as shown in Figure 3. Solder the socket in place and then insert and solder the four jumper wires on the rotor. Trim any excess wire from the bottom side of the rotor, and then bend the four wire tips as shown in Figure 4.

Next, take the wall transformer and cut off any connector from the end of the wires. Then separate the two wires for a distance of 1 inch and strip back about 1/2 inch of the insulation from each wire. Identify the positive (+) wire and twist it together with the red wire on the high voltage power supply. Use a plastic wire nut to hold the two wires together. Take the nega-



tive (or ground) wire from the transformer and twist it together with the black wire on the high voltage power supply. Solder the two wires to the metal ring lug as shown in Figure 5.

Place the high voltage power supply on the aluminum base plate and attach it to the plate with a #4-40 screw and hex nut. Make sure to place the ring lug under the nut as shown.

Now insert the remaining pin socket in the plastic case. Turn the case over and solder the high voltage output wire to the pin socket as shown in

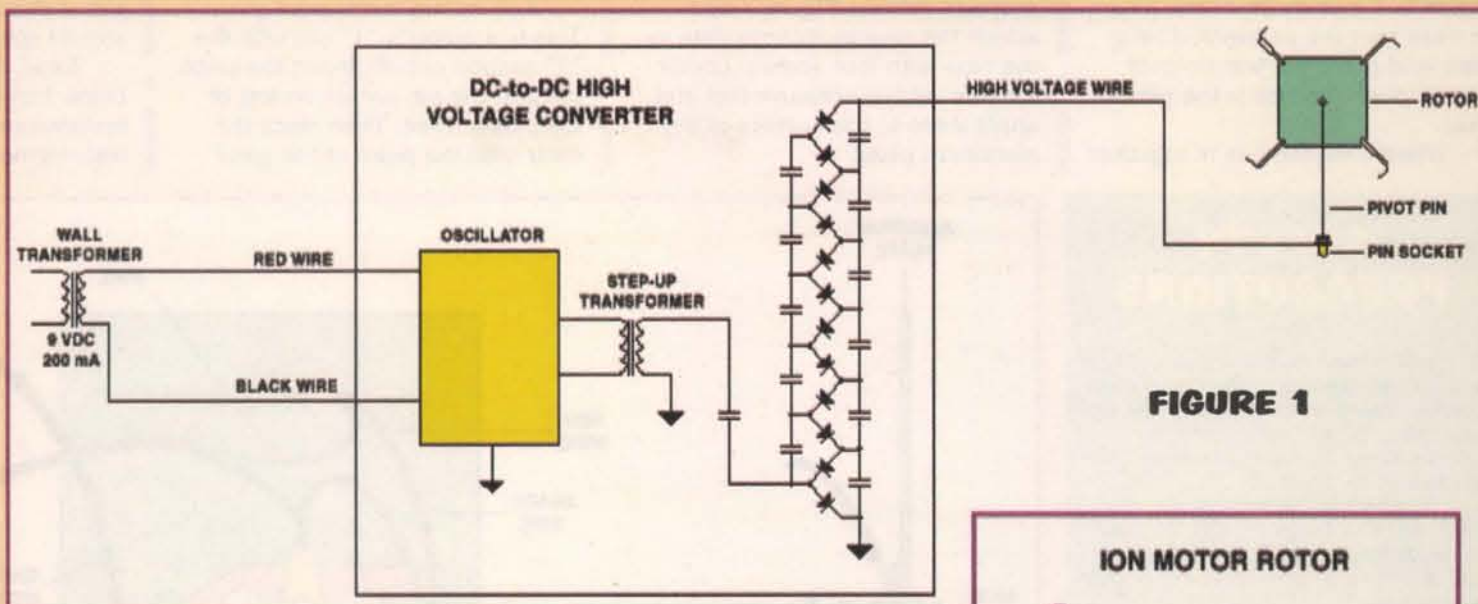


FIGURE 1



FIGURE 2
PC Board Rotor


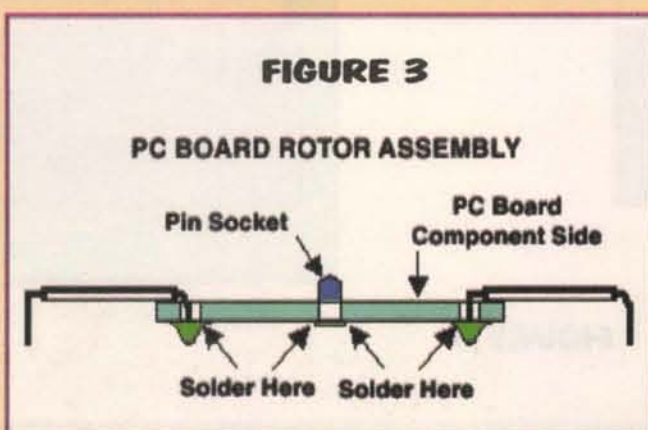


FIGURE 3

FIGURE 4

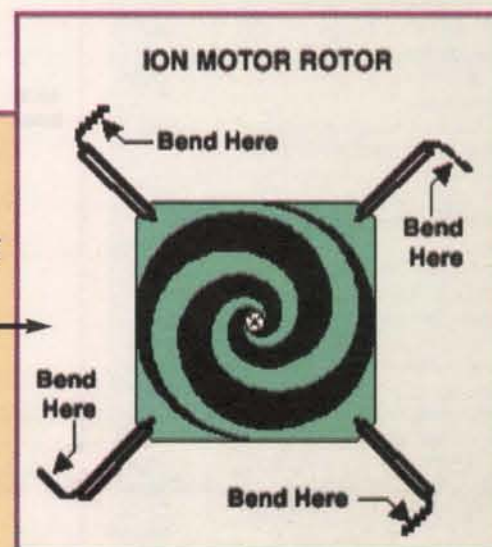

Panasonic Color Camera



MB-45cB - \$99.95
Size: 1.25" x 1.25" sq. w/ Footprint

Micro Color MB-45cB: \$99.95

- Wide Voltage Range, 5-12 Volts!
- Horizontal Res. More than 380 lines.
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

Flat Screen TFT-LCD Monitors

TFT-4 \$179.95

Color 4" Screen.
(Size: 6"(W) x 4.5"(H) x 2"(D))
An excellent 4" monitor for one camera monitoring or for setting up cameras during installation or maintenance.



Color TFT Monitors

Cameras with Built-In Infrared Illuminators.

LP-850w
Operates on 0.0 LUX in Total Darkness. Weatherproof Video Camera!

NEW MB-810B - High Powered IR-LED's. 10 X's the power!



MB-810B
• New BLC
• Multi-Mount option
• High Resolution
MB-810B \$119.95

The Door Video Camera Is Designed to replace a Standard Front Door Peep Hole!


- For Home or Office.
- Shipping/Receiving.
- Employee Entrance.
- Viewing without Moving.



INCLUDES 60 Feet of Cable!

DV-810 \$199.95

Micro Video Specialist

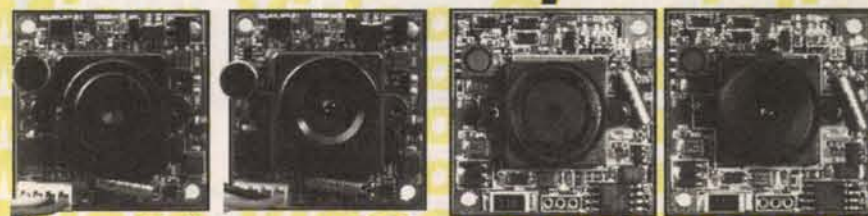

MB-650PA - \$Call 2.8mm Pinhole Lens.
MB-650UA - \$Call 4.3mm Micro. Lens.
MB-750P - \$Call 2.8mm Pinhole Lens.
MB-750U - \$Call 4.3mm Micro. Lens.

MB-650a Series
• Built-In Audio
• 1.18" sq.
• 380 TV Line

MB-750 Series
• 1.25" sq.
• 420 TV Line

Call and Compare! We Match or Beat All Prices!

WIRELESS TRANSMITTER MODULES

Makes any Camera Wireless. When wires are impossible to run, our wireless transmitters & receivers are lightweight and excellent for Hobbyist or Remote Control-Airplanes, Boats & Helicopters enthusiast. Small enough to place anywhere. Can operate off of 12VDC or Battery power supply.

MPX-900HP
900 Mhz High Power \$Call
MPX-900
900 Mhz \$119.95
MPX-1200
1.2 GHz \$149.95
MPX-1300
1.3 GHz \$149.95
MPX-2400
2.4 GHz \$119.95
All complete with FM Module 4 Channel Transmitter with Audio/Video cables, Power Switch/LED and Antenna.

Antenna's Included!

GW-2400S - \$449.95
Includes: 2.4 Ghz Color Wireless Camera. Receiver with Built-In Monitor.

"Portable" Color Wireless System



GC-2400 \$229.95
(Camera)

GM-2400 \$269.95
(Monitor/Receiver)

Polaris Industries
<http://www.polarisusa.com> **1-800-752-3571**

470 Armour Drive NE • Atlanta GA 30342-3943 • Tech Info 404.872.0722 • FAX 4-4.872.1038



FREE
Polaris Products Catalog

100's of Video Products

Figure 6. Carefully place the plastic case over the assembled baseplate and guide the transformer wire through the slot in the plastic case.

When everything is fit together

properly, refer to Figure 7 and attach the aluminum baseplate to the case with four screws. Locate the four rubber adhesive feet and apply them to the corners of the aluminum plate.

Locate the metal pivot pin. This is a quilter's "T" pin with the "T" section cut off. Insert the pivot pin into the pin socket on top of the plastic case. Then place the rotor onto the point of the pivot

pin. It should be balanced and should spin freely.

Read the safety precautions below before you plug in the wall transformer. As soon as the wall transformer is plugged into a wall

SAFETY PRECAUTIONS


This project contains high-voltages and a sharp pivot pin. The current has been limited to a safe level, but the unit can deliver small "static electricity" shocks. Keep the Ion Motor away from children at all times.

Never leave the point of the pivot pin exposed. Always remove the pivot pin from the pin socket whenever the unit is not in use or whenever the rotor is removed.

Do not touch any metal surfaces on the ion motor while power is on. The Ion Motor can generate "static electricity" sparks, so do not operate the unit near combustible materials or gases.

Do not run the Ion Motor near electronic equipment including computers. The Ion Motor can cause an electrical charge build-up inside nearby equipment that could damage electronic circuits. Do not use any electronic equipment to make measurements on the Ion Motor.

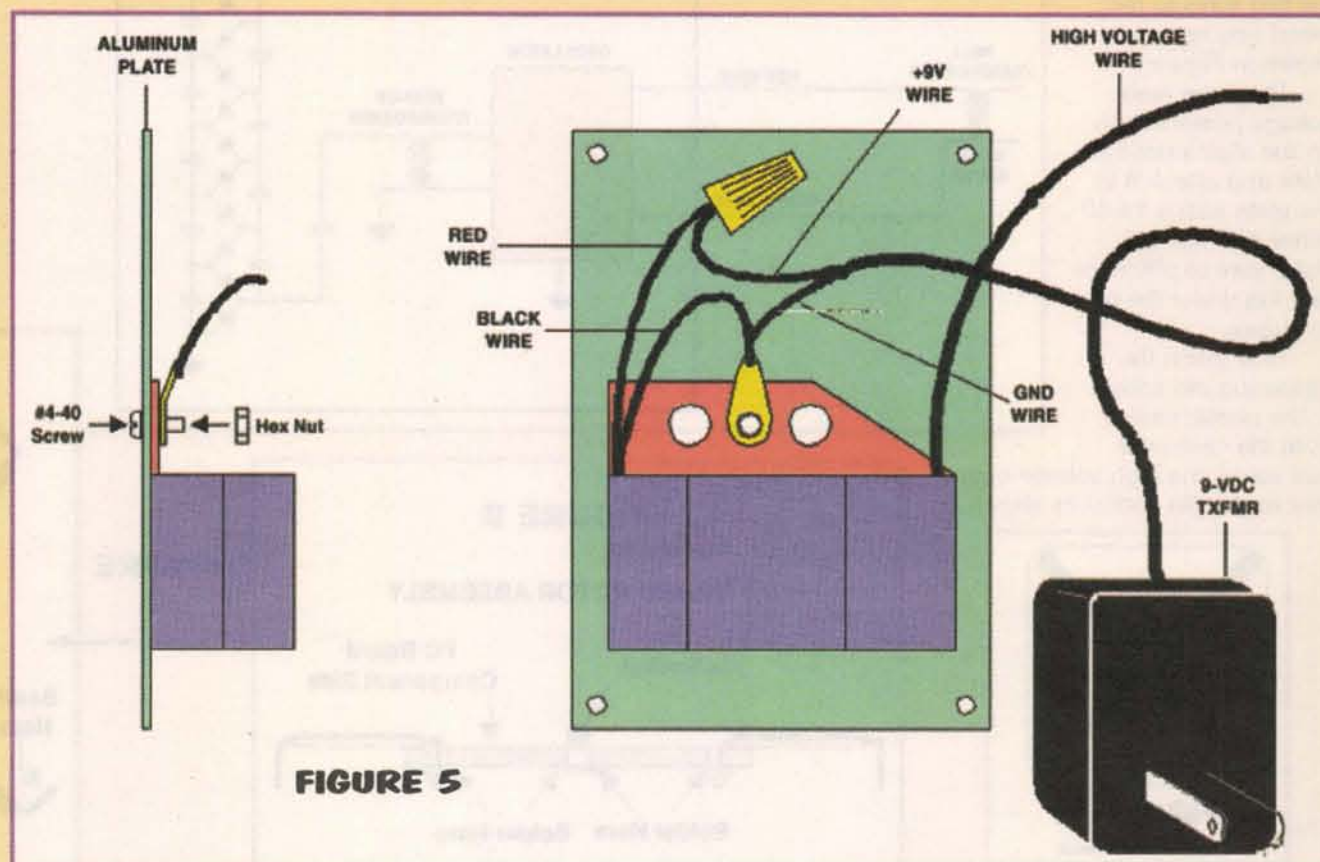Never use the Ion Motor to charge a capacitor or Leyden jar. Fatal voltage and current levels can result.



We accept Visa,
Mastercard, AmEx,
and Discover

Attention: Gearheads

www.shrevesystems.com

To Order Call 1-800-227-3971

Fax: 318-424-9771



PowerMac 7200
75 Mhz PPC 601
4 168 pin DIMM slots
Build your own Mac!
\$79 Brand New!



Peltier Junction
with heat sink
1 3/16" x 1 3/16"
\$10 each or 3 for \$25



Texas Instruments
Color Composite
Display
Great for Surveillance
Refurbished \$99



Apple IIE Logic Board
\$19



LC Power Supply
+5V, -5V, +12V Output
\$5 New

Global Village Bronze

External Modem
2400 Bps/9600 Fax
\$1 Each



CMS Tower SCSI Case

Holds 4 5.25 full height drives
\$99



Logic Boards

Q610 Logic **\$79**
Q660 Av Logic
Q650 Logic
Q800 Logic
Q840 Logic
Q900 Logic
No Processor



MacAllly ADB Keyboard
\$19



PDA Genuine
Leather Carry
Case
Let your palm
pilot lead the life
of luxury!
\$10

Power Supplies

Apple IIE \$59
Apple IIGS \$69
Mac IICX, Ci \$99
Mac II, X, FX \$49
Mac IISI \$49
Q610, 660AV, 6100 \$149

Newton 130

Without Lid **\$179**
Newton Carry Bags \$19
Newton Fax Modems \$19
16 MB Flash Cards \$79
20 MB Flash Cards \$99
24 MB Flash Cards \$129

RAM

1 MB 30 Pin 4 For \$1
4 MB 72 Pin 2 For \$5



Claris Works
3.0 For
PC/Mac
EDOCs **\$29**

Miscellaneous

Apple 8 bit Video Card \$19
LaserWriter IINT \$199
Apple ADB Keyboard \$19
1.44 Super Drive \$49
Clone ADB Mouse \$19
Quicktake 100 Camera \$129
Bernoulli 90 MB EXT \$10




Membrane
Track Pad for
laptop **\$2**

\$25 minimum
order

Shreve Systems
1200 Marshall St
Shreveport, La 71101

Returns subject to a 15% restocking fee.
Prices are subject to change without notice. We accept Visa,
Mastercard, AmEx, Discover

FIGURE 6

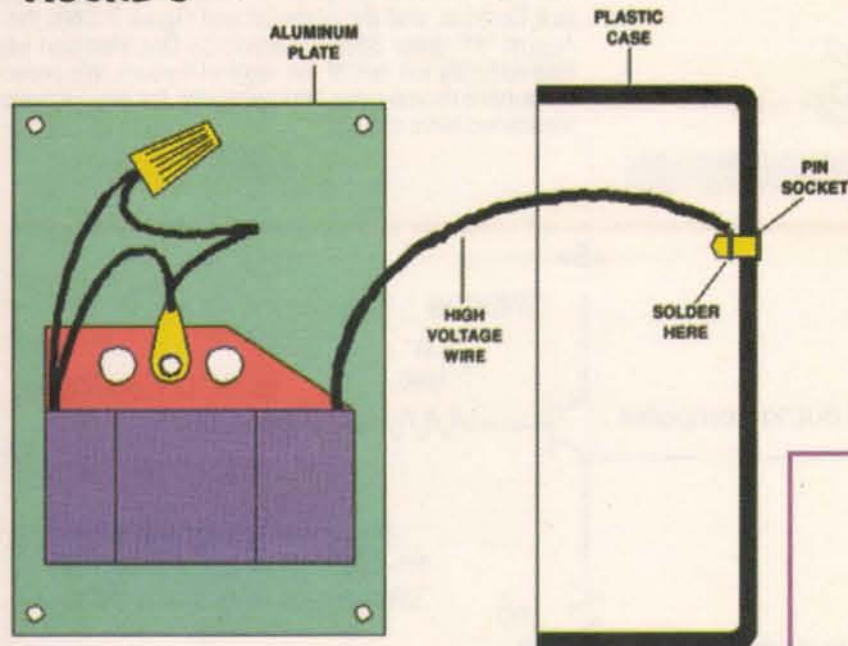

outlet, the rotor should begin to turn and then gradually pick-up speed.


You can leave the Ion Motor running continuously, and it will add negative ions to the room. There have been many studies of the effect of negative ions on people. The results indicate several positive effects including: mood enhancement, reduced airborne contaminants, and improved physical performance. The FDA limits health claims on negative ion generators, but you can experiment and determine the benefits for yourself.

ADDITIONAL EXPERIMENTS

It was mentioned earlier that the aluminum plate on the bottom of the enclosure attracts the ions and increases the speed of the rotor.

You can investigate this phenomenon further by getting another metal panel and connecting a wire from it to the aluminum plate on the bottom of the ion motor. Place the new movable metal panel near the rotor and watch the rotor speed increase. Be careful to not get the metal so close to the rotor that sparks occur.

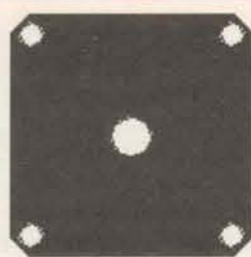How does this work? Well, the attractive force between two different voltage potentials varies inversely as the square of the distance between them. This means



SOLDER MASK SCALE 1:1

the forces are much stronger as the surfaces get closer together. In fact, that is why you get a spark if the plate is too close to the rotor. With 10KV and a small gap, the attraction is so incredibly strong that the air ionizes to a plasma and the voltage jumps across the plasma in the gap.

Refer to Figure 8 for other ways the unit can be used for high voltage experiments. A neon bulb will glow when one leg is grounded and the other leg is brought near the pivot pin. A fluorescent bulb will generate an even more interesting glow in a similar configuration. In both cases, you are seeing the ionization of the gases in the tubes.

Note that using neon or fluorescent bulbs for high voltage experiments may leave the bulbs unusable. - NV

FIGURE 7


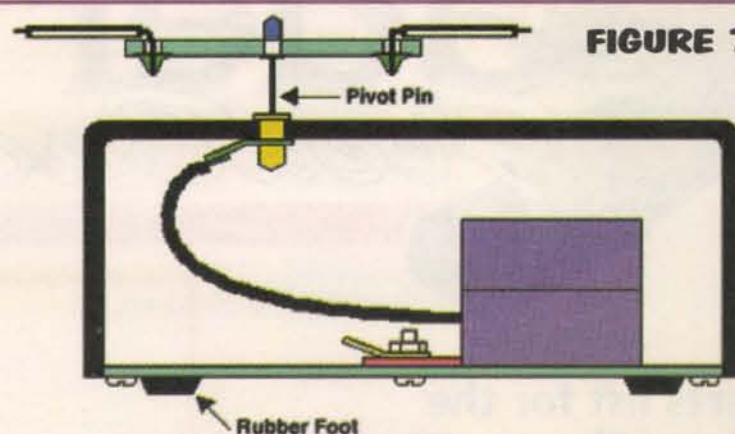


FIGURE 8

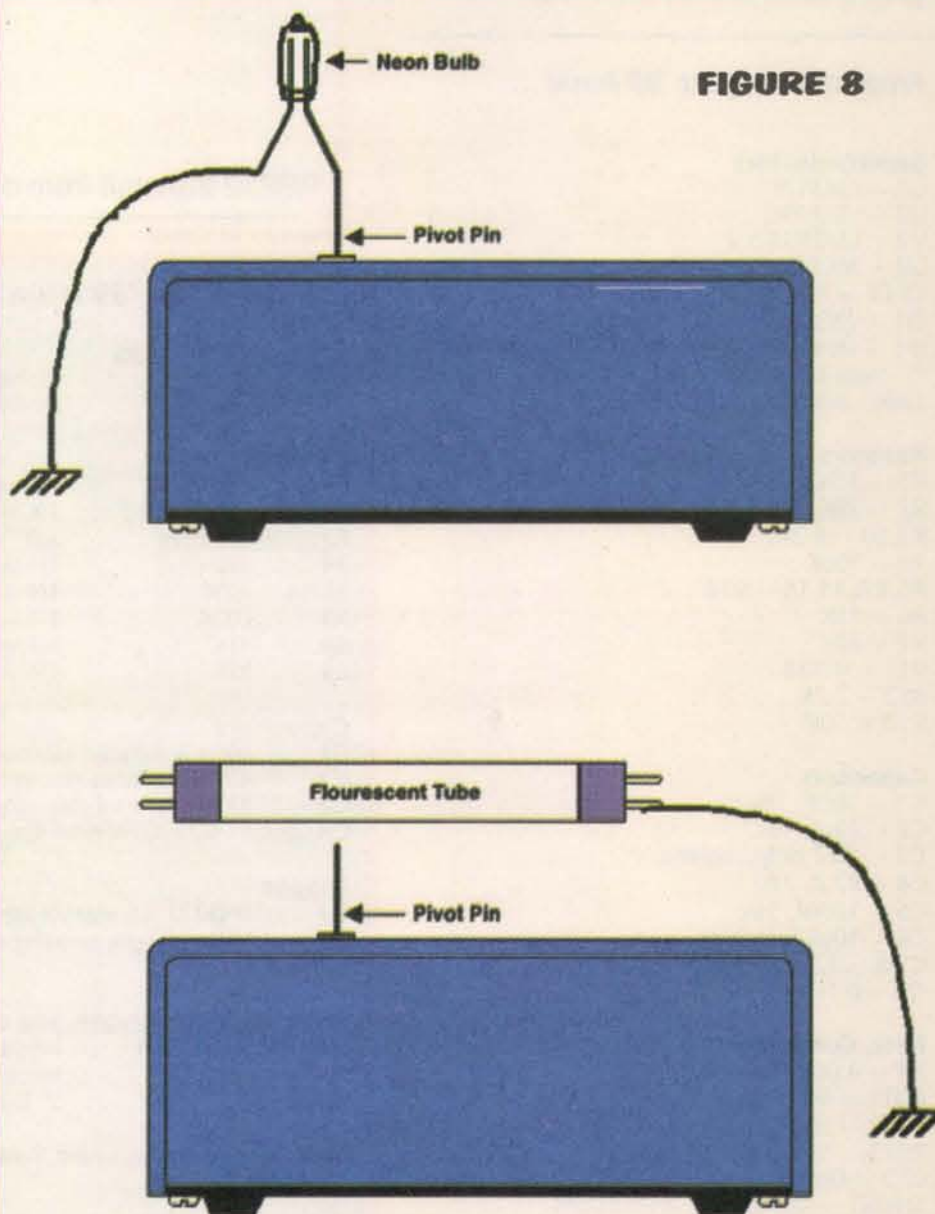

PARTS LIST FOR THE ION MOTOR

TXFMR Nine-volt DC, 200mA Wall Transformer.
PS 10KV DC Step-up Power Supply.
ENCL Phenolic Plastic Enclosure.
PCB PC Board for Rotor (ION0399).
JP1-4 Solid Wire Jumpers (four each).
SOK1-2 Metal Pin Sockets (two each).
PIVOTPIN Quilter's "T" Pin used as Rotor Pivot.
BASEPANEL Aluminum Panel Enclosure Bottom.
FEET Adhesive Rubber Feet (four each).

MISC. PARTS

- #4 Screws (5 each) - #4 Nut - Wire Nut - Metal Solder Tab

The following items are available from:

LNS Technologies, P.O. Box 67243, Scotts Valley, CA 95067;
Phone: 831-768-9155; www.techkits.com

ION MOTOR-KIT: Complete kit of parts for the Ion Motor including printed circuit board rotor, drilled plastic case, high-voltage power supply, transformer, and all other components listed above \$29.00. Please add \$5.00 shipping/handling. California residents add 8% sales tax. MC/VISA orders accepted. No COD orders.

reader FeedBack

Ooops!!

The parts list from the July '99 *Voice Changer* article by Jack Dennon, and the parts list and Figure 7 from the August '99 *Watts Showing* article by Dan Harrison were inadvertently left out of the original layouts. We present them here to you now, and apologize for any inconvenience we have caused.

Parts list for the Watts Showing™ printed circuit board

From the August '99 issue ...

Semiconductors

U1 — LM317L
U2 — LM393N
U3 — LM2931-5.0
U4 — MC68HC705P6 *
OPT1 — PS2501 (PANASONIC)
Q1 — 2N3906
D1 — 1N4148

* - must be programmed with dwm.s19 code - available from web site

Resistors

R1 — 3.9K
R2 — 39K
R3,10 — 8.2M
R4 — 100K
R5,8,9,14,15 — 91K
R6 — 15K
R7 — 30K
R11 — 470Ω
R12 — 2.2K
R13 — 10K

Capacitors

C1 — 10UF, 16v
C2 — 22uf, 16v
C3 — .022 polypropylene
C4 — 22uf, 16v
C5 — 100uf, 16v
C6 — 10uf Tantalum
C7,8 — 22pf ceramic
C9 — 0.1uf

Misc. Components

X1 — 4.00MHz crystal
POT1 — 500ohm
POT2 — 500k ohm
POT3 — 10k ohm
LCD — Optrex
SHUNT — see text for instructions

Other Parts

16ga, three-wire extension cord
Enclosure
Strain reliefs (2)
6-9vdc wall transformer
SPST power switch
Wire nut for 16ga wire

Kit of all PCB mounted parts, PCB, LCD, and enclosure with LCD cut-out is available from **Harrison R&D** for \$79.00 + \$5.00 S&H. Does not include extension cord or wall transformer. PC board and programmed U4 is available for \$25.00 plus \$3.50 S&H. Phone 281-485-7107 or write to 9802 Sagequeen Dr., Houston, TX 77089.

www.ghg.net/dharrison

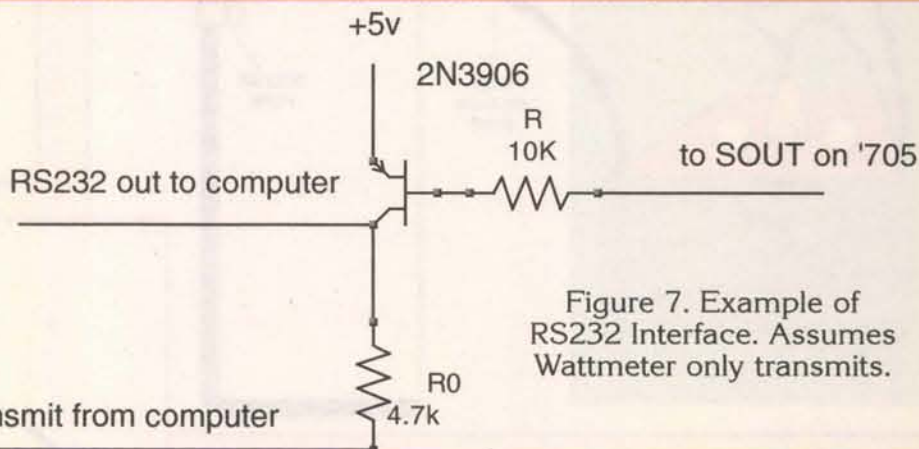


Figure 7. Example of RS232 Interface. Assumes Wattmeter only transmits.

From the July '99 issue ...

Integrated Circuits

U1	HT8950A	Holtek voice modulator	Digi-Key HT-8950A-ND
U2	LM386	Audio power amp	Digi-Key LM386N-I-ND

Resistors

R1,R10	1K	1/4 watt resistor	Mouser 29SJ250-1K
R2	330 ohm	1/4 watt resistor	29SJ250-330
R3	500 ohm	3/8" sq. trimpot	569-72P-500
R4	470 ohm	1/4 watt resistor	29SJ250-470
R5,R6	4.7K	1/4 watt resistors	29SJ250-4.7K
R7	100K	1/4 watt resistor	29SJ250-100K
R8	47K	1/4 watt resistor	29SJ250-47K
R9	33K	1/4 watt resistor	29SJ250-39K

Capacitors

C1	100 microFarad electrolytic	Mouser 140-XRL25V100
C2	4.7 microFarad electrolytic	140-XRL25V4.7
C3	22 microFarad electrolytic	140-XRL25V22
C4,C5,C6	0.1 microFarad film cap	Digi-Key P4525-ND

Diodes

D1	1N5227 3.6 volt Zener	Mouser 583-1N5227B
D2	LED red light emitting diode	604-L53HD

Switches, microphone, and speaker

Sw1, Sw2, Sw3, Sw4	keypad switches	Mouser 101-0461
MIC	electret microphone	Digi-Key P9970-ND
SPKR	2" 8-ohm speaker	Jameco 135589

Misc: Printed circuit board, 9-volt battery clip, power switch, hookup wire, solder, suitable enclosure.

Kit

A kit consisting of the printed circuit board and board-mounted components is available for \$9.95 plus \$3.00 for shipping and handling, from:

MicroMethods

P.O. Box 909, Warrenton, OR 97146.
(503) 861-1765 voice/fax.

We can accept check, money-order, Visa, or Mastercard. No CODs. Charge card orders do have to be submitted via fax; signature is required.

Add \$5.00 for shipping outside the U.S. The kit is easy to build but unless you have some experience assembling circuit boards you may want

someone else do the assembly as we cannot accept returns once you start soldering. The etched and drilled printed circuit board is available for \$6.50 postpaid to U.S. addresses.

The HT8950A is available from:

Digi-Key - (800) 344-4539; (218) 681-3380 fax
<http://www.digikey.com>

Digi-Key part number: HT-8950A-ND Voice modulator IC 16-Dip \$3.14 @ 1 ea., but of course they do have a minimum order.

The other parts are available from either Mouser or Jameco:

Mouser Electronics - (800) 346-6873
Jameco Electronics - (800) 831-4242

Parts List

Voice Changer

Reader Feedback is continued on page 68

Very Affordable NEW FLAVORS

Netcom #1 in Customer Service Since 1983

IBM ROAD WARRIOR Professional Road Equipment

MAXIMUM ABUSE

strictly for professionals
Blazing Sunlight or Rain Storm

On the DESERT or SNOW

Instant ON - ZERO boot up time

Drop 3' to Concrete

Rain: (4"/hr Rain w/ 40 MPH Winds)

Silicone Rubberized & Diecast Case!

Ultra Shock Mounted 1GIG EIDE Hard Drive!

ESD / EMF & RF Resistant, Works from -4 to 120 Deg F & Vacuum to 15,000 ft

- > 1- PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear
 - > 16m Ram / 1m Video / 32 Bit Local Bus 486-50 Mhz & Math Co-processor, 28.8k Modem (Internet Ready)
 - > Long Lasting Hydride Battery (\$150 Value)
 - > Sound & Microphone, External Mini 3.5 Floppy
 - > 8.25" Display-64 Shade Monochrome REFLECTIVE
 - > (Optional) Touch Screen with Handwriting Recognition
- Rough Service Handle with Loops for optional Shoulder Strap
Roxanne's Voice Annotates all Windows 3.X Functions
- OPTIONS
> W95 \$89 > 12V Car cord \$29
> Touch Screen \$200 > 33k Baud PCMCIA Fax- Modem Upgrade \$35 / 56k \$89

This was a unique (one shot) purchasing opportunity
IT'S NOT OPEN STOCK

WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD
Sold till recently by IBM through their Local Area Network Div at \$4,699 & \$6,912 as shown here. (they were never discounted)

Actual Selling Price From IBM
\$6,912



Tough!

233MHz

Fully Loaded SubNotebook

2 easy payments of
Wow \$499!
0% Financing!
On Credit Cards only



Looks so nice in person, it gives you Goose Bumps

Low Price / High Performance

233mhz

3.2Gig

32m ram

56k modem

CD 24x

USB (2)

W98

- External Mini CD 8" SVGA Color Display Built-in Stereo Speakers & Mic
- External Mini Floppy Convenient Touch Pad Mouse (nice)
- Lithium Ion battery 2 USB ports IR Port All standard ports on rear
- 2 PCMCIA Ports 3.3lb Subnotebook 9.5 x 7 x 1.5 Built in palm rests
- Dark Gray One year Manufacturer Direct Warantee FREE Lifetime NetcomTech support

SOYO is a leading maker of Desktop Computer Motherboards. They brand label them for FAMOUS NAME BRAND desktop computers. Now SOYO has come up front with their own "State of the Art" Sub Notebook. Sells for more on QVC! (Home Shopping Channel)
OPTIONAL CUSTOM Carrying Case \$24 SOYO Embossed LOGO, Tailored fit, Pockets, Handle & includes Sholder Strap

IBM Thinkpads

Pentium P-75 -or- 486 DX4-100

Huge 10.5" Active Matrix SVGA Color Display (the Best)
(Much Sharper & Brighter than a standard display, a \$300 value)
33k FAX MODEM - 2 PCMCIA Expansion Slots
Dual Infrared Ports (Front & Rear)
Track Point Mouse All Standard Ports (1S, 1P, 1VGA, 1Kbd)
Pop out - Hard Drive, Ram, & Battery
Ram & Hard Drive Expandable & Upgradable.
Includes Power Supply & Hydride Battery
Free Lifetime Tech Support Web Site Creator Software
Internet Ready, America On Line 4.X Latest Version
Fax Modem Software, Searchable Owners Manual s/w, W95
DX4-100 810Meg Hard Drive Standard -or- (2Gig only \$59!)
16M Ram Standard -or- (optional 24M Ram \$24!)
Pentium P-75 2Gig Hard Drive & 24 Meg Ram Standard



Sturdy Handle
Rubber Sides

3 easy payments of
DX4-100 \$218!
Wow 0% Financing on Credit Cards only
3 easy payments of
Pent-75 \$286!
DX4-100 Dock \$119 with purchase
Docks \$189 alone
Pent-75 Dock \$39 with purchase

Over a Quarter Million Devices
2 Easy Payments
\$49!
FREE Upgrade which will include Separate Asian Transistor Spec Data (a \$69 option in the new version)

"REFEREE" CROSS REFERENCE & SPEC Transistors, ICs & Diodes

A Specialist in "Hard to Cross House Numbers"
Easy, Powerful & Fast.
The Most Comprehensive Software Sold.

Yields Device Specifications & 75 to 250 Potential Replacements!

Replacement Numbers are Totally Global including Domestic, Asian, European, House, Branded, as well as ECG, NTE, SK & GE. Displays Case Drawings Lead Configuration & Pin-outs for many Devices. Coverage of Replacement Numbers is Very Impressive. 7 Disk Set (17 Meg decompressed) For DOS, W3.1 & 95, 98 & NT. Current Version 7.11

Includes:
4 HUGE Consumer Electronics Industry Directories
1- Consumer Electronics Parts Sources (Service) 2- Consumer Electronics Manufacturers 3- The Entire Computer Industry 4- Semiconductor Manufacturers

#1 Choice of Service Centers



Limited Time
IC Master \$29!
Oh My GOD!

ICM Bible of the IC Industry Every Cross-reference 3 Volume Set with Tons of Information

ICMaster Earlier Editions Perfect for Service or Lite Design. Later Editions Perfect for Advanced Design

ICM 95 3Book Set \$29 !!!!!!!
96 3Book Set \$49 !!!!!!!
97 3Book Set \$69 !! CD Rom \$99!!
98 3Book gone CD " \$135!
99 3Book gone CD " \$189!

EEM Contains the Complete Catalogs of Most Electronic Component Manufacturers & Distributors

97 4 Book Set only on CD \$35
98 4 Book Set only on CD \$55



IBM Docking Stations

From IBM \$350


This is not just a port expander it's a full blown docking station. You can add ANY desktop ISA card and it will work with your IBM laptop. Imagine the possibilities. Add a TV card and watch TV while you compute! ISA computer card hides in the base of the unit.

FREE Local Area Network (LAN) card (a \$79 value) Notebook Snaps onto the dock. Expansion Port for optional CD Rom Built-in Speakers Built-in Power Supply & Fan SCSI Expansion Port / Parallel / Serial / Keyboard / Mouse / Monitor / Stereo in & out Front panel headphone Jack Hidden Carry handle LED Status Indicators Color Black (matches notebook) ISA Port cover & Key optional (not required)

1 Year Warranty - Satisfaction Guaranteed - The Friendliest People - The Best Customer Service
PAYMENT PLAN with Credit Card -or- Layaway ONLY 843-650-5700 For Questions-or- email: netcomd@aol.com
COD's SINGLE PAYMENT ONLY ORDERS ONLY 800-733-3733 ORDERS ONLY FAX 843 650 5777 10 - 8 EST Mon - Fri

STAMP APPLICATIONS

by Lon Glazner

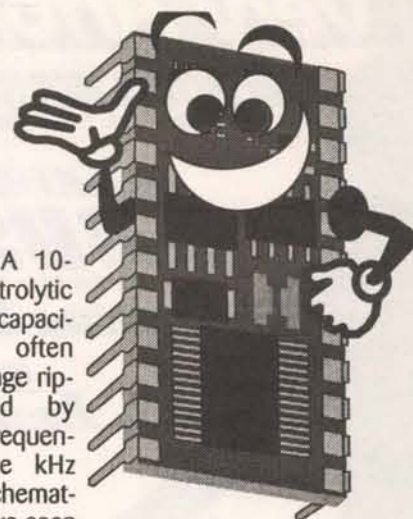

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

Protecting Your Stamp From The Cold, Cruel World

1 I've spent the last few months working on a design that is going to be located in a very inhospitable environment. I've had to deal with widely varying temperatures, a noisy power bus, high current loads, and a slew of other factors which don't look upon electronics in a friendly manner.

Overview

All of this work started me thinking about some of the things that I take for granted. There are a few tried and true circuits that I regularly use for protecting my microcontroller designs. I thought it might be nice to cover a few of these concepts, as well as

some techniques for powering your BASIC Stamp designs. These are circuits and/or techniques that have helped me to ensure successful electronic designs. I'm no analog guru — nor do I pretend to be one — but the concepts that I'm laying out here can help you to avoid many of the pitfalls that the real-world often presents.

It is also helpful to keep in mind that no matter how well thought out your PBASIC program is, a noise spike can still scramble the brains of your BASIC Stamp. This can lead to unpredictable behavior, or a complete system failure of your BASIC Stamp design.

De-coupling Capacitors

It is good practice to isolate your local circuit (which can be an IC or group of ICs) from your supply impedance. This is termed "de-coupling," and is routinely accomplished with capacitors.

Each IC in your circuit could benefit from de-coupling capacitors, but it is essential to use de-coupling capacitors on any high-speed logic chips that you may be using (the BASIC Stamp). The fast rising and falling edges of your logic level signals as they switch states require additional current pulses from your power supply. Small ceramic capacitors can supply these currents, when kept in close proximity to your ICs. Placing the de-coupling capacitor within a half inch of your IC will typically do the trick. In most cases, the actual value of the de-coupling capacitor can vary. A good rule of thumb is to use a value between 0.1uF and 0.01uF.

For circuits that are driving large loads, it may be necessary to use low frequency de-coupling

capacitors. A 10-47 uF electrolytic or tantalum capacitor can often reduce voltage ripple caused by switching frequencies in the kHz range. All schematics that I have seen of the various BASIC Stamps have shown a 22uF capacitor on the output of the on-board linear regulator, so some protection of this type may already be in place.

I have found that placing a 0.022uF de-coupling

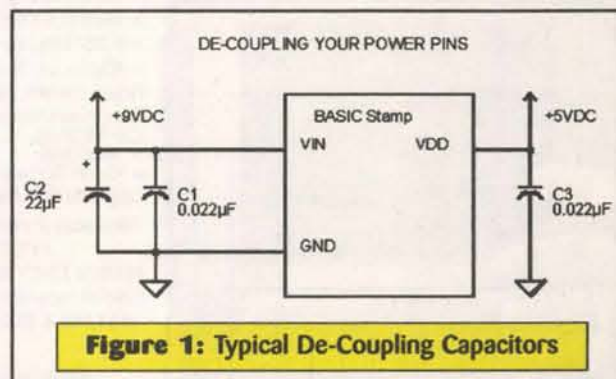


Figure 1: Typical De-Coupling Capacitors

capacitor as close to each IC as possible reduces noise on the power bus significantly. I also ensure that at least one 22uF capacitor is included in each design, and that a few 2.2uF ceramic capacitors are located next to any IC that may be driving additional circuitry.

I think the best philosophy regarding de-coupling capacitors is that they are cheap, so use them with great vigor, and sprinkle them throughout your design.


Power Supplies

Electronics these days tend to end up in just about any place you can imagine. Cheap power supplies, car batteries, or noise caused by switching inductive loads (like turning on motors or lamps) can create enormous problems for logic level parts such as the BASIC Stamp.

Filtering your incoming power supply can be done several ways. A resistor in series with the Stamp VIN pin, as well as a low-frequency de-coupling capacitor, can act as a low-pass filter which will smooth out noise spikes. Pre-regulating your supply, such as with a zener diode, can help reduce the damaging characteristics of an inductive spike on your input voltage.

The zener diode will act as a "rough" regulator acting to keep the voltage on your VIN pin at the zener's rated voltage. The zener can clamp positive going voltage spikes, and reduce the effects of negative going voltage spikes. Figure 2 shows an input clamping circuit that can be used to protect your BASIC Stamp. Figure 3 is a simulation of the zener clamping circuit and how it handles both

INTRODUCING

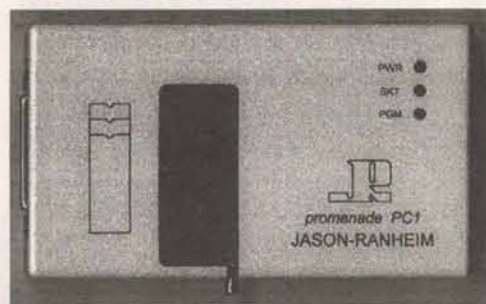

THE promenade PC1 EPROM/FLASH PROGRAMMER


- Connects to the parallel port of your PC, compatible, laptop or notebook computer
- Programs and verifies thousands of device types to 8Mbits with supply voltages as low as 1.9 v
- Use the PC1's battery pack to power the programmer to get complete portability
- The PC1 costs just \$159.50. Call, write or visit us on the web for complete information.

JASON RANHEIM

3105 GAYLE LANE AUBURN, CA 95602
800-421-7731 530-878-0785
<http://www.jasonranheim.com>

PCB LAYOUT Software For Win95 - FREE

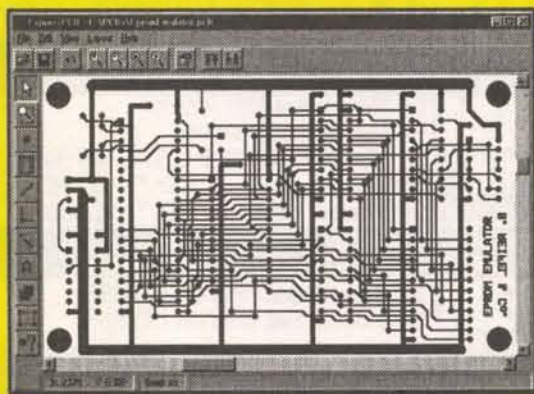- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

STAMP APPLICATIONS

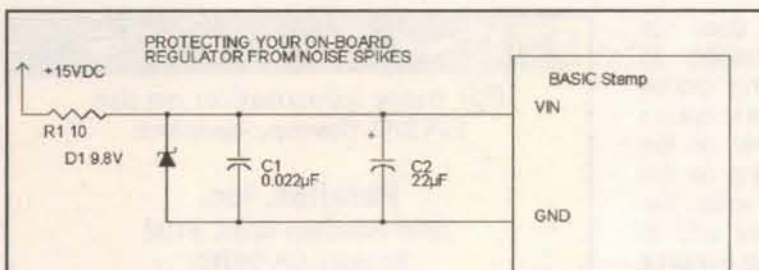


Figure 2: Zener Clamp on Your Power Input Supply

positive and negative voltage spikes of 9µs duration.

Power dissipation in your clamping circuit can be a problem if you select a zener diode that is rated at a voltage below your input voltage (as I did in my simulation). Your series resistor is then dissipating power based on the difference between your input voltage and the voltage that your zener diode is regulating at.

What usually works best is to select a low value series resistance (or none if your circuit is drawing a significant amount of current) and a zener diode whose voltage rating is slightly higher than the power supply you are using. For instance, if you were powering the BASIC Stamp with a 12VDC supply, you might select a 10-ohm series resistor, and a 13V zener diode. The goal here is to protect the BASIC Stamp from voltage spikes that might damage its on-board regulator.

Power dissipation can often be a problem with the BASIC Stamp on-board linear regulator. The power dissipated by a linear regulator can be characterized by $(V_{in} - V_{out}) \times I_{supply}$. The higher the input voltage, the less current required to overheat a linear regulator. With a 30VDC input voltage, a five-volt regulator will have to dissipate one watt of power, as heat, when supplying just 40mA. Placing another, higher value linear regulator between the input voltage and the Stamp's VIN pin can allow both regulators to share the power dissipation requirements.

As your input voltage gets higher, this becomes more difficult since many linear regulators are rated for 30-35VDC maximum input voltage. A transistor and zener diode pre-regulator can sometimes allow you to get the job done. Many transistors can handle large voltage drops from their collector to emitter (denoted in the data sheet as V_{ce}), but heatsinking will still be required, and may be extensive. Figure 4 shows an example of a zener diode-NPN voltage regulator.

Protecting Your Input Pins

The BASIC Stamp is based on a Microchip PIC

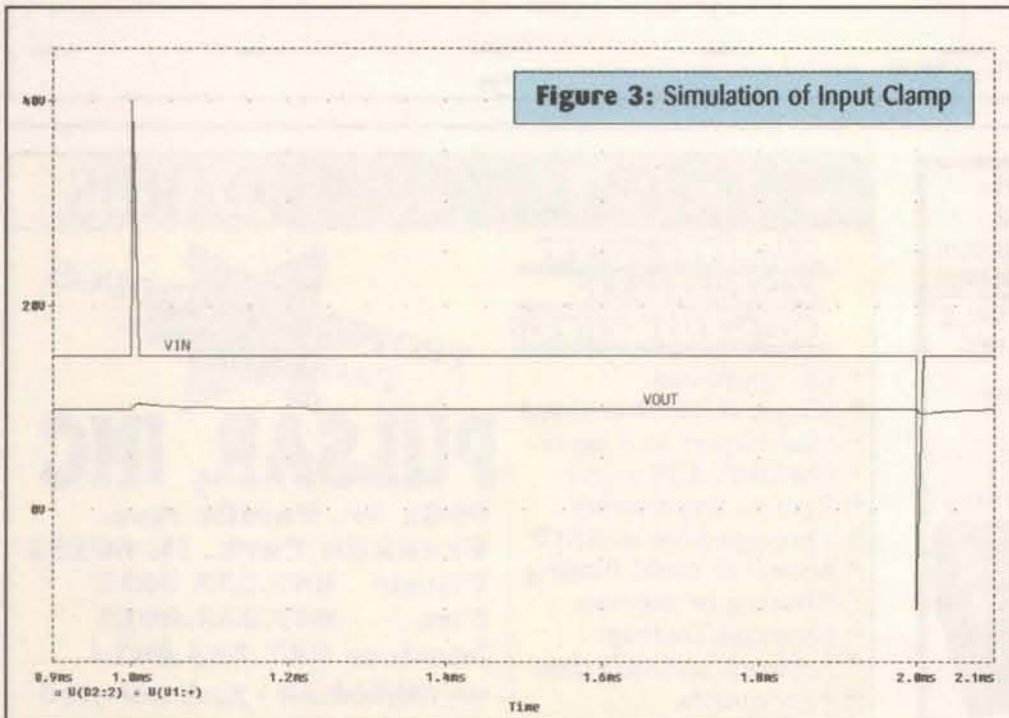


Figure 3: Simulation of Input Clamp

microcontroller. These microcontrollers have internal protective diodes that shunt signals higher than about 5.6V to the +5VDC bus, and signals lower than -0.6V to the ground bus. There can be some interesting unintended consequences regarding these protective diodes.

One of the more interesting is that the BASIC Stamp can be powered off of one of its I/O pins. For example, if the BASIC Stamp was not powered, but a +5.7VDC signal was present on one of its I/O pins, the protective diode would be forward biased (turned on), and about 5VDC would then be present at the Stamp's +5VDC bus, and could power

the BASIC Stamp.

Furthermore, positive voltage spikes present on your I/O pins can be translated directly to your BASIC Stamp +5VDC output (or negative going spikes to your ground bus). This can create problems which are hard to diagnose. Imagine turning on a relay with your BASIC Stamp, and watching your temperature sensor go up in smoke. There is no apparent connection between the two devices, yet they are only separated by diodes internal to the microcontroller which the BASIC Stamp is based on.

Protecting your input pins can be done in a manner similar to the zener diode clamp used on the power supply. Yet, in this case, the series resistor can be much larger and can be a more active instrument in attenuating voltage spikes. The input impedance for a BASIC Stamp pin set as an input is about 1 megohms (very rough estimate). The input impedance can be estimated from the leakage current that is typical of an input pin (about 1µA maximum).

Any series resistors should be selected so as not to form a voltage divider with the input impedance of a BASIC Stamp pin configured as an input. This is especially important if your input signals are already attenuated by external devices such as op-amps which do not have rail-to-rail outputs (like the LM741).

A series resistor of about 1k ohms, in conjunction with a zener diode rated for 5.1-5.6V, and a capacitor can effectively protect input pins from voltage spikes, and reduce noise that might affect your BASIC Stamp's program flow. The series resistor forms a low-pass filter with the capacitor in this circuit. If you are measuring pulses or frequencies with a particular Stamp pin, be sure to select component values so that your signals are not attenuated out of existence by the protective circuit. You can calculate the frequency threshold of a low-pass filter with the equation ...

$$f = 1/(6.28 \times R \times C)$$

When measuring short pulses, keep in mind that the rise time of your pulse will be limited by the low-pass RC filter described above. The

time it takes for a signal to rise from 10% of its maximum voltage to 90% of its maximum voltage through an RC filter can be approximated by $2.2 \times R \times C$. This is also considered the rise-time of the signal in question. For the circuit in Figure 5, this rise-time is roughly 48µs. This is the time it takes for a five-volt pulse to rise from 0.5V (10% of 5V) to 4.5V (90% of 5V).

This means that if you are intent on measuring short pulses, you should consider the effects of filtering on the BASIC Stamp's ability to make the measurement in question. Figure 6 provides a graphical representation of the

JFETS

ULTRA LOW NOISE
LS843 - 3nV/Hz typ

TIGHT MATCHING
LS843 - 1 mV max

- ♦ N & P Channel
- ♦ Duals & Singles
- ♦ Custom Screening
- ♦ Die, SMT, Thru-Hole
- ♦ No Order Minimum
- ♦ COD's Accepted

Second Source for Domestic
& Foreign JFETs & Bipolars

Full Service U.S. Manufacturer
of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court
Fremont, CA 94538
510-490-9160/510-353-0261(Fax)
E-mail: 3623671@MCIMAIL.COM

Write in 33 on Reader Service Card.

MINI-PC \$27

OEM (1k) PRICE, EVAL (1) \$95
INCLUDES:
- 3 SERIAL/2 PARALLEL (2260)
- UP TO 4MEG ROM (27C040)
- BUILT-IN RAM & EPROM
- MEM EXPANDABLE TO 640K
- REAL TIME CLK/INTERRUPT
- LCD AND KEYBOARD PORTS
- ON-BOARD LED DISPLAY
- STANDARD PC ISA BUS
Perfect when a full-size PC is too large, expensive, or power hungry. A fully functional single board computer, needs only program and power source. Runs DOS, Use Turbo C, BASIC, MASM. All utilities to do this included. 386 versions available starting at \$55. Learn embedded technology!

UNIVERSAL PROGRAMMER

\$95 SINGLE
PIECE
PRICE
EEPROM, UVEPROM, FLASH,
NVRAM, DOES UP TO 8 MEG
(27080). ADAPTERS FOR
MICROS, PLCC, OTHERS.
PARALLEL PORT VERSION.

SINGLE CHIP COMPUTER \$1.99

BUILT-IN BASIC!!!
20MIPS-16BIT-10X FASTER THAN 16c54
2K FLASH-64 EE-REPROGRAMMABLE
ZERO EXTERNAL COMPONENTS
32MATHREGS-ANALOG COMPARATOR
15 I/O (6 SERIAL, 8 PARALLEL, 1 ANALOG)
RS232C DOWNLOADER-NO DEVKIT NEEDED
3IRQ-RTC-2.7 TO 7VOLT OPERATION

**\$21 PC SOLID
STATE DISK**
OEM (1k) EVAL 75.00
FLASH/RAM/EPROM
25-16M/PCMCIA/DIPS

**NO MORE HANGUPS...
PC WATCHDOG!** 640x480 CARD
FOR SBC OR PC
REBOOTS PC 1K \$21 1 \$95

VGA LCD 640x480 CARD
FOR SBC OR PC
1K \$27 1 \$95

web site: www.mvsweb.com
MVS BOX 850
MERRILL, NH 03054
(508)792-9507

Write in 32 on Reader Service Card. 13

STAMP APPLICATIONS

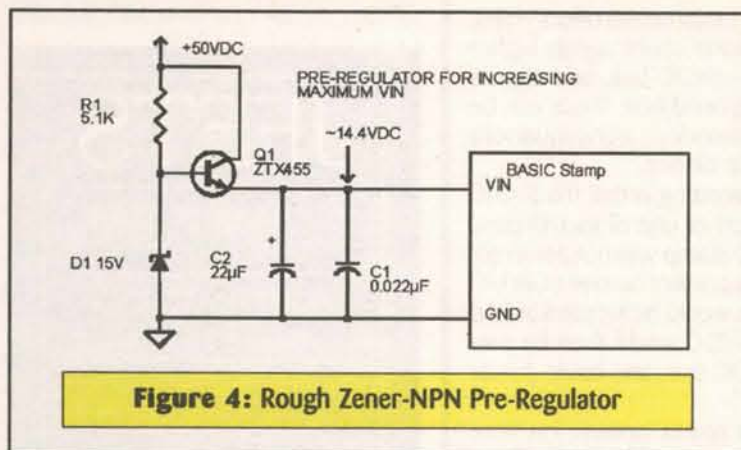


Figure 4: Rough Zener-NPN Pre-Regulator

rise time for the filter circuit in Figure 5.

Figure 7 shows the input signal versus the signal as seen by the BASIC Stamp after the signal passes through the protective circuitry in Figure 5. The incoming signal has a 50kHz 0.5V peak-to-peak noise signal, a logic level pulse, and a 1µs glitch. As you can see, the protective circuit filters out most of the noise and prevents the glitch from reaching the BASIC Stamp. The glitch is too short and, due to the rise time of the RC filter, it never reaches a logic high level which could be measured by the BASIC Stamp.

One killer of electronic components is electrostatic discharge (ESD). If you don't believe me, try walking across your carpet with just socks on — be sure to shuffle your feet — and then touch your finger to your favorite BASIC Stamp project. Of course, if you do this, you'll be shelling out some bucks for a new BASIC Stamp, and probably a handful of other replacement components. On second thought, just take my word for it.

But you can see from being shocked by your friends, neighbors, and loved ones that we humans have quite a capacity (or is it potential?) for carrying potential (or is it capacity?). Anyway, we can all carry a healthy enough charge to zap a BASIC Stamp into next week. This can be particularly common in designs with keypads.

Figure 8 shows a commonly used method of protecting I/O pins on microcontrollers from ESD when interfacing to switches or buttons. The pull-up resistor (82k ohm) is required to ensure that

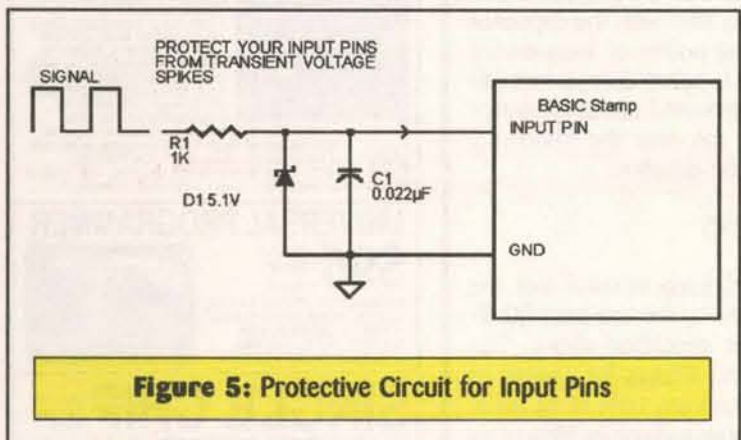


Figure 5: Protective Circuit for Input Pins

pressing the switch does not short your power supply to ground. The switching diodes allow transient voltages to open a path to either ground or the +5VDC bus, depending on the polarity of the voltage spike. The 1k ohm series resistor acts to limit the current during transient voltage spikes and protects the diodes which limit the voltage on the microcontroller input pins.

The diodes which are internal to the Stamp I/O pins (that I had mentioned earlier in the article) can be used in place of the external switching diodes, but should probably not be considered as robust a form of protection.

Conclusion

I think two general rules apply to protecting your BASIC Stamp designs:

Rule 1: If any connection interfaces to the outside world, PROTECT IT.

RESOURCES

For more information on the BASIC Stamp, contact:

Parallax, Inc.

3805 Atherton Road, #102
Rocklin, CA 95765
phone (916) 624-8333
<http://www.parallaxinc.com>

Scott Edwards Electronics, Inc.

1939 S. Frontage Rd. Ste. F
Sierra Vista, AZ 85635
phone 520-459-4802
fax 520-459-0623

www.seetron.com info@seetron.com

Solutions Cubed

Lon Glazner

3029 Esplanade Suite F
Chico, CA 95973

E-Mail: lon@solutions-cubed.com

www.solutions-cubed.com

Phone: 530-891-8045

Fax: 530-891-1643

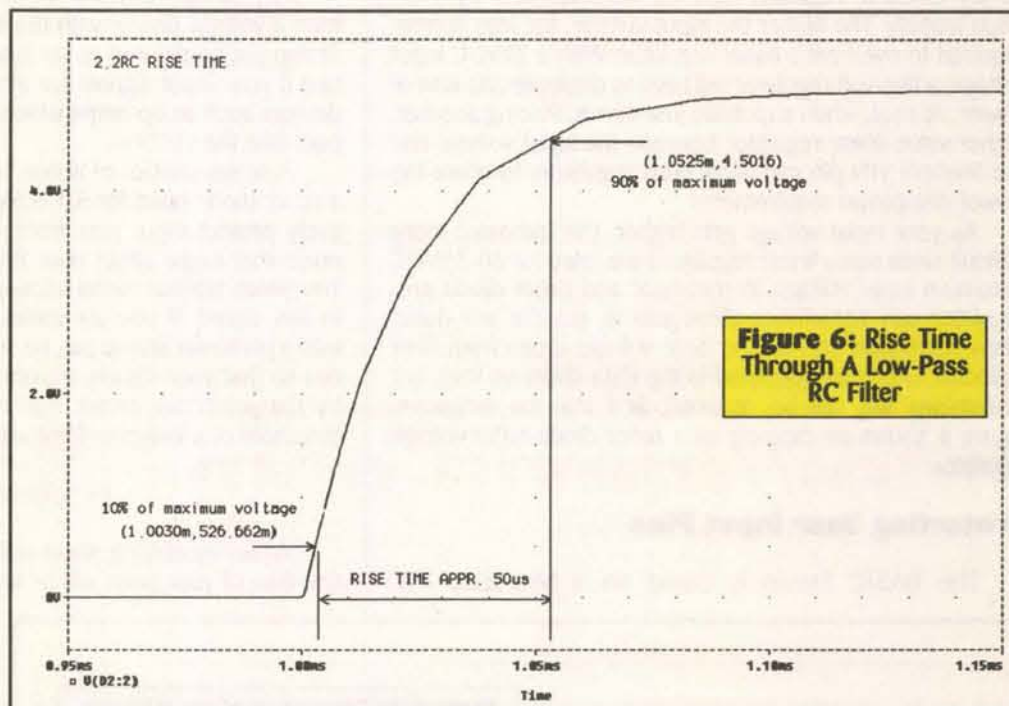


Figure 6: Rise Time Through A Low-Pass RC Filter

BRIGAR ELECTRONICS
7-9 ALICE ST.
BINGHAMTON, NY 13904



PHONE: (607) 723-3111
FAX: (607) 723-5202
EMAIL: BRIGAR2@aol.com
<http://members.aol.com/brigar2/brigar.html>

15" SVGA COLOR MONITOR
Various Manufacturer
IBM PC/XT or Higher compatibles
.26 mm dot pitch - Max resolution
1280 x1024 Includes power cable
Weight 32 lbs.
Removed from svce.
Mint cond.
SALE
PRICE
\$ 69.95



UNBEATABLE COMPUTER SALE

IBM COMPATABLE CPU'S VARIOUS MFG.
COMES WITH THE FOLLOWING:
■ 486 66MHZ ■ 4 MEG & UP MEMORY
■ 170 TO 540 MEG HARD DRIVES.
■ 3-1/2" 1.44 MB FLOPPY DRIVE
■ KEYBOARD

THE COMPUTERS ARE OBVIOUSLY USED
BUT IN GREAT
CONDITION.

**BLOW
OUT
\$ 59.95**



PRINTED CIRCUIT BOARDS

**QUALITY PRODUCT
FAST DELIVERY
COMPETITIVE PRICING**

- * UL approved
- * Single & Double sided
- * Multilayers to 8 layer
- * SMOBC, LPI mask
- * Reverse Engineering
- * Through hole or SMT
- * Nickel & Gold Plating
- * Routing or scoring
- * Electrical Testing
- * Artwork or CAD data
- * Fast quotes

**PROTOTYPE THROUGH
PRODUCTION**

PULSAR, INC

9901 W. Pacific Ave.
Franklin Park, IL 60131
Phone 847.233.0012
Fax 847.233.0013
Modem 847.233.0014
yogii@flash.net - flash.net/~yogii

STAMP APPLICATIONS

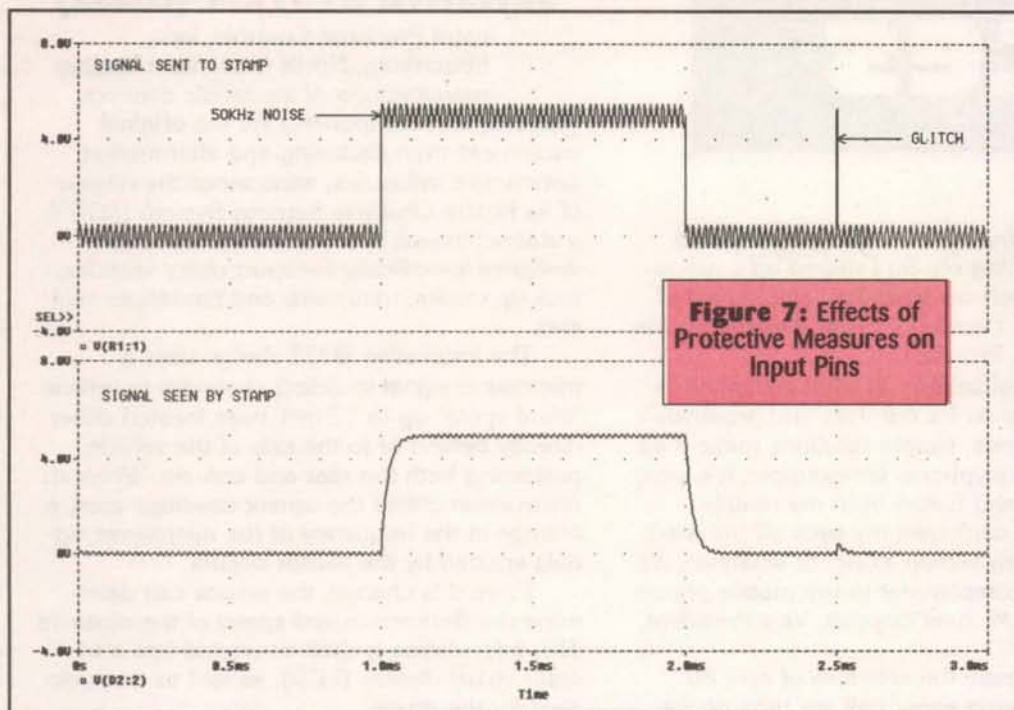


Figure 7: Effects of Protective Measures on Input Pins

Rule 2: If you can think of something bad that somebody could do to your design, assume it WILL HAPPEN.

When you are planning a BASIC Stamp design, always take time to look at where each connection is going. And try to figure out what odd things may happen to it. If you have a keypad or LCD display, can somebody spill liquid on it? If you have a relay that you are controlling, what happens if it can't close or open? If you are using switching transistors, can

they over-heat? If a part blows up, will it blow up open or shorted? Spending ample time figuring out both how to protect your electronics, as well as what to protect them from, can be surprisingly beneficial. There are certainly cases where protection is not much of a concern. Most chip-to-chip connections are short and don't require much in the way of filtering or protective circuitry.

There are also situations that cry out for protective measures. For example, you may have a small robot using an IR detector for wall sensing. It's a good idea to mount IR detectors of this nature at a point where they are unobstructed by objects on the

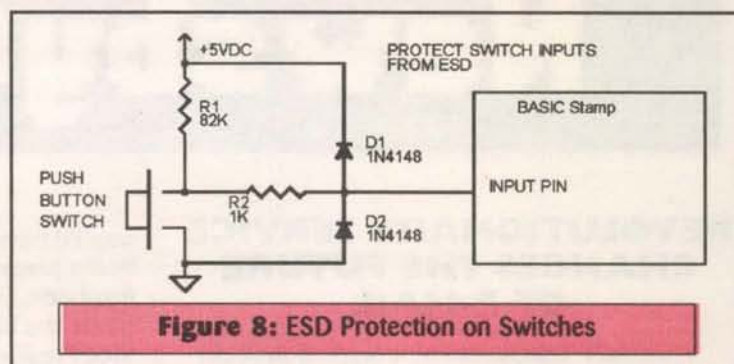


Figure 8: ESD Protection on Switches

robot itself. This may be at a distance from your BASIC Stamp. Any wires or ribbon cables connecting these two devices will act as antennae and can conduct noise generated by your motors, battery chargers, or any other "noise generators." These kinds of connections are good candidates for protective circuitry.

After a while, protecting your circuits becomes second nature, and you start making trade-offs such as cost versus the level of protection you may receive from a specific circuit addition. I always try to add all of the protective circuitry that I can think of and, after the design is up and running, I whittle away the things that may be overkill.

In the end, good engineering is about one-third experience, one-third forethought, and one-third time in (or sometimes out) of lab testing. I think there is another \pm one-third or so wrapped up in test equipment, time of day, amount of beer you had the night before, and a few other important factors. Of course, the most indisputable measure of good engineering is design survivability. So protect your Stamps, and give them good safe homes! **NV**

Electro Mavin

**Has To Much for the AD !!!!
We are Busting at the Seams!!!
So Please....**

Stop by and Check Us Out on the WEB

<http://mavin.com>

**This is all you'll need to get to the
fabulous world of Mavin Specials**

Like....

Soyo Super Stable Socket 7

Mother Boards #SY5EMA

Bus Over Clocks to 124 MHz -

Uses Pentium class CPU up to 500 MHz

Check out our low price.....

Other Items Include....

SCSI Hard Drives 3 cents a meg

GPS Engines w/Antenna

Microwave Goodies and Stuff

56K V.90 Modems, 40X CDROM Drives

Dealers Special on Designer Mice

We Also Buy Connectors, Contacts, Raychem

Electro Mavin

800-421-2442 or FAX 310-632-9867

E-Mail john@mavin.com

or

E-Mail mark@mavin.com

SUPERCIRCUITS

America's #1 Microvideo Source

**MICRO
VIDEO
TOP 10**

OVER 120 NEW VIDEO PRODUCTS!

1. World's Smallest Video Camera* 1 lux, 3oz. \$59.95
2. Pinhole Video Camera..... 410 lines, 0.5 lux, Sharp chip \$39.95
3. Color Video Camera 350 lines, 2 lux, Remote head \$69.95
4. Live Aerial Video R/C Videotape..... How to & more \$24.95
5. Wireless Covert Tape Cam 300' range, FCC OK \$349.95
6. Super Tiny Color Pinhole..... 350 lines, less than 1" sq. \$99.95
7. Micro Video Transmitter..... 1000' range, ATV band \$159.95
8. Complete Wireless ATV Video Set .. 3 Miles Range \$419.95
9. World's Smallest Wireless Video Cam Please Call
10. Video Goggles Dual hi-res LCD's, 3D capable \$599.95

**Buy your microvideo equipment where NASA, The Air Force, JPL, Lawrence Livermore Labs and the FBI does.
Call us today.**

For the best in high performance microvideo equipment, call the experts at Supercircuits. We've grown to be America's microvideo leader by consistently offering the best equipment at the lowest prices, with unbeatable service...compare our plug 'n play ease of use, warranties and return policies. Of course, Supercircuits microvideo is used by some of the biggest names in science, industry and national defense. But with prices starting at under \$40 for tiny high resolution video cameras, it is technology that is as affordable as it is amazing. Call us today, and get our free 72 page Microvideo Catalog, loaded with photos, specs and more.

1-800-335-9777 ext NV

Or fax us at 512-260-0444

One Supercircuits Plaza Leander, TX 78641

www.supercircuits.com

*Supercircuits PC-21XP and PC-51XS are listed as world's smallest pinhole and spy video cameras

Write In 36 on Reader Service Card.

Nuts & Volts Magazine/SEPTEMBER 1999 15

Newsbytes

REVOLUTIONARY SERVICE CHANGES THE FUTURE OF E-MAIL

ACT TeleSolutions, a leading provider of live operator messaging solutions, will revolutionize person-to-person mobile communications today with **ibyphone**, an exciting, innovative E-Mail service. This is the first initiative in the company's plans to make all that is available on the internet accessible via telephone, paving the way for the future of the wireless world.

Pioneered by XACT, ibyphone is the first subscription-based E-Mail service that enables its customers to send E-Mail from any telephone, at any time, via live operator. Unlike other companies' attempts to fill the mobile E-Mail void with technology-driven solutions, ibyphone offers a simple, personalized, device-free alternative. "ibyphone is the customer-driven evolution of mobile communications for the E-Mail generation," says Dan Joseph, co-founder and CEO. "It enables users to bridge the gap between themselves and technology, through human interaction. Technology alone is an inadequate answer to problems inherent in mobile messaging. And who wants to have to drag around bulky machinery just to stay in the loop? The real answer is simplicity, customizability, and flexibility. Busy people seek solutions that give them — not the technology — control over their communications. ibyphone offers that solution and that control in an affordable package. The response from our test subscribers has been phenomenal."

Using ibyphone is easy. Subscribers just call a toll-free number from any telephone, and dictate their message to a highly skilled Telephone Service Representative, who can send it instantaneously to any number of individuals or groups. It's that simple. ibyphone optimizes and personalizes the user's experience. Subscribers identify themselves with a PIN number, and are greeted by name. Service Representatives access the subscriber's online address book for rapid addressing to groups or individuals, and can add new addresses upon request. Representatives are trained to take messages quickly and accurately, and can read back and edit each message to ensure content quality. The ibyphone system was developed to mirror all E-Mail capabilities, enabling a host of service options and features. Subscribers register online at www.ibyphone.com, where they can customize delivery, signoff and confirmation options, build an address book for mobile access, and select a usage plan. Activation is immediate.

XACT's test market shows that professionals who rely on both mobile telephony and E-Mail could identify numerous situations in which ibyphone has met their needs in a way nothing else could. Such "ibyphone moments" speak for themselves. For instance:

* "I was running late, and needed to reach my team with an update and game plan before getting on a long flight. I realized there was no

way I'd have time to boot up my laptop and find a place to log on. So I zipped off a group ibyphone, (which my team had already acted on by the time I landed.)" Scott Mataya, Senior Vice President, Petopia.

* "I'm a real believer in what advances in technology can do for our lives and productivity. But sometimes, simple solutions make a lot of sense. Take ibyphone, for example. It's great to be able to send E-Mail from my mobile phone, when I can't take my eyes off the road, or don't have my laptop along, or whatever. It's a very useful complement to my mobile phone and laptop." — Michael Doppelt, Vice President, Bear Stearns.

* "I coordinate the activities of over 80 people, and spend about half my time on the road. I like ibyphone because it allows me to set up groups for the teams I need to manage. I often want to communicate the same thing to 10 or more people. Before, I would have had to make a half dozen calls to do this, and still I couldn't be sure everyone got the message. Now I can take care of things with one phone call! — Dan Feldstein, President, Shopper's Advantage.

* "I started using ibyphone to E-Mail in a pinch. Then it occurred to me that I could use it in the car to actually accomplish something useful during my commute. That means less time I have to spend on E-Mail in the office or when I get home. Plus, getting CC'd means I don't forget to follow-up. ibyphone is a great tool." Mitch Smith, President and CEO, On the Go Hosiery.

"ibyphone adds control, convenience and power to the way people interact with one another," says Dave Guttman, co-founder and President of ibyphone and XACT TeleSolutions. "It allows customers to take advantage of a direct phone-to-E-Mail solution without a costly investment in high-tech devices that will be obsolete in a matter of months. With over 38 million professionals already carrying cell phones, and over 40 million professionals sending an average of 30 E-Mails a day, ibyphone meets a critical and unmet need. Communication via E-Mail whenever and from wherever one chooses."

Beyond its advantages as a completely mobile solution, ibyphone is affordable and accessible. XACT invites interested parties to try ibyphone free for a month. Thereafter, subscribers can select a usage plan from a range of packages designed to meet the requirements of target customer groups, such as "The Entrepreneur" or "The Road Warrior." Packages start at as little as \$9.95 per month.

From unrivaled simplicity, accuracy, and flexibility to complete control and mobility, the first generation of ibyphone is undoubtedly a missing link in mobile telecommunications. True pioneers in the person-to-person communication industry, the ibyphone team has created the first complete and custom-designed solution to sending E-Mail.

<http://www.ibyphone.com> • 212-813-1700

ROSTRA OBSTACLE SENSING SYSTEM (ROSS)

Rostra Precision Controls, Inc., Laurinburg, North Carolina, a leading manufacturer of electronic controls, systems, and components for the original equipment manufacturing and after-market automotive industries, announced the release of its Rostra Obstacle Sensing System (ROSS), a state-of-the-art obstacle detection system designed specifically for sport utility vehicles, pick-up trucks, mini-vans, and passenger vehicles.

The innovative ROSS design uses a microwave signal to detect obstacles in vehicle "blind spots" up to 12 feet away located either directly behind or to the side of the vehicle, protecting both the rear and corners. When an obstruction enters the sensor coverage area, a change in the frequency of the microwave signals emitted by the sensor occurs.

From this change, the sensor can determine the distance to and speed of the obstacle. This information is then converted into a tri-color visual display (LED), as well as an audio alert for the driver.

The ROSS technology is a major improvement over existing obstacle detection systems, because the sensor can be mounted out of view behind the vehicle bumper. Also, unlike obstruction detection systems currently on the market, the ROSS is not affected by adverse weather conditions such as snow, fog, hard rain, sleet, darkness, extreme heat, or bright sunlight, any of which can prevent obstacles from being detected in time to prevent an accident.

"The ROSS is an economical way to greatly reduce and/or eliminate the risks and repair expenses associated with the low speed obstacle collisions that frequently occur while driving in reverse gear," says Raymond Ford, President, Rostra Precision Controls.

According to a recent Allstate Insurance Company survey, 27% of all automobile accidents occur while driving in reverse gear. These types of mishaps are surprisingly costly to repair. A 1999 study conducted on six different sport utility vehicles by the Insurance Institute for Highway Safety revealed that typical repair bills for low-speed (five miles per hour), reverse gear collisions between the vehicles and stationary objects can range from \$3,000.00 to \$6,000.00.

The suggested retail price for the ROSS is less than \$300.00 installed, which includes a three-year, 36,000-mile warranty.

Easily mounted on both newer and older vehicle models, the ROSS comes with a universal installation kit and can be installed in less than 30 minutes without drilling holes in the vehicle, unlike other obstacle sensors. Rostra Precision Controls plans to make the ROSS available through automotive retail outlets by early September 1999.

Rostra Precision Controls is an ISO 9001 and QS 9000 certified manufacturer of automotive products and is the single largest supplier of cruise controls and transmission modulators and solenoids to the automotive after-market industry in the U.S.

Rostra Precision Controls specializes in the areas of vehicle speed control systems, transmission components, and vehicle comfort seating systems such as seat heaters, lumbar supports, and the industry-leading technology of the 'Active Seat'. Rostra Precision Controls employs 185 individuals at its headquarters in

WORLD'S SMALLEST
... 100mW ...

VIDEO TRANSMITTER, ON SALE

Incredibly only 0.98" x 0.8" x 0.037" in size. Transmits crystal controlled hi-res. images with 100mW output! The transmitter you've been waiting for. **Shown actual size.** Smaller than the 9V battery which powers it. Draws only 35mA! Factory tuned. Receive on cable channel 59. Will work with color or B&W cameras. UHF Bow tie antenna with balun and 3' cable for TV included. Perfect with our GM1000A. Both will fit in a cig. pack with battery!

SEPTEMBER SPECIAL TVX-100.\$159. with GM1000A CAM.....\$209.

ULTRA PRECISE, KENSINGTON LABS, XY STAGE.

Model 8500-6X, 6"x6" of high performance travel. One of the best linear stages available. Highly repeatable, ultra-precise. Precision ground surfaces result in unmatched laboratory-grade performance. Linear glass scale, internally attached to the table, eliminates all drivetrain errors not measurable when an encoder is attached to the motor. System provides up to 0.025µm res. over 100 mm. Built from stress relieved 7075 aluminum. Crossed-roller bearings for excellent stiffness, load capacity and lifetime. Combined with a very low friction preloaded lead screw and DC servo motor drive provides 20,000 hour MTBF. 100 mm/sec maximum speed and >50kg load capacity. Size: 15" x 9" x 2.75" H. Regular price > \$4K. X&Y stage with motors. USED, Very good condition. **SEPTEMBER SPECIAL, 8500-6, XY STAGE.....\$1295**

IR SOURCE with 1,000,000CP ! Hand held, long range illuminator. One of the most powerful available. Quartz halogen spotlight combined with the best military, glass IR filter. Because it's solid glass & not laminated plastic it can take the heat. Includes a coiled cord, std. cig. lighter plug. Operates from 12VDC. **SEPTEMBER SPECIAL, IR-SPOT \$99**

ARGON LASER POWER SUPPLY.

INDUSTRY STANDARD, AMERICAN LASER 60X

We were fortunate to obtain these unused and factory refurbished ALC 60X power supplies. Always in demand but hard to find. They can power most Argon heads up to 12AMPS. We have no manuals at press time. If you have a 60X series head or similar this is the unit for you. 110VAC power. Rugged anodized aluminum, housing with internal fan. Size: 8"x8"x11" L. 22 lbs. Don't miss out. Very Ltd. Qty.

ALC60X...\$299ea. or 2 for \$549

NEW! 0.008lux, COLOR NIGHT VISION CAMERA!
UNBELIEVABLE LOW LIGHT PERFORMANCE.
Our GMV-2K, DOES it in COLOR TOO!

For covert, military and scientific applications that must be color, this is it. Performance is enhanced through low speed electronic shuttering and digital frame memory. With an auto iris lens, 24 hour monitoring is possible. Auto sensitivity mode starts as it becomes dark. Eight Gain/Shutter modes are user selectable. Normal, X4, X8, X16, X24, X32, X64, X128. These provide frame rates of 60, 15, 8, 4, 3, 2, 1, and 0.5 frames per second. Auto/Manual white balance. Aluminum housing with dual 1/4x20 mounts. Specs: 1/3" CCD, with 291K pixels, 320 Lines, <1 Lux std. mode sens., 12VDC @200mA, Std. video out on BNC. Size: 54mmx50mmx94mm long. With pwr. adapter. All functions can be externally controlled via an 8 pin mini DIN. Uses std. c-mount lens not included.

Special Item, GMV2K.....\$589ea.
4mm, f1.4 A/I lens with custom cable.....\$119ea.

SEPTEMBER SPECIAL, PRICE BUSTER DEAL
NEW, SHARP, YH-7B50, COLOR, CCD CAMERA.

Now available for a fraction of its' original price. Great looking styling. Camera has a very stable, manually adjustable pan and tilt base. Base is removable for tripod mounting via standard 1/4-20 mount on bottom. Front panel LED power indicator. Excellent video performance packaged in a sturdy 2.7" x 1.4" x 5.8" L, 11 oz. package. Simply connect camera to any "Video Input." RCA cable supplied. Camera has 5.6mm lens with fixed focus from 18" to infinity. No adjustment required! Power is 6VDC from power adapter also included. 1/3" CCD, 300Lines resolution 25% better than standard VHS! Auto white balance. Perfect for any general purpose video application. Brand new, in original sealed boxes. Don't miss out on this super special deal.

YH-7B50 COLOR CAMERA...\$59ea. Super deal 2 for \$99

MINIATURE and, PRECISE, PORTESCAP, SWISS, GEARMOTOR.

State of the art "ironless" type, mini motor type M11-210-54-0 with approx: 40:1 gearbox. Size: 16mm d. x 43mm L. Operating parameters: @6VDC input, 8mA, 141RPM No Load, @ 12VDC input, 12mA 290RPM No Load

PORTESCAP, TYPE B: \$15ea. 2 for \$27, Special....10 for \$125

PORTABLE, PERIMETER, PROTECTION PPS-15V, SURVEILLANCE RADAR SYSTEM!

Up to 3000 Meter range. Provides audible indication of objects w/ alarm. Control panel with LED display of battery, signal strength, range and azimuth. Can be operated remotely via supplied cable and detachable control panel. 12VDC or 28VDC powered. Includes heavy duty, military, aluminum transit case, headphones, battery and tripod. Only 14 lbs. Latest flat antenna design. Motorized sweep.

SEPTEMBER SPECIAL.....\$1295

ALL TYPES of COVERT CAMERAS, all available with audio,

Specification for all models include: 1/3" CCD, 410 Lines Res., 0.3 Lux sensitivity, Power from 9 to 12VDC @100mA, 90° FOV lens except dome and IR which are 80°. All focus from 2 ft. to infinity. Standard NTSC video out. SENSITIVE to IR. note: Smoke & Motion detectors not functional, Clock & Exit operate normally. Dome is 3.5" H x 5.5" Diam. Don't see what you want? We can put a camera in anything you desire.

Smoke Det., Motion Det., Clock or Dome Camera, Special...\$79ea.
Exit Sign, Special...\$99ea. Please add \$10 for audio. (any model)

6V@12AH SEALED, RECHARGEABLE, BATTERY

New Panasonic, LCR6V12P. Tough to get at a discount. Very compact. Two top mounted 1/4" faston connectors. Perfect for high drain projects. Size: 5.9" L x 3.7" H x 1.9" D

2 for \$20, 10 for \$89

NEWPORT TRANSLATION STAGES.
also a few other goodies too!

MODEL:	DESCRIPTION:	EACH
270	LAB JACK	\$249
RSA-2T	360 deg. Rotary Stage with Clear Aperture.	\$129
625A-4	Laser Holder	\$149
481A	Rotary Stage	\$189
M36	Translation Stage	\$249
460A-XY	X-Y Translation Stage	\$189
M37	3 Axis Trans. Stage	\$289
415	Vertical Trans. Stage	\$129
M360-90	Mnting. Plate 90deg.	\$29
M436	Translation Stage	\$199
M150	Magnetic Mtg. Base	\$129
420	Linear Trans. Stage	\$119
HP10703A	INTERFEROMETER	\$129
HP10702A	INTERFEROMETER	\$129
HP10780A	RECEIVER	\$199
RUCKER & KOLLS 222	X-Y-Z MICRO POSIT.	\$ 50

10V @ 2.5 AH SEALED, LEAD ACID, B&W Each pack consists of five, 2 Volt cells. Each cell the size of a "D" battery. Arranged as 1X5 cells. Enclosed in an ABS outer shell. (removed for photo) Perfect for high drain applications. Make custom packs of any rating. Size: 7.5" L x 2.8" H x 1.5" D

5-five packs for \$20, 30 for \$99

IS ANYBODY OUT THERE?

RESOURCES UN-LTD.

VISA, MC, AMEX, DISCOVER, COD.

ORDER: 800-810-4070 TECH: 603-668-2499

FAX: 603-644-7825 E-MAIL unlt4u@j20.net

300 BEDFORD STREET, MANCHESTER, NH 03101

MOTORIZED 10X ZOOM, SURVEILLANCE LENS

New, 11mm to 110mm, f1.8, C-Mount, Fujinon, industrial quality optics paired with precision drive enable smooth remote operation of FOCUS, ZOOM and IRIS. Unit is open frame, black anodized alum. structure supports the sophisticated drive. Two models: Mod Z5 std. or Mod Z10 has HP optical encoders for position feedback (128ppr) on zoom & focus Edmunds sells the lens w/o drive for \$869ea. Motorized unit sells for >\$2000. Very limited quantity.

Model Z5.....\$349ea. Model Z10.....\$399ea.
New ZOOM LENS CONTROLLER.....\$169ea.

NEW! 4 or 8 CHANNEL, VIDEO AUTO SWITCHERS

Model GM34 or GM38. Connect to any four standard video signals and they will be sequentially output to the dual rear panel BNC outputs. Front panel user adjustable, variable dwell 1 to 15 sec per channel. Auto or manual switching with channel bypass. Compact only 8.6" W x 3.7" D x 1.75" H, ac powered. Video loop through.

GM-34.....\$79, GM-38.....\$99

WEATHER RESISTANT Camera Enclosure,

Solid, extruded aircraft aluminum. Glass window. Strain reliefs for cables. Size: 3.5" w x 3.7" h x 14" L.

Special:\$59ea. w/110V heater..\$69ea.
Heavy Duty Alum. Adj. Mount...\$29ea.

NEW GM182, 580 LINE, CCD CAMERA,

1/3" CCD, 580 Lines Res., 0.1 Lux sens., AGC, Auto Shutter, Pwr. 12VDC @120mA, 3.6mm, 71° FOV, Real glass lens. Focus from 10mm to infinity. Standard NTSC video out. 1/2 ounce SENSITIVE to IR. Size: 1.7" sq. x 1" d. with 6' leads. Superior quality for demanding applications.

GM182, with AC power adapter.
SEPTEMBER SPECIAL.....\$169ea.

MICRO CAMERA, with MIRROR IMAGE

Perfect for "rear view." 1/3" CCD, with 266K Pixels, 410 Lines Res., 0.3 Lux sens. AGC and Auto/Man Shutter. Low Power 12VDC @100mA 3.6mm, 92° FOV, focus from 10mm to infinity. A real glass lens! WHY BUY DISCONTINUED OR SURPLUS? New first quality Standard NTSC video out. 1/2 ounce! IR SENSITIVE!

GM251, with AC power adapter.....\$69ea.

ULTRA MINI and WEATHERPROOF, "LIPSTICK" CAM

Sleek black anodized, alum. housing. O-Ring sealed & RAINPROOF. Adj. tilting mount. 1/3" CCD, 380 Lines, 0.3 Lux, AGC, Auto Shutter, 9-12VDC @100mA, 4mm, f1.8, 78° FOV real glass lens, NTSC video. <1ounce! IR SENSITIVE. 23mmx45mm, 36" cable with BNC video & DC barrel jack.

PINHOLE Model. So tiny you can install it directly into a door. Only a 0.9" diameter hole! Specs as above. 90° FOV Pinhole lens. 1/2 ounce! Size only 23mm d.x.35mm long. Think of the places you could put this little jewel.

GM-200K-STD.....\$99 OR GM-200K-PH lens.....\$99

NOW YOU CAN SEE WHAT THE "FISHES ARE DOIN' (down 60 ft.)

UNDERWATER B&W CAMERA with INTERNAL, INFRA-RED ILLUMINATOR!

Sleek black anodized, BRASS, housing. O-Ring sealed & WATERPROOF. Adjustable mount incl. Specs: 1/3" CCD, 400 Lines res., 0.05 Lux sensitivity, AGC, Auto Shutter. 12VDC @225mA, 4mm, 78° FOV lens. A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small size only: 1.25" diam. X 2" long. With 60 ft. cable. Great for general outdoor use also. **GM-300KIR.....\$199**

DAYLIGHT/LOW LIGHT MINI CAM & A/I LENS. For down 'till dusk applications. Rugged alum. housing, dual mtg. sockets. 1/3" CCD, 420 lines res., 0.1 Lux sens., AGC, 12VDC @120mA. Take full advantage of camera sensitivity with super, 4mm, f1.4, 78° FOV Auto Iris lens included. BNC video out. 50mm sq. X 65mm L. Power adapter included. **GM-510A/I.....\$199 or 2/\$369**

SUPER, MINI C-MOUNT CAMERAS,

Super sensitive, GM410 or the general purpose GM412,

The GM-412 specs: B&W, size 1.5" sq. X 2.4" L, 250,000 Pixels, 380 Lines Resolution, Sensitivity 0.3 Lux, The GM410 specs: size only 1.5" sq. x 1.6" L, >270,000 Pixels, 410 Lines Res., Sens. 0.05 LUX. Both cameras are 1/3" CCD with AGC & Electronic shutter. 12V @110mA power. NTSC out. IR SENSITIVE, BNC video out. Both use std. DC pwr. jack. Aluminum housings with dual threaded top and bottom mounting. True performance not hype! These cameras will outperform ANY camera in this magazine. Multi-lens options are available to exploit their superior performance. GM412 shown bottom. GM410 shown top.

GM412, less lens..\$119, GM410, less lens..\$169

low cost MICRO CAMERA, w/audio 1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter.

Pwr. from 9 to 12VDC @100mA, 250k PIXELS, Std. model, 4mm, 78° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size Std: 1.25" sq. x 1" d. PH is 0.6" d, 1.6M long wiring harness with connectors included. **WARNING:** Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS.

GM-1000A-STD.....\$59 GM-1000A-STD/Aud.....\$64
GM-1000A-PH.....\$59 GM-1000A-PH/Aud.....\$64
GM-1000A-CMNT.....\$59 GM-1000A-CMNT/Aud.....\$64

Micro Lenses for GM1000 series

2.5mm, 150°.....\$22	8.0mm, f2.0.....\$22
4.3mm, 78° f1.8.....\$22	12.0mm, f2.0.....\$22
6.0mm, f2.0.....\$22	5mm, 70°PH.....\$22

C-MOUNT LENSES

LOW LIGHT	STANDARD
16mm, f1.6, 15° FOV.....\$39	4mm, 80° FOV.....\$24
8mm, f1.3, 40° FOV.....\$49	8mm, 40° FOV.....\$24
4mm, f1.4, 78° FOV.....\$49	12mm, 28° FOV.....\$24

MOTORIZED ZOOM LENS SPECIAL

6X magnification, 12X on a 1/3" camera! Auto iris too!

New, fabulous hi-res. optics with std. C-Mount. Superior Fujinon and Vicon lenses. Normally cost from \$600 to \$1500. There is no substitute for a good lens! All drive motors will operate from 6-12VDC. Auto iris has a built in amp which works with any cameras video output for control.

Type B-6, 12.5 to 75mm, 6X, f1.2 \$179 or 2 for \$349
ZOOM LENS CONTROLLER, NEW \$169

Brand New, Video Motion Sensor. Model VM10. Attach to any standard video signal and you've got an electronic "watchman" diligently watching the entire scene. Or any adjustable sized area within the scene. Such as a doorway or even a drawer or cabinet. A state of the art security aid. The unit will close a contact when it senses a change. Use it to turn on a VCR or call the hounds. Auto or manual reset. Compact, ac powered. Adjustable sensitivity. Video loop through.

NEW, VM10.....\$189ea.

NEW, 2.4GHz VIDEO + STEREO AUDIO TRANSMITTER with SONY, CCM-PC5 COLOR CAMERA.

Originally sold for \$500! Now available for a fraction of that price. Great looking styling. Camera has a very stable, adjustable tilting base, front panel LED pwr. indicator and sensitive built in electret mic, providing excellent audio and video performance from one compact package. Simply connect camera to the completely self contained 2.4GHz transmitter. All cables supplied. You can transmit up to 700 feet clear line of sight Companion matching receiver works with any TV or VCR. Internal patch antennas. Camera has adjustable focus 6mm lens. (1" to infinity, macro capable) Auto power off when the privacy shutter is closed. Power is 7-13VDC. (all pwr. adapters and cables included) 1/3" CCD, 330Lines res. 35% better than standard VHS! Can also be used to transmit VCR output to another TV to remote viewing.

SPECIAL, 2.4GHz SONY-ASTROVIEW.....\$189ea. or 2 for \$339
addtl. 2.4GHz TRANSMITTER/RCVR. less Camera...\$129ea.

Events

SEPTEMBER 1999

SEPTEMBER 4

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

CANADA - ONTARIO - CARP - Hamfest. Ottawa ARC, Jim Cummings VE3XJ, 613-446-1225.

E-Mail: fleamarket@oarc.net
Web: http://oarc.net/fleamarket

NM - ALAMOGORDO - Hamfest. Otero County Fairgrounds, US 54 & Fairgrounds Rd. VEC testing. Alamogordo ARC, Larry Moore WA5QNO, 505-437-0145

PA - UNIONTOWN - Hamfest. Uniontown ARC, Carl Chuprinko WA3HQK, 304-594-3779

SEPTEMBER 4-5

NC - SHELBY - Hamfest. Shelby ARC, John Ledford N4GOQ, 704-482-4507.

E-Mail: n4goq@shelby.net
Web: http://www.shelby.net/n4fan

SEPTEMBER 10-11

AR - MENA - Hamfest. Queen Wilhelmina Hamfest Assn., Charlotte Lee KC5DOR, E-Mail: blee@ipa.net. Ray Lively W5DLC, 903-764-5599, E-Mail: raysoft@intrastar.net
Web: http://qwha.intrastar.net

SEPTEMBER 11

AR - MOUNTAIN HOME - Hamfest. Twin Lakes ARC, Miles Waldron N5QMI, 870-492-4466. E-Mail: mpwaldron@centuryinter.net

AZ - KINGMAN - Hamfest. Hualapai ARC, Ron Miller KK6BM, 520-757-3770. E-Mail: rmler@kingman.com Web: http://www.qsl.net/harc-az

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

DE - DOVER - Hamfest. Kent County ARC, Larry Roll K3LT, 302-678-4841. E-Mail: yodoc@aol.com or k3lt@magpage.com

IN - SPENCER - Hamfest. Owen County ARA, Kathryn Smith K9INU, 812-829-2140

ME - WINDSOR - Hamfest. Fairgrounds. AARA, Frank N1ITR, 207-623-9217

MN - RUSH CITY - Hamfest. East Central MN ARC, Larry Jilek KA0MEN, 320-358-4205

MO - COLUMBIA - Hamfest. Good Time Country, 5551 S. Hwy. 63. 8am-2pm. VE Exams. Central Missouri Radio Assn., Nathan Odle KB0NNV, 573-474-9247. E-Mail: nathano@odle-associates.com
Web: http://www.qsl.net/~cmra

NY - BALLSTON SPA - Hamfest. County Fairgrounds. 7am-3pm. VEC Exams. Talk-in: WA2UMX 146.40/147.00 & 147.84/147.24. Saratoga County RACES Assn., Darlene Lake N2XQG, 518-587-2385 E-Mail: lake@capital.net

PA - ERIE - Hamfest. Franklin Twp. Firehall. VE Exams, 9am, Franklin Center Methodist Church, Rt. 98. Talk-in: 146.01/61. Radio Assn. of Erie, Dr. Tom McClain N3HPR, 814-833-1640.

E-Mail: TEM@ERIE.NET
Web: http://www.erie.net/~n3ntj/hamfest.htm

WA - PUYALLUP - Tacoma Electronics Fleamarket. (Pierce County Fairgrounds), Frontier Park, 21718 Meridian Ave. E. 9am-3pm. Talk-in: 147.38+ PL 103.5, simplex 146.58. RCT, Roger 253-475-4293. E-Mail: rtwig@worldnet.att.net
Web: www.mashell.com/~robtee/rct.htm

SEPTEMBER 11-12

FL - MELBOURNE - Hamfest. Auditorium. Platinum Coast ARC, Tim Madden KI4TG, 407-724-9339. E-Mail: ki4tg@msn.com

KY - LOUISVILLE - ARRL KY State Convention. Bullitt County Fairgrounds, I-65 (South 25 min.). Greater Louisville Hamfest Assn., Herbert Rowe W4WQD, 812-282-7007 or 812-948-0037 (commercial), 502-935-7197 or 606-284-9090 (FleaMkt/TailGate) E-Mail: wd4xl@juno.com
Web: http://www.thepoint.net/~glha/

SEPTEMBER 12

DE - FELTON - Hamfest. Kent County ARC, Larry Roll K3LT, 302-678-4841.

E-Mail: W3HZW@hotmail.com

IL - JOLIET - Hamfest. Bolingbrook ARS, Marti Barton KA9ZJJ, 815-436-0559.

E-Mail: mkbarton@flash.net

MA - SOUTH DARTMOUTH - Hamfest. At club. SE MA ARA, Bill K1IBR, 508-996-2969

OH - FINDLAY - Hamfest. Hancock County Fairgrounds. Talk-in: 147.15+, 444.15. Findlay RC, Bill Kelsey N8ET, 419-423-4604.

E-Mail: kanga@bright.net
Web: http://www.bright.net/~kanga/w8ft/

PA - BUTLER - Hamfest. Butler County ARA, Gerald Wetzel W3DMB, 724-282-6777.

E-Mail: w3dmb@aol.com Web: http://www.nauticom.net/www/cliff/hamfest.html

CALENDAR

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

Nuts & Volts Magazine

Events Calendar

430 Princeland Court

Corona, CA 91719

Phone 909-371-8497

Fax 909-371-3052

E-mail events@nutsvolts.com

COMPUTER SHOWS

AGI Shows, 317-299-8827.

E-Mail: info@agishows.com
http://www.agishows.com

Blue Star Productions

612-788-1901.

http://www.supercomputersale.com

Computers And You, 734-283-1754.

www.al-supercomputersales.com

Computer Central Shows

847-412-1900 & 1-888-296-6066.

E-Mail: compcent@megsnet.net
www.computercentralshows.com

Five Star Productions

810-379-3333. E-Mail: jeff@fivestar
www.fivestarshows.com

Georgia Mountain Productions

706-838-4827.

E-Mail: gamtnpro@blrg.tds.net
georgiamountain.com

Gibraltar Trade Center, Inc.

734-287-2000. Taylor, MI.

Gibraltar Trade Center, Inc.

810-465-6440. Mt. Clemens, MI.

KGP Productions

1-800-631-0062, 732-297-2526.

E-Mail: kgp@mail.com

MarketPro, Inc., 201-825-2229.

http://www.marketpro.com

MarketPro, Inc., 301-984-0880.

E-Mail: md@marketpro.com

http://marketpro.com

Narisaam Computer Show

770-663-0983.

E-Mail: narisaam@aol.com

Web: http://www.showsale.com

Northern Computer Shows

978-744-8440.

E-Mail: inquiries@ncshows.com

Web: ncshows.com

Peter Trapp Computer Shows, 603-

272-5008. Web: www.petertrapp.com

HAMFEST@EXIS.NET or Lewis B. Steingold

W4BLO, 757-486-3800

Web: WWW.VAHAMFEST.COM

SEPTEMBER 19

CT - NEWTOWN - Hamfest. Edmond Town Hall,

Rt. 6. 9am-2pm. Talk-in: 146.67. Candlewood

ARA, Jeff Cantor WB3DLG, 203-798-6860.

E-Mail: wb3dlg@earthlink.net

Web: http://www.danbury.lib.ct.us/org/cara/

MA - CAMBRIDGE - Flea at MIT. Albany and

Main Sts. 9am-2pm. Talk-in: 146.52 &

449.725/444.725 W1XM/R PL 114.8 (2A). Nick

Altenbernd KA1MQX, 617-253-3776 (9-5). Web:

http://web.mit.edu/w1mx/www/swapfest.html

MI - ADRIAN - Hamfest. Lenawee County

Fairgrounds. VE Exams. Adrian ARC, Brian

Sarkisian KG8CO, 517-265-1537. E-Mail:

kg8co@lni.net Web: http://www.lni.net/~w8tqe

NJ - TRENTON - Hamfest. Tall Cedars of

Lebanon picnic grove, Sawmill Rd. Talk-in:

146.67-. Delaware Valley Radio Assn., Darryl

Foyuth N2JVP, 609-882-2240.

E-Mail: n2jvp@amsat.org

Web: www.slac.com/w2zq

NY - BETHPAGE - Long Island Hamfair.

Briarcliffe College, 1055 Stewart Ave. 8:30am-

1pm. VE Exams. Talk-in: W2VL 146.85 repeater

(136.5PL). Long Island Mobile ARC, Rich N2WJL,

E-Mail: n8exv@yahoo.com

SEPTEMBER 25

AL - MOBILE - Hamfest. Mobile ARC, Tommy

Thompson KC4OLV, 334-653-9239 or 334-431-

2019. E-Mail: kc4olv@zebra.net

Web: http://www.angelfire.com/al/marc3/

FL - DAYTONA BEACH - Hamfest. Embry Riddle

Aeronautical University Campus, Clyde Morris

Blvd. 9am-5pm. ARRL Exams. Talk-in: 147.150

+600. DBARA, E-Mail: munsey@mindspring.com

Web: http://www.america.com/~dbara/ or http://

www.db.erau.edu/campus/student/club/erara

NJ - MT. HOLLY - Hamfest. Mt. Holly Armory, Rt.

38. 7am-2pm. South Jersey Radio Assn. Joseph

Cramer N2XYZ, 609-268-2135.

E-Mail: n2xyz@sjra.org Web: http://www.sjra.org

NY - HORSEHEADS - Hamfest. Chemung

County Fairgrounds. 6am-3pm. FCC Exams. Talk-

in: 147.96/36, 444.20. ARST, Dave Lewis, 607-

589-7495. E-Mail: info@arast.org

hamfest@arast.org or winterfest@arast.org

WA - WALLA WALLA - Hamfest. Walla Walla

Valley ARC, Jack Babbitt, Sr. WA5ZAY, 509-525-

7003. E-Mail: wa5zay@valint.net

SEPTEMBER 25-26

AK - ANCHORAGE - State Convention.

Anchorage ARC, Rick Marvin KL7YF, 907-277-

Events CALENDAR

E-Mail: arcie@thisistrue.com

Web: <http://www.thisistrue.com/barc.html>

FL - NEW PORT RICHEY - Hamfest. Recreational

Center. 9am-3:30pm. Talk-in: 145.35 & 147.15.

SARC, Mike Whitmore WB8ONY, 727-934-0228

MA - FRAMINGHAM - Hamfest. High School.

FARA, Bev N1LOO, 508-626-2012

MD - BOWIE - FARFEST '99. Prince George's

Stadium, Rt. 301, 1/4 mi S of Rt. 50. 6am (tail-

gate). VE Exams. Talk-in: 147.075 & 146.52.

Foundation for Amateur Radio, Al Brown KZ3AB,

301-490-3188, Mary Morris N4TCI, 703-971-3905.

E-Mail: Al Brown@ix.netcom.com

E-Mail: amateur.radio@hotmail.com

Web: <http://www.amateurradio-far.org>

NC - BUTNER - Hamfest. Falls Lake ARC, Wiley

Ayscue N4NCK, E-Mail: n4nck@bellsouth.net

<http://www.angelfire.com/nc/n4nck/flarc.html>

NY - YONKERS - Flea Market. Lincoln High

School, Kneeland Ave. 9am-3pm. VE Exams.

Talk-in: 440.425 PL 156.7, 223.760 PL 67.0,

146.910, 443.350 PL 156.7. Metro 70cm Network,

Otto Supliski WB2SLQ, 914-969-1053

OH - BEREIA - Hamfest. Cuyahoga County

Fairgrounds. 8am-2pm. VE Exams. Talk-in:

146.73-PL110.9. Hamfest Assn. of Cleveland, Ron

Nichols N8LZA, 1-800-CLE-FEST or 216-999-

7388. E-Mail: info@hac.org

Web: <http://www.hac.org>

OCTOBER 1999

OCTOBER 1

WI - RACINE - Auction. Racine Megacycle Club,

Dennis Doonan W9DAD, 414-552-6RMC.

E-Mail: w9dad@arrl.net

Web: <http://www2.wi.net/~hamradio/auction.html>

OCTOBER 1-2

AR - SPRINGDALE - Hamfest. Northwest AR

ARC, Clarence Morrow KC5UEW, 501-631-9231

OCTOBER 1-2-3

CA - LONG BEACH - ARRL Southwestern

Division Convention. Nate Brightman K6OSC,

562-427-5123.

OCTOBER 2

AK - FAIRBANKS - Hamfest. Arctic ARC, Fred

Brown KL7CUS, 907-452-3452. E-Mail:

fbrown@mosquitonet.com. Jim Movius KL7EGO,

907-452-6347. E-Mail: ajmovius@gci.net

Web: <http://www.aarc.uaf.edu>

CA - SANTEE - ARC of El Cajon Ham, Computer

& Electronic Swapmeet. Santee Drive-in.

619-561-0052

FL - MAITLAND - Hamfest. Bahia Shrine AR

Unit, Cecil Morehouse K4KEN, 407-281-9169

MO - WARRENSBURG - Hamfest. Warrensburg

Area ARC, Keith Haye WE0G, 816-697-3426.

E-Mail: we0g@microlink.net

NJ - LEONARDO - Hamfest '99. Croydon Hall,

Leonardville Rd. east of Hosford Ave. 8am. VE

Exams. Talk-in: 145.485 (-). Middletown Township

OEM & Garden State ARA, Mario Sellitti N2PVP,

732-787-7184. E-Mail: gsara@monmouth.com

Web: <http://www.monmouth.com/~gsara>

NY - SYRACUSE - Hamfest. Pompey Hills Fire

Dept., off Rt. 20. 8am-2pm. Talk-in: 147.90/30.

RAQS, Vivian Douglas WA2PUU, 315-469-0590.

E-Mail: ragsonline@hotmail.com

Web: <http://www.pagesz.net/~rag>

PA - LEWISBURG - Computer, Amateur Radio &

Electronics Show & Flea Market. Silver Moon

Antique & Flea Market Show Area. Rt. 15, 2.3 mi

N of Rt. 45. 9am-4pm. Talk-in: 147.270 Repeater

& 146.52 simplex. Susquehanna Valley ARC,

George Machesic 570-286-2086. E-Mail:

gpmac@netscape.net. Dave Welker k3si@hot

mail.com Web: <http://loveland.dynip.com/svarc>

SC - ROCK HILL - Hamfest. York County ARS,

Haney Howell K2XN, 803-323-4534.

Web: <http://www.ycars.org>

TX - BELTON - Hamfest. Bell County Expo

Center. Temple ARC, Mike LeFan WA5EQQ, 254-

773-3590. E-Mail: hamexpo@tarc.org

Web: www.tarc.org

OCTOBER 3

IA - WEST LIBERTY - Hamfest. Iowa City &

Muscatine ARCs, Bruce Dagel WB0GAG, E-Mail:

wb0gag@excite.com Web: <http://www.netins.net>

t/showcase/mrc/pictures/hamfl.jp

NY - QUEENS - Hamfest. Hall of Science parking

lot, Flushing Meadow Park Corona, 47-01 111th

St. 9am-3pm. Talk-in: 444.200 repeat, PL 136.5,

146.52 simplex. Hall of Science ARC, Stephen

Greenbaum WB2KDG, 718-898-5599.

E-Mail: WB2KDG@Bigfoot.com

PA - WRIGHTSTOWN - Hamfest. Middletown

Grange Fairgrounds, Penns Park Rd. Talk-in:

146.52 simplex. Mt. Airy VHF RC, Mark Schreiner

NK8Q, 610-847-2285, E-Mail: nk8q@amsat.org.

Bob Minch N3XEM, 215-822-0779,

E-Mail: raminch@bellatlantic.net

Web: <http://www.ij.net/packrats/>

OCTOBER 8-9

FL - STARKE - Hamfest. Bradford County

Fairgrounds, US 301 N. Fri: 2pm-8pm, Sat: 8am-

4pm. Talk-in: 145.150-. Bradford Area ARC, Walt

Terrell 904-755-4964 or Tony Spatafore 904-964-

9328. E-Mail: wb2fgl@techcomm.net

Web: www.angelfire.com/fl/arcba/index.html

NH - ROCHESTER - Hamfest. Fairgrounds. Hoss

Traders, Joe Demaso K1RQG, 207-469-3492.

E-Mail: k1rqq@aol.com

Web: <http://www.qsl.net/k1rqq/>

OCTOBER 8-10

CA - BAKERSFIELD - Hamfest. Bakersfield ARA,

Robert Gerner Jr. KB6JFL, 661-588-7065.

E-Mail: w6bar@hotmail.com Web:

<http://members.tripod.com/~w6bar/bar.html>

OCTOBER 8-9-10-11

CA - SAN DIEGO - 17th Space Symposium &

AMSAT-NA Meeting. Duane Naugle KO6BT, 619-

273-4088. E-Mail: ko6bt@amsat.org

Web: <http://www.amsat.org>

OCTOBER 9

CA - FONTANA - Inland Empire ARC Amateur

Radio & Electronics Swapmeet. A B Miller High

School. Bill 909-822-4138 eves

GA - AUGUSTA - Hamfest. ARC of Augusta,

Terry Brown KE4MHN, 706-796-1128. E-Mail:

cookie4u@cheerful.com Henry Arostegui KN4AV,

706-793-1625, E-Mail: kn4av@bellsouth.net Web:

<http://www.gabn.net/kd4ahqweather/arca.html>

WA - BREMERTON - Hamfest. President's Hall,

Kitsap County Fairgrounds. License Exams 10am.

Talk-in: WW7RA repeater 146.620, tone 103.5,

simplex 146.520. North Kitsap ARC, Marcie

Stilwell, 360-697-2797. E-Mail: nkarc@yahoo.com

Web: <http://www.silverlink.net/nkarc>

OCTOBER 9-10

FL - TAMPA - Hamfest. 4050 Dana Shore Dr. Sat

& Sun 9am-3pm. Egypt Temple ARA, George

Dixon 813-933-4350; Len Smith 813-684-4408;

Larry Padgett 813-948-6500, E-Mail: kf4iti@ij.net

TN - MEMPHIS - Memfest '99.

OCTOBER 10

CT - WALLINGFORD - Connecticut State ARRL

Convention. Mountainside Special Event Facility,

High Hill Rd. 9am-3pm. Nutmeg CT Conv.

Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	10	6.67	4.00	39.95	39.95
HP 720C, 722C, 712C, 880C, 890C, 895C 1120C, 1170C	6	10	6.67	4.50	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Apple StyleWriter 2400, 2500						
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs, 1500 (Black)	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200, 3200	15	17	2.67	2.35	39.95	39.95
Compaq IJ700, IJ900, Xerox XJ9C	15	17	2.67	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK	COLOR
	CARTRIDGE	CARTRIDGE
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$12.00	\$19.00
Epson Stylus Color II, IIs	\$14.00	\$19.00
Epson Stylus Color 500, 200	\$14.00	\$19.00
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	\$14.00	\$19.00
Epson Stylus Color 440, 640, 740	\$14.00	\$19.00

- BULK Inks, Refill Accessories
- Glossy card stock & Coated Paper
- School & Government PO's Welcome
- 2 - 3 Day Shipping

Inkjet
Southwest



Quality Inks for:
HP • Epson • Lexmark
Canon • Apple • DEC

Call or see us online!

Monday - Friday
8:30 - 5:30 PST 11:30 - 8:30 EST

www.inkjetsw.com

1-800-447-3469

(480) 668-1069 Fax

(480) 668-0959

Write In 75 on Reader Service Card.

Nuts & Volts Magazine/SEPTEMBER 1999 19

Events CALENDAR

Nutmeg Hamfest Alliance, Gordon Barker K1BIY, 860-342-3258 E-Mail: k1biy@juno.com.
E-Mail: nutmeghamfest@qsl.net
Web: <http://www.qsl.net/nutmeghamfest>
MD - WEST FRIENDSHIP - CARA Hamfest. Howard County Fairgrounds, S of I-70, E of Rt. 32. 8am-3:30pm. VE Exams. Talk-in: 147.135 (-) repeater, 146.52 simplex. CARA, 410-796-2587. Web: <http://www.ocbs-nt-server.umaryland.edu/cara/hamfest.htm>
MI - MASON - Hamfest. Ingham County Fairgrounds. 8am-2pm. Talk-in: 145.390. Central MI ARC & Lansing Civil Defense Repeater Assn., Don Tillison WB8NUS, 517-321-2004. Web: <http://www.qsl.net/cmarc/hamfair.html>
NC - MAYSVILLE - Hamfest. Jo Ann Taylor

WD4JYR, 252-393-2120
OH - LIMA - Hamfest. Northwest OH ARC, Greg Schwark N8WBD, 419-647-6321. E-Mail: gas1950@aol.com
OCTOBER 15-16
MS - BILOXI - Hamfest. MS Coast ARA, Wayne Miller KB5AAU, 228-539-9929. E-Mail: kb5aau@worldnet.att.net Web: <http://www.ametro.net/mcara>
OCTOBER 15-16-17
CA - CONCORD - Pacific Div. Convention. Mt. Diablo ARC, Dick Brown KT6X, 925-676-9048. E-Mail: paccon99@pacbell.net
OCTOBER 16
AZ - TUCSON - Hamfest. OPRC/ARCA, Glenn

Henderson WA7OBG, 520-749-5478. E-Mail: linus@primenet.com
CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052
IL - GODFREY - Hamfest. Community College, River Bend Arena. VE testing. Talk-in: 145.230, 442.225. Lewis & Clark RC, Harold Elmore N9HE, 618-466-1909. E-Mail: n9whh@ezl.com Web: <http://www.ezl.com/~lmiller/lcrr.html>
MT - BOZEMAN - Hamfest. Gallatin Ham Radio Club, Laura Marino Lubner KJ7UN, 406-586-6659. E-Mail: ghrc@bigfoot.com Web: <http://ghrc.webjump.com>
TN - GRAY - Hamfest. Appalachian Fairgrounds, off I-181. Kingsport, Bristol, and Johnson City Radio Clubs, POB 3682 CRS, Johnson City, TN

37602
TX - DENTON - Hamfest. Denton County ARA, Don Mathis KB5YAM, 972-292-1203. E-Mail: dmathis@lsic.net. Web: <http://lsic.net/dhf>
OCTOBER 16-17
FL - PALM BEACH GARDENS - Hamfest. AMARA Shrine Temple, 3650 RCA Blvd. Sat: 9am-4pm, Sun: 9am-2pm. Talk-in: 147.165/147.765. Palm Beach Repeater Assn., Ken Summerell KD4CTG, 561-640-9447. E-Mail: sum@flinet.com
OCTOBER 17
MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XMR PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>
MI - KALAMAZOO - Hamfest. County Fairgrounds. Talk-in: 147.040 K8KZO. Kalamazoo ARC & SW MI AR Team, Charles Burgstahler KA8BLO, E-Mail: ka8blo@net-link.net Web: <http://www.qsl.net/ka8blo/hamfest.html>
OH - ASHLAND - Hamfest. County Fairgrounds, Claremont Ave. 8am-2pm. Talk-in: 147.105+, 71.9PL. Ashland Area ARC, David Fike N8UCA, 419-289-1082, daytime. Mike Stroub KC8LCH, 419-945-2777, nighttime. E-Mail: aaarc@hotmail.com
PA - SELLERSVILLE - Hamfest. NEW Sellersville Fire House, Main St. Bethlehem Pike. 7am-1pm. VE Exams. Talk-in: 145.31 (144.71 input) W3AI repeater. R. F. Hill ARC, Linda Erdman KA3TJZ, 215-679-5764. Web: <http://www.rfhill.ampr.org>
WA - CHEHALIS - Hamfest. The Southwest Washington Fairgrounds. Talk-in: 147.06+ 110.9 pl, simplex 146.46. Chehalis Valley ARS, Jim Kruger KK7AB, 360-748-1930; KK7AB@ARRL.net or Bill Harwell KC7QHJ, 360-748-8086. E-Mail: bharwell@localaccess.com Web: <http://www2.localaccess.com/teaser/cvars/>


OCTOBER 23
LA - LAKE CHARLES - Hamfest. Southwest LA ARC, Dick Rogers WB5TUG, 318-474-7947. E-Mail: hotred@linknet.net
NH - NASHUA - Hamfest. Res Ctr Church, Antique RC, 617-923-2665
OK - ALTUS - Hamfest. Altus Area ARA, Mike Schenkel W5VXU, 580-846-5578. E-Mail: w5vxu@juno.com
OR - RICKREALL - Swap-Toberfest. Polk County Fairgrounds. 9am-3:30pm. Talk-in: 146.86-. Mid-Valley ARES, Bob Boswell, W7LOU 503-623-2513, E-Mail: w7lou@goldcom.com Web: <http://www.teleport.com/~n7lfj/swaptober.htm>
TN - CHATTANOOGA - Hamfest. C. Jordan in E. Ridge. Chattanooga ARC, David Hoffman KE4FGW, 423-877-7398. E-Mail: w4am@qsl.net Web: <http://www.qsl.net/w4am>

OCTOBER 24
IN - LEBANON - Hamfest. Boone County Fairgrounds. 8am-1pm. VE testing. Boone & Clinton County ARC, Sara Lecklitter KB9OEZ, 765-482-9152
MD - WESTMINSTER - Mason-Dixon Computer & Hamfest. Carroll County Ag Center. 8am. VE Exams. Talk-in: 145.410 CCARC Repeater. Carroll County ARC, Wayne Wilson N3UN, 410-795-2556 (ph/fax). E-Mail: k3pzn@qsl.net. Web: <http://www.qsl.net/~k3pzn>
MI - WARREN - Hamfest. Utica Shelby Emergency Comm. Assn. Debby Cokewell KB8YYB, 810-263-0227. E-Mail: cuer@juno.com Web: <http://www.useca.org>
NY - LINDENHURST - Hamfest. Great South Bay ARC, Tom Carrubba KA2D, 516-422-9594. E-Mail: info@gsbarc.org Web: <http://www.gsbarc.org>
PA - GREENSBURG - Hamfest. 8am-2pm. Talk-in: 147.180+. Foothills ARC, Jim Yex WB3CQA, 724-864-6228. E-Mail: jpyex@sgl.net Web: <http://www.geocities.com/Heartland/Acres/7896/>

OCTOBER 29-30
FL - JACKSONVILLE - Greater Jacksonville Amateur Radio & Computer Show. Morocco Shrine Auditorium, 3800 South St., Johns Bluff Rd. Fri: 1-8pm, Sat: 9am-5pm. VE Exams. Greater Jacksonville Hamfest, Woody Parker KF4GSK, 904-743-3121. E-Mail: sbarber@mediaone.net. Web: <http://www.ccse.net/~lrich/hamfest98.htm>
OK - KINGSTON - Hamfest. Texoma Hamarama, Herb Sleeper WB5PHM, 940-855-5820. E-Mail: retmarine@cst.net Web: <http://www.qsl.net/kc5sig/hamarama>

OCTOBER 30
MN - ST. PAUL - Hamfest. The New RiverCentre. 8am-4pm. VE Exams. Twin City FM Club, Dale Reak KB0VCV, 612-687-9535. Web: <http://www.hamfestmn.org>

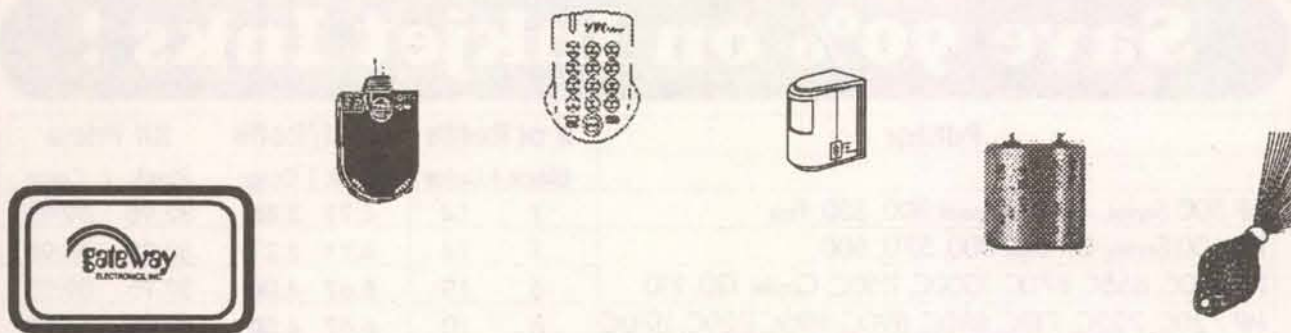OCTOBER 31
IA - DES MOINES - Hamfest. Tikva Tracer ARC, Randall Lees N0LMS, 515-279-4241. E-Mail: hamfestiowa@juno.com Web: <http://www.bestofia.com/hamfestiowa/>



Looking for these and other
clever gadgets?

Try Gateway's Online Ordering

www.gatewayelex.com

Place an order online with our secure server, and get a free gift with your purchase! Simply include the 'free gift' item in your selections, and along with your purchase you will receive a little something extra, just for trying our online ordering system!

*Don't forget to check the box for your
free gift*



8123 PAGE BLVD * ST. LOUIS, MO 63130 * (314)427-6116
9222 CHESAPEAKE DR. * SAN DIEGO, CA 92123 * (619)279-6802
2525 FEDERAL BLVD. * DENVER, CO 80211 * (303)458-5444
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810
FAX ORDERS (314)427-3147

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE * GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS * MASTERCARD, VISA AND DISCOVER ACCEPTED * YES, WE'LL TAKE YOUR CHECK -- SORRY, NO C.O.D.'s * \$10 MERCHANDISE MINIMUM ON MAIL ORDERS * SUPPLY OF SOME ITEMS IS LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * YOU'RE JUST JEALOUS BECAUSE THE VOICES ARE TALKING TO ME AND NOT YOU!



DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209
RT Systems
Amateur Radio Supply
8207 Stephanie Dr.
Huntsville 35802

ARIZONA

Batteries Plus #330
3014 N. Dobson
Chandler 85224
Batteries Plus #334
1155 S. Power Rd. #108
Mesa 85206
Batteries Plus #331
2404 E. Bell Rd.
Phoenix 85032
Batteries Plus #332
3415 W. Glendale Ave. Ste. 4
Phoenix 85051
Batteries Plus #333
1829 E. Southern Ave.
Tempe 85282
Elliott Electronic Supply
1251 S. Tyndall Ave.
Tucson 85713
Power Quality, Inc.
642 E. 39th Pl. Ste. 5
Yuma 85365
Tower Records
3 E. 9th St.
Tempe 85281

AUSTRALIA

DonTronics
P.O. Box 595
29 Ellesmere Cres.
Tullamarine 3043
www.dontronics.com
CALIFORNIA
Abletronics
9155 Archibald Ave. Unit E
Cucamonga 91730
Advanced Computer Products, Inc.
1310 "B" E. Edinger Ave.
Santa Ana 92705
All Electronics
905 S. Vermont Ave.
Los Angeles 90006
14928 Oxnard St.
Van Nuys 91411
Allen's To Go
13461 Hwy. 88
Lockeford 95237
Alltronics
2300-D Zanker Rd.
San Jose 95131
Centerfold International
716 N. Fairfax Ave.
Los Angeles 90046
Del Amo Books & News
3758 Sepulveda Blvd.
Torrance 90505
Electro Mavin
2985 E. Harcourt St.
Rancho Dominguez 90221
Ford Electronics
8431 Commonwealth Ave.
Buena Park 90621
Harding Way News
113 W. Harding Way
Stockton 95204
Harold's Newsstand
524 Geary St.
San Francisco 94102
Hi-Fi Doctor
1814 E. Ball Rd.
Anaheim 92805

HSC Electronic Supply

4837 Amber Ln.
Sacramento 95841
3500 Ryder St.
Santa Clara 95051
5681 Redwood Dr.
Rohnert Park 94928
Hyatt Electronic Surplus
371 N. Johnson Ave.
El Cajon 92020
JK Electronics
6395 Westminster Ave.
Westminster 92683
Laurel Park News
4346 Laurel Canyon Blvd.
Studio City 91604
Lion Electronic Labs
4948 E. Townsend Ave.
Fresno 93727
Netseller
7207 Arlington Ave. Ste. G
Riverside 92503
Op Amp Technical Books
1033 N. Sycamore Ave.
Los Angeles 90038
Panorama Electronics
8761 Van Nuys Blvd.
Panorama City 91402
Sandy's Electronics Supply, Inc.
20655 Soledad Cyn. Rd. #15
Santa Clarita 91351
Sav-On Electronics
13225 Harbor Blvd.
Garden Grove 92643
Sierra Madre Newsstand
55 N. Baldwin Ave.
Sierra Madre 91024
The Red Barn
Hwy. 299
Bieber 96009
Tower Books
211 Main St.
Chico 95928
7840 Macy Plaza Dr.
Citrus Heights 95610
1280 E. Willow Pass Rd.
Concord 94520
630 San Antonio Rd.
Mountain View 94040
1600 Broadway
Sacramento 95818
5950 Florin Rd.
Sacramento 95823
2538 Watt Ave.
Sacramento 95821
Tower Records/Video
220 N. Beach Blvd.
Anaheim 92801
2520 Durant
Berkeley 94704
212 F St.
Davis 95616
5703 Christie Ave.
Emeryville 94608
6310 E. Pacific Coast Hwy.
Long Beach 90803
2280 Market St.
San Francisco 94114
3205 20th Ave.
San Francisco 94132
2525 Jones St.
San Francisco 94133
871 Blossom Hill Rd.
San Jose 95123

Video Electronics

3829 University Ave.
San Diego 92105

CANADA

Corn-West Radio Systems Ltd.
8206 Ontario St. #100
Vancouver, BC V5X 3E3
Muir Communications Ltd.
3214 Douglas St.
Victoria, BC V8Z 3K6

COLORADO

Tower Records/Video
2500 E. 1st Ave.
Denver 80206

CONNECTICUT

Archway News
64 Bank St.
New Milford 06776
Electronic Service Products
437 Washington Ave.
North Haven 06473

DELAWARE

Newark Newsstand
70 E. Main St.
Newark 19711

DISTRICT OF COLUMBIA

Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Alfa Electronic Supply
1502 S. St. Rd. #7
Hollywood 33023
Al's News
8219 S.W. 124th St.
Miami 33156
Astro Too
2854 Sarno Rd.
Melbourne 32935
Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301
Mike's Electronic Distributing Co.
1001 N.W. 52nd St.
Fort Lauderdale 33309
Skycraft Parts & Surplus, Inc.
2245 W. Fairbanks
Winter Park 32789
Sunny's At Sunset, Inc.
8260 Sunset Strip
Sunrise 33322
GEORGIA
Tower Records
3400 Around Lenox Dr. N.E.
Atlanta 30326
HAWAII
SolarWorks!
525 Lotus Blossom Ln.
Ocean View 96737
Tower Records
4211 Waialae Ave.
Honolulu 96816
611 Keeaumoku
Honolulu 96814
IDAHO
The Current Source
5159 Glenwood
Boise 83714
ILLINOIS
Tower Records/Video/Books
383 W. Army Trail Rd.
Bloomington 60108
2301 N. Clark St. #200
Chicago 60614

1209 E. Golf Rd.
Schaumburg 60173

INDIANA

Harbourtown Sales
108 Park 32 W. Dr.
Noblesville 46060

KANSAS

Hollywood At Home
9063 Metcalf Ave.
Overland Park 66212
Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

LOUISIANA

Lakeside News
3323 Severn Ave.
Metairie 70002

MARYLAND

Tower Records/Video
2566 Solomons Island Rd.
Annapolis 21401
1601 Rockville Pike #210
Rockville 20852

MASSACHUSETTS

Newsbreak, Inc.
579 G.A.R. Hwy. Rt. 6
Swansea 02777

MICHIGAN

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124
Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Accurate Instruments
11201 E. 24 Hwy.
Independence 64054
Electronics Exchange
8644 St. Charles Rock Rd.
St. Louis 63114

NEVADA

Amateur Electronic Supply
1072 N. Rancho Dr.
Las Vegas 89106

Less Buster's Electronics
2930 N. Las Vegas Blvd.
VSTG-22
North Las Vegas 89030

RADIO WORLD

1656 Nevada Hwy.
Boulder City 89005
Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102
6450 S. Virginia
Reno 89511

NEW JERSEY

Tech-Systems Electronics, Inc.
1309 Hwy. 71
Belmar 07719

NEW YORK

All Phase Video Security, Inc.
70 Cain Dr.
Brentwood 11717
Computer Warehouse
137 E. Bridge St.
Oswego 13126
Ham Central

3 Neptune Rd.
Poughkeepsie 12601

Hirsch Sales Corporation
219 California Dr.
Williamsville 14221

TOWER RECORDS/VIDEO

105 Old Country Rd.
Carle Place 11514

350-370 Route 110
Huntington 11746

1961 Broadway
New York 10023

383 Lafayette St.
New York 10003

OHIO

Compustuff
241 Great Oaks Trl.
Wadsworth 44281

DIGITAL ONE

7603 Mentor Ave.
Mentor 44060

FOOTSTEPS

4925 Jackson Rd. Store #58
Toledo 43613

HOSFELD ELECTRONICS, INC.

2700 Sunset Blvd.
Steubenville 43952

KEYWAYS, INC.

204 S. 3rd St.
Miamisburg 45342

LEO'S BOOK SHOP

333 N. Superior St.
Toledo 43604

POWERMAXX, INC.

1587 U.S. Route 68 N.
Xenia 45385

OKLAHOMA

Steve's Books & Magazines
2612 S. Harvard
Tulsa 74114

TAYLOR NEWS & BOOKS

133 W. Main, Ste. 102
Oklahoma City 73102

OREGON

News & Smokes

2295 W. Main St.
Medford 97501

News & Smokes #8

259-C Barnett Rd.
Medford 97501

NORVAC ELECTRONICS

7940 S.W. Nimbus Ave. Bldg. 8
Beaverton 97005

960 CONGER

Eugene 97402

1545 N. COMMERCIAL N.E.

Salem 97303

POWELL'S TECHNICAL BOOKSTORE

33 N.W. Park
Portland 97209

TOWER BOOKS

1307 N.E. 102nd Ave.
Portland 97220

PENNSYLVANIA

Bedford St. News

308 Bedford St.
Johnstown 15901

Genes Books, Inc.
King of Prussia 19406

Lehman Scientific
2997 F. Cape Horn Rd.
Red Lion 17356

Tower Books
425 South St.
Philadelphia 19147

Tower Records
340 W. Dekalb Pike
King of Prussia 19406

SOUTH CAROLINA

555 Electronics

5646 Farrow Rd.
Columbia 29203

TENNESSEE

Tower Books

2404 W. End Ave.
Nashville 37203

TEXAS

BDL News, Inc.

809 Pierce
Houston 77002

Electronic Parts Outlet

3753-B Fondren Rd.
Houston 77063

Mouser Electronics

958 N. Main St.
Mansfield 76063

Tanner Electronics

1301 W. Beltline #105
Carrollton 75006

Tower Records

2403 Guadalupe St.
Austin 78705

VIRGINIA

American Computer Clearance

1609 Rhoadmiller St.
Richmond 23220

Tower Records/Video/Books

4110 W. Ox Rd. #12124
Fairfax 22033

1601 Willow Lawn Dr.

Richmond 23230

8389 E. Leesburg Pike

Vienna 22182

WASHINGTON

A-B-C Communications, Inc.

17541 15th Ave. N.E.
Seattle 98155

Bohica Concepts

214 2nd St.
Morton 98356

Cody Books Ltd.

1125 Fir Ave.
Blaine 98230

Service Request

3304 W. Rowan Ave.
Spokane 99205

Supertronix

16550 W. Valley Hwy.
Seattle 98188

Tower Books

10635 N.E. 8th St.
Bellevue 98004

20 Mercer St.

Seattle 98109

WISCONSIN

Amateur Electronic Supply, Inc.

5710 W. Good Hope Rd.
Milwaukee 53223

Greenfield News & Hobby
6815 W. Layton Ave.
Greenfield 53220

Cudahy News & Hobby Ctr.
4758 Packard Ave.
Cudahy 53110

WYOMING
Western Test Systems
2701 Westland Ct. #B
Cheyenne 82001

SCROLLING LED CLOCK

Precision timekeeping clock. Most digital clocks show time in a static four-digit display. This scrolling clock creates an interesting time-piece by presenting the digits in a dot-matrix format and scrolling the time in a ticker-tape fashion. Includes AC wall adapter. Size: 4.5" X 5.5" X 1"

99K002 \$49.00

FUNCTIONALLY CHALLENGED SIGNMAIL UNITS

These units don't work! What you get are three sets each consisting of one 9V, 49.0xxMHz crystal-controlled FM transmitter, and a matching dual conversion narrow-band FM crystal-controlled receiver/tone decoder/signal unit that runs on 6VDC. With documentation.

98Z011 3 for \$10.00

PULSE CAPACITOR

.002uF 36kV high current pulse capacitor. It has 3/8" x 2" flat strap leads. 2.3/4" W x 1 3/4" L x 8/10" T.

99P005 \$49.95 each

Extension Cord and Holiday Light Tester

Indicates location of break in appliance or lamp cords, batteries included.

GVD500 \$2.49

RACK MOUNT CABINETS

High-quality rackmount enclosures come in an attractive charcoal grey epoxy finish. The top, bottom and sides have ventilation holes to assist in cooling. The front and back panels are made of 0.059" thick aluminum for easy custom design. The top, bottom and sides are 0.035" steel. Choose from six sizes. All include handles except RC3120A. All front panels are 19" wide.

RC3120A - 1.5"H x 16.75"W x 9.5"D \$38.00

RC3120B - 3.25"H x 16.75"W x 9.5"D \$46.00

RC3120C - 3.25"H x 16.75"W x 13"D \$53.00

RC3120D - 5"H x 16.75"W x 13"D \$58.00

RC3120E - 5"H x 16.75"W x 16.75"D \$63.00

RC3120H - 8.5"H x 16.75"W x 16.75"D \$83.00

NEC AMPLIFIED SPEAKERS

Use to amplify output of tape or portable radio, or as multimedia speakers. Excellent sound quality for their size. Approx. 30 watts, line out for recording, and earphone jacks. Simple schematics to build your own power supply included. ±15VDC @ 1A. Approximate size: 11"H x 5"W x 5"D.

98V013 \$9.95/pr.

NEC SPEAKERS with POWER SUPPLY SEMI KIT

Provided are the transformer, rectifier, and cable; everything needed to power our NEC speakers (98V013), which are also included.

98V015 \$14.95

NEC SPEAKERS with POWER SUPPLY

Pair of amplified NEC speakers, factory power supply, and cables.

98V016 \$19.95

ROTARY COAXIAL CABLE STRIPPER

For RG-58, RG-59, RG-62 type cables.

97Z025 \$9.95 each

L297 BIPOLAR DRIVER CONTROLLER

Controller chip for bipolar stepper motors. These are solder pulls with trimmed leads. They have tested good.

99S002 \$3.95 each

L298 BIPOLAR STEPPER DRIVER

Drives a bipolar stepper motor. They are solder pulls with trimmed leads. These ICs have tested good.

99S003 \$4.95 each

MINI TOWER POWER SUPPLY

Pulled from unused equipment.

96C009 \$9.95 each

'486 MOTHERBOARD

Comes with a 25MHz 486-SX CPU. Board supports SX25, SX33, DX25, DX33, DX40, DX50, DX2-50, DX2-66, DX2-80. All info silkscreened on board. Seven ISA slots and 2 VESA local buss extensions. Used, tested good. While supplies last...

98C014 \$29.95 each

PELTIER JUNCTION

1-3/16" sq. x 1/16" copper plate soldered to opposite side of module that is soldered to 2" x 3" x 1/2" heatsink.

Nominal Voltage: 12V @ 0.72A. Use to cool Pentium CPUs or devise your own applications. Units may be paralleled for increased capacity. Voltage is reversible and this device can be used to either heat or cool.

98U001 \$19.95 each

24V DIAPHRAGM AIR PUMP

24VDC @ 400mA (max.), Free air 0.3 CFM. Max. pressure approx. 11 lbs. Max. vacuum approx. 20"Hg. Dimensions 4"W x 4 1/2" L x 3 1/2" H.

99U002 \$19.95 each

LONGWAVE ULTRAVIOLET LAMP

Pocket-sized longwave ultraviolet light may be used for detecting invisible inks, minerals in rocks, etc. It's the size of a pocket pager and even has a belt clip to keep it handy. Runs on two "AA" batteries (not included). 3.25"W x 1.75"H x 1"D.

95L007 \$7.95 each

LIQUID CRYSTAL SHUTTER/VARIABLE DENSITY FILTER

0.5" x 1.625" active area. 0% to 23% transmission. Switching rate up to 4 KHz. Specs included.

92L012 Only \$9.95 each

ORANGE LED

T 1 3/4 package, waterclear, 8000mcd.

SE5044J \$0.95 each

14-DAY PROGRAMMABLE TIMER

Originally used to control a satellite receiver through its IR port. Time on/off for eight distinct events. Modify it for your needs or dismantle it for its parts. Programmable with a 2732 EPROM in a removable "personality" module, the unit may be modified to control any IR device through its IR port. Contains Z80 CPU, clock display and associated parts. Operates from 9VDC 500 mA wall transformer which is included.

92V014 \$9.95 each

ATX CASE

Three 5.25" bays, 1 floppy bay, 250W power supply. New. Use with ATX motherboard.

98C033 \$69.95 each

CAMERA GUTS WITH FLASH

Was a 35mm camera! Now, some interesting parts, lens assembly and internal flash unit. Install AA battery to make flash unit functional.

94Z028 3 for \$5.00

LASER PATTERN PROJECTOR

Create dazzling laser light show displays! Our solid state laser kit features a high-tech design that gives you a brilliant laser beam in a compact package at a breakthrough price! This laser is small enough to fit into the palm of your hand and it can be powered by a single 9-volt battery for portable use (battery not included). The kit includes a wall transformer that gives continuous laser power for experiments or light shows.

99K004 \$75.00

REMOVABLE HARD DRIVE

Syquest SO555 44MB removable SCSI cartridge hard drive. (Removed during upgrade)

97C024 \$9.95 each

SOLDERING IRON STAND

Stand for pencil type irons. All metal construction. It is easy to assemble.

SD114 \$2.49

ALPHA SOLDER

1lb spool of .036 diameter, 60/40 rosin core solder.

99Z002 \$9.95

6 METER FSK RECEIVER

Crystal controlled on 50.675 receive frequency. Superhet with 10.7MHz IF. Three ICs and one transistor. Not a kit! New, with schematics and spec sheet for major components.

92A067 \$9.95 each

BOOM MIKE

Electret condenser type. This versatile microphone may be wired for handy-talkie, sound card, telephone, base station, aircraft radio, CB radio, motorcycle intercom, etc. An earphone or miniature speaker may be installed in either or both muffs. The microphone unit can be easily removed and installed on another headset or helmet.

92A001 \$4.95 each

"Semiuniversal" RCA 39-BUTTON REMOTE CONTROL

"Semi-universal" unit works on several products and brands. Just press desired function button and enter the 3-digit code provided. Requires four AAA batteries (not included). Unused.

97V010 \$9.95 each

WALL WART ASSORTMENT

A random selection of wall power supplies with assorted voltages and current ratings.

94E004 10 for \$14.95

2 CHANNEL UHF SWITCH KIT

Uses two button keying UHF transmitter to toggle two relays on/off on a receiver PCB up to 40 meters away. 300MHz to 375MHz transmission frequency set by trimcap.

KIT82 \$47.50

STEPPER MOTOR

400 step/rev. (0.9°/step). NEMA 17 size, 2.5 cm deep, ball bearing, 5mm dia. shaft front and rear. Front shaft has a sleeve pinned to it to make it 7mm dia. by 1.5cm long. Bipolar 70 Ohm coils. Menebea (Japan) P/N 16PY-Q203-01.

96M005 \$4.95 each

BIPOLAR STEPPER MOTOR DRIVER IC

600mA output current capability per channel. 1.2A peak output current (non-repetitive) per channel. Enable facility. Temperature protection. Logical "0" input voltage up to 1.5V (high noise immunity). Internal clamp diodes. With documentation.

L293D \$3.00 each




ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronics.com>

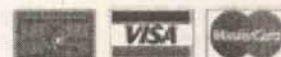(408) 943-9773 - Fax (408) 943-9776

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific
Visa, M/C, AmEx Accepted. All Sales Final.
California Residents Add Sales Tax.
Shipping Additional on All Orders
Prices Subject to Change Without Notice.
Prices Good 60 Days from Date of Publication



Visit our website and
download our catalog.

9909

Put the **Op**eration back in **Op**-Amps

Almost every project today uses an op-amp to amplify analog signals.

The reasons are multiple, as they can perform as gain blocks, they are economical, they have a small package outline, and provide excellent performance. Some manufacturers even supply the op-amp with internal resistors to establish the fixed gains without the external components and lost real-estate.

Today, most op-amps are also frequency compensated to provide stable unity gain and even drive capacitive loads without going into oscillation.

The term op-amp, however, refers to **Operational** amplifiers that were originally designed to perform mathematical operations in analog computers. They can do more than just amplify.

Op-amp circuits routinely employ negative feedback to achieve their performance, and positive feedback is avoided unless one wants to build an oscillator. Generally, the difference between negative feedback and positive feedback is understood as the difference between stability and instability.

There is, however, a large range within these limits. In fact, the designer of op-amp circuits quite often intends to employ negative feedback, and the circuit oscillates. Then the circuit stability must be analyzed and the feedback properly compensated to produce unconditional stability. The compensation is used to alter the phase of the feedback signal as a function of frequency to maintain stability. It is, of course, the phase of the feedback that is referred to as positive or negative.

Circuits can be designed either intentionally or inadvertently that exhibit marginal stability that will ring on the edges of high frequency

pulses or go entirely into oscillation.

The condition necessary for stability is simply that the total phase shift through the amplifier and feedback network must never reach 360° for any frequency where the gain of the amplifier and feedback network is greater than one. Since the inverting terminal of the op-amp produces 180°, the feedback network must provide less than 180° additional phase shift at a loop gain of one. In practice, the phase shift must remain less than 135° to maintain sufficient damping and avoid conditional stability. Nyquist and Bode diagrams are often used to determine the stability criteria and are discussed in most reference books.

The following collection of circuits employ negative feedback, as well as positive feedback to obtain useful parameters. They can be duplicated for testing by any means of construction such as wire wrap, perf-board, or solderless plug-in

breadboards. The circuits were constructed with an FET op-amp (such as the TL082) and the component values listed. The power connections for the TL082 are +15V on pin 8 and -15V on pin 4. The equivalent input circuit is also illustrated, as well as a typical load where applicable.

It should be noted that the Negative Immittance Converter (NIC) circuits utilize about 1K output impedance which limits the current drive and/or voltage swing. It is more difficult to illustrate the AC characteristics such as positive or negative capacitance, whereas the DC characteristics of negative resistance are more easily demonstrated.

Figure 1 illustrates the application of bootstrapping the input bias resistor to achieve high input resistance. A conventional high impedance non-inverting buffer amplifier requires an input resistor from the non-inverting input to ground to furnish a path for its bias currents. If

this resistor is made very large, it will degrade performance by introducing large DC offsets due to the bias current.

On the other hand, if a lower value of bias resistance is used, the input impedance will suffer. An alternate design employs feedback

The term op-amp, however, refers to **Operational** amplifiers that were originally designed to perform mathematical operations in analog computers. They can do more than just amplify.

so that the signal applied at each end of the input resistor is very nearly equal so that the resistance appears much larger. Without C₂, the input resistance is simply R₁+R₂.

With the addition of C₂, the input resistance becomes R₁+R₂+(R₁R₂)/XC₂. Input resistance in this circuit can approach over

Miniature Transmitters and Receivers

2 Button / 3 Channel Transmitter



RF300T

1....\$22.95
5....\$19.95 ea
10....\$16.95 ea


RF300XT

1....\$25.95
5....\$22.95 ea
10....\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

4 Button / 15 Channel Transmitter

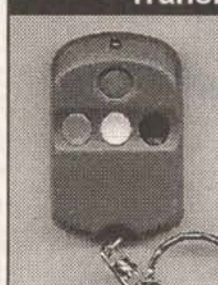

RF304XT

1....\$27.95
5....\$24.95 ea
10....\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

- Magic Props
- Medical Alert
- Monitoring Systems

2-4 Data / 3-15 Channel Receivers



**RF300RL
RF300RM**

1....\$27.95
5....\$24.95 ea
10....\$22.95 ea

**RF304RL
RF304RM**

1....\$29.95
5....\$26.95 ea
10....\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com
Visa / Mastercard, COD

1000 megohms. R_3 is made equal to $R_1 + R_2$ to balance the voltage offsets produced by bias currents in the input terminals of the op-amp, since the bias currents tend to be similar at each input.

Figure 2 illustrates another non-inverting amplifier with the application of judicious positive feedback to cancel out the input capacitance. Such a circuit can be used to cancel the combined effects of transducer capacitance plus those from the shielded input cable.

A typical input circuit might use a piezoelectric transducer such as a sonar receiver. The transducer can be modeled as a high impedance source that is parallel with a large capacitance that limits the frequency response of the transducer. The non-inverting buffer will provide a high input impedance and the addition of negative capacitance at the input can reduce the effects of the internal transducer capacitance to widen the bandwidth. The value of C_1 should be less than $(R_2/R_3) \cdot C_s$ where C_s is the input source capacitance (the inequality is required to maintain some capacity to stabilize the circuit). It should be noted that the techniques of Figure 1 can also

Another useful circuit is the NIC. The NIC can be built in two flavors, namely the Current Negative Immittance Converter (INIC) and the Voltage Negative Immittance Converter (VNIC).

be combined with this circuit to increase the effective resistance of R_1 .

Figure 3 is a related non-inverting buffer that can be used to multiply the value of a capacitor. The effect of R_2 and C_2 is to form a low pass filter at the input of the non-inverting amplifier that is coupled back at its output through R_3 . R_1 is equal to $R_2 + R_3$ to reduce resultant bias current offsets. The effective capacitance is given as $C_2 \cdot (R_2/R_3)$. R_3 is effectively the series resistance

of the multiplied capacitance.

Another useful circuit is the NIC. The NIC is a two port device that has the properties that the impedance connected to one port is the negative at the opposite port. The NIC can be built in two flavors, namely the Current Negative Immittance Converter (INIC) and the Voltage Negative Immittance Converter (VNIC). The two port network of the INIC is illustrated in Figure 4A.

The INIC has equal port 1 and 2

voltages with the currents at port 1 and 2 inverted. The INIC can also be recognized as a current mirror with $k = 1$. When a resistor is connected to port 2, the defined current and voltage designations are constrained to $E_2 = -I_2 \cdot Z_2$. Substituting this expression into the input impedance that is defined as $Z_1 = E_1/I_1$, we find $Z_1 = -Z_2/k$. Thus, the input impedance is related to the negative of the output impedance.

The two port network of the VNIC is illustrated in Figure 4B where the voltages at port 1 and 2 are inverted while the currents at port 1 and 2 flow in the same direction. The current or voltage inversion, of course, can be used to transform positive impedances into negative values. In this case, the input impedance is found to be $Z_1 = -k \cdot Z_2$.

Both the INIC and VNIC are often used in the construction of active filters, but should be recognized as devices that actually generate negative impedance, such as negative resistance, negative capacitance, or negative inductance. Of the two flavors, the INIC is more commonly employed as it is simpler to construct. Although the VNIC is seldom encountered, an example is given later.

Figure 5 illustrates the INIC, where the value of $k = 1$. In theory, the unity gain INIC will give the same results even if the two ports are reversed. In practice, this is not the case, and stability requirements do not permit the ports to be interchanged.

For stability, the requirement is that $V_1 \geq V_2$. The input port 1 is customarily referred to as the open-circuit-stable port (OCS) while the

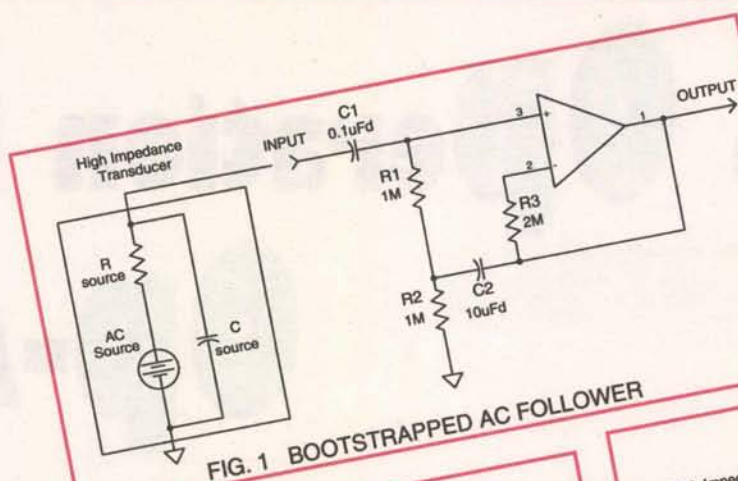


FIG. 1 BOOTSTRAPPED AC FOLLOWER

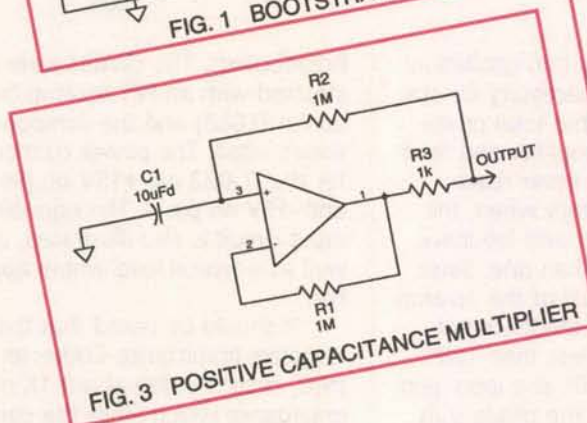


FIG. 3 POSITIVE CAPACITANCE MULTIPLIER

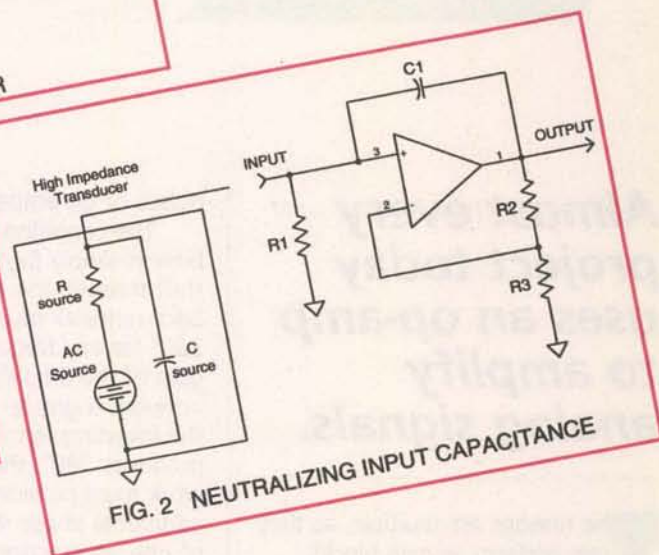


FIG. 2 NEUTRALIZING INPUT CAPACITANCE

AMAZING PRODUCTS!

BOX 716 AMHERST, N.H. 03031

INFORMATION

UNLIMITED adnv699o

VISIT OUR "ACTION" WEB SITE@
<http://www.amazing1.com>

Laser Window Listener

Access Internal Sounds Via A Beam Of Light!!

Remarkably simple concept uses a beam of laser light to illuminate a window acting as a microphone vibrating to the sounds and reflecting back to a sensitive filtered optical receiver that now reproduces this modulated light back into the actual sounds as heard thru a set of headphones.

LWB9 Plans for Three Complete Systems.....\$20.00

Complete System for Demonstration of Concept

LWB60 Demo System with 5mw VisRed Laser...\$159.95

Below Electronics for Two High Performance Infra Red Systems Shown Built From Above LWB9 Assembly Plans

LLR40 Optical Receiver/Processor.....\$199.95

CWL10 10 mw Infra Red Class IIIB Laser.....\$149.95

PLASMA FIRE SABERS

All New Duplicate the Effect Used in the SCI-FI Motion Picture Epic of the Century!!

Visit our web site at amazing1.com and see many Plasma Fire Saber Devices Ready to Use Sabers Parts and Accessories

Patented effect by Robert Iannini

Visual plasma field is controlled by grip pressure and adjusts saber length. No switches are used.

Active energy field produces weird and bizarre effects.

Specify available colors of Photon Blue, Neon Red, Starfire Purple, and Phaser Green.

PFS36K Kit of 36" Active Length....\$79.95

Please add \$20.00 for special handling of above

PFS26K Kit of 26" Active Length....\$59.95

Please add \$10.00 for special handling of above

PFS15K Kit of 15" Active Length....\$29.95

FM Transmitter Kits

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter
- 2 1 Mile+ Phone Transmitter
- 3 Line Powered Phone Transmitter Never Needs Batteries!
- 4 Tracking/Homing Beacon "Beeping Transmitter"
- 5 Video/Audio Rebroadcaster+1 Mile
- 6 TV/FM Radio Disrupter Neat Prank!!! Discretion Required

Includes Tricks Using Wireless Devices

COMBOX Above 6 Kits/Plans...\$59.95

COMBOP Above 6 Plans Only...\$10.00

Kinetic Electric Gun

Pioneer a Futuristic Weapon

500 Joules Energy Storage Constant Current Charging Triggered Spark Switch Ballistic Velocities Handheld, Battery Operated Labeled "Dangerous Product"

EGUN1 Plans.....\$20.00

All Parts are Individually Available

250 KV Tesla Coil

10-14" Explosive Bolts of Lightning! Transmits Energy, Ion Motors Anti Gravity. Size - 20"H x 8" Square Weight - 25 Pounds Input - 115 VAC/2Amps See in "Action" on web www.amazing1.com

BTC3 Plans.....\$15.00

BTC3K Kit/Plans.....\$349.95

BTC30 Ready to Use.....\$449.95

BTC4 Plans 30" Sparks.....\$20.00

Ion Ray Gun

Projects Energy

Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments

IOG7/9 Plans.....\$10.00

IOG7K Kit/Plans.....\$99.95

IOG70 Assembled/Tested.....\$149.95

Higher Powered Device

IOG9K Kit/Plans.....\$129.95

IOG90 Assembled/Tested.....\$199.95

Gravity Generator

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build a small mock space ship from simple materials and use our power supply for energizing. Excellent demonstration of a fascinating method of levitation.

GRA3 Plans with Book.....\$20.00

GRA3K Pwr Sup Kit/Plans/Book.....\$99.95

GRA30 Assembled with Book.....\$149.95

Shock Force Field Vehicle

Object Electrifier

Hand shock balls,wands. Mini circuit is easily hidden Great payback for those wise guys.

SHK1K Kit/Plans.....\$19.95

Attention

High Voltage Experiments Battery Powered Mini Sized Modules For Research In:Hovercraft, Ion Guns, Force Fields, Shockers Etc.

MINIMAX4 4KV@10ma.....\$19.95

500,000 VOLTS!

SIZZLER Produces Explosive Stunning and Stopping Power Intimidatingly Effective to 20' SIZZ500 Complete.....\$79.95

1 800 221 1705 Orders Only! Fax 1 603 672 5406 Information 1 603 673 6493 Free Catalog on Request

Pay by MC,VISA,Cash, Check, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for Proforma

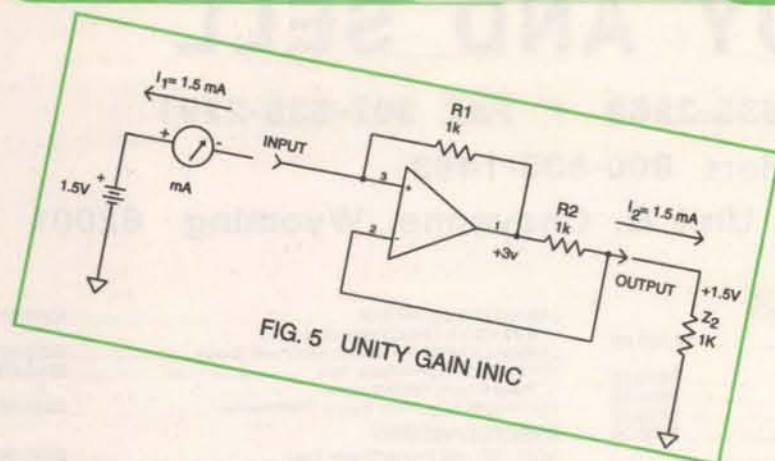


FIG. 5 UNITY GAIN INIC

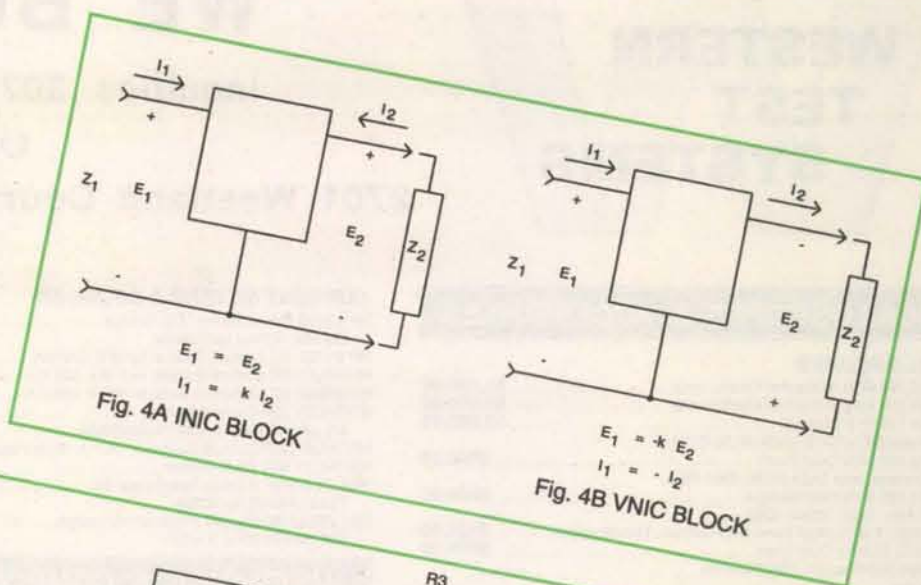


Fig. 4A INIC BLOCK

Fig. 4B VNIC BLOCK

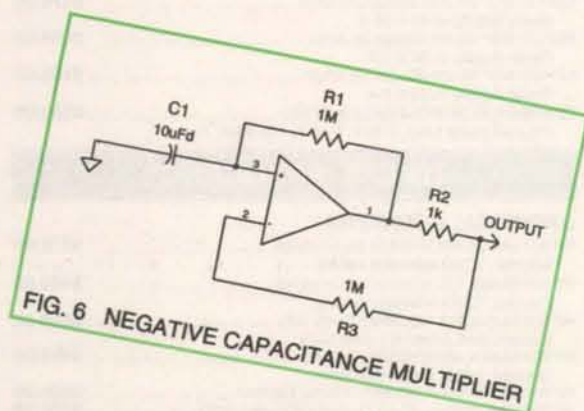


FIG. 6 NEGATIVE CAPACITANCE MULTIPLIER

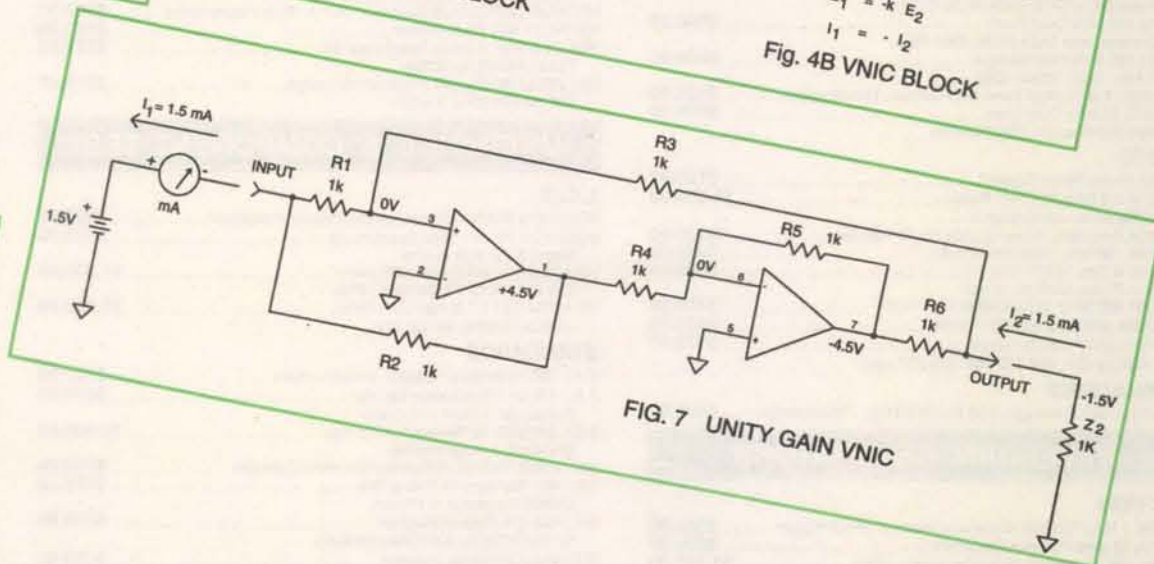


FIG. 7 UNITY GAIN VNIC

output port 2 is referred to as the short-circuit-stable port (SCS). The OCS and SCS port can be easily determined by placing two unequal value resistors on the input and output ports to determine stability. When the smaller value is placed on the SCS port, the op-amp will not reach saturation. Note that the effect of R_2 also gives the INIC a high output impedance that may be loaded by subsequent stages and require additional buffering.

In the example, the input impedance of the INIC is -1,000 ohms. If a +1.5V battery is applied to the input, the circuit will source about 1.5 mA to the battery. A battery is convenient to use in this case as it will maintain +1.5V while sinking current.

It is interesting to measure this effect and convince yourself that the circuit indeed sources current proportional to the applied voltage rather than sinking the current, since this phenomenon is contrary to our normal experiences.

Reversal of the battery will similarly reverse the current flow to maintain negative resistance. A unipolar power supply that can only source current should not be used as the current will continue to

charge the output filter capacitor and the applied voltage will continue to ramp up.

Figure 6 illustrates an INIC used as a negative capacitance multiplier. The negative capacitance presented at the output terminal is given as $-C_1(R_1/R_2)$, where R_3 is again made approximately equal to R_1 to

reduce the effects of bias currents.

Figure 7 illustrates a design of the VNIC that requires two op-amps. The summing point at the non-inverting input of the first stage is drawn correctly and is also a virtual ground. The voltages indicated make it easier to establish the direction of current flow and circuit

operation.

These circuits employ both negative and positive feedback and require some thought, as well as circuit analysis. They can be quite intriguing to electronics students and occupy them for a long time. They can also provide a lot of fun on a rainy day. **NV**

PRINTED CIRCUIT BOARDS

Since 1969

Prototype to Production
Quick • Quality • Service • Price

- Single Sided
- Double Sided
- Multi-Layer
- Surface Mount
- Punch Press Capability
- LPI

QUICK TURN AROUND
COMPLETE IN-HOUSE CAPABILITY

CIRCUIT ETCHING TECHNICS

Since 1969

700 Lee Street
Elk Grove Village
Illinois 60007

Phone: 847-228-1722
Fax: 847-228-1816
Modem: 847-228-6549
Toll Free: 888-657-3827


E-MAIL — CET@MET-NET.COM
WEB ADDRESS —
WWW.MET-NET.COM/USERS/CET

The OCS and SCS port can be easily determined by placing two unequal value resistors on the input and output ports to determine stability.

MORE POWER!


68HC11, 80C51 & 80C166

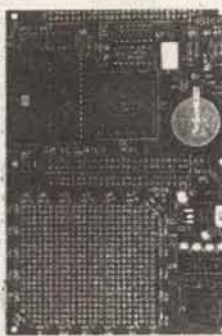AM Research supports over 30 of the most popular Embedded controllers with both **hardware** and **software**.



- ✓ More Microcontrollers
- ✓ Faster Hardware.
- ✓ Faster Software.
- ✓ More Productive.
- ✓ More Tools & Utilities.
- ✓ IIC Peripherals.
- ✓ Single Chip Capable.
- ✓ Outstanding Support.
- ✓ Custom designs.

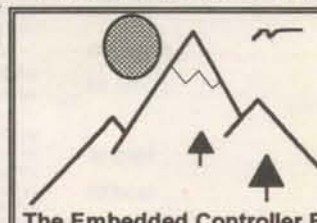Call or email for a free full line brochure



Orders (800) 949-8051
Info (916) 652-7472
fax (916) 652-6642
www.amresearch.com

AM Research, Inc.

PO Box 43

The Embedded Controller Experts

Loomis, CA 95650



WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

OSCILLOSCOPES & ACCESSORIES

OSCILLOSCOPES

TEK 2445 150 MHz 4-channel Oscilloscope	\$1,400.00
TEK 2465 300 MHz 4-channel Oscilloscope	\$2,250.00
TEK 7104 1 GHz 2-Channel Oscilloscope, w/7A29,7A29-04,7B10,7B15	\$3,000.00
TEK 7844 400 MHz Dual Beam Oscilloscope with 7A24,7A26,7B80,7B85	\$900.00
TEK 7904 500 MHz Oscilloscope, with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series	\$325.00
TEK SC503 10 MHz Dual Trace Storage Oscilloscope, TM500 series	\$375.00

PROBES

HP 1122A Probe Power Supply	\$150.00
HP 54701A 2.5 GHz 10X FET Probe, for 54700 series oscilloscopes	\$1,000.00
TEK 1101A Accessory Power Supply, for FET probes	\$200.00
TEK P6046 100 MHz Differential Probe	\$500.00
TEK P6150 9 GHz 10X/3 GHz 1X 50 Ohm Probe, SMA(m) output	\$400.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$250.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW: DC-700 MHz, ST conn.	\$175.00

CALIBRATIONS

TEK SG503 Level Generator, 250 kHz-250 MHz, TM500 series	\$600.00
--	----------

WAVEFORM GENERATORS

FUNCTION

HP 3310B 5 MHz Function Generator, variable phase trigger	\$350.00
HP 3312A 13 MHz Function Generator	\$500.00
HP 3314A-001 20 MHz Function Generator, HP1B	\$1,500.00
HP 3325A 21 MHz Synthesized Function Generator, HP1B	\$1,000.00
HP 3325A-002 21 MHz Synthesized Function Generator, HV output option	\$1,500.00
HP 8165A-002 Prog. Signal Source, 1 MHz-50 MHz, log sweep	\$1,250.00
HP 8904A-001,002,004 Multifunction Synthesizer, DC-600 kHz	\$2,500.00
TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$900.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$1,250.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's	\$275.00
TEK FG501 1 MHz Function Generator, TM500 series	\$225.00
TEK FG502 11 MHz Function Generator, TM500 series	\$300.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$750.00

PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz	\$750.00
HP 214B 10 MHz 100 Vpk Pulse Generator	\$1,200.00
HP 8007B 100 MHz Pulse Generator	\$600.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$600.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$800.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8112A 50 MHz Programmable Pulse Generator, HP1B	\$4,000.00
HP 8115A 50 MHz Dual Channel Pulse Generator, HP1B	\$2,750.00
HP 8116A-001 50 MHz Pulse / Function Generator, burst & log sweep	\$3,900.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series	\$275.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$500.00
WAVETEK 802 50 MHz Pulse Generator	\$300.00

VOLTAGE & CURRENT

VOLTMETERS

FLUKE 845A High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HP1B	\$500.00
HP 3457A 7-1/2 digit Voltmeter, HP1B	\$1,200.00
HP 3478A 5-1/2 digit Voltmeter, HP1B	\$600.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$900.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,250.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,000.00
VALHALLA 2703 AC Volt.Std., 0-120V/10 Hz-100 kHz; 120-1200V/10 Hz-1 kHz	\$1,500.00

VOLTAGE SOURCES

HP 6114A Precision Dual Range Power Supply, 20 V 2 A/40 V 1 A	\$850.00
HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$850.00
KEITHLEY 228 Programmable Voltage/Current Source	\$1,900.00

CURRENT METERS & SOURCES

HP 4140B Picoammeter / DC Voltage Source, without test fixture	\$2,000.00
HP 6177C DC Current Source, to 50 V, 500 mA	\$500.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance	\$500.00
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance	\$800.00
KEITHLEY 614 Electrometer	\$650.00
TEK CT-5 High Current Transformer for P6021/A6302, to 1000A	\$375.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$275.00

IMPEDANCE & COMPONENT TEST

L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
HP 4262A-101 3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz test, HP1B	\$1,500.00
HP 4275A-001 5-1/2 digit LCR Meter, 10 kHz-10 MHz, int./ext. bias	\$3,250.00

STANDARDS

E.S.I. SR-1 Standard Resistor, various values	\$125.00
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step	\$2,000.00
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1432-U 4-Decade Resistor, 0-111.10 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms, 1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-111,100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-N 5-Decade Resistor, 0-11,110 Ohms, 0.1 Ohm resolution	\$200.00
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms, 0.1 Ohm res.	\$250.00

HI & LO RESISTANCE

HP 4328A Milliohmeter	\$1,200.00
T.D.R.	
TEK 1502-opt.04 Time Domain Reflectometer, 0-2,000 feet, chart recorder	\$1,400.00
TEK 1503B-03.04 T.D.R., 0-50,000 ft., chart recorder & battery power	\$3,000.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,400.00

POWER SUPPLIES

SINGLE OUTPUT

HP 6200B Dual Range Supply, 0-20 V 0-1.5 A/0-40 V 0-750 mA CV/CC	\$200.00
HP 6201B 0-20 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6266B 0-10 V 0-20 A CV/CC Power Supply	\$250.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$400.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$550.00
HP 6269B-028 0-40 V 0-50 A CV/CC Power Supply; 230 VAC line	\$900.00
HP 6274B 0-60 V 0-15 A CV/CC Power Supply	\$650.00
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply	\$150.00
HP 6282A 0-10 V 0-10 A CV/CC Power Supply	\$200.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$200.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP 6574A 0-60 V 0-35 A CV/CC Power Supply	\$1,675.00
HP 6672A System DC Power Supply, 0-20 V 0-100 A CV/CC, HP1B	\$2,750.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SORENSEN DCR 20-25B2 0-20 V 0-25 A CV/CC Power Supply	\$550.00
SORENSEN DCR 300-1.25A 0-300 V 0-1.25 A CV/CC Power Supply	\$400.00
SORENSEN DCR 600-0.75B2 0-600 V 0-0.75 A CV/CC Power Supply	\$550.00
SORENSEN DCR 600-1.5B 0-600 V 0-1.5 A CV/CC Power Supply	\$700.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$400.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$600.00
TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00

MULTIPLE OUTPUT

HP 6205C Dual Power Supply, 0-40 V 300 mA & 0-20 V 600 mA, CV/CL	\$300.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$450.00
HP 6236B Triple Output Supply, to +/-20 V 0.5 A & 0-6 V 2.5 A	\$375.00
HP 6237B Triple Output Supply, to +/-20 V 0.5 A & 0-18 V 1 A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$450.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$450.00
KEPCO MPS-620M Triple Output Supply, dual 0-20V 1A tracking & 0-6V 5A	\$250.00

LAMBDA LPD-422-FM Dual 0-40 V 0-1 A CV/CC Power Supply	\$300.00
LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$650.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00

MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
ELGAR 501C/400SD AC Power Source, 45 Hz-5 kHz, 500 VA, 0-135 VAC	\$1,150.00
HP 59501B HP1B Isolated DAC/Power Supply Programmer	\$175.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A	\$400.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5314A-001 100 MHz/100 nS Universal Counter; TCXO reference option	\$275.00
HP 5315A-001 100 MHz/100 nS Universal Counter; TCXO reference option	\$450.00
HP 5315A-002,003 100 MHz/100 nS Univ. Counter; batt. power & 1 GHz C-ch.	\$650.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$550.00
HP 5315B 100 MHz/100 nS Universal Counter	\$500.00
HP 5316A 100 MHz/100 nS Universal Counter, HP1B	\$600.00
HP 5316A-001,003 100 MHz/100 nS Univ. Counter, HP1B, TCXO, 1 GHz C-ch.	\$750.00
HP 5316B 100 MHz/100 nS Universal Counter, HP1B	\$750.00
HP 5370B 100 MHz/20 pS 11 digit Universal Time Interval Counter	\$1,200.00
PHILIPS PM6672/411 120 MHz/100 nS Universal Counter, C-channel 70-1000 MHz	\$450.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$250.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$400.00
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series	\$950.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series	\$275.00

FREQUENCY COUNTERS

EIP 545A 18 GHz Frequency Counter	\$750.00
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5340A 18 GHz Frequency Counter	\$450.00
HP 5342A 18 GHz Frequency Counter	\$1,250.00
HP 5343A-001 28.5 GHz Frequency Counter, OCXO reference	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00
HP 5351B-001 26.5 GHz Frequency Counter, HP1B, OCXO reference	\$4,250.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$3,000.00
HP 5385A-004 1 GHz Frequency Counter, HP1B; OCXO ref. osc. option	\$800.00

STANDARDS

HP 105B Quartz Oscillator, 0.1/1.0/5.0 MHz, battery power	\$1,500.00
HP 5087A-opt.032 Distribution Amplifier, 12 outputs at 5 MHz	\$1,750.00

AUDIO & BASEBAND

SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,200.00
TEK 7L5/L3/R7603 Spectrum Analyzer, 20 Hz-5 MHz, 10 Hz min. res., w/frame	\$1,500.00

DISTORTION ANALYZERS

HP 8903A-001 Audio Analyzer, 20 Hz-100 kHz; rear panel input	\$1,500.00
TEK DA4084 Programmable Distortion Analyzer	\$750.00

RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz	\$450.00
---	----------

OSCILLATORS

HP 3336C Synthesizer / Level Generator, 10 Hz-21 MHz	\$1,000.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$200.00

MISCELLANEOUS

HP 3575A-002 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$850.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$350.00
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$450.00
KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$900.00



90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



KROHN-HITE 3750 LP/HP/BR/BR Filter, 0.02 Hz-20 kHz, 6/12/18/24 dB/oct.	\$600.00
ROCKLAND 852 Dual Highpass/Lowpass Filter, 0.1 Hz-111 kHz	\$900.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series	\$475.00
WAVETEK 716 Brickwall Filter	\$1,500.00

RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$500.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$1,400.00
HP 70620B Preamplifier, 1.0-26.5 GHz, for 70000 series	\$3,900.00
HP 8559A/853A-001 Spectrum An., 0.01-21 GHz, 1 kHz res., w/rackmount frame	\$3,750.00
HP 8568B Spectrum Analyzer, 100 Hz-1.5 GHz, 10 Hz min. res.	\$8,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$7,500.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for 7L13/7L14	\$950.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$1,500.00

NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit, APC7	\$600.00
HP 35676A Reflection/Transmission Test Kit, 5 Hz-200 MHz	\$1,000.00
HP 4195A Network/Spectrum Analyzer, 10 Hz-500 MHz	\$12,500.00
HP 8405A Vector Voltmeter, 1-1000 MHz	\$450.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port	\$650.00
HP 85027C Directional Bridge, 0.01-18 GHz, N(f) test port	\$1,750.00
HP 85044A Reflection/Transmission Test Set, 300 kHz-3 GHz	\$1,500.00
HP 85054A Type N Calibration Kit, for HP 8510 series	\$1,800.00
HP 8756A Scalar Network Analyzer	\$2,500.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$1,200.00
WILTRON 560-98K50 SWR Autotester, 10 MHz-40 GHz, for Wiltron 560 series	\$1,800.00

SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$1,900.00
FLUKE 6060A/AN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB	\$1,500.00
FLUKE 6060B/AB Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res.	\$1,900.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res.	\$4,500.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 840-18 Freq. Multiplier, 18-26 & 26-40 GHz outputs 0 dBm	\$2,750.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$2,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$3,750.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$2,500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$3,750.00
HP 8640B Signal Generator, 0.5-512 MHz, AM, FM, pulse modulation	\$950.00
HP 8656B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., OCXO ref.	\$2,500.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B	\$3,250.00
HP 8660C/86602B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod. w/86635A	\$2,750.00
HP 8660C/86603A Synthesizer, 1-2600 MHz, AM / FM, w/86633B	\$3,250.00
HP 8672A Synthesized Signal Generator, 2-18 GHz, +3 dBm output	\$6,000.00
HP 8673D-H16 Synth. Signal Generator, 50 MHz-26 GHz, AM/FM	\$18,500.00
HP 8673C Synthesized Signal Generator, 2-18 GHz, +8 dBm output	\$9,500.00
HP 8673G-004, 008 Synth. CW Signal Generator, 2-26 GHz, +8 dBm output	\$12,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM/ WBFM Pulse	\$3,500.00

SWEEP GENERATORS

HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$4,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten.	\$1,250.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$375.00
HP 86240C RF Plug-in, 3.6-8.6 GHz, +16 dBm levelled	\$700.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86242D-004, 008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$300.00
HP 86245A-001 RF Plug-in, 5.9-12.4 GHz, +17 dBm levelled	\$600.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$500.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm unlevelled	\$500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$500.00
HP 86290A-004 RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled, rear output	\$1,750.00
HP 86290B-004 RF Plug-in, 2.0-18.6 GHz, +10 dBm levelled, rear output	\$1,850.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$1,250.00
WILTRON 6847M Sweep Generator, 10 MHz-20 GHz, +10 dBm levelled	\$4,500.00

POWER METERS

ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$2,500.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$450.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 435B/8481B Power Meter, 0 to +43 dBm, 10 MHz-18 GHz	\$1,500.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A-022/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz, HP1B	\$1,400.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$500.00
HP 8900D/84811A Digital Peak Power Meter, 10 MHz-18 GHz, 0- +20 dBm	\$2,300.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series	\$350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8	\$1,500.00

RF MILLIVOLTMETERS

BOONTON 92B-opt.05 RF Millivoltmeter, 10 kHz-1.2 GHz, 75 Ohms scale	\$500.00
RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$875.00

AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RES. 1W1000 Amplifier, 30 dB gain, 1-1000 MHz, 1 Watt output	\$500.00
BOONTON 82AD-opt.01A Modulation Meter, AM, FM, 10-1200 MHz, GPIB	\$750.00
ENI 1040L Amplifier, 55 dB gain, 10-500 kHz, 400 Watts	\$2,750.00
HP 11729C-130, 140 Carrier Noise Test Set, AM Noise & Rear Panel Inputs	\$9,500.00
HP 415E SWR Meter	\$200.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms	\$125.00
HP 8406A Comb Generator, 1/10/100 MHz increments, to 5 GHz	\$500.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +8 dBm output	\$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$750.00
HP 8447F-H64 Dual Amp., 25 dB, 0.1-1300 MHz & 28 dBG 9 kHz-50 MHz	\$900.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$2,500.00
HP 8901B-1,2,3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext. LO	\$3,000.00
HP 8970A Noise Figure Meter	\$4,000.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$5,000.00

COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out	\$450.00
BAYTRON 328-300/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
BIRD 4410A/4410-3 Wattmeter, 2-30 MHz, 10 W - 1 kW f.s., N(f/f)	\$400.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
BIRD 8201 500 Watt Oil Cooled Load, DC-2.5 GHz, N(f)	\$350.00
CONTINENTAL MW. RAE28-K-M WR28 x K(m) Endfire Adapter	\$225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$125.00
FXR/MICROLAB SL-03N Stub Tuner, 0.3-6.0 GHz, 100 Watts max., N(m/f)	\$75.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11636A 2-Way Power Divider, DC-18 GHz, N(m/f/f)	\$300.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33321K Programmable Step Attenuator, 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,000.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$150.00
HP 8472A Crystal Detector, 10 MHz-18 GHz, negative polarity, SMA	\$175.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA	\$400.00
HP 8496A-002 Step Attenuator, 0-110 dB, DC-4 GHz, SMA	\$375.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz	\$2,900.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,000.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R532A WR28 Frequency Meter, 26.5-40 GHz	\$500.00
HP R752C WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$450.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$900.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45716H-1000 WR10 Frequency Meter, 75-110 GHz	\$900.00

HUGHES 45721H-1000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$900.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$1,000.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$400.00
HUGHES 45773H-1100 WR19 Thermistor Mount, -20 to +10 dBm, 40-60 GHz	\$650.00
HUGHES 45774H-1100 WR15 Thermistor Mount, -20 to +10 dBm, 50-75 GHz	\$750.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz	\$800.00
HUGHES 45776H-1100 WR10 Thermistor Mount, -20 to +10 dBm, 75-110 GHz	\$850.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$600.00
HUGHES 47741H-2310 WR28 Phase Locked Gunn Osc., 32.000 GHz, +18 dBm	\$2,000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42.000 GHz, +18 dBm	\$2,750.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$375.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(t/m)/SMC	\$200.00
MA-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
MICA C-121S06 Circulator, 17.5-24.5 GHz, SMA(t/m/m)	\$75.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m/f) "NEW"	\$40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$300.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 368BNM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4226-10 Directional Coupler, 10 dB, 0.5-18.0 GHz, SMA(f)	\$275.00
NARDA 4227-16 Directional Coupler, 16 dB, 1.7-26.5 GHz, 3.5mm(f)	\$325.00
NARDA 4242-20 Directional Coupler, 20 dB, 0.5-2.0 GHz, SMA(f)	\$100.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 4247B-10 Directional Coupler, 10 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 562 DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/f)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$165.00
NARDA 768-10, 20 dB or 20 dB Attenuator, 20 Watts, DC-11 GHz, N(m/f)	\$120.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
TRG B510 WR22 Direct Reading z Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
TRG B528 WR22 Direct Reading Phase Shifter, 0-360 deg., 33-50 GHz	\$1,250.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00
HP 3780A Pattern Generator / Error Detector, 1 kb/s - 50 Mb/s	\$1,000.00

COMMUNICATIONS

HP 4935A-001 Transmission Test Set, 20 Hz-110 kHz, battery option	\$700.00
HP 59401A HP1B Bus Analyzer	\$400.00
TEK 1410R NTSC Gen., w/SPG2 sync. generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen., w/SPG12 sync; TSG11 color bars; TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/SPG12, TSG11, TSP11, TSG13, TSG15, TSG16	\$1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

MISCELLANEOUS

FLUKE 2180A RTD Digital Thermometer	\$500.00
HP 7090A Measurement Plotting System	\$1,500.00
KEITHLEY 705 / 2x7055 Scanner	\$400.00
P.A.R. 5206-95, 98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$600.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM508 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$750.00

Questions & Answers

TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

QUESTIONS

Send all material to **Nuts & Volts Magazine**, 430 Princland Court, Corona, CA 91719, OR fax to (909) 371-3052, OR E-Mail to forum@nutsvolts.com

Where can I get HV supplies 0-60KV, 0-10mA variable? I need a source for used induction heaters, water cooled.

9991 Anonymous

I need information on IBM OS/1 server connections. What can be done with it?

**9992 S. Grimm
New Bern, NC**

Any suggestions on how to build a reasonably priced speech synthesis board for our BASIC II based robot? (It seems that the SPO256 chip is near extinct on the market right now.)

**9993 Jack Ivory
New Hartford, NY**

I have a very large and "used to be" useful engineering calculations program "ECALC" written in IBM BASICA. It will not run in Windows or even in DOS on the new Pentium processor computers.

The basic problem is that none of them will run IBM BASICA. Compiling isn't a good solution because the program chains to several sub programs to get around the 64K program size limit of BASICA. It also uses the differences in BASIC

and BASICA so the BASICA is a must.

How can I get IBM BASICA to run on a Windows machine?

**9994 Harvey Cappel
Bayou Vista, TX**

Two years ago, I mounted an electrical window system to my car. The driver's window used to go automatically up or down — a complete course — at a single touch of the button. When the motor was blocked, it was turning itself off automatically, because of the increased current passing through the alimentation system.

Now, this system is broke. I have to keep pushing the button to completely open the window.

Here is my question: I want to make a simple circuit that would keep the motor running until the window opens completely, and then turn it off. Would it be a kind of short-circuit protection? It must not burn the motor!

**9995 Gil Stoian
via Internet**


I have a NEC model #DX-1000U VCR that has encountered a micro-processor failure. I have a complete service manual and have been able to determine some of the damage.

500 mA.

I do have one schematic for the -12 VDC, but I find it a little impractical. There has to be a much simpler way.

I attached the schematic I am talking about.

**Vicken Mouradian
via Internet**

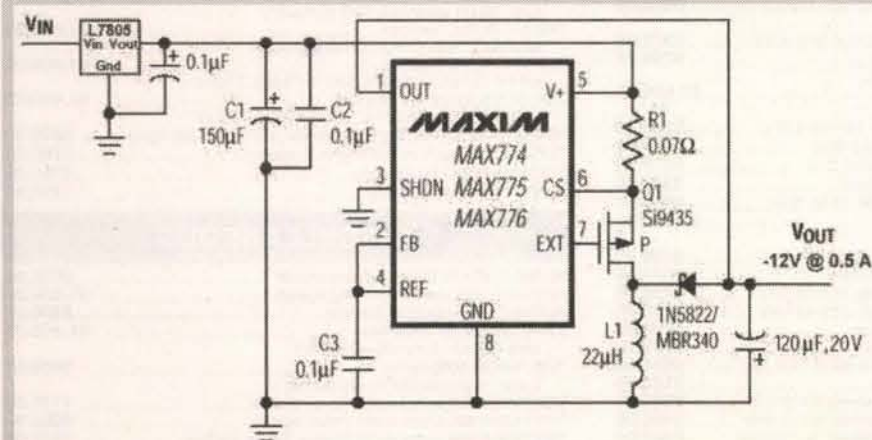

I am looking for a NEC part #PD7516HCW-2-82. The unit is well-built with features that are just not available today.

Can you direct me to someone who can supply me with old NEC parts?

**9996 Anthony Hanudel
Williston, VT**

Do you know of any services, accepted, hacker, or phreaker to remove the [Automatic Number Identification] ANI from calls to 800 or 900 numbers for home-originated telephone calls, functioning similarly to E-Mail's Anonymizer?

Probably the service would redial the calls and then patch them to the original caller. Consider both POTS and Internet phone calls.

Can you supply contacts or addresses?

**9997 Dave English
via Internet**

I am building a robotics platform using two stepper motors for locomotion.

Is there any formula for figuring how much weight a stepper motor can carry, and what about two together?

**9998 Tzvi Frankel
via Internet**

I always thought that the output impedance of an emitter follower was the resistance of the emitter resistor.

I recently built a class A, two-stage single ended emitter follower transistor amplifier to provide a low Z output. Measurements reveal a lot lower impedance than the 100-ohm load resistor would lead me to believe. Am I missing something?

**9999 John Nelson
via Internet**

Where can I get the plans to build a 6 VDC to 12 VDC converter?

I want to install a new radio into an old [1951] six-volt car.

**99910 Douglas Faubion
New Palestine, IN**

I am a university student currently doing a project involving the usage of MC68HC811E2FN52PLCC. I failed to locate the microcontroller

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

in my country (Malaysia).

Can someone give me any guidance on how to get the MCU?

**99911 Jen Wen Chia
via Internet**

I bought a Toshiba T4600C notebook computer at a local hamfest. The power-on password has been set. I have tried disconnecting the CMOS battery (and the clock battery too, for good measure) and left them unhooked for days. The computer still wants a password when I power it up.

Toshiba said to send it back and

TECH FORUM

they'll delete the password for a small fee.

99912 **Sam Roberts**
Kannapolis, NC

I am looking for a way to hook up my Apple Personal Laserwriter NT to my new IBM Clone PC running Windows 98. My Apple Laserwriter has a DIN connection on it.

99913 **Susan Mestres**
via Internet

I am looking for a way to keep my car engine at about 1,000 RPMs while I have my A/C on.

My car idles at about 1K RPMs in neutral and goes down to about 850 RPMs when in drive, at idle, and when I have the A/C on. Also, the RPMs drag even lower than I would like.

With the RPM being this low, it's hard on the engine, and the charging of the alternator stops (drops out) until the RPMs come back up. Usually, I put the car in neutral and give it a little gas to get the RPMs up, until the light changes to green, then it's back to drive again.

I need something like a governor to maintain the RPMs regardless of the load, until I press the gas myself, the governor should engage when my foot is off of the gas pedal, and disengage when I press the gas pedal.

My car is a 1977 Plymouth Fury station wagon (land yacht) with A/C. The engine is a 360CC two-barrel carb., eight cylinder.

Every year, I have to put up with a battery going dead because the alternator drops out at low RPMs and the car also overheats due to slow fan when the RPMs are low.

99914 **Ray Samples**
via Internet

I am looking to use a 556 timer IC and two or more bi-color LEDs in parallel (red, green, or yellow/green).

I tried to do this myself, but it just doesn't work right. I connected the outputs pin 9 and 5 to the LEDs, so that when the timing is right, one output will be low and the other will be high, and flip-flop back and forth (polarity switching) causing the LEDs to blink red and green.

I also want this circuit to start blinking red/green slowly and then get faster and faster until its polarity goes null (both outputs go either +, + or -, - causing the LEDs to go out) then the cycle starts all over again. I have tried this and sometimes it works and sometimes it doesn't. It is unstable.

Can someone tell me how to do it correctly with a schematic?

99915 **Ray Samples**
via Internet

I need to locate a hard drive caddy (the frame/casing which the

hard drives mounts in, and which has the connector which mates with the body of the computer) for a Dell Latitude 433MC laptop.

Dell no longer supports this model, and they were not able to suggest any third-party sources that sell this item.

Any suggestions on vendors that I might be able to purchase this from?

99916 **Mike Kluger**
via Internet

A friend of mine has a restored antique automobile with a six-volt electrical system. He would like a source of 12-volt power for a modern radio.

I have been following your switching power supply articles, but he needs a more robust current than your articles suggest.

I believe he needs approximately 5 amperes at 12 volts. Any supply will do, I just want to help him get some tunes.

99917 **Michael P. Koryciak**
Flint, MI

Where can I find a circuit layout to build my own garage door opener?

99918 **Dave Trefry**
via Internet

Where can I find the color controls for the Zenith D & Z lines? The manufacturer does not make them anymore.

99919 **John Brown**
via Internet

I am looking for a keyboard for an old EPSON ActionNote 500C. The

plastic foil PCB has broken traces, so the enter key and couple of keys around it don't work.

I need this dinosaur for work (modem compatibility reason). Epson doesn't carry old parts and authorized dealers can't get them either. I plugged in an external keyboard, but it's not portable PC anymore.

If someone has this notebook with a broken screen and good keyboard, I'm willing to buy it.

99920 **Dusan Benko**
Brooklyn, NY

I am looking for a circuit design for a ISO-9141-2 to RS-232 converter.

This converter will allow me to see the information coming out of the On Board Diagnostic II system found on all '96 and higher Chrysler and import vehicles.

I believe I can handle the software. Does anyone know of such a circuit?

99921 **Joe**
via Internet

I need a thermo switch normally open at 90%.

99922 **Millard Middleton**
via Internet

ANSWERS

ANSWER TO #89912 - AUG. 1999

Recently, the 1.35-volt KX-625 battery failed in my Olympus OM-1 camera.

Since mercury batteries are no longer commonly available, I am wondering if anyone knows of an adaptive

circuit I could use, perhaps with an externally mounted six- or nine-volt battery?

[I understand some commercial replacements use 1.5-volt silver oxide batteries which snap into some sort of voltage reducing circuit.] Any ideas?

Lack of mercury batteries isn't the problem it used to be. There is actually a new replacement for the 625 mercury cell. Same voltage as before.

This is essential for some higher priced cameras, since using a higher voltage replacement has actually caused damage.

One source for the ZA625PX (zinc air), which replaces the EPX625, V625PX, H-D, PX13, etc. for \$1.95. Call **Wholesale Advantage** at 1-800-574-7253.

The Wein Zinc Air Cell, which costs about \$8.00 and is carried by many camera shops, delivers 1.35 volts and is intended to replace the PX625/13 mercury cells.

Another option is to buy a genuine mercury cell from a Canadian source. **Canadian Quality Concepts**, 101 Fife Rd., Guelph, Ontario, Canada N1H 6X9; They offer the PX625 and PX675 priced at (1-3) \$4.69 US.

Rick
via Internet

ANSWER TO #8995 - AUG. 1999

I have the LabTec CS-150 stereo computer speakers. I need the headphone plug for one wire to play the tape cassette or portable radio.

I also need another small headphone, this one connected to the

Use your PC as a scope and datalogger!

Parallel Port Scope

spectrum analyzer, and digital multimeter



\$79 - \$799

ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333KS/s versions. Great for schools, test depts, etc. Input to Excell! LabView/NT drivers included.

Environmental Logging

record temperature, humidity, etc.



\$129 - \$645

ENVIROMON - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use **TC-08** for most thermocouples.

osziFOX

20MS/s handheld scope



\$129

osziFOX - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

pico
Technology Limited

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See www.saelig.com for Product of the Month!

PC-based Instruments!

TECH FORUM

right speaker from the left amp speaker. I need three in all.

RadioShack has the plugs and cables you need to do this. Take your LabTec speakers down to the nearest dealer, look at the plugs and extension cords they have in stock,

and be sure they fit your speakers.

The plugs you need are fairly common items. You'll be better off buying an assembled shielded cable, with a plug on each end, as the plugs are rather small, and it's difficult to solder the wires onto them.

RadioShack also stocks numerous adapter plugs, which you can use to connect to other standard audio sources, such as RCA type plugs, etc. I've been able to adapt several different audio sources to my computer using this method.

You might also want to hook up a small AM-FM radio, (such as a Sony Walkman) to your computer, using such an adapter cord. This will provide a fairly good sounding radio, using your computer sound system. Just remember, the headphone cord

ANSWERS TO #89916 - AUG. 1999

My Caller ID unit sometimes displays Private or Out of Area. Most of those blocked calls are people trying to sell me something.

There are times that my work, or family living outside my area are trying to call me.

I know that it is possible to get the caller info even though it's blocked or out of the area. I was told the 911 operator and Police can see it. How can I see it too?

#1 Contrary to popular belief, there just isn't any "hidden" Caller-ID data for you to use. It is true that the 911 operator, police, and other agencies can identify incoming calls, but they are not using Caller-ID information.

Instead, they rely on other central office technologies that are not available to the general public. Also, you should be aware that any call to a Toll Free number (800, 888, etc.) is always identified to the called party either on their monthly bills or in real time, since they pay for your "free" call.

Calls placed from telemarketers normally originate from large "call centers" and they do not use standard phone lines. Because of their call volume, they use digital T-1 lines or other similar central office connections that currently do not support Caller-ID. These calls are always marked as Out-Of-Area (same as Unavailable or Unknown).

You will also get the Out-Of-Area message from large corporations, and folks calling from areas that have older central office equipment.

Calls that are received as

"Blocked" are typically from Caller-ID supported lines, but the caller has elected to mask their identity (either on a per-call basis or permanently via their instructions to the phone company). Again, there isn't any secret data that is sent.

There are Caller-ID display boxes that will help you screen callers. I have used the Bel-Tronics Limited #AD100 (\$60.00) and it will automatically answer a "Blocked" call and tell the caller to unblock their number and call back. Although normal calls are not interrupted, unfortunately, so are Out-Of-Area calls.

Ameritech, a midwest telephone service provider, is now offering a nifty service called Privacy Manager. This central office based service interrupts any call that is marked as Out-of-Area/Unavailable/Unknown and requires the caller to identify themselves at the sound of a beep tone. After their name is recorded, you are called in private and asked if you wish to connect the call.

According to an associate of mine that manages a call center, this feature is becoming increasingly popular. Perhaps one day it will be licensed for use in other areas.

The Caller-ID data has been discussed in previous Q & A dialogs, but here is a summary.

The first incoming ring, called the power ring, awakens the Caller-ID display unit. Immediately after the ring (and before the second ring), a BELL 202 type 1200 baud modem signal is sent from the central office. But unlike normal modem communications, the receiving end does not seize the line during the broadcast,

nor does it communicate back to the central office.

Unless the caller has invoked to block it, the directory information is extracted from phone company records and sent about 1/2 second after the first ring. The Caller-ID signal must finish well before the second ring.

For full details, just search the web. Here is one such link: http://www.repairfaq.org/filipg/LI/NK/F_CallerID.html

Thomas Black
Folsom, CA

#2 You cannot get the information you want out of the Caller-ID signals because the central office does not send the information down your analog line.

For example, I think you can successfully *69 a phone number that doesn't show up on your Caller-ID box. Clearly, the central office knows the number to call even though that number does not show up on your Caller-ID display.

Yes, 911 operators get all the information — as do 800 numbers. If you want to know everybody who calls you, then get an 800 number.

Things are different if you have a digital phone line such as an ISDN, PBX, T1, or fractional T1 line. Some of the backbone signalling information may be accessible in these systems (it is the LSB of the eight-bit PCM sample), but accessing and decoding it is a significant chore.

Many years ago, RadioShack had a good technical text on the telephone system that ran several hundred pages. It covered many of the exotic features of the phone system,

such as frames, their format, and their synchronization. If they've kept it up to date, then it should include some information about ISDN and maybe even DSL.

The book was one of a series; maybe Texas Instruments was the original publisher. I cannot find my copy, so I cannot give you a better pointer. The books are not in my 1999 RadioShack catalog, either, so I presume RadioShack no longer sells them.


The intimate details of the telephone system are described in CCITT standards. Those standards describe fax machines, modems, encoding, and switching systems in more detail than most mortals would ever want.

Individual standards are expensive, so find a good university engineering library where you can browse.

If you don't want telemarketers to call you, start getting on Do-Not-Call lists. There is a national list that should stop a lot of calls, but consumer advocates say it doesn't work well.

Whenever a telemarketer calls and tries to sell you something, ask them to put you on their Do-Not-Call list. Then they should not call you back for the next 10 years. You can also ask them to mail you a copy of their written Do-Not-Call Policy. Also check out www.PrivateCitizen.com. For \$20.00 they will shut off 1,500 telemarketing firms; if one of these firms does call you, then you can sue them for \$500.00.

Gerald Roylance
Mountain View, CA

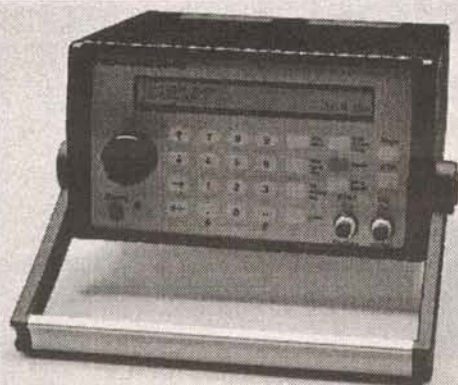

Telulex Inc. model SG-100A

New Features:
✓ 21.5 MHz
✓ .01 Hz steps
✓ multi-unit phaselock

Telulex Inc.

Any waveform you want!

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy!
.01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator


Ramps, Triangles, Exponentials, Noise & more.
0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator

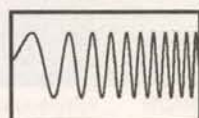
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

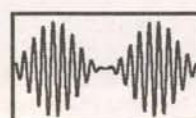


Int/Ext AM, SSB, Dualtone Gen.

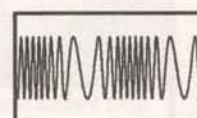


Int/Ext FM, PM, BPSK, Burst

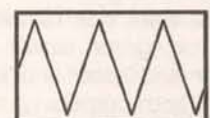


Ramps, Triangles, Exponentials

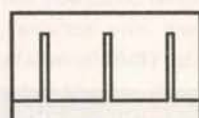


Pulse Generator

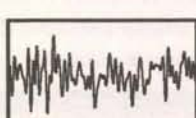

Noise

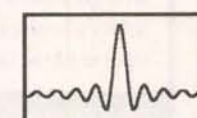

Arbitrary Waveforms

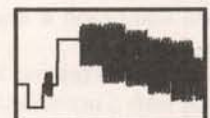

Unlimited Possibilities!

2455 Old Middlefield Way S
Mountain View, CA 94043

Tel (650) 938-0240
Fax (650) 938-0241

<http://www.Telulex.com>
Email: sales@Telulex.com

TECH FORUM

of most of these portable devices also serves as the receiving antenna for the radio, so the orientation of this cord will affect radio reception. (Don't coil it up, or sit a steel cabinet on it, or you won't receive much!)

I've used a RadioShack audio cable — about four-five feet long — to listen to radio, CDs, and cassette players at the office, using my computer speakers. This works really well, when my favorite team is playing on a day when I have to work.

Dwight Johnson
Booneville, MS

ANSWER TO #7998 - JULY 1999
I need to know if the HP Ergo

1024 (D2805A) color monitors are standard SVGA monitors and, if so, the pinout data to make an adapter cable which will take the DB-9 socket to a standard HD-15 male SVGA connector.

Judging from the connector alone, it's either an EGA or CGA monitor.


Although this is not a VGA display, it may be possible to make a cable. (Although all digital signals could not be used by the display and the only resolution supported will probably only be 320x240 or 480x640.)

Continued on page 84

ANSWERS TO #89911 - AUG. 1999
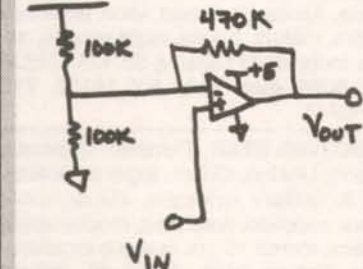
#1 I have a two-axis accelerometer that has an output of 2.5 VDC in the level state. In the pitched up state, the output will go to 2.812 VDC. In the pitched down state, the output will go to 2.188 VDC.

What can I do to increase the voltage swing without changing the 2.5 VDC center? Example: pitch up 3.5 VDC, pitch down 1.5 VDC?



Here is a simple circuit that will amplify the sensor's output by about 10. The gain is proportional to the 470K resistor, so you can adjust the gain up or down by changing that resistor.

There may be some problems with what you want to do. Accelerometers do not measure pitch, so you may have the wrong sensor or the wrong terminology. An inclinometer measures pitch (or roll).

You may also have trouble closing the servo loop. Just matching the sensor signals to the servo motor input voltage does not guarantee a stable loop or good performance.


You may need a lot of gain to minimize the servo error, and then you may have stability problems because the loop is underdamped and sensitive to noise and backlash.

You have a difficult task ahead.

Gerald Roylance
Mountain View, CA
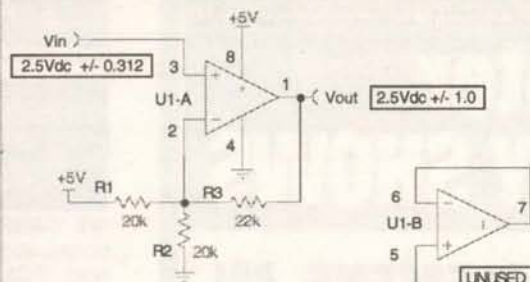
#2 Here is a simple circuit that should convert the voltages for your two-axis accelerometer.

The circuit is a non-inverting amplifier modified to operate off of a single 5-volt supply. The voltage gain of the circuit is $R3 / (R1 // R2) + 1$ (or 3.2 for the indicated resistor values). Note: The symbol " $//$ " means "in parallel with" where $R1 // R2 = (R1 * R2) / (R1 + R2)$.



Parts List

U1	Dual Op-Amp LM358
R1, R2	Resistor 20k
R3	Resistor 22k

For your application, a change of ± 0.312 volts at the input should cause a change of ± 1.0 volts at the output. The DC offset of 2.5 volts is achieved with R1 and R2.

Stephen J. Bitar
Sutton, MA

#3 Your application is well-suited to what is known as a "low-cost, single-supply differential instrumentation operational amplifier."

Analog Devices AD626 is very compact and easy to use. It works off of a single +5V supply, it has a built-in gain of 10X.

To obtain such parts and simple application notes (included in *Designer's Reference Manual*), contact: Analog Devices, 1 Technology Way, P.O. Box 9106, Norwood, MA 02062-9106. Voice: 617-329-4700, Fax: 617-326-8703.

Thomas Ng
San Jose, CA

Go Wireless With Our Modules

SILRX/TXM

SILRX — \$26.00 ea.
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz

AVAILABLE NOW

RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ sales@lemosint.com

All products available in either 418 or 433 MHz

Write in 80 on Reader Service Card.

ALLTECH ELECTRONICS

WWW.COMPUTERCHOPPER.COM

WE CHOP

PRICE\$!

SCSI CD ROM

Matsushita / Apple OEM
PC or Mac SCSI
4x \$19 24x \$79

486 Mini System

486SX25 • Great for Linux
DX266 Upgradable • 2 ISA
Slots • VGA, LPT,
2COMs • FD \$29

250VA Isolation

Transformer
115V Pri - 115V 250VA Sec
Magnetek Triad
6" x 4" x 5" \$39

10" Open Frame SVGA

Metal Enclosed - Displays Up
to 1024 x 768 • 110V AC
Also Available in a
standard case. \$129 \$119

6 SCSI CD's in a Tower

6 CR-504-L
Drives in a SCSI
Tower \$149

Ball Bearing Slide

Drawer Sliders • Extends 2'
Three piece telescopic extension.
See the web for
more detail 6 Pair for \$29

10" SVGA

The same 1024x768 26dp
monitor but with a slight burn in
spot in the center.
Our Pain is Your Gain! \$59

Cellular Data Adapter

For Motorola Flip Phone
and compatible. Use ANY
landline device,
modem, fax, etc. \$39

9" Mono VGA

Small footprint monitor
Great for servers, test benches,
etc. 640 x 480 only.
Refurbished. \$49

9.75" Mono, 8.6" and 10.4" Color LCDs



\$89 & up.

Great for Servers:
ISA Controller Included!!
All screens are 640x480. The
controller supports 256 Colors.

9.75" Mono Passive.....\$89.00
9.5" Color Passive.....\$199.00
10.4" Color Active.....\$319.00

Touch Screen Option
Available.

See our web site
for more details.

Cheaper Ethernet Stuff

Industrial Surplus
PC Parts • Mac Parts

For more information
on these products and
hundreds of other
products check out:

WWW.
ComputerChopper
.Com

760/724-2404
Fax 760/724-8808

Computer Circulation Center, Inc.
2618 Temple Heights Drive
Oceanside, CA 92056

Mon-Fri 9AM-5:30PM - Or see us on the internet.

VISA • Mastercard • Discover • American Express

Prices & Availability subject to change without notice • Government
& Educational PO's Accepted. • Not Responsible for Typographical Errors

Write in 79 on Reader Service Card.

Nuts & Volts Magazine/SEPTEMBER 1999 31

Quality Used Test Equipment

90 DAY WARRANTY Parts & Labor - 10 DAY INSPECTION

HEWLETT PACKARD

11975A, 2-8GHz Amplifier (use w/ 11970 series mixers)	\$1750
214B, 10 MHz Pulse Generator, 200W Pulse/50 ohms	\$975
3325A-2, 21MHz Synth Func Gen, 40Vp-p, HPIB	\$1000
33322H, Prog Attn, DC-18GHz, 110dB range, 10dB steps	\$250
3403C, Digital RMS Voltmeter, 2 Hz-100 MHz	\$200
3421A-201/44462A, Data Acquisition Control Unit, HPIB	\$325
3455A, 6.5 digit Multimeter, HPIB	\$300
3456A, 6.5 digit Multimeter, HPIB, calibrated w/cert	\$450
3465A, 4.5 digit Multimeter	\$75
3478A, 5.5 digit Multimeter	\$400
3488A, Switch/Control Unit	\$400
3852A, Data Acq/Control Unit	\$800
435A, Power Meter w/sensor cable	\$200
436A-02-022, Power Meter w/ sensor cable, HPIB	\$675
4437A, Step Attenuator, 600 ohm, DC-1MHz, 0-119.9dB	\$75
44462A/63A, 8 Chan MUX/2 Chan Actuator (3421A)	\$135
44702A, 13-Bit High-Speed Voltmeter (use w/3852A)	\$375
44711A, 24 Chan FET Multiplexer (use w/3852A)	\$175
44723A, 16-Chan Hi-Speed Sense/Control (use w/3852A)	\$200
44725A, 16-Chan General Purpose Switch (use w/3852A)	\$200
44728A, 8-Chan Relay Actuator	\$200
491C, Amplifier, 2 GHz-4GHz, 1 Watt, 30dB Gain	\$375
5316B, 100MHz Counter, HPIB	\$275
5300A/5302A, 50MHz Counter	\$50
5300A/5303A, 50MHz Counter	\$80
5314A, 100MHz Counter	\$150
5328A-011-020-030, 512 MHz Counter w/DVM, HPIB	\$225
5334A-060, 100 MHz Counter, front & rear input, HPIB	\$400
5334B, 100 MHz Counter, HPIB	\$500
5335A, 200 MHz Counter, HPIB	\$625
5342A, Microwave Counter, 18GHz	\$700
5342A, Microwave Counter, 18GHz, Oven Osc, HPIB	\$1000
6034A, Dig Autoranging Pwr Sup, 60V/10A/200W, HPIB	\$700
6034L, Dig Autoranging Pwr Sup, 60V/10A/200W, HPIB	\$600
6110A (Harrison), Pwr Sup, 3KV @ 6mA	\$200
6253A, Dual Pwr Sup, 0-20V @ 3A	\$275
6255A, Dual Pwr Sup, 0-40V @ 1.5A	\$350
6267B, Pwr Sup, 0-40V @ 10A	\$450
6268B, Pwr Sup, 0-40V @ 30A	\$600
6284A, Pwr Sup, 0-20V @ 3A	\$100
6289A, Pwr Sup, 0-40V @ 1.5A	\$100
6294A, Pwr Sup, 0-60V @ 1A	\$100
6515A, Pwr Sup, 0-1.6KV @ 5mA (cable kit incl)	\$200
69422A, Hi-Speed A/D Card (use w/6940B)	\$200
69501A, Resistance Programming Card (use w/6940B)	\$125
69602A, Timing/Pacer Card (use w/6940B)	\$150
7090A, Measurement Plotting System, HPIB	\$900
8160A, 50MHz Programmable Pulse Generator, HPIB	\$1800
8444A, Tracking Generator, 0.5-1300 MHz	\$350
8447A, RF Amp, 0.1-400MHz, 20dB gain, +6dBm out	\$325
8492A, Attenuator, 10dB or 20dB, APC-7	\$100
85041A, Transistor Test Fixture Kit	\$700
85131D, 3.5MM Test Port Cable Set (new) use on 8515A	\$700
8569B, Spectrum Analyzer, 0.01-22GHz	\$6500

8620C/86290A, Sweep Generator, 2-18GHz	\$1250
8660C/86633B/86603A, 2.6GHz Synth Sig Gen	\$2000
8761B-555, SPDT RF Switch, DC-18GHz (SMA)	\$75
8770A-K01, Sync Sys Interface (use w/8770A Arb Gen)	\$300
8903B-001, Audio Analyzer, 20 Hz-100 KHz, rear input	\$1500
9411B, Switch Controller, HPIB	\$575
E1407A, VX1A/B-C-Size Active Adapter	\$200

TEKTRONIX

013-series, 576/577 Curve Tracer Adaptor Set	\$300
1240-05/(4)D1's, Logic Analyzer w/ (4) P6460 probes	\$750
2465B, 400MHz O'Scope, 4-channel	\$3800
7854, Keyboard Only	\$125
7A24, 400MHz Dual Trace Amplifier	\$225
7A26, 200MHz Dual Trace Amplifier	\$70
7B53A, 100MHz Dual Time Base	\$70
7B92A, 500MHz Dual Time Base	\$150
AM503, Current Probe Amplifier	\$300
P6133, 10X Probe, 150 MHz, use w/2400 series o'scopes	\$70
P6136, 10X Probe, 350 MHz, use w/2400 series o'scopes	\$90
P6452, Data Acquisition Probe (use w/ DAS9100)	\$150
P6460, Data Acquisition Probe (for 1240/1241 Analyzer)	\$150
PG502, 250 MHz Pulse Generator, use w/TM500 series	\$300
TDS460-1M, 350 MHz Digital O'Scope, 4-Channel, extra memory, includes 2 new P6138A probes & manuals	\$4800
TDS540A-1F-1M, 500 MHz Digital O'Scope, 4-Channel, extra memory, 1.44 floppy, 4 new P6139A probes, manuals	\$8500

MISCELLANEOUS

AstroMed ASC902, Medium Gain Amplifier Plug-in	\$100
Bird 10A, Wattmeter Element, 10W, 25-60MHz	\$35
Bird 100A, Wattmeter Element, 100W, 25-60MHz	\$35
Boonton 92BD, RF Millivoltmeter, 10KHz-1.2GHz	\$250
Cal Inst 850T-1, Oscillator Plug-in, 45Hz-10KHz	\$375
EIP 545A-05-08, Microwave Counter, 10 Hz-18 GHz	\$600
EMI SCR150-5-OV, Pwr Sup, 0-150V @ 5A	\$350
Fluke 6010A, Synthesized Func Gen, 10Hz-11MHz, GPIB	\$375
Fluke 8922A, Digital RMS Voltmeter, 2 Hz-11 MHz	\$400
GenRad 1454AH, 4-Decade Voltage Divider	\$50
Heise 711B, Digital Pressure Gauge, 0 to 30 PSI, .05%	\$350
Interface 553, Mil-Std-1553 Analyzer	\$1200
Keithley 614, Electrometer (add \$130 for new 6011 probe)	\$600
Kepco ABC1000M, Pwr Sup, 0-1000V @ 20mA	\$100
Kepco BOP20-10M, Op Amp/Pwr Sup, +/-20V, +/-10A	\$300
Microdyne 1400-MR Telemetry Receiver w/Plug-ins	\$1200
Narda 791FM, Variable Attenuator, 0-35dB, 2-12.4GHz	\$150
Oram Power Supply, 0-270V @ 10A	\$475
PAR 128, Lock-in Amplifier, 0.5Hz-100KHz	\$675
RF Power Labs M102L, RF Amp, 30Hz-100MHz, 2W	\$450
Simco SS-2X, Electrostatic Locator Meter w/case & probe	\$90
Sorensen DCR20-115B, Pwr Sup, 0-20V @ 115A	\$600
Sorensen DCR60-45B, Pwr Sup, 0-60V @ 45A	\$650
Sorensen SRL40-25, Pwr Sup, 0-40V @ 25A	\$475
Valhalla 4440, 3.5 digit DMM / 20 MHz Counter Combo	\$50
Wavetek 178, 50MHz Programmable Waveform Synth	\$900
Wavetek 271-02, 12MHz Pulse/Func Gen, GPIB	\$400

TEST EQUIPMENT PLUS

(520) 575-6967, FAX (520) 575-6936
3331 W. Bright Terrace, Tucson, AZ 85741




Write in 55 on Reader Service Card.

HAM GEAR FOR SALE


WANTED: ROCKWELL-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net

FOR SALE: ORBIT 360 antenna rotator. Full instructions. Never used, \$40 obo. 949-494-0072.

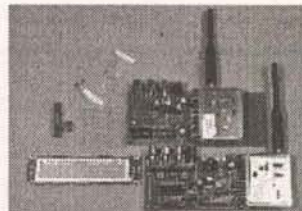LML RADIO & electronics. Let us be your one stop shop for all your radio equipment, test equipment & other surplus needs. Free catalog 909-873-1319 or fax on demand 24 hr. 909-820-1885 & our new web catalog: <http://members.aol.com/hrh6> LML, 424 E. Shamrock, Rialto, CA 92376.



GET FULL control of frequencies from 2.2GHz to 2.7GHz on your existing RF link or Matco transmitters and receivers. These easy-to-assemble kits are fully PIC controlled, have an easy-to-read LCD and store set frequencies in memory. Kits are \$59.95 ea. or \$99.95 ea. pre-assembled. Additional price breaks are available when sold with transmitter and receiver combination. Inquire at: atvcam@excite.com

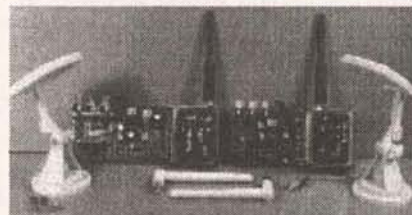

ATV-2400, 2.4GHz 8 channel designed for legal use in ham bands. EZATV, www.4atv.com

50KW RF generators. made by Westenhous. Call Mike, phone/fax: 828-684-7672. [HTTP://WWW.CHIGEOR.COM](http://www.chigeor.com)

HAM GEAR WANTED

CB - SCANNERS

SALES & SERVICE: CB equipment, modification kits, meters, antennas, mics, radios, transistors, repairs & hard-to-find items. Complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492 or RTed821836@aol.com

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. www.cbciintl.com

240+ CHANNEL CB/HAM/COMMERCIAL radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.


SHOOTING STAR, Palomar, Superstar, Galaxy, Uniden, Cobra, exports, police & fire & military scanners, microphones, power supplies, antennas, modifications, repairs, more! 15 yrs. in same location, 5 page picture price sheets \$1 (refundable). Galaxy, Box 1202, Akron, OH 44309. (Also, Red Devil & Messenger Products.)

HALCON COMMUNICATIONS Wholesale only: Cobra, Uniden, Midland, Galaxy, CTE, Super Star, Kenwood, Yaesu, Icom. Free catalog, Free call 1-800-683-6999.

MUSIC & ACCESSORIES

COMPUTER HARDWARE

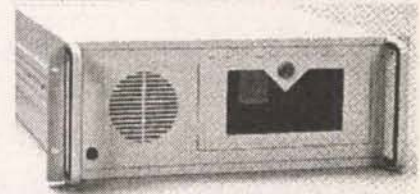WE CARRY a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at www.rogerssystems.com or call 1-800-366-0579.



19" RACKMOUNT ATX PC chassis, \$169 (with ad). 972-242-8087, www.cti-tx.com

PC CABLES: <http://www.cablesusa.com> 100s of hard-to-find new cables and parts, pictures, free technical information. Low prices, RS232, SCSI, keyboard, network, VGA, Cat-5, USB, Firewire, fast secure online ordering & browsing. 954-418-0817.

Gibraltar Trade Center COMPUTER & TECHNOLOGY SHOWS

ATTENTION VENDORS

3 DAY SHOW
FRIDAY
OPTIONAL

\$65⁰⁰

PER 8' TABLE

OVER 200 TABLES

ADMISSION ONLY \$2.00 PER CARLOAD!

- TREMENDOUS ADVERTISING SUPPORT
- IMPRESSIVE CROWDS
- EASY SET UP & TEAR DOWN
- CONVENIENT NEARBY HOTELS

TAKE A LOOK www.gibraltartrade.com

Gibraltar
TRADE CENTER, INC.

MT. CLEMENS, MI

I-94 & N. RIVER RD.
(EXIT 237) • 810-465-6440

TAYLOR, MI

I-75 & EUREKA RD.
(EXIT 36) • 734-287-2000

MT. CLEMENS, MI

SEPTEMBER 24-26, 1999

OCTOBER 15-17, 1999

NOVEMBER 19-21, 1999

TAYLOR, MI

OCTOBER 1-3, 1999

OCTOBER 29-31, 1999


NOVEMBER 26-28, 1999

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.



366MHz PII system with Intel CELERON/A 128K cache MMX CPU, 4.3 gigabyte hard drive, 44X CD-ROM, 1.44 floppy, 32 megabytes SDIMM memory, 8MB AGP 3D video, 56K modem/voice/fax, 32 voice 3D sound, 360 watt speakers, multimedia keyboard, Internet mouse, ATX case, 2 year parts and labor warranty. Only \$499! Installed FULL versions WIN95B \$49, WIN98 \$99, order and find latest prices at **847-657-1160 or www.saveware.com**

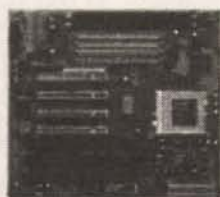NewComputer.com! OVER 50,000 hardware and software products. Orders over \$500 shipped free. Our unique product categories and search features let you quickly locate the item you're looking for. The next time you need computer equipment, try NewComputer.com



366MHz INTEL CELERON/A 128K cache CPU and Pentium II motherboard combo deal, AGP 3D 8MB video, 3D 32 voice digital sound, 1 floppy port, 2 UDMA 66 IDE ports, 56K modem/FAX/voicemail, 3 168 pin DIMM/SDIMM sockets, 2 serial, 1 parallel, 2 USB, PS/2, infrared ports, ATX or normal power, 2 year warranty, only \$179. Order and find latest prices at **847-657-1160 or www.saveware.com**

EVERYTHING NEW w/warranty! Motherboards 400MHz \$165, CPUs \$5, monitors 15" \$125. Pentium systems from \$195. Modems, multimedia kits, scanners, 2.5 gigabytes hard drive \$65. Call 714-778-0450. E-Mail: cci@surfside.net

486 COMPUTERS \$99. Motherboards \$20, 1.44/1.2 floppies, speakers \$10. Call 714-778-0450.

CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. **3 year warranty.** Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in **hi-resolution video/computer CRTs.** T.M.C. 215-226-0749/215-223-0388.

COLORADO BACKUP tape drives, \$35; notebook floppies, \$45; bar code scanners, \$45; thermal wire strippers, \$25; microscopes, \$135. <http://downtown.ala.net/~myoung/flyer.htm> 334-889-4637.

NEW HARDWARE & software, RETAIL: \$1,295, purchase at HALF-PRICE. Contact: kenweger@jps.net The complete Internet solution for small business. Web server for web hosting and Internet access. Easy-to-use software to build a web site. Internet access and E-Mail for a small office. Complete e-commerce solution for selling products over the Internet. For more information: www.encanto.com



181 CHANNEL cable ready computer TV card with capture and remote control \$69. USB port 644x484 pixels color camera \$69. 847-657-1160 or www.saveware.com



SONY PLAYSTATION GAME ENHANCER, mod-chip function plays backup COPY of CD. Simply plug the enhancer in back of playstation! Skips both Sony Logos and uses many cheat codes on bootup! Memory management function, view video/movie files from CD, \$29. Quantity prices available. 480 block memory card \$39. 847-657-1160 or www.saveware.com

LOW-COST 12-BIT A/D KITS. \$59 LPT: Analog! PC printer-port interface acquires 8 analog signals. Also features two 12-bit D/As, current sources for sensor excitation and digital I/O lines. QuickBasic and VB software included. 1-channel A/D only \$39. <http://www.tgn.net/~adnav/> or E-Mail: adnav@tgn.net

COMPUTER SOFTWARE

MICROSOFT OFFICE97 Professional Edition. New factory sealed, unopened. CD only. **WORD, EXCEL, POWERPOINT, OUTLOOK, and ACCESS** included. CD only. **ONLY \$49.95! FREE SHIPPING!** Quantity discounts available. brucesullivan@msn.com

QuikSwitch™

REMOTE CONTROL TV A/B SWITCH



CONTROLLED BY ANY TV REMOTE!

QuikSwitch solves the big problem with remote A/B switches - the need for a separate A/B remote. Thanks to its patented infrared receiver, QuikSwitch gives virtually any TV/VCR/CABLE/SAT remote the power to switch between A & B video sources! Switching is accomplished simply by holding down any button on any infrared remote for 2 seconds. A button such as "0" or "STOP" is used, one that won't cause unwanted operation of the TV/VCR/etc. Volume control adjustments of over 2 seconds may be "pulsed" to avoid accidental A/B switching. QuikSwitch has color coded A/B indicators, and runs for a full year on 2 "AA" alkaline batteries (not included). No AC outlet required! What's more, QuikSwitch is a top quality RF device, highly immune to crosstalk and signal leakage for the best possible TV picture. Time to upgrade that old A/B switch!

SPECIFICATIONS:

BANDPASS:	50 to 1000 Mhz	CONNECTORS:	3 "F" type (R.F.)
INSERTION LOSS:	1 dB typical	CIRCUITRY:	All solid state (no relay)
VSWR:	1.5 typical	AC/DC PASSIVE:	No
INGRESS SHIELDING:	> 90 dB typical	POWER SUPPLY:	3 VDC ("AA" x 2)
A TO B ISOLATION:	> 90 dB to 300 Mhz > 75 dB to 550 Mhz > 60 dB to 800 Mhz	BATTERY LIFE:	Alkaline 1 yr, Lith 3 yrs
		SIZE:	5 1/2" x 2 1/2" x 7/8"
		WEIGHT:	1/2 pound

Verified to comply with Part 15 of the FCC Rules for use with cable television service.

Autumn Special!

\$19.95

**3/\$50
10/\$140**

Shipping Charges Additional - 30 Day Money Back Guarantee - One Year Warranty



MILESTONE PRODUCTS
P.O. Box 30789 - Columbus, OH 43230
1-800-831-0184



ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT

Visit www.alfaelectronics.com for complete info

Call **1-800-526-2532** for Order and Free Catalog

DMM	POP/COUNTER	TRUKE	SPECIALTY
DMM-895 (\$179.00): true rms, AC/DC (V,A), Ω , bar graph, freq, capac, dBm, logic, diode	CAP-15 (\$49.95): 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution, zero adjustment	12B \$94.95 70-III \$99.00 73-III \$125.00 75-III \$155.00 77-III \$173.00 79-III \$195.00 87-III \$325.00 92B-III \$1,445 96B-II \$1,695 99B-III \$2,095	AC Current Probe \$34.95 DC/AC Current Probe \$79.95 Mini AC Clamp \$59.95 AC Clamp w/temp \$89.95 DC/AC Clamp \$109.95 Thermometer \$69.95-\$89.95 IR Thermometer \$189.95 Sound Level Meter \$169.95 Tachometer \$169.95-\$219.95 EMF Tester \$69.95 Pressure Meter \$299.95 Watt Meter \$129.95 High Voltage Probe \$59.95 pH Meter \$79.95 Light Meter \$79.95-\$89.95
DMM-23T (\$99.95): 4 1/2 digit, true rms, high resol. (10 μ V, 10nA, 10m Ω), hFE, diode, contin.	LCR-24 (\$119.95): 0.1 μ H-200H, 0.1pF-2000 μ F, 0.01 Ω -20M Ω , diode test. New Model	FC-1200 (\$129.95): 1.25GHz counter Handheld, 8 digits display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (440MHz)	
DMM-20 (\$74.95): AC/DC (V,A), Freq, cont., Capac, Induct., Ω , hFE, diode, duty cycle	LCR-131D (\$219.95): autorange, 0.1 μ H-10kH, 0.1pF-10mF, 1m Ω -10M Ω , Q Factor, serial/parallel, 120Hz/1kHz testing mode		
DMM-122 (\$59.95): DC/AC(V,A), Ω , hFE, diode, capacitance, freq, logic, continuity			
DMM-123 (\$44.95): DMM + capacitance, DC/AC(V,A), Ω , hFE, diode, continuity			
DMM-10 (\$19.95): 3 1/2 digit, DC/AC V, Ω , hFE, diode, signal output (+3V, -0.5Vsq, 50% duty)			

DC POWER SUPPLIES		FUNCTION GENERATOR		BENCHTOP DMM
20 MHz Scope	100MHz Cursor	Triple Output	Single Output	Programmable
OS-620 \$304.95 • Most economical scope • Dual CH X-Y operation • 1 mV/div sensitivity • Z-axis input, CH1 output • TV syn, ALT trigger • 2 probes (x1, x10)	OS-6103 \$1199.95 • Cursor Readout a meas • Dual CH / Delay sweep • 10 panel setting memory • Time base auto-range • Z-axis modulation input • 2 probes (x1, x10)	• 2 variable out 0-30V, 0-3A • One fixed 5V, 3A output • Auto track, serial, parallel • Const. volt, current mode • 4 analog or 2 digital display PC-3030D (\$499.95) digital	• Const voltage, current mode • Voltage regulation $\leq 0.01\%$ • Current regulation $\leq 0.2\%$ PS-1830 (\$198.95) 18V/3A PS-1850 (\$214.95) 18V/5A PS-1830D (\$214.95) 18V/3A PS-1850D (\$244.95) 18V/5A	• Auto serial/parall. (PPT ser) • Auto track (PPT series) • IEEE-488.2 and SCPI compatible command set PPS-1860G (\$1,149.95) 18V/6A PPS-3635G (\$1,499.95) 36V/3.5A PPT-1830G (\$1,499.95) 18V/3A PPT-3615G (\$1,499.95) 36V/1.5A
		FG-8015G (\$157.95) • 0.02Hz-2MHz • Sine/Sqr/Tri/Pulse/Ramp FG-8020G (\$209.95) • 0.02Hz-2MHz w/counter FG-8050 (\$449.95) Sweep • 0.05Hz-5MHz w/counter • INT/EXT AM/FM mod		DM-8034 (\$179.95) 3 1/2 dgt • AC/DC(V,A), Ω , diode DM-8040 (\$339.95) 3 1/2 dgt • ACV to 50kHz, true rms DM-8055G (\$889.95) 5 1/2 dgt • 0.006% accuracy, GPIB • dBm, auto, REL, min/max

ALFA ELECTRONICS
P.O. BOX 8089
PRINCETON, NJ 08543-8089

TEL: (800) 526-2532 / (609) 897-1135
FAX: 609-897-0206
E-mail: sales@alfaelectronics.com

Call / Write / Fax / Email for FREE CATALOG
Visa, MC, AMEX, COD, PO Accepted. OEM Welcome.
1 Year Warranty (2 Years for GW/Instek)

Y2K COMPLIANT SOLAR POWERED / DYNAMO AM/FM RADIO

This radio is great for emergencies, camping, vacation travel, remote living, etc. It does not require batteries to operate because it has built in nicad rechargeables that can be recharged by the sun or a built in hand crank. The sound from the built in speaker is good quality and has room filling volume. These are blue in color and feature a tuning LED, power LED, charge switch, built in dynamo crank, built in solar panel, AM/FM switch, tuning control knob, volume control, carry strap, built in extendable antenna and a battery compartment for 2AA batteries (not included and not needed-for backup use only). Brand new in retail box-nothing else to buy. Makes a great gift for anyone!

G1539 \$29.95 ea.



50FT ALL-WEATHER MARINE POWER CORD

High quality 3 conductor grounded 14 gauge heavy duty blue power cord made by West Marine Dockmates™. Repels moisture, is abrasion resistant and resists deterioration from the sun. Flexible high quality power cord for all dock-side power needs is rated AWG 14/3 SJTW-A 15amp 125V. Has 3 prong male on one end and 3 prong female on other. Brand new!

G1540 \$15.95 ea.

SMALL 12VDC 10AMP RELAY

Small 12VDC relay by MSD Inc. features SPST 10amp 250VAC contacts. Size only 3/4" L x 3/8" H x 15/32" W. Sealed case. Brand new high quality.

G1541 \$1.95 ea.



DELUXE EQUIPMENT HANDLE

Small blue insulated grip equipment pull handle. Features a 1/4" Dia. metal stud to mount onto your equipment. Total length is approximately 2 1/4". Brand new, very high quality!

G1542 \$2.00 ea.



METAL LOCATOR COIL ASSEMBLY

This is the coil head assembly from a small metal locator. It consists of a 7 1/16" plastic head which has a coil assembly inside connected to a 4 lead + shield flexible insulated cord. Head has a 16" aluminum pole attached by means of a wing nut. Sorry, no specs or data available. Removed from new equipment by a manufacturer who only wanted the metal locator main circuit board and case.

G1543 \$6.00 ea.



AB MOD POT®

High quality Allen Bradley Mod Pots® with standard panel mount 3/8" bushing and panel mount nut. Features screwdriver, adjust shaft and gold plated pins for hookup. AB part # 70MIN024S.

Model 70MIN024S103U (10K) G1544 \$1.00 ea.

Model 70MIN024S104A (100K) G1545 \$1.00 ea.



SCHAFFNER FN2080-12-06 LINE FILTER

High quality heavy duty EMI filter is rated 110/250VAC 50-60Hz@12Amps. Brand new. Size is 1 1/8" x 2 3/16" x 1 3/4".

G1546 \$3.49 ea.



GIANT T03 HEAT SINK

Perfect for high power audio amplifiers and high power transmitters or power supplies. Made of solid anodized (gold color) aluminum. Size is 8" Long x 4 3/4" Wide x 1 1/4" Thick. Predrilled for 6 T03 metal case semiconductors. Brand new!

G1547 \$10.00 ea.



RING SHAPED RARE EARTH COBALT SUPER MAGNET

This 1 1/16" Dia O.D. with 3/16" Dia. I.D. Super Magnet is only 1/16" thick yet is very powerful for its size. Worth much more than our price!

G1548 \$1.50 ea.



Write in 58 on Reader Service Card.

CAM & MOTION SW/HW: Z-trace, PCB toolpath. Plotcam motion control, step drivers. www.megabits.net/ddt MSG/ FAX 407-452-7197, 407-459-2729. Heater@megabits.net

LIQUIDATION WIN 95/98, Office suites \$10-69. Windows tutorials \$5, grabbag 10 compact disks \$10. Computer books 60% off list. 714-778-0450.

GCODE95 For Windows 95/98/NT. Reads AutoCad DXF files and converts data to GcodeMcode RS274. Writes DXF files or ASCII. RS 232 serial connection to machine tool. Full function editor and 3D graphing. For milling, turning, flame-cutting, etc., easy to customize for almost any machine. Download a free trial copy. <http://members.aol.com/andrewc119/index.htm> E-Mail: andrewc119@aol.com

FORBIDDEN SUBJECTS³ hacking CD-ROM \$12 postpaid. Free troubleware diskette catalog. Amazing subject matter. No commercial or shareware here, just lots of technical fun! Peregrine Dynamics, 720 Portage Trl., Cuyahoga Falls, OH 44221-3035.

FREE IBM DISK CATALOG of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE <ASP>**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. momnpop@gate.net

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

WANTED: HPI5C calculators. Will pay. Call Hugh Adams 850-864-2414.

WANTED: TERMINALS + PRINTERS: DEC, Wyse, IBM, ADDS, Okidata, Data South, Epson, C.I.TOH, etc. Call for quote on any surplus computer equipment. Call Jeremy, 603-673-8077.

HP CALCULATORS wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, rkmorrow@aol.com

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

TEST EQUIPMENT

POWER SUPPLIES: EMI TCR 10S90, \$200; EMI TCR 150S7, \$250; EMI TCR 40S25, \$250; Fluke 4216A, \$150; Fluke 4265A, \$200; Fluke 4265A/GPIB, \$250; HP 6186C, \$300; HP 6265B, \$150; HP 6267A, \$250; HP 6268B, \$450; HP 6274B, \$550; HP 6299A, \$100; HP 651B, \$85; HP 6521A, \$500; Lambda LK351FM, \$250; Lambda LK362, \$350; Sorenson SRL60-35, \$400. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

MORE INEXPENSIVE NEW ARRIVALS. HP 8656A, \$500; HP 8447D/010, \$550; TEK PS2520G, \$500; HP 8447A, \$250; HP 436A, \$500; HP 85046A, \$2,250; HP 54600B, \$1,800; HP 853A/8558B, \$2,000; HP 141T/8552B/8553B, \$1,000; HP 8444A, \$250; CAL INSTR 501TC W/849 OSC, \$1,500; BOONTON 92B, \$350; HP 86603A, \$875; HP 54201A, \$900; HP 5370A, \$350; HP 5345A, \$200; FLU 2175A, \$100; FLU 1953A, \$100; WAV 1038, \$500; HP 3400A, \$100; HP 5340A, \$500; HP 3580A, \$500; HP 16510B, \$100; EFRATOM BALL M-100 (NEW), \$1,500; EIP 351D, \$500; ETC., ETC., ETC. **TRU CAL INT'L**, ISO 9002 & A2LA ACCREDITED CALIBRATION LABORATORY. CALL 1-800-681-5540 OR 630-238-8100 FAX: 630-238-8101. E-MAIL: trucal@aol.com

TEK TM500: AM502, \$100; AM502/A6302, \$650; DC503A, \$100; DC504, \$75; DC509, \$100; FG5010, \$500; PG501, \$50; SC502, \$200; TM5006, \$300; TM501, \$50; TM503, \$65; TM504, \$75; TM506, \$85; TM515, \$85. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

Modern Communications • (405) 691-0594 TEL & FAX

Converters:	10	50	100
Panasonic: TZPC-175	\$49.00	\$45.00	\$39.00
Panasonic: TZPC-145	\$45.00	\$39.00	\$35.00
Centurion CF-3000 (NEW)			
True 99 Channel	\$65.00	\$60.00	\$55.00
Regal: CR-83	\$39.00	\$35.00	\$32.00

Remotes:	10	50	100
Jerrold: 400, 450, 550	\$4.50	\$4.00	\$3.75
CFT: 2XXX	\$4.95	\$4.50	\$4.25
S/A: 175, 475	\$4.95	\$4.50	\$4.25
S/A: 8600 Display	\$4.95	\$4.50	\$4.25
Panasonic: 170, 175	\$4.95	\$4.50	\$4.25
Zenith (ALL)	\$4.95	\$4.50	\$4.25
Pioneer (ALL)	\$4.95	\$4.50	\$4.25
Tocom 5503-VIP	\$4.95	\$4.50	\$4.25
4-in-1 Universal	\$5.95	\$5.50	\$5.25



Parts, Parts, Parts

	10+	50+	100+
PIC16C622	\$3.15	\$2.95	\$2.75
PIC16C54RC/P	\$2.15	\$1.95	\$1.75
PIC16C56RC/P	\$2.15	\$1.95	\$1.75
Micro 68H705C8P	\$6.50	\$6.15	\$5.95
4 MHz (Resonator 2 pins)	\$0.45	\$0.40	\$0.35
4 MHz (3 pins)	\$0.45	\$0.40	\$0.35
Crystal: 117, 119	\$3.75	\$3.50	\$3.25
18 pin IC Socket	\$0.15	\$0.12	\$0.10
Toggle Switch on/on	\$0.95	\$0.85	\$0.75

Call for Larger Quantity Quotes

Remotes

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

INEXPENSIVE NEW ARRIVALS (MOST UNITS LOOK NEW AND WERE RECENTLY CALIBRATED). HP 8901B, \$1,000; HP 8903B, \$1,500; HP 8901A, \$750; HP 8903A, \$750; HP 8590D, \$4,500; HP 8657A, \$2,000; HP 8657D WITH HI STAB & DQPSK IQ MODULATOR, \$3,000; HP 3852A, \$750; HP 44705A, \$300; HP 44725A, \$300; FLUKE 6071A, \$1,250; HP 6034L, \$500; HP 6002A, \$500; HP 4191A, \$9,000; ENI 603L, \$1,200; MARCONI 2955A, \$2,500; MARCONI 2955, \$1,500; HP 8175A, \$2,500; HP 3562A, \$4,900; HP 8496H, \$350; HP 8590B, \$3,900, ETC., ETC. SHOP AND COMPARE! MANY MODELS PRICED MORE THAN 50% OFF COMPETITOR'S PRICES. TRU CAL INT'L, ISO 9002 & A2LA ACCREDITED CALIBRATION LABORATORY. tru-cal@aol.com Toll free# 1-800-681-5540, phone# 630-238-8100, fax# 630-238-8101. ASK ABOUT OUR BRAND NEW HANDHELD 3-1/2 DIGIT KEITHLEY DMMs FOR \$50.

INSTRUMENT REPAIR Labs. Excess equipment for sale. Tektronix 7834 analog scope mainframe, \$600; Tektronix 7904 analog scope mainframe scrap parts, \$200; Tektronix 7A15A 1 ch. amplifier, \$100; Tektronix 7A18 dual trace amplifier, \$100; Tektronix 7A18N dual trace amplifier, \$75; Tektronix 7A19 amplifier plug-in, \$250; Tektronix 7A24 dual trace amplifier, \$100; Tektronix 7A26 dual trace amplifier, \$150; Tektronix 7B53A dual time base, \$150; Tektronix 7B85 delayed time base, \$75; Tektronix 7B92A dual time base, \$200; Tektronix 7D11 digital delay, \$50; Tektronix C4 scope camera, \$250; Tektronix C28 scope camera, \$150; Tektronix C53 scope camera, \$150; Tektronix C59 scope camera, \$150; Tektronix C5C scope camera, \$350; Tektronix wavewriter analog waveform editor, \$100. sales@calibration.com http://www.calibration.com phone: 303-469-5335 fax: 303-469-5336. Used listings web page: http://www.calibration.com/sale/index.html

HEWLETT PACKARD 141T, \$300; 141T w/8552B, 8553B, \$850; 141T w/8552B, 8555A, \$1,100; 1630A w/pods, \$300; 1741A, \$200; 1980B, \$300; 331A, \$75; 3325A, \$600; 3325A/1/2, \$850; 333A, \$175; 3330B/3571A, \$650; 33320H, \$200; 33322H, \$200; 3400A, \$85; 350D, \$35; 350D, \$35; 355E, \$50; 355F, \$50; 3575A, \$300; 423A, \$75; 4260A, \$200; 435B/scales, \$250; 436A, \$500; 436A w/cable & 8484A, \$750; 436A/022, \$550; 456A, \$100; 5006A, \$200; 5257A, \$75; 5300A/5302A, \$100; 5314A, \$150; 5315B, \$300; 5326A, \$50; 5328A/11/96, \$150; 5335A, \$350; 5335A/10/20, \$500; 5342A/1/3/11, \$900; 5345A/011/5354A, \$300; 5370A opt 1, \$500; 5383A, \$200; 54100A w/pods, \$1,250; 54201D, \$650; 59401A, \$75; 8660C with opts 1, 5, 100, 86603A, 86633B, \$1,750; 911A, \$50. All with 30-day warranty, 10-day inspection. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

TEKTRONIX OSCILLOSCOPES: 2235, \$400; 2246A, \$600; 434, \$125; 454, \$125; 454 w/cover, \$175; 465M, \$250; 466/DM44, \$300; 7603/2-7A18/7B53A, \$200; 7603/2-7A26/7B53A, \$225; 7633R/2-7A26/7B53A, \$250; 7834/7A19/7A26/7B85/7B80, \$450; 7934, \$400; 7904A, \$300; 7904/7A19/7A26/7B53A/7B92A, \$500; 7A18A, \$40; 7A18, \$35; 7A29, \$150; 7B10, \$125; 7B15, \$125; 7B53A new-in-box w/manual, \$75; P6019 probe kit w/134 amp & pwr supply, \$150; P6021 probe kit w/134 amp & pwr supply, \$150; P6021 probe \$75; P6201 kit, \$250; P6202A kit, \$175. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471. FAX 520-760-7780.

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS

EASY PIC'n - Beginner \$29.95

PIC'n Up The Pace - Intermediate \$34.95

NEW!

PIC'n Techniques - Intermediate \$34.95

- 8-pin PICs
- Timer 1, timer 2 and the capture/compare/PWM (CCP) module
- Talking to a PIC with a PC using a terminal program
- Test equipment and data logger experiments


See Table Of Contents: <http://www.sq-1.com>
Secure Online Ordering is Available

+ \$4 s/h in US for 1 book, \$5 for 2 books, \$6 for 3 books
VISA, MC, AMEX, MO, Check
CA residents please add 7.25% CA sales tax
PIC and MPLAB are trademarks of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451
Voice (707) 279-8881 FAX (707) 279-8883
<http://www.sq-1.com>
E-Mail sqone@pacific.net

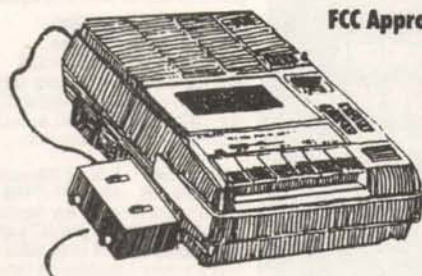TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



FCC Approved

Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.


For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 407-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

Write In 60 on Reader Service Card.

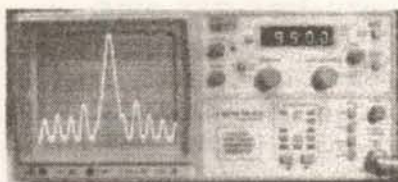

ENGINEER TESTED: Spectrum analyzers, frequency counters, frequency standards, meters, scopes, generators, curve tracers, and more. **VISA, MASTERCARD, AMEX.** "Performance tested." **NIST calibrated.** Warranted. **New & used.** Gary N6ZD. <http://TECH-SERVICES.COM> 831-385-7519.

DESOLDERING EQUIPMENT: Pace MBT250 PPS85 base, \$350, MBT220, \$700; hot air reflow, \$600; hot tweezer, \$50; ultrasonic cleaner \$100; hot plate, \$100; heat gun, \$40; solder pot w/read-out, \$175; hot air pencil, \$200. **Solder stations:** Weller EC2000, \$100, EC2000, \$100, EC2002M2 new, \$225; WTCP w/nu modified Ungar trouble free heater, \$50. **Trade, repair, buy,** 310-515-2058.

HP 4815A Z-meter: Expert restoration or verification to HP/QA factory specs. Former HP tech/supv, tel 908-852-7989 or E-Mail: GeoSA4815@compuserve.com Webpage: <http://ourworld.com/puserve.com/homepages/GeoSA4815>


**FOR THE BEST
PRICES ON PROFESSIONAL TOOLS,
CALL ELECTRO-TOOL**



platt - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95
800T Case Only ... \$121.80



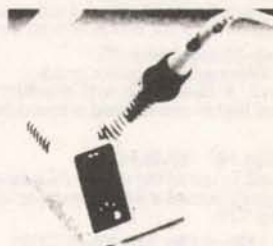
platt - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00
660ZT Case Only ... \$59.45
Optional Sperry meter #DM6510 as shown ... \$65.00



Weller WCC100 - Electronically controlled station, temperature adjustable from 350°F-850°F, Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90



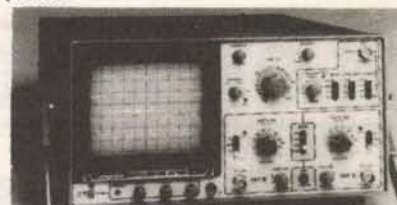OptiVISOR - Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



GoldStar - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div., high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00

Electro Tool, Inc.

9103 Gillman, Livonia, MI 48150
Customer Service: (734) 422-1221
ORDERS ONLY: 1 (800) 772-3455
FAX: (734) 422-3432

"Tools American Made."



AFFORDABLE HP power sensor repair! Most 8481As repaired for \$255 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

EMI EQUIPMENT: Tektronix spectrum analyzer 2755P programmable, GPIB 10KHz to 22GHz. HP 8447D amplifier .1 to 1300MHz, HP plotter 7479A GPIB, HP printer GPIB, Biconnical antenna, log periodic antenna, Robert's antenna set, LISNs, ESD simulator, surveillance receiver 1.6GHz to 10GHz with antennas. Much more including RF cables, adapters, and etc. Please call and ask for Bob at 925-449-3961.

TEST EQUIPMENT: Tektronix: scopes 7904 500MHz, 7912AD 500MHz, plug-in 7A16, 7B90, 7B80, 7B85, 7A24. Spectrum analyzer 2755P programmable, GPIB 10KHz to 22GHz tracking generator TR501. Hewlett Packard: spectrum analyzer 3582A, swept amplitude analyzer 8755, 8750 storage normalizer, (3) 11664A detectors, 182T mainframe, 1007A cart. amplifiers, 8447D 1-1.3GHz +26dBm 8447A 1-400MHz +20dB 465A 20/40dB, 467A power amp, 493A 4-8GHz, 489A 1-2GHz, 8616A 1.8-4.5GHz 230B 10-500MHz sweep oscillator 8620B, 86220A 10-1300MHz, 86250A 8-12.4GHz. Much more including power supplies, electronic loads, and etc. Please call and ask for Bob at 925-449-3961.

KENTRONIX TEST EQUIPMENT SPECIALS. Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$98. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>

DIGITAL VOLTMETERS: Fluke 8050A/hard case/probes, \$100; Fluke 8050A/soft case/probes, \$100; Fluke 8600A/probes, \$55; HP 3437A, \$75; HP 3455A, \$200; HP 3456A, \$300; HP 3466A, \$100; Keithley 616, \$500. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING, 3198-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.

Subscribe to Nuts & Volts Today!
Call 1-800-783-4624
and Use Your Visa or MasterCard.

TEST EQUIPMENT for sale/wanted (NEW/USED): RF, Microwave, video and fiber optic. Cable TV, Broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. **PTL Test Equipment, Inc.** Phone 561-747-3647 FAX 561-575-4635. E-Mail: PTLTE@aol.com <http://www.PTLTEST.com>

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

QUALITY EQUIPMENT SALE: HP 3488A switch control unit \$500 (cards available); HP 4140B pA meter, DC voltage source with HP 16055A \$2,000; HP 436A/022 RF power meter with cable \$925; HP 5343A/1,6,11 26.5GHz microwave frequency counter \$2,995; HP 6033A autoranging power supply (20V, 30A) \$900; HP 8112A 50MHz pulse generator \$3,600; HP 8161A/020 100MHz dual channel pulse generator \$2,300; HP 83522A .01-2.4GHz 8350B plug-in \$2,500; HP 83570A 18-26.5GHz 8350B plug-in \$3,400; HP 8410C, 8410B network analyzer mainframes \$575, 400; HP 8411A/018, 8411A harmonic frequency converters \$350, 175; HP 8743B/018, test set \$425; **Audio Precision SWR-122F** switcher \$600. All with warranty, excellent condition. Pepper Systems (<http://home.earthlink.net/~peppersys>) 214-353-0257 (Fax 214-902-9511). E-Mail: peppersys@earthlink.net

PICMASTER EMULATOR system, new, complete, all parts, documentation, boxes, w/16C63 probe, MPLAB software, registered w/Microchip, \$900 obo. 818-349-7920.

EQUIPMENT CLEARANCE. Electronic test, avionics test, NDT. Most 8 yrs old+. For list, E-Mail: amslsovt@sover.net Andrew Smith, AMSL, Vermont, USA 802-254-9459.

NEW, FASTER POCKET TESTBENCH, tiny, inexpensive, portable RS-232 instrument. Scope, logic, counter, generator modes. **Oricom Technologies**, 303-449-6428. www.sni.net/~oricom

SCIENTIFIC EQUIPMENT: Varian 3700 gas chromatograph PID, FID detectors, gas regulators, strip chart recorder and etc. Complete set of manuals. Perkin Elmer 139 UV-visible spectrophotometer. Labco glove box, B&L zoom microscope with stand and light. B&L quad microscope. Binocular viewing, video camera port and Polaroid camera port. 10X, 40X, and 100X objectives. Research illuminator, Polaroid camera, video camera, video monitor and video printer. Much more including electrophoresis apparatus, and etc. Please call and ask for Bob at 925-449-3961.

TEST EQUIPMENT: Bird Termaline 8833 1 KW load, \$225; Boonton 4200 w/5E sensor, \$450; CAL INST. 1503T, \$850; EIP 371, \$650; GenRad 1863, \$350; Interstate Elect. 860, \$400; RFL 5950 XTAL tester/254/460, \$250; TEK DA4084, \$400; Wavetek 157, \$400; Wavetek 271, \$300; Wavetek 3000, \$300. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

CALIBRATION EQUIPMENT: Boonton 25A, \$200; Boonton 8200 opt S-10, \$650; Fluke 8840AF, has AC, DC, ohms & amps opts, \$300; Guildline 9577 7.5 digit DMM w/leads, \$550; Valhalla 2720GS opt HSR, \$2,000; Eaton 380K11, 1MHz-4GHz, \$2,000; ESI 1045AS1, \$500; 435-K05, \$100. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, FAX 520-760-7780.

PROFESSIONAL DESOLDERING with the World's Best Transportable, Totally Self-Contained Desoldering Tool

Mike Murphy - Service Center - Van Nuys CA 818-785-7805

The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

Dick Manning - Dicks Electronics - Hartland WI 414-367-8339

The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

Don Scott - LAV Electronics - Healeah-Miami Lakes FL

I am a constant user of the SC7000 Desoldering Tool and for quick component removal, this unit has no equal. It also comes with excellent company support. I am very satisfied and highly recommend it to anyone in the servicing field.

George Hefner - Hefner Electronics - Coleridge NE 402-283-4333

Being a one-man service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. It has cut my desoldering time by 50%.

Don Cressin - Certified Electronics Service - Ellicott City MD 301-461-8008

We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400

We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

DEN-ON SC7000Z

Sale Price \$395.00

MSRP \$475.00
Sale Price \$395.00

FREE TRIAL
Available on Request

Price includes
stand worth \$25.00
one extra filter and
two tip cleaners.

Timothy Kraft - Monikraft, Inc.

Cherry Hill NJ 609-751-3252

We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

Bill Warren CET/CSM -

Warrens Audio & Video -

Knoxville TN - 234-546-1128

We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

Keith Sahs - J & M Electronics

Omaha NE 402-291-7100

It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

For More Info
and 5% Savings Go To

www.howardelectronics.com/den-on/sc7000zb.html

New Features

- ◆ Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- ◆ 100 Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- ◆ Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- ◆ Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.

Howard Electronic Instruments, Inc.
6222 N. Oliver Kechi, KS 67067

New Specifications

- ◆ Voltage—AC 100v, 120V, 230V, 50/60 HZ
- ◆ Power Consumption—120W
- ◆ Pump—Diaphragm Type
- ◆ Motor Output—12W
- ◆ Vacuum Attained—650mm Hg
- ◆ Temperature Range—300° C—500° C (572° F—932° F)
- ◆ Air Flow Rate—15 Liter/Minute (Open)
- ◆ Heater—100W (Ceramic)
- ◆ Control System—Feed Back Zero Cross-over Type
- ◆ Net Weight—420 Grams

Visa - M/C - Discover - American Express - Terms to Qualifying Companies
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

HOWARD ELECTRONIC INSTRUMENTS INC.
Your Desoldering Specialists

Toll Free U.S. and Canada

1-800-394-1984

www.howardelectronics.com
sales@howardelectronics.com
International (316) 744-1993
or Fax (316) 744-1994

2539 W. 237th Street, Bldg. F, Torrance, CA 90505
 Order desk only: USA: (800) 872-8878 CA: (800) 223-9977
 LA. & Technical Info: (310) 784-5488 Fax: (310) 784-7590
 OEM INQUIRIES WELCOME

TIMELINE INC.

Over 14 years and 31,000 customers and still growing

Minimum Order: \$20.00. Minimum shipping and handling charge \$3.00. We accept cashiers checks, MC or VISA. No personal checks or C.O.D.'s. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

LIQUID CRYSTAL DISPLAYS

240x64 dot LCD with built-in controller.

AND 4021ST-EO. Unit is EL back-lit. \$59.⁰⁰ or 2 for \$109.⁰⁰ or OPTREX DMF5005 (non back-lit) \$49.⁰⁰ or 2 for \$89.⁰⁰

20 character x 8 line 7HL x 2 1/4H The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface

16x1.....\$7.00	20x2.....\$10.00	32x2.....\$8.00
16x1 (lg. char.).....\$10.00	20x4.....\$15.00	40x1.....\$8.00
16x2.....\$7.00	20x4 (lg. char.).....\$10.00	40x2.....2 for \$20.00
16x2 (lg. char.).....\$10.00	24x2.....\$10.00	40x4.....\$20.00
16x4.....\$15.00	32x4.....\$10.00	4x2.....\$5.00

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mr.	price	size	Mr.	price
640x480 (backlit)	Epson	\$25.00	480x128	Hitachi	\$10.00
640x400 (backlit)	Panasonic	\$20.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$10.00	240x64	Epson	\$15.00
			160x128	Optrex	\$15.00

6" VGA LCD 640X480, Sanyo LMDK55-22 \$25⁰⁰

MONITORS

9" COLOR SVGA MONITOR \$179.⁰⁰

Fully Enclosed - Tilt and swivel type.

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15Khz • Ability to do 40 and 80 column.

5 inch Amber \$25.00 • 7 inch Amber \$25.00
 9 inch Amber or Green \$25.00

5" COLOR MONITOR \$39.⁰⁰

• Flat Facplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
 • 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
 • Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mr. Samtron

2 for \$69⁰⁰

HACKER CORNER

Encased Spread Spectrum RF Modem \$99.⁰⁰

The ProxLink Radio Module is a small communication device which replaces cables between RS-232 devices with wireless RF (Radio Frequency) technology. Attaching a pair of ProxLinks to any two devices with three wire asynchronous RS-232 ports allows wireless data transmission at rates up to 19.2 Kbaud (full duplex) over a range of 500 - 800 feet. Modules use 900 MZ spread spectrum radio for communication which does not require an FCC site license. A variety of configuration information (radio channel, baud rate, serial port configuration, etc.) can be programmed into module's non-volatile memory by host PC to provide compatibility and avoid overlapping systems. Configuration changes are supported by menu driven, on-board software. Commonly used Terminal Emulation software and transfer protocols can be used for configuring modules and transferring data between computers. ProxLinks require only 6-9 VDC (350 mA), RS-232 (9 pin sub-D) interface, and small (~4") whip antenna for operation. Unit size is 4.0" x 6.5" x 0.75". Installation schematics and application details available. These are 100 Mw power.

4 INCH LCD MONITOR \$49.⁰⁰

Compact (4.4" x 3.8" x 1.4") TFT active matrix LCD color monitor including fluorescent backlight. Analog RGB and composite sync input with switchable horizontal / vertical viewing. Low power consumption and long life backlight make it ideal for security and door phone use. Single 8 VDC supply and good resolution allow mobile operations or use with laptops. Standard ribbon cable - Molex connector interface. Complete specifications included.

EMBEDDED 486 COMPUTER \$99.⁰⁰

Complete enhanced Intel 486SX-33 based computer in ultra small (9-7/8" x 6-5/8" x 3-1/8") case. Ideal for embedded operations or as a second computer. Features include: • One 16 bit ISA slot • 3 serial ports plus dedicated printer port • Parallel optical coupled adapter port • Built in IBM PC/AT keyboard port • On board VGA video and port • Uses standard SIMM up to 32 MB • BIOS is PC/AT compatible

Unit has a backup Ni-Cd battery system in case of power failure (5 min. backup time) and lockable front cover to prevent floppy drive access. Mounting / interface provisions for standard 3.5" laptop floppy and 2.5 inch hard drives. Comes with very comprehensive manual.

SONY Miniature Color LCD Display (LCX005BK) \$29⁹⁹

• 1.4 CM (0.55 inch) Diagonal Full Color Display • Built In Horizontal and Vertical Drivers • Delta Dot Pattern for High Picture Quality • 537 dots (H) x 222 dots (V) • Compatible with NTSC & PAL Format and Sync Inputs • 12 VDC Operation with -1 to +17 V RGB Signal and Driver Input Voltage • Excellent Display for Virtual Reality Projects, Viewfinders, and Miniature Test Equipment Displays • Pin Outs and Specification Included • Unit Requires Clock, Synchronization and Video

CELL SITE TRANSCEIVER \$49.⁰⁰ 2 for \$99.⁰⁰

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

NTSC COMPOSITE

4" LCD MONITOR \$69.⁰⁰

SECURITY



COUNTER-SURVEILLANCE=\$250 HR!
 Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

SURVEILLANCE-COUNTERSURVEILLANCE: I buy and sell used equipment. Steve 410-879-4035.



CONVERTS PC MONITOR to SECURITY MONITOR. The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; \$69 each. Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com




SALE! PS 102: Built-in pin hole CCD, lens size: 3.6mm. 5-1/2" (D) x 1.7" (H). \$79 @ 5 pcs., \$72 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. www.tsc-global.com




SPECIAL IC 113: PIR motion detector with audio! W/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

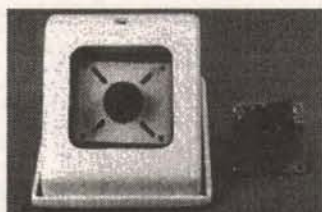
Closing Date
 For Next Issue - September 7th



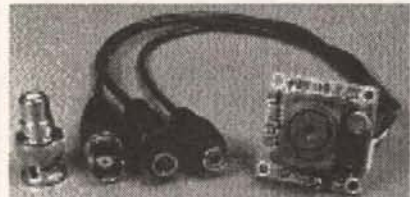WEATHERPROOF ENCLOSURE for board cameras, fits all 30-42mm color/back & white cameras, \$59. Matco, Inc., Schaumburg, IL 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com



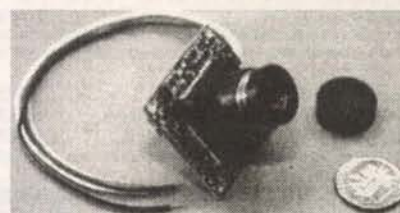B/W BOARD camera w/audio, \$49 @ qty 10, 1.27" x 1.27". Enclosure available for \$10. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com



B/W 430 LINE CCD CAMERA with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., \$44 each. Enclosure: \$8; optional lens: \$18. Dealers welcome. MATCO, Inc. 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com

STOP THEM from listening in or recording your telephone conversations with the **TELEPRIVACY-PLUS.** Send \$49 to Vakis, 1402 Pine Ave., Niagara Falls, NY 14301.

Davilyn CORP.

13406 Saticoy Street
 North Hollywood, CA 91605
 800-235-6222
 818-787-3334 • F-818-787-4732
 HTTP://WWW.Davilyn.com/Electronics



SEXTANT

Aircraft or marine navigation. No case. AS-IS \$50



SINGER CSM-1 COMMUNICATIONS SERVICE MONITOR



Functions: generate 2mV to 2mV. AGC: manual or auto. \$395 \$295

RF signal source: 0 to 600MHz in 100MHz steps plus 100Hz vernier. RF output: 110 to 0 dBm, built-in oscilloscope monitor. Inputs: RF, detected, vertical, horizontal, AM/FM. Outputs: audio, tone, RF.

TELEGRAPH KEYS

Unique item for military collectors. J37 telegraph key, new in original government package. \$49.95




MORGAN DATA SYSTEMS MODEL 8609

Constant voltage or current power supply voltage range: 0 to 50 volts. Current range: 0 to 1.5A. Readout: 3 digit with 0.1 volt and 1mA current resolution. Regulation: linear; input voltage: 115V/220V. Adjustments: voltage and current has remote control adjustment capability. NEW. Price: \$95




LAMBDA LK344A-FM POWER SUPPLY

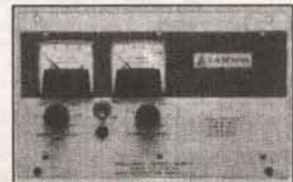Front panel voltage and current meters. Convection-cooled, no blower. Voltage adjustable from 0 to 60 VDC at a maximum current of 4A. Regulation 0.015% or 1mV. Line or load. Series/parallel operation. Remotely programmable by voltage or resistance. Less than 500µV RMS ripple. Constant current/constant current. NEW Price: \$995 NEW LOWER PRICE: \$295



JONES MODEL 1600-1 TACHOMETER

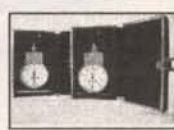Instrument tachometer centrifugal mechanical tach measures RPM scale 0-500 RPM, coupling shaft 1/8" accessories, various size rubber tipped drive couplings, case new. Also Jones Model 1600-7 RPM scale 0-11,000 RPM w/accessories.



New \$35/ea. or 2 for \$50

HP 8640B SIGNAL GENERATOR OPT 003




CONDITION CODE "A"

Frequency: 500KHz to 512MHz. Indicates to 1024MHz. Requires external frequency doubler for 1024MHz (supplied with unit). Readout can be used as a frequency counter. Accuracy: 6.5 digits expandable to X10 and X100. Output: 145dBm to +15dBm (0.5 to 512MHz). Modulation: AM, FM, pulse, 400 and 1KHz, 1mV to 1V internal. Has input and output of modulation sources.


BEST BUY

\$1,695 \$775

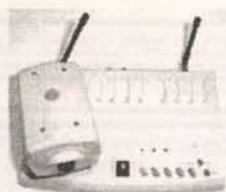

AS-1004, FCC approved. 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. **\$189 a pair @ 5 pcs.**, \$179 @ 10 pcs. Additional camera \$119 @ 10 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

ALL NEW: THE COVERT CATALOG 2000. The MASTER LIST of information suppliers, specialized newsletters, OEM lock picks, reverse engineers, spy shops, alternate IDs, program crackers, and more. Locate impossible equipment, shop where the smart guys shop. Provides hundreds of addresses, sample pages, catalog prices and recommendations that will save you money on everything from break-in books to undetectable bugs. Catalog #COVCAT-2, price \$34.95 + S&H \$6 US, \$7 CAN. NY state add \$3.38 tax. Visa, MC, Discover, money orders. Mail: CRB, PO Box 56-NV, Commack, NY 11725. Phone: 516-543-9169.

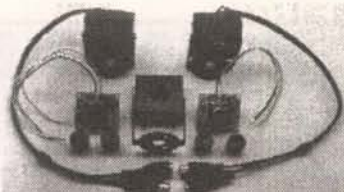

COLOR — Low light CCD pin hole and standard lens available, only 1.27" x 1.27", \$109. Sony sensor with audio. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

SEEKING DISTRIBUTORS FOR SECURITY PRODUCTS. Matco, Inc., Schaumburg, IL 630-350-0299. www.mat-co.com

SATELLITE EQUIPMENT



FREE BIG dish catalog. Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com Call 1-800-543-3025.



BEST PRICING on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. www.skyvision.com Call 1-800-543-3025.

1999 DSS SOFTWARE COOKBOOK 700+ CD-ROM COLLECTION: CLONING, REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIAL: 1ST 700 ORDERS GET 700+ ADDITIONAL PROGRAMS!) WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE!!!). DSS TEST-CARD INFO SOURCE MANUAL \$10. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS, USA. CALL NOW 407-654-9677.

THE BEST is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at www.acdinc.com for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

FREE FLYER on DBS files, hacking, hardware info. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Bill 1-800-879-9657.

SATELLITE RADIO BOOK AND GUIDE. New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

MILITARY SURPLUS ELECTRONICS

WANTED: ARC-5 & SCR-274N receivers and manuals. John Broussard, 312 Guilbeau, Breaux Bridge, LA 70517.

AUDIO — VIDEO — LASERS

FREE LASER CATALOG. Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 www.midwest-laser.com

ATV 2.2GHz to 2.7GHz wireless video data link module tuner & transmitter 100mW. Picotronic, web: <http://members.aol.com/picotronic/atv.htm>

World's Smallest TV Transmitters

We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air!

C-2000, Basic Video Transmitter Cube.....\$89.95
C-3000, Basic Video & Audio Transmitter Cube.....\$149.95
C-2001, High Power Video Transmitter Cube.....\$179.95
C-3001, High Power Video & Audio Transmitter Cube.....\$229.95

CCD Video Cameras

Top quality Japanese Class 'A' CCD array, over 440 line line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infrared) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1 volt p-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for audio sound pick-up and super easy direct wire hook-up to any Video monitor, VCR or TV with A/V input. Fully assembled, with pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens.....\$69.95
CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$69.95
CCDC-1, Color CCD Camera, wide-angle lens.....\$129.95
IR-1, IR Illuminator Kit for B&W cameras.....\$24.95
IB-1, Interface Board Kit.....\$14.95

Mini Radio Receivers

Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for short-wave and FM broadcast which has handy SCA output. Add our snazzy matching case and knob set for that smart finished look.

AR-1, Airband 108-136 MHz Kit.....\$29.95
HFRC-1, WWV 10 MHz (crystal controlled) Kit.....\$34.95
FR-1, FM Broadcast Band 88-108 MHz Kit.....\$24.95
FR-6, 6 Meter FM Ham Band Kit.....\$34.95
FR-10, 10 Meter FM Ham Band Kit.....\$34.95
FR-146, 2 Meter FM Ham Band Kit.....\$34.95
FR-220, 220 MHz FM Ham Band Kit.....\$34.95
SR-1, Shortwave 4-11 MHz Band Kit.....\$29.95
Matching Case Set (specify for which kit).....\$14.95

Tiny FM Transmitters

Gosh, these babies are tiny - that's a quarter in the picture! Choose the unit that's best for you. FM-5 is the smallest tunable FM transmitter in the world, picks up a whisper 10' away and transmits up to 300'. Runs on tiny included watch battery, uses SMT parts. FM-4 is larger, more powerful, runs on 5-12 volts, goes up to a mile. FM-4.5 operate in standard FM band 88-108 MHz. FM-6 is crystal controlled in 2 meter ham band, 146.535 MHz, easily picked up on scanner or 2 meter rig, runs on 2 included watch batteries. SMT (surface mount) kits include extra parts in case you sneeze & loose a part!

FM-4MC, High Power FM Transmitter Kit.....\$17.95
FM-5, World's Smallest FM Transmitter Kit.....\$19.95
FM-6, Crystal Controlled 2M FM Transmitter Kit.....\$39.95
FM-6, Fully Wired & Tested 2M FM Transmitter.....\$69.95

Super Pro FM Stereo Transmitter

Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set freq with Up/Down buttons, big LED display. Input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for max 'punch' in audio - without over mod, LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

FM-100, Pro FM Stereo Transmitter Kit.....\$249.95
FM-100WT, Fully Wired High Power FM-100.....\$399.95

FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Excellent audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strapable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes case, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized FM Stereo Transmitter Kit....\$129.95

Lower cost alternative to our high performance transmitters. Great value, tunable over FM band, plenty of power and manual goes into great detail about antennas, range and FCC rules. Handy kit for sending music thru house and yard, ideal for school projects too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or power from 5 to 15 VDC. Add our matching case and whip antenna set for a nice 'pro' look.

FM-10A, Tunable FM Stereo Transmitter Kit.....\$34.95
CFM, Matching Case and Antenna Set.....\$14.95
FMAC, 12 Volt DC Wall Plug Adapter.....\$9.95

RF Power Booster

Add muscle to your signal, boost power up to 1 watt over a freq range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set.

LPA-1, Power Booster Amplifier Kit.....\$39.95
CLPA, Matching Case Set for LPA-1 Kit.....\$14.95
LPA-1WT, Fully Wired LPA-1 with Case.....\$99.95

FM Station Broadcast Antenna

For maximum performance, a good antenna is needed. Properly tuned and matched antenna is fully PVC enclosed for weather protection and rugged use. Vertical or horizontal mounting, 'F' style connector, 5' long.

TM-100, Tru-Match FM Station Antenna Kit.....\$39.95

AM Radio Transmitter

Operates in standard AM broadcast band, set to clear channel in your area. AM-25 'pro' version is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 has tunable transmit oscillator, runs FCC maximum 100 mW power, expected range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded wire antenna. Entry-level AM-1 has an available matching case and knob set for a finished, professional look. High level modulation for low distortion.

AM-25, Professional AM Transmitter Kit.....\$129.95
AM-1, Entry level AM Radio Transmitter Kit.....\$29.95
CAM, Matching Case Set for AM-1.....\$14.95

RAMSEY Binocular Special

Wow, did we nab a deal on these first rate binoculars! Absolutely identical to a famous big name brand here in Rochester, NY - but without 'their' name. Well made with fully coated optics, super nice rubber armored housing over hi-alloy aluminum, includes lens cleaner cloth, neck lanyard and carry case. 4 styles: roof prism 10x25 (10 power, 25 mm), 10x25 high performance roof prism ruby coated objective lens model for demanding use in bright sun, 10x25 high-end BAK-4 lens porro prism ruby coat with Tac-Grip housing, and Ultra-View 10x50 porro prism ruby coats. First quality, yet at a close-out price on the exact same units as the 'Trademarked' units - but at half price!

BNO-M, 8x21 Mini Monocular.....\$14.95
BNO-1, 10x25 Roof Prism Binoculars.....\$24.95
BNO-1EX, 10x25 Ruby Coated Porro Prism.....\$29.95
BNO-2, 10x25 TacGrip Ruby Coat Porro Prism.....\$59.95
BNO-6, 10x50 Ultra-View Ruby Coat Porro Prism.....\$69.95

World's Smallest FM Radios

Everyone who sees one of these babies says they just gotta have one! Super cute tiny FM radios have automatic scan/search tuning, comfortable ear bud earphones and we even include the battery. The pager style unit looks like a shrunken pager and even has an LCD clock built-in. You will be amazed at the crystal clear amazing sound! That's a quarter in the picture for size comparison - pretty tiny, huh?

MFMT-1, World's Smallest FM Radio.....\$11.95
PFMR-1, Pager Style LCD Clock & FM Radio.....\$12.95

Speech Descrambler

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. Speech inversion technology is used, which is compatible with most cordless phones and many police department systems, hook it up to your scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC. Our matching case set adds a professional look to your kit.

SS-70A, Speech Descrambler/Scrambler Kit.....\$39.95
CSS, Custom Matching Case and Knob Set.....\$14.95
SS-70AWT, Fully Wired SS-70A with Case.....\$79.95
AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

Call for our Free Catalog!

See our complete catalog and order on-line with our secure server at: www.ramseyelectronics.com

RAMSEY ELECTRONICS, INC.
793 Canning Parkway Victor, NY 14564

Order Toll-free: 800-446-2295

Sorry, no tech info, or order status at this number

For Technical Info, Order Status
Call Factory direct: 716-924-4560

VISA MasterCard AMERICAN EXPRESS DISCOVER


ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

LOWEST COST LCD'S ON EARTH



VIDEO LCD

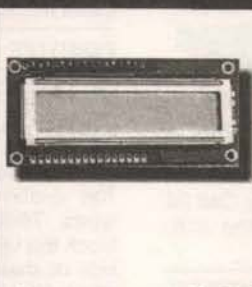4 Inch Video NTSC \$150
Sharp P/N 4LU4E
Composite NTSC & RGB Input
12:00 OR 6:00 Viewing Angle
Integrated Backlight & Inverter
Extended Temp: -10 to + 60 C
Brightness: 260 nits
Power Consumption: 4.3 Watts
Contrast: 50 to 1



CHARACTER LCD

OPTREX DMF-5005SN-EW
240 x 64 Graphic EL Backlit STN \$30
OPTREX DMF-5005N
240 x 64 Graphic Reflective STN \$30
SANYO DM2023-7G1
2 x 20 Character Reflective STN \$8
SHARP LM20A21
2 x 20 Character Reflective STN \$8
VIKAY 2035TNLD NOTW-D
2 X 16 Character LED Backlit STN \$8



LCD MONITOR

10.4" DSTN or 12.1" TFT
Analog SVGA Input
Autosync
Auto Sizing
Automatic Expansion of VGA
images to SVGA (On 12.1")
Very Aggressive Pricing
Starting under \$500!



TOUCH MONITOR


EarthVue 10.4
10.4" VGA TFT
Analog VGA Input
105 Nit Brightness
RS-232 Touch Screen Option
Only 9.9"W x 7.7"H x 1.5"D
Ideal For Factory Automation
Fully Articulating Ball Mount
Only \$1095 With Touch



LCD DISPLAYS

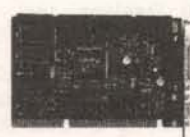6.3" Mono STN \$60
9.4" Mono Reflective \$60
8.4" TFT \$250
9.4" DSTN \$150
10.4" TFT \$350
10.4" DSTN \$240

NoteBook Screens
340 Models in Stock
Obsolete Screens Stocked
Hard To Find LCD? Call!



CONTROLLERS

ISA
PCI
PC/104
NTSC
Analog VGA
Complete LCD Kits with LCD,
Controller & Cable Starting
under \$200



EARTH

Computer Technologies

"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

Write in 63 on Reader Service Card.

SYNC-A-LINK UNIVERSAL video sync generators. For more details phone or fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.



ANTIQUE VIDEO TRANSFER SERVICE: transfer any 2" QUADRUPLIX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.



SYNC-A-LINKS's 3-D Scopers™ digital color CCD cameras for stereoscopic imagery. At a reasonable cost. Phone or Fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.

SONY PLAYSTATION MODCHIPS. Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

BROADCAST VIDEO equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.

LASER SHOW SYSTEMS AND COMPONENTS. Hobby and professional projectors. www.redline-lasers.com



STEREOSCOPER VR is a stereo multiplexer that creates 3D stereoscopic video from two genlock cameras. Stereoscopers VR comes with LCS glasses and driver. 90 day warranty \$247 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352. Phone or fax 918-479-6451.

FACTORY VIDEOS: \$5-\$10. Sony camcorder videos hi 8mm, \$2.50; reg 8mm need fix, 75¢, VHS factory videos need fix, 75¢. 310-515-2058.

WANTED: PRO video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

From the Masters of Hi-Tech Security & Survival...

INTERNET SECURITY COMPUTER SECURITY POWER METER SECRETS

The latest tricks and methods hackers use on the Net to pirate software (warez), and hack websites. Includes examples, countermeasures, password defeats, Packet-Switched Networks, UNIX, Sprintnet, X.25, anonymous FTP, brute force techs, lots of tips. More! \$29. wrds=29.4K

INTERNET TRACKING & TRACING: Scammers, spammers, stalkers, infectors, and others hide behind the Internet's anonymity to commit serious offenses. Learn from master hackers best methods to track, trace IDs and origins, and to protect your own privacy. More! \$29. wrds=17.0K

INTERNET FRAUDS DATABOOK: Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously with impunity. Details how they're done, how to ID them, how to protect yourself. More! \$25. wrds=19.1K

COOKIE TERMINATOR! \$25. wrds=8.4K
Any 2 for \$49, 3 for \$64

ATM SECURITY
100+ ATM crimes, abuses, vulnerabilities, defeats exposed - TEMPEST, mag stripes, false fronts, supercool, More! Case histories, labeled internal photos, figures. \$39. wrds=41.0K

PBX SECURITY
PBXs hacking losses of \$5-\$10 Billion/yr! Detailed vulnerabilities (especially for out-dial), countermeasures. Exclusive author interview in Forbes! \$24. wrds=17.4K

CELLPHONE/CORDLESS GUIDE
How cellphones operate; mods. Vulnerabilities to hack attack; countermeasures. Cloning details for NAMS, ESNs, etc. control data formats, computing encoded MINs, ESNs, SIDNs, Op Sys, PROMs, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, step-by-step to keypad-reprogram 100+ popular cellphones. One FREE database search. Plus much on Cordless phones. More! \$49. wrds=80.0K

PAGER (BEEPER) MANUAL: How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How phreaks hack Pagers; countermeasures. Plus plans for a Personal Pocket Paging System (xmitter and receiver). More! \$29. wrds=11.7K Both for only \$69

THE DIRTY-2 DOZEN!
24+ Hot Hack/Phreak Exposés! Disks!
See Web CATALOG NOW!

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39. wrds=49.5K

THE HACKER FILES: Exposé 3 HD PC disks filled with choice raw, colorful, highly informative hacker, phreaker text files covering many topics! \$39.

Both for only \$69

BEYOND VAN ECK TEMPEST
Remote eavesdropping plans of TV video "noise" signals. Range up to 1 KM. Describes how van Eck systems work, and are also used in surveillance of computer systems. Plus TVRO vs phone privacy detailed! \$29. wrds=14.9K. Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

CALLER ID & ANI SECURITY
How they work and the many vulnerabilities of Caller ID, ANI, *69, *57, Call Blocking, *67, et al. Describes ESS, SS7, CNA, CAMA, DNR, Diverters, Centrex! \$25. wrds=15.2K

FAX MACHINE SECURITY
All known methods used to hack faxes and countermeasures. Includes computer fax modems, crimes, interceptions, fax servers, fax-on-demand, protocols, parameters, compression, encryption, and fax surveillance-type mods. More! \$29. wrds=29.0K

MANY MORE TITLES!
(See Catalog for prices & descriptions)

POWERFUL STOCK SOFTWARE
BEYOND PHONE COLOR BOXES
ANSWER. MACHINE SECURITY
CASINO SECRETS
CHECK & M.O. SECURITY
CREDIT CARD SECURITY
CONS & SCAMS DATABOOK
SOCIAL ENGINEERING
POLYGRAPH SECRETS
BY AN ORDER OF THE MAGNITUDE
ULTIMATE SUCCESS MANUAL
STEALTH TECHNOLOGY
SIMPLE/CHEAP SECURITY ELEC.
SECRET & SURVIVAL RADIO

As reported on "60 MINUTES!" 6th Edition! Details devices that can slow down (even stop) power meters while loads draw full power - great science projects! Devices plug into one outlet and normal loads into other outlets. Describes meter creep, overload droop, pole meters, etc. \$29. wrds=10.4K

SPM THE VIDEO: Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPMEM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM-related manuals! \$29. (20 min)

THE I.G. MANUAL: Details external magnetic ways (applied to meters) outlaws use to slow down and stop power meters while drawing full loads. \$25. wrds=4.9K

KW-HR METERS: How watt-hour energy meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow, stop power meters by others. \$25. wrds=24.2K

VOICE MAIL SECURITY
VMSs are hacked to penetrate PBXs to make outgoing calls, get free VMB usage, secretly read/change/delete messages, control/damage the VMS (or its PBX) itself. Details how they do it, countermeasures. A must for users, sysops, security personnel! \$29. wrds=14.2K

THE "GOLDFINGER"
THE "SILKWOOD"
SECRETS OF SOLDERLESS BBS
HIGH VOLTAGE DEVICES
MIND CONTROL
UNDER ATTACK!
RADIONICS MANUAL
HEAL THYSELF!
SECRET & ALTERNATE IDS
CRYPTANALYSIS TECHNIQUES
GOVERNMENT LAND GRAB
ROCKET'S RED GLARE
VORTEX GENERATOR
SURVIVAL GUNS & AMMO
THE ULTIMATE DRIVER
Plus Many More - Order Today!



CONSUMERTRONICS

2430 Juan Tabo, NE, #259, ABQ, NM 87112
P.O. Box 23097 ABQ, NM 87192
Fax: 505-292-4078 (all hours, orders only) Voice: 505-237-2073 (9-5)

FREE FULL WEB CATALOG! www.tsc-global.com

Established in 1971 by John Williams, MSEE, former DOD weapons engineer and NIH physicist. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). Postal MO is fastest! VISA, MC OK. NO C.O.D.s. 10% OFF all Orders over \$100; \$2.00 OFF all New Orders over \$20 placed by Mail or Fax. wrds=Estimated Word Count
Sold for legal educational purposes only. Some publications are controversial! We take no responsibility for anything we publish. See Catalog for WARRANTY, SPECIAL PROJECTS and all other applicable policies.



CONVERTS PC MONITOR TO SECURITY MONITOR. The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; \$69 each. Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com

M3 GALVOS by General Scanning. New! 6 available @ \$400 ea. Call Roger @ GS&E, 716-338-7001. Visa-MC.

CABLE TV

CABLE PARTS & EVERYTHING. Best prices & quantity discounts. WE DON'T SELL BOXES. 1-800-MODULE-0.

SONY PLAYSTATION MODCHIPS. Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

GENUINE UNMODIFIED JERROLD DPBB 7312. 410-485-7772. E-MAIL: CLEWIS7298@AOL.COM

CABLE BOX repairs and upgrade. Most models, warranty lowest prices. Call 214-695-5982.

DTV & DISH NETWORK INFORMATION (36 pages) only \$15. Mainline Electronics, Inc. Call toll-free 1-877-856-0923. Cable television supplies DIRT CHEAP! Plus descrambling plans for all systems, call 1-877-880-0197. WWW.MELECTRONICS.COM

CABLE CONVERTERS. Original equipment with remote. Like new, ready to go. Lowest prices guaranteed. Limited models. Novicor Electronics, 412-833-0773.

NEW! CABLE converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erny Electronics. 24 hr. order and information hot line 516-389-3536.

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

SURPLUS TEST EQUIPMENT

HEWLETT PACKARD

11666A, Reference Bridge, 0.4-18GHz	\$800
11667A, Power Splitter, DC-18GHz	\$600
11975A, Amplifier, 2-8GHz	\$2000
16500A, Logic Analyzer Mainframe	\$750
3312A, Function Generator, 1Hz-13MHz	\$700
3325A, Synthesizer/Function Generator	\$1000
3325A/01/02, Synthesizer/Function Generator	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz w/Opt. 01	\$4500
339A, Distortion Analyzer	\$1000
3456A, Digital Multimeter, 6.5 Digits	\$800
3478A, Digital Multimeter	\$700
3488A, Switch Control	\$600
3551A, Transmission Test Set	\$600
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3581C, Selective Voltmeter	\$800
3582A, Spectrum Analyzer, 0.02Hz-25.5KHz	\$1600
3585A, Spectrum Analyzer, 20Hz-40.1MHz	\$4750
4192A, LF Impedance Analyzer w/16097A Accy. Kit	\$8000
4342A, Q-Meter	\$1800
435B, Power Meter	\$500
436A, Power Meter w/Opt. 022	\$1000
438A, Power Meter	\$2750
4935A, Transmission Impairment Test Set w/Opt. 003	\$1100
5087A, Distribution Amplifier	\$1000
5316B, Universal Counter	\$1000
5328B, Universal Counter	\$1000
5340A, Frequency Counter w/Opt. 01/02/011	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz	\$900
5355A, Frequency Converter	\$1000
5364A, Microwave Mixer Detector	\$4500
54100A, Digitizing Oscilloscope	\$1700
54100D, 1GHz Digital Oscilloscope	\$2700
54110D, 1GHz Color Digitizing Oscilloscope	\$2500
54120A, Digitizing Oscilloscope Mainframe	\$5750
54201D, Digitizing Oscilloscope	\$2650
6011A, Autoranging Power Supply, 20V/120A, 1000 Watt	\$1200
6012A, DC Power Supply, 0-60V/0-50A, 1000 Watt	\$1200
6034A, DC Power Supply, 0-60V/0-10A, 200 Watt	\$1000
6274B, DC Power Supply, 0-60V, 0-15A	\$1250
6475C, DC Power Supply, 0-110V, 0-100A	\$3500
6632A, DC Power Supply, 0-20V, 0-5A, 100 Watt	\$1000
778D, Dual Directional Coupler	\$400
8013B, Pulse Generator	\$750
8082A, Dual Pulse Generator, 250MHz	\$1200
8112A, 50MHz Pulse Generator	\$4000
8116A, 50MHz Programmable Pulse/Function Generator	\$3350
8116A, 50MHz Pulse/Function Generator, Opt. 001	\$4000
8165A/002, Programmable Signal Source w/AM	\$2200
8347A, RF Amplifier, 100KHz-3GHz	\$2500
8349B, Microwave Amplifier, 2-20GHz	\$4000
8350A, Sweep Oscillator Mainframe	\$1000
8350B, Sweep Oscillator Mainframe	\$1500
83522A, Sweeper Plug-in, .01-2.4GHz, w/Opt. 02	\$4000
83545A, Oscillator Plug-in, 5.9-12.4GHz	\$1750
83590A, Sweep Oscillator Plug-in, 2-20GHz, Rear Output	\$5500
8411A/018, Frequency Converter, .11 to 18GHz	\$500
8449A, Pre-amplifier, 2-22GHz	\$3000
8495H, Programmable Attenuator (unused)	\$600
8501A, Storage Normalizer	\$1000
85021B, Directional Bridge	\$1200
8505A, Network Analyzer w/8501A & 8503A	\$4000
8510B, Network Analyzer w/Opt. 010	\$13,000
8511A, Harmonic Frequency Converter, 45MHz-26.5GHz	\$5500
8554B, RF Spectrum Analyzer Plug-in, 500KHz-1250MHz	\$800
8562A, Spectrum Analyzer, 1KHz-22GHz	\$15,000
8566AB, Spectrum Analyzer, 100Hz-22GHz	\$16,000
86222B, Sweep Oscillator Plug-in, .01-2.4GHz w/Opt. 04, Rear Output and 8620C Mainframe	\$1250
8640A, Signal Generator, 0.5-512MHz	\$700
8640B, Signal Generator, Opt. 002, .5-1024MHz	\$2100
8640C, Signal Generator, Opt. 1, 2	\$2200
8654A, Signal Generator, 10-520MHz	\$450
8656A, Signal Generator, 100KHz-990MHz	\$1700
8656B, Signal Source, .01-2500MHz	\$2500
8660C, Synth. Signal Generator w/Opt. 1 & 100	\$1000
8660D, Synthesized Signal Generator	\$4000
86603A, RF Plug-in, 1-2600MHz	\$800
86603A, RF Plug-in, 1-2600MHz w/Opt. 02	\$950
8662A, Signal Generator, 10KHz-1280MHz w/Opt. 001	\$17,500
8663A, Synthesized Signal Gen., 100KHz-2560MHz w/Opt. 001 & 002	\$30,000
8672A, Synth. Signal Gen., 2.0-18.0GHz	\$4000
8672A, Synth. Signal Gen., 2GHz-18GHz, w/Opt. 08	\$5000
8748A, S-Parameter Test Set w/Opt. 026	\$1350
8756A, Scalar Network Analyzer	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz	\$4000

8970A, Noise Figure Meter \$4500

TEKTRONIX

1503, TDR Cable Tester w/Opt. 04 Recorder	\$1550
2215, 60MHz Oscilloscope	\$500
2236, 100MHz Oscilloscope w/Counter/Timer/DMM	\$1000
2246, 100MHz Oscilloscope	\$1600
2247A, 100MHz Oscilloscope w/Counter/Timer/Voltmeter	\$2500
2337, 100MHz Oscilloscope w/DMM	\$1650
2430A, 150MHz Digital Oscilloscope	\$2850
2432A, 300MHz Digital Storage Oscilloscope	\$3000
2445, Four Channel 150MHz Oscilloscope	\$1500
2465, Four Channel 300MHz Oscilloscope	\$2500
2465A DV, Four Channel 350MHz Oscilloscope	\$3850
2467, Four Channel 350MHz Oscilloscope	\$3000
2467B, Four Channel 400MHz Oscilloscope	\$6000
2630, Fourier Analyzer	\$2500
466, 100MHz Storage Oscilloscope w/DMM4	\$800
475, 200MHz Oscilloscope	\$650
475A, 250MHz Oscilloscope	\$800
492P, Programmable Spectrum Analyzer, 50KHz-21GHz w/Opt. 1/2/3	\$8000
576, Curve Tracer	\$2750
577/D2, Curve Tracer, Non-storage w/177 Fixture	\$1750
7D20, Programmable Digitizer	\$400
7L5/L3, Spectrum Analyzer, 20Hz-5MHz, w/Opt. 025 Tracking Generator	\$1850

**VISIT OUR WEBPAGE AT
WWW.RSSURPLUS.COM**

7L12, Spectrum Analyzer, 100KHz-1.8GHz	\$1500
7L18, Spectrum Analyzer Plug-in, 1.5-18GHz Capable of 60GHz with Mixers	\$2500
7S12, TDR Sampler	\$450
AFG5101, Arbitrary Function Generator	\$1500
CG5001, Programmable Calibration Generator	\$4000
RTD710A, Digitizer w/Opt. 1R (Rackmount)	\$3750
TM5003, Three Slot Power Mainframe	\$450
TM5006, Six Slot Power Mainframe	\$550

MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load	\$850
Datron 1061A, 6.5 Digit Autocal Multimeter, DC Only	\$700
Datron 1062, 6.5 Digit Autocal Multimeter, DC/AC/Ohms	\$900
EIP 545A, Microwave Frequency Counter	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz	\$3250
EIP 578, Source Locking Frequency Counter	\$2500
Electro-Metric EMC 11 MK IV, Interface Analyzer, 16Hz-50KHz	\$2000
Electro-Metric NTR-51C, Receiver	\$1250
Fluke 5101B/03, Calibrator	\$3000
Fluke 5200A, AC Voltage Calibrator w/5205A Amp	\$1850
Fluke 7261A, Universal Counter/Timer, 0Hz-125MHz	\$350
Fluke 8010A, Digital Multimeter	\$175
Fluke 8012A, Digital Multimeter	\$175
Fluke 8050A, Digital Multimeter	\$250
Fluke 8502A, Digital Multimeter, DC Only	\$225
Fluke 8520A, Digital Multimeter	\$350
Fluke 8600A, Digital Multimeter	\$65
Fluke 8810A, Digital Multimeter	\$250
Fluke 8840A, Digital Voltmeter w/Opt. 059	\$600
Keithley 195A, Digital Multimeter	\$700
LeCroy 9424, 350MHz Oscilloscope	\$3500
Marconi 2019A, Signal Gen., 80KHz-1040MHz	\$2200
Polarad 1105E-FT, Signal Generator, 0.8-2.4GHz	\$400
Syston Donner 1730B, Frequency Synthesizer, .01-26.5GHz	\$6000
Trans. Devices DLR400 15 3500A, Dynamic Load	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load	\$800
Trans. Devices DLVP 130-110-1000	
Electronic Load	\$950
Valhalla 2703, AC Voltage Standard	\$2350
Valhalla 4150ATC, Digital Ohmmeter	\$750
Wavetek 22, 11MHz Sweep Generator	\$500
Wavetek 171, 2MHz Synth. Function Generator	\$450
Wavetek 172, Programmable Signal Source w/Opt. 01/02	\$1500
Wavetek 178, Automatic Synthesizer	\$1700
Wavetek 650, Precision 2MHz Variable Phase Synthesizer	\$1550
Wavetek 852, Dual Hi/Lo Filter	\$1000
Wavetek 2001A, Sweep Generator, 1-1400MHz	\$450
Wavetek 2500A, Signal Generator, 2-11MHz	\$2250
Wavetek 3000-200, Signal Generator	\$900
Wavetek 8003, Precision Scalar Analyzer, 10MHz-40GHz	\$2000
Wavetek 8501, Peak Power Meter	\$2000
Wavetek 8502, Power Meter, 30MHz-40GHz	\$3500
Wiltron 560-7550, RF Detector, 10MHz-18.5GHz	\$300
Wiltron 6747B-20, Frequency Synthesizer, 10MHz-20GHz, w/Opt. 01 & 02	\$13,500



NOTCH FILTERS 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

UNMODIFIED CABLE CONVERTERS. Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VR, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

THE BEST is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at www.acdinc.com for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

PLAYSTATION MOD chips. Works with all models up to 750x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

CABLE TV. Unmodified converters DP5 \$35; DPBB7 \$80; 8500 series \$15, etc., good prices over 100 pcs. Minimum 10 pcs. any qty., plus all major brands available. Lowest price new/refurbished/field pulls. Phone: 1-800-929-1549.

CABLE CONVERTERS, DBS, remotes, schematics, etc., free flyer. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Jake 419-385-3100.



EXPLOSIVE CABLE TV GRAB! BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middleman. Let others get fined & zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! **LIFETIME GUARANTEE!** VISA/MC/AMEX/COD/MO/CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). **SUPER ZAPPER MODULES ONLY \$16! (3/\$33)!** Use **SUPER ZAPPERS** if you have COX, TCI, WARNER in: CA, TX, FL, NY, PA, MI. **DESCRAMBLER PLANS (4=\$5, 20=\$15) 130+ DESCRAMBLER SOURCES (\$5). FREE SHIPPING. OPEN 24 HOURS! 407-654-9677. BRINKER ENGINEERING LABS, USA.**

CABLE STOP, one stop for all your cable needs, a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, 1-800-280-7830 12pm-7:30pm EST.

PLAIN CONVERTERS: Brand-new, the most reliable in the market today. Philips ECG-TV-3000, 181-channel only \$75 ea.; Refurbish Panasonic TZPC-145, \$35; Panasonic-TZPC-175, \$39 minimum 10-lot, 1 full year warranty, same day shipping. 405-634-1535.

RAW CONVERTERS: We have the best quality to your cable needs. PI-5135 \$45 ea.; Zenith ST-1600 \$75; S/A 8590 (11-B) \$85 ea.; S/A 8590 (10-B) \$75 ea. Please call for others not listed. 405-634-1535.

CABLE DESCRAMBLER plans!!! Plus two free bonuses: radar jammer plans & cable manual, \$14. 1-888-367-9972.

POSITIVE NOTCH filters. Channels available: 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, and 25, \$16 each. Channels 26, 27, 28, 29, 30, and 31, \$19 each. Channel 39 \$25 each. Order by single channel. Top quality non-tunable metal cylinder types. 75dB deep on notch. Need to block the video on a cable channel til the kids do their homework, order a negative notch filter from our company. We carry large stock on all channels. Visa, MasterCard, Discover and UPS COD. "The Filter Company" Quantity pricing on 5 or more. 100 pcs. \$7 each. Call 1-800-235-8080. On the web go to www.gofilters.com lots to see. Open 8am to 5pm Central Standard Time, Monday-Friday. All sales must comply with FCC 1996 cable act.

AUCTION AUCTION Auction. Join us online to buy and sell. www.cabletv-auctions.com We have a lot to see. Companies and individuals can put equipment up on the Internet. Cable TV equipment, computers, electronics, telephony, and anything else related. Sell surplus electronic equipment. Phones, faxes. Join us online or call for details. 1-888-451-0083. We advertise in the following publications: USA Today, Nuts & Volts, Popular Electronics, Electronics Now, Popular Science, and Popular Mechanics. Our website is taking 10,000 hits per month. Call to advertise your company. We also advertise in small newspapers in the USA and Canada. You now have pure exposure to the world. Let us help you sell your equipment.

ATTN. DEALERS: Are you a current dealer or just getting started? Buy factory direct & save. New 125 channel volume control converter, 800MHz tuner. Also available non-volume converters. Call for lot pricing. A & S Wholesale, 1-800-370-0801.

TOCOM UNMODIFIED 5503 cable converters, untouched, \$6 ea. 10 lot min. Call 706-657-4445.

BRAND NEW basic converters, 550MHz w/remotes, \$19.95 ea. 10 lot min. Call 706-657-4445.

UNMODIFIED CABLE converters. SA 8590, \$39.95 ea. 10 lot min. Call 706-657-4445.

ZENITH UNMODIFIED converters. ST 1000-288, \$16 ea. 10 lot min., ST 1086, \$25 ea. 10 lot min., ST 1600, \$59.95 ea. 10 lot min. Call 706-657-4445.

BOARD R US, for all your cable needs or computer software, programming service available. 4 MHz resonators 3 pins as low as 34¢. For info call 909-948-3736 or visit us at our web site <http://members.aol.com/BoardRUs>

DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.

CALL US TOLL FREE FOR ALL YOUR CABLE NEEDS. OFFICE HOURS: M-F 9AM-5PM EST. COD ONLY, FREE SHIPPING ON FIRST ORDER. TOLL FREE 1-877-282-7641.

CABLE BROKERS has bought out several cable companies and would like to wholesale the following equipment to other cable companies. The following are field pulls and in 100 lot: Zenith ST1000, \$12; Tocom 5503A, \$3; Tocom VIP, \$14; BBV5S8, \$65; 5135, \$40; 5507 \$25. Sample lots are available with prepay only. Call Jesse 1-888-757-1757.



R & S Surplus

1050 E. CYPRESS STREET, COVINA, CA 91724



(626) 967-0846 • FAX (626) 967-1999

CABLE PARTS! Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

ZENITH ST1086 ST1600, \$5 ea., SA 8510, \$2 ea., plus postage. Bob-Frieders@hp.com or 630-585-2933.

TELEPHONE/FAX

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.



CELLULAR CLONING COLLECTION. 1999 CELLULAR CLONING INFO BIBLE \$22, 1999 CELLULAR CLONING SOFTWARE COLLECTION \$33, 1999 CELLULAR SECRETS & PROGRAMMING MANUAL \$11. ALL 3 FOR \$44, WOW!! (SAVE \$22). FOR EDUCATIONAL/TECHNICIAN TESTING USE ONLY. (VISA/MC/AMEX/COD). OPEN 24 HOURS! 407-654-9677. **BRINKER ENGINEERING LABS, USA.**

12 HOUR fully automatic heavy duty professional **TELEPHONE RECORDER**, \$79 including shipping. Send check or money order to: **VAKIS**, 1402 Pine Ave., Niagara Falls, NY 14301.


CELLULAR PHONES & equipment. 1-800-735-6944, 24 hrs., include area code.

FOR SALE: All items new in MFG box. Toshiba, computer, telephony-system, PC Strata, DK 424, Iwatsu-build Adix, vs to suit your needs. Cortel Co., Aries, digital, key-system, ADKS 144, ACB cards for many applications. Send for mfg. items list. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711.

FOR SALE: GTI phones, send for specifications. Toshiba, Strata DK 424 and Z80 DK 14 and 40, computer telephony integration, wireless telephone system, Aries digital GTI key system, ADKS 144, send for specifications. Applications made to order, desktop #2500 \$3,600 ea. prepaid. Small business guestrooms. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711.


COMPONENTS

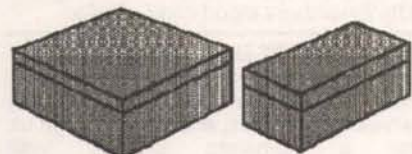WIRE & CABLE: Stranded teflon wire in many colors and gauges. Multi conductor stranded cable on large rolls. Crimp pins for many manufactures connectors, all gold plated, Burndy, AMP, etc. Please call and ask for Bob at 925-449-3961.



POCKET MINI-BOXES: Small plastic boxes. High quality, **LOW COST!** Low as \$0.49. Attention manufacturers! Great for products! 805-339-0702. www.ElectronicsUSA.com

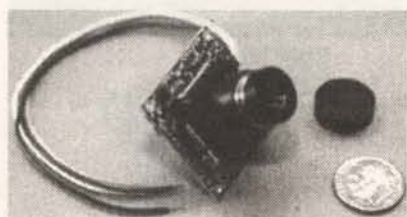SEE OUR ad on 4-channel 2.4GHz wireless system in the AdMart section on page 66. Matco, Inc.



B/W 430 LINE CCD CAMERA with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are avail-

able. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., **\$44 each**. Enclosure: \$8; optional lens: \$18. Dealers welcome. **MATCO, Inc.** 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronicsurplus.com

WANT TO Buy: ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. **Hoffy Electronic Ent.**, 818-718-1165, FAX 818-341-5506. E-Mail: Hoffie1165@aol.com

RF TRANSISTORS, TUBES, SD1446, MRF455, MRF454, 2SC2290, 2SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1947, TIP42C, KIA7217, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG, 4CX250B, 572B, 3CX400A7/8874, 3CX3000A7, 4CX400A, silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS


FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 96 Page CATALOG. Outside the U.S.A. send \$3.00 postage.

PM89 SERIES PANEL METERS

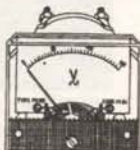3.15" x 2.5" x 2" depth. 2.5% accuracy. Large clear scale, black lettering on white background. Available in a variety of ranges.



DC AMMETERS	CAT #	EACH	10+
0-100 mA DC	PMD-100MA	\$12.00	\$10.00
0-1A DC	PMD-1A	\$12.00	\$10.00
0-5A DC	PMD-5A	\$12.00	\$10.00
0-15A DC	PMD-15A	\$12.00	\$10.00

DC VOLTS	CAT #	EACH	10+
0-15V DC	PMD-15V	\$12.00	\$10.00
0-30V DC	PMD-30V	\$12.00	\$10.00

AC AMMETERS	CAT #	EACH	10+
0-5A AC	PMA-5A	\$12.00	\$10.00
0-15A AC	PMA-15A	\$12.00	\$10.00

AC VOLTMETERS	CAT #	EACH	10+
0-150V AC	PMA-150V	\$12.00	\$10.00
0-300V AC	PMA-300V	\$12.00	\$10.00

1.5 Volt Mini-Vibrating Motor

Tiny 1.5 Volt motor with offset-weighted shaft. Typically found in pocket pagers and cell phones for vibrating alert signal. Operates on 1.5 Volts, 80 mA. Motor body is 0.28" dia. x 0.67" long. Shaft is 0.03" (1mm) dia. x 0.16" long.

CAT# DCM-131 **\$2.50** each

10 for \$22.50 • 100 for \$200.00
500 for \$875.00 (\$1.75 each)

3000 MCD ULTRA-BRIGHT RED LED

Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs "Tape-and-reel" parts. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.

CAT# LED-50

2 for \$1.00 100 for \$35.00
1000 for \$250.00



INCREDIBLY LOW PRICE! Sony Color Video Camera with Audio

Sony# CCX-Z11/S1. Brand new color video camera with audio. Ideal for surveillance or video conferencing. Good-looking, compact design, only 3.5" X 2.33" X 1.05". Adjustable lens. On-off power switch. RCA jacks for video and audio outputs. Includes 4.5 Vdc power supply, output cables and adjustable desktop camera stand which can easily be used as a wall or ceiling mount bracket. Get one now...at this price they won't last. CAT# VC-1100



3 or more \$85.00 each **\$90.00** each

40 RPM Gearhead Motor



Pittman # GM8212C127-R2. Small, powerful gearhead motor. 187:1 ratio. No load specs: 40 RPM @ 19.1 Vdc, 130 mA. 24 RPM @ 12 Vdc, 160 mA. Overall dimensions 3" long X 1.37" diameter. 0.185" (3/16") diameter X 0.75" long shaft. A brass 0.56" diameter gear with 16 cogs is fastened to the shaft. 17" leads.

CAT# DCM-135 **\$15.00** each
10 for \$125.00

"Hi-8" Video Cassette

SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8 **\$3.00** each
10 for \$28.00 • 100 for \$250.00

20 Character X 4 Line LCD

Optrex # DMC 20434-CEM (PWB 20434-CEM) 5 x 8 dot format. 3" x 1" viewing area. 3.88" x 2.38" module. Removed from new equipment. May have felt padding on metal bezel. 14 pin single row header is pre-attached. Spec/hook-up sheet included.

CAT# LCD-46 **\$7.00** each
10 for \$60.00

AIWA "Surround" Bookshelf Speakers



AIWA# SX-ANA72. Great sounding, great-looking set of AIWA "Front 180" bookshelf speakers with a unique "expanded imaging" feature. Uses an array of speakers and ports to project the sound forward and toward the center at a 45 degree angle to create an expanded stereo listening area and the impression of a "center-channel." Each speaker has two channels with two separate input cables. The AIWA stereo system for which they were designed had separate outputs for the center-projecting part of each speaker, but the center-angled speakers sound good when connected in parallel with the front-facing channel. Titan silver and charcoal. Removable front grills. 9.75" wide X 11" deep X 12.25" high.

CAT # SK-72 **\$49.95** per pair

Small Irregular Neodymium

Small arc shaped neodymium magnets with a shiny finish. Sizes vary. The smallest are 0.39" long x 0.15" x 0.085" thick. Some are slightly larger.

CAT# MAG-49 **4 for \$1.00**
100 for \$17.00

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
www.allelectronics.com
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

C and H SALES COMPANY

2176 E. Colorado Blvd. • Pasadena, CA 91107

TOLL FREE:
1-800-325-9465

.....
FREE
148 PAGE
CATALOG!
.....

C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS.
WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!

ELECTRONIC COUNTER

HEWLETT PACKARD, Model 5328A. Universal counter. Usable to 100 MHz, 100 ns single shot resolution. Has frequency, period, period average, ratio, totalize, scale functions. A built-in digital voltmeter allows measurements of input voltages. Two input channels provide individual slope, polarity and level settings. Has 9 digit LED readout. Input power 100-240 VAC 48-66 Hz 100 VA max. Dimensions: 17" wide x 17-1/4" deep x 3-1/2" high.

Stock #TE9808

\$250.00



MILLIOHMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 u ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special 4 terminal probes which are not supplied, but probably are available from Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.

Stock #TE9812

\$200.00



ALTIMETER/BAROMETER

KOLLSMAN, #MC-2 MS28074-2. Scale type altimeter with barometric setting scale window. Altimeter scale range -1000 to 80,000 feet. Barometric range 28.1 to 31.0 inch of mercury. An adjustment knob is provided for scale setting to local altitude or barometric pressure. Has white numerals on a black background. Illumination is provided. Electrical input is rated 115 VAC 400 cycles. Pressure input port is female 7/16" X20 thread. Standard aircraft panel 3-1/8" mount. Dimensions: 2-17/64" sq. x 7-1/2" deep.

Stock #STOCK #IN9900

\$79.50




SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #93-13-150. Harmonically neutralized constant voltage transformer. Rated at 500 watts. Input voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC. This unit is designed for rack or bench mounting. The meters on the front panel indicate output current and input/output voltage. A toggle switch is provided for selection of input or output voltage. The input voltage is connected at the rear of the unit via a covered electrical panel. Two standard 3-wire grounded electrical outputs are supplied on the front and rear panels. Dimensions: 19" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR9900

\$225.00

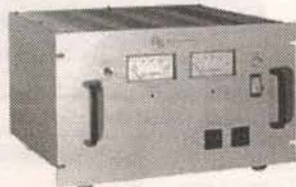


☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

WE BUY & SELL!

Write in 65 on Reader Service Card.

MICROCONTROLLERS

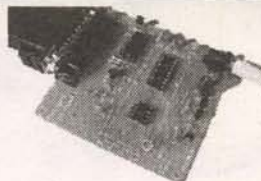

PIC MICROCONTROLLER PROGRAMMER KIT. Super value at \$19.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. www.electronics123.com

Programming and Customizing BASIC Stamp Computers. By well known author Scott Edwards, originator of the *Nuts & Volts* Stamp Applications column. Only \$34.95. **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

WIN \$500 USD cash dontronics.com

ANTIQUE ELECTRONICS

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

Sell Nuts & Volts
in your store and earn \$\$\$!
Contact us for details.
909-371-8497
E-Mail distributors@nutsvolts.com

AVIATION ELECTRONICS

BUY, SELL, trade, avionics equipment, Collins, King, Sperry: test equipment, IFR, Litton LTN series INUs. 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

PUBLICATIONS

Discount electronics books. See the NV Bookstore ad on page 91.

WEBBOOKS OFFERS discount prices on technical/engineering books plus free assistance to authors. Please visit us at <http://webbooks.net>

Handbook of Radio and Wireless Technology, by Stan Gibilisco \$44.95 **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

Programming and Customizing BASIC Stamp Computers. By well known author Scott Edwards, originator of the *Nuts & Volts* Stamp Applications column. Only \$34.95. **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

NEW SURVIVAL COMMUNICATIONS BOOK. How to build complete home communications systems. Covers all needs: shortwave radio, amateur radio, citizens band, scanners, federal, weather, alternate news, satellite radio, equipment sources. How to build and use alternate emergency power sources, solar, generators, backup batteries. 200 pages. \$24 Fast delivery Priority Mail. MC or Visa. Call Universal Electronics 1-800-241-8171.

TORMET'S ELECTRONICS BENCH REFERENCE is now at REV03. More laser, op-amp and Tesla coil circuits. New optics and statistics pages. Check the web site at www.ohio.net/~rtormet/index.htm or send \$19.95 + \$2.50 postage to RMT Engineering, 6863 Buffham, Seville, OH 44273.

ROBOTICS

ROBOT BOOKS.COM visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

ARobot KIT from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

H-BRIDGE MOTOR controllers, 12VDC, 35A average, 50A peak PWM out. Forward, reverse, ramp-up and ramp-down on acceleration/deceleration. Current foldback when hot, reverse polarity protected, conformal coated, regenerative braking, compact, approx. 3.75"x5.5". \$25 & S&H. 570-735-5053. <http://members.tripod.com/~divelec>

S.A.M. ROBOT kit. Build this great looking small robot with your servos, microcontroller, and sensors. Or buy servos, wheels, controllers, and sensors from us for a complete project. Visit <http://www.smallrobot.com> for details.

3 AXIS stepper motor driver \$85, 2 amp, controlled through parallel port, 5 inputs, 4 outputs. 110 oz/in stepper motors, \$15 each. www.brewingtons.com

CABLE TV CONVERTERS

WILL NOT DECODE

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

TIMELESS PRODUCTS

New! "TP 125 V"
128 Channel Converter with Volume


Special Prices for
TP1550PC
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES

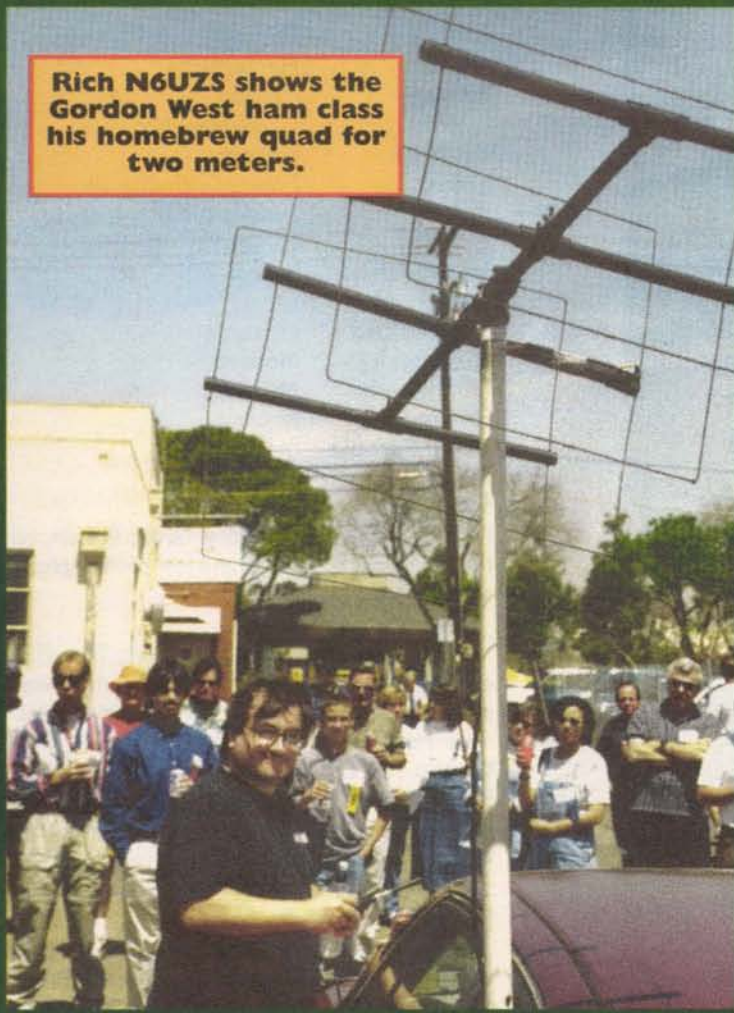Rich N6UZS shows the Gordon West ham class his homebrew quad for two meters.



HAMS HAPPY IN HOLDING PATTERN

Ham radio operators throughout the United States are getting the royal treatment from equipment manufacturers and dealers in preparation for the long-awaited amateur radio service restructuring rules.

be up! Look for ULS going "on line" this month as you read this article.

The amateur radio rules restructuring continues in a holding pattern with the majority of hams hoping it will become law, soon. There is GOOD NEWS for ALL hams when restructuring goes through at the beginning of next year:

1. Technician-Plus operators will gain worldwide radio-band privileges.
2. Proponents of Morse Code will see more No-Code Technician class hams actively learning the code at the required 5 wpm than we have ever seen before.
3. Present General class hams could be grandfathered to the next license class higher with no additional code test.

The teaching of ham operators from start to Technician-Plus (plus the code at 5 wpm) will be a lot easier after the ham rules restructuring. The Novice written examination will probably be eliminated, cutting out 483 questions that need to be memorized. This would leave just Technician class written questions — now 441 with 35 multiple-choice Q & A's on the test — plus the Morse Code. This will allow instructors more time to teach the real world of ham radio operating, rather than the simple memorization of test question answers. And for proponents of all hams knowing the code, General worldwide privileges will certainly cause the new ham to want to learn the code at a basic 5 wpm. And for Technician operators who just want VHF and UHF privileges only, no code is required!

For the present General class operators, chances are they will be grandfathered to the next license class up. And we still don't know whether or not they are going to combine the Advanced class and Extra class into one single license class, nor do we know whether the top class code test will stay at 20 wpm, or drop to

13 wpm.

Right now, no-code ham operators are learning the code at 5 wpm, and passing the code test to become Technician-Plus operators. When the new restructuring rules go into effect next year, they MAY be grandfathered to the 5 wpm new General class license, and may or may not need to take one additional relatively simple General theory test. We must wait until the rules are finally announced before we see the precise details. But if you are a No-Code Technician class operator now, or are thinking of getting your ham license soon, get the 5 wpm code test out of the way and then let the rules catch up to you.

JUST ANNOUNCED — 5 WPM FOREIGN WORLDWIDE APPROVAL

Late-breaking news here! On June 7th, 1999, our

AT THE FCC

The FCC is behind schedule on several items originally intended for the "fast track" Rulemaking. More important business comes first before the amateur radio hobby service. The FCC is undergoing moving pains — leaving their long-time M Street location to less-expensive digs. The FCC is also focused on the start-up of the Universal Licensing System (ULS) which will shortly eliminate the need for filing complicated forms by snail mail.

The ULS has been a long time coming, and thanks to the amateur radio service, our Volunteer Examiner Coordinators have proved that the system indeed works because ham test bosses have been filing applications electronically (before any other service!) for the last several years with superb results.

But under the new ULS where YOU may get to do your own electronic filing, you're going to need to divulge something that you may have kept secret for some time — your Social Security Number. No one will see it but the FCC, who may share it with government tax collectors, so don't worry about other hams knowing your secret SSN. But if you have been dodging some back taxes, the feds are now comparing electronic applications, and your "number" might

High-frequency
privileges to
the TechPlus
ham means
more antennas
on the vehicle!





Kid's Day on ham radio, with author West teaching 80 kids ham radio basics.



FCC announced an agreement with European countries to allow USA Technician-Plus hams full worldwide operating privileges when vacationing or visiting the following participating CEPT countries:

Austria	Belgium
Bosnia	Herzegovina
Bulgaria	Croatia
Cyprus	Czech Republic
Denmark	Estonia
Finland	France (including all possessions!)
Germany	Hungary
Iceland	Ireland
Italy	Latvia
Liechtenstein	Lithuania
Luxembourg	Monaco
Netherlands	Norway
Portugal	Romania
Slovak Republic	Slovenia
Spain	Sweden
Switzerland	Turkey
United Kingdom (including Great Britain, Northern Ireland, Channel Islands, and Isle of Man, plus UK possessions)	

At present, your amateur radio Tech-Plus license doesn't afford you all worldwide bands of voice operation in our country — not until the rules change over here sometime this winter. But right now in Europe, you can go over there with your ham Tech-Plus ticket and instantly operate on all worldwide ham bands using voice or any other type of approved emission. And for boaters, this gives you instant operating privileges when cruising some of the French possessions in the South Seas.

And more good news — some Latin American countries are coming onboard with this same type of agreement, too. And for operation in Mexico, a little paperwork and paid pesos down there can also give you instant worldwide privileges with the Technician-class license.

So, it looks like the entire world will soon allow worldwide operating privileges for voice with a maximum required code speed of only the simple 5 wpm level.

INDUSTRY REACTION

Ham radio equipment manufacturers, ham accessory makers, and ham dealers are just as happy as the hams are over the proposed rule restructuring. Even those hams who hold learning Morse Code as a sacred initiation to the hobby concede that they are now seeing their Morse Code learning classes



Moving Sale

Equipment Management Technology

Tel 650-631-1700 Fax 650-631-1200 Email sales@emt1.com

SELECTED SPECIALS!		
HP 16505A \$250	HP E1345A Make Offer!	<p>We buy, rent, and sell high quality test and measurement products. We occasionally offer great deals on computers as well.</p> <p>HP OmniBook 600C color subnotebook weighs a mere 3.7lbs for ultimate portability. Special Nuts & Volts price is only \$250!</p> <p>Dave is test equipment! Bigdave@emt1.com</p> <p>Kerry is computers! kwhite@emt1.com</p>
HP 16510A \$100	HP E1347A Make Offer!	
HP 16515A \$100	HP E1364A Make Offer!	
HP 16516A \$400	HP E1400B Make Offer!	
HP 3314A \$1400	HP E1401A Make Offer!	
HP 5335A \$500	HP E1662A Make Offer!	
HP 59501B \$250	HP E1671A Make Offer!	
HP 6266A \$250	HP E1672A Make Offer!	
HP 8016A \$500	HP E1681A Make Offer!	
HP 83545A \$3850	HP E1682A Make Offer!	
HP 8493B \$100	HP E1693A Make Offer!	
HP 8958A \$5000	HP E1725A Make Offer!	

NEW ADDRESS

956 Bransten Road
San Carlos, CA 94070

WHOLESALE CABLE

COMPLETE LINE OF CABLE PRODUCTS

- ☒ Quality merchandise by brand name manufacturers
- ☒ Satisfaction guaranteed ☒ Free gift on first order
- ☒ Technical support
- ☒ 2 year warranty on new converters
- ☒ COD shipping & overnight shipping by request
- ☒ Experience where it counts ☒ Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES

WHOLESALE CABLE M-F 11am-6pm EST (718) 206-0879
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.

Tell us the best price you were offered, where you got it from, and let us try to beat it.



brim full with everyone looking to pass the ultra-easy 5 wpm FCC code test. "At first I was against a slower code test, but now that I see the popularity of learning the Morse Code coming back, I am beginning to think that 5 wpm is an easy way to pack our classrooms with students who want to learn the code, and many who will continue to go beyond 5 wpm for the higher grade tickets," comments William Alber WA6CAX, an amateur radio code instructor in the San Francisco Bay area.

A pro-code group called FISTS indicated their displeasure with the proposed rules and felt that equipment manufacturers were behind the rules to simply sell more high-frequency gear. I can tell you first-hand that equipment manufacturers had NOTHING to do with the proposed Rulemaking. All of the initial proposed Rulemaking and comments to the Rulemaking are in the public domain, and you won't see any of the manufacturers who made any petition to the FCC for changing the ham rules for increased worldwide radio business.

But I can also tell you that they are gearing up for some exciting high-frequency and VHF/UHF equipment sales! ICOM America and Yaesu are battling it out with a \$1,349.00 transceiver that goes from 500 kHz all the way up to the 440 ham radio band, multi-mode, full transmit and receive operation, with power outputs to rival separate home-station equipment. For ICOM, it is their new IC-706 MKII-G, and for Yaesu it is their new FT-100. The only ham band they don't include is 222 MHz, and this being only a USA band from an international style radio, we can see why maybe it was left out. But no problem — you get all of the ham 440 MHz for transmit and receive, all of two meters multi-mode transmit and receive, six meters, and all of the HF worldwide ham bands lower in frequency. The equipment is not much larger than a 50-watt mobile single-band ham set, and the equipment can also separate the head from the body allowing for remote installations.


The most often asked question, lately, is which set is better — I am continuously testing both units, and they both are PHENOMENAL!

Kenwood continues with their popular TS-50 high-frequency transceiver, and this set has been such an incredible performer for so many years that they will probably keep it in line when the new rules change. And same thing for Alinco — their DX-70 and DX-77 have been around for several years, and continue to be price-busters like the Kenwood equipment seen selling for under \$799.00. In fact, at a recent hamfest, I found the Alinco DX-70 selling for an incredible \$579.00 brand new, including 10 watts on six meters, too!

And the color LCD thin-film transistor (TFT)

panel from ICOM's IC-2800 is making quite a hit. This transceiver covers the two-meter band and the 440

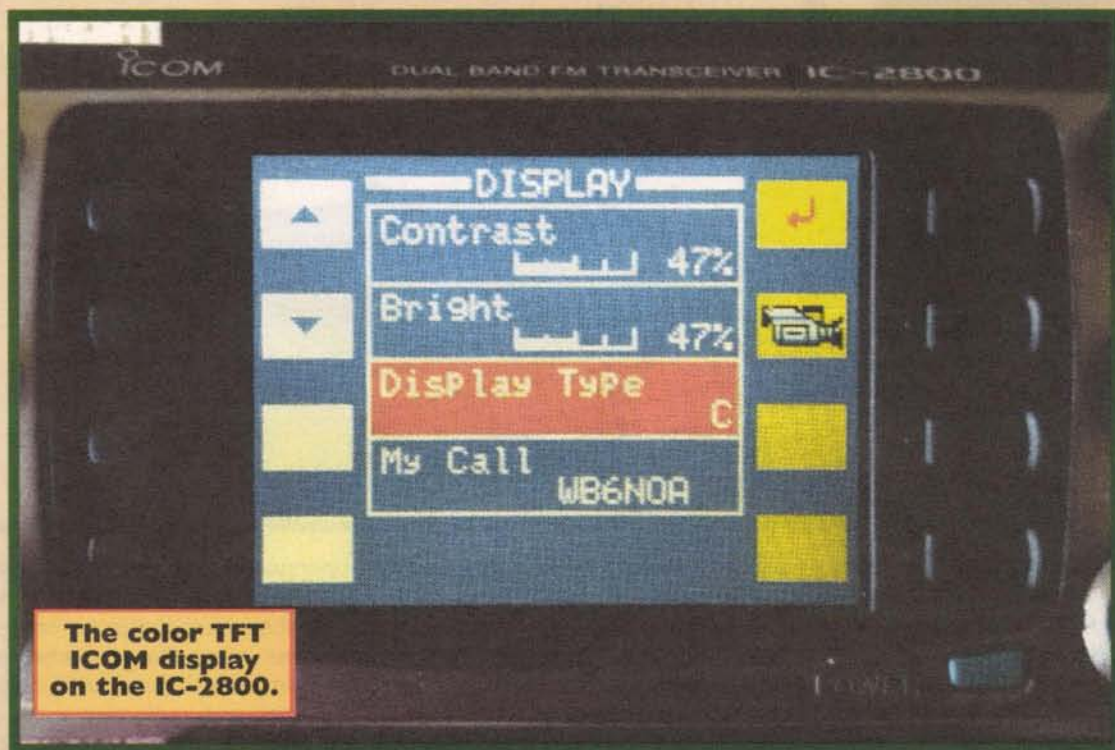MHz band, and the remote head three-inch TFT color LCD works great under the dash, and can even




The color TFT ICOM display on the IC-2800.

The new ICOM IC-2800 full-featured mike.



5 Axis Robotic Arm Kit

\$195.00 Plus S&H

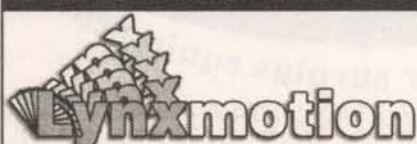

You can build this Robotic Arm!

Impressive, fast, accurate and repeatable motion. Any computer capable of sending 2400 or 9600 baud serial data can control the arm, even a Basic Stamp! This arm makes a great foundation for AI and motion control experiments. Position the arm in an X, Y, Z, grid with a joystick or keyboard using the new RoboMotion for Windows. The kit includes all of the hardware and structural components, six quality Hitec HS-300 servos, pre-assembled SSC servo controller, DOS and Windows software, and an illustrated assembly manual.



We have many more cool robots, check out our web page or ask for our free catalog!
3 Axis Version \$155.00 • Mobile Version \$250.00 • Mobile Robots Book \$32.00

Lynxmotion, Inc.
104 Partridge Road
Pekin, IL 61554-1403 USA
<http://www.lynxmotion.com>



Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com

Write in 186 on Reader Service Card.



EPROM+

A device programming system for design, repair and field service

- ◆ EXCEPTIONAL POWER FOR THE PRO
- ◆ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EPROMS* (24, 25, 85, 93, 95, 80011A) PLUS ERI400/MS8657* BIPOLAR PROMS* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATTEL MICROS*(89S, 90S)(AVR) PIC MICROS* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

\$289

- Includes step-by-step tutorial plus explanation of EPROM fundamentals
- 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE
- *REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)


ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150

(513) 831-9708 FAX (513) 831-7562

website - www.arlabs.com

email - arlabs@worldnet.att.net

MADE IN THE U.S.A.

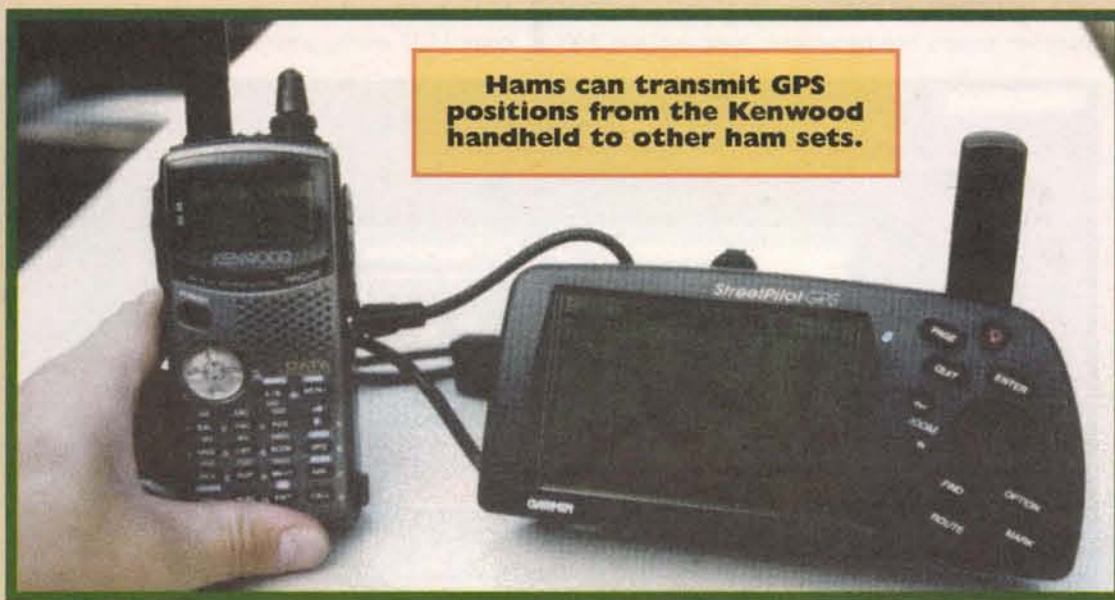

take an external video from a VCR or back-up camera and show it on the screen, too. The display could also show a GPS map in conjunction with car navigation equipment, as well!

Premier Communications ADI Company is also poised and positioned to satisfy the anticipated influx of new hams with a new two-meter mobile — the ADI AR-147 — along with ADI Premier handheld accessories including one of the neatest earphone/concealed hand mic systems for any type of HT. The FBI and CIA would be envious where they could see the almost invisible earphone and the concealed hand mic for clandestine HT operation.

Call Ken and Heather at ADI for their fact sheets at 714-257-0300. Also ask to see their catalog on their ultra-small, camouflaged FRS, 14-channel, UHF handie-talkie. By the way, when I get calls from parents who question whether or not their kids might

make good ham operators, I tell the parents to get a pair of Family Radio Service handhelds and see how the kids take to operating them. If they try to figure out ways to get further range than the advertised one or two miles from the 1/2-watt UHF output, chances are this tinkering with radio electronics is a good sign that the kids will probably make terrific ham radio operators. Try that trick; it works!

Ham radio accessories giant MFJ Enterprises (601-323-5869) is also gearing up for the influx of new hams entering the hobby, as well as existing hams wanting to upgrade their equipment for high-frequency worldwide capabilities. MFJ has announced some lightweight switching power supplies that can handle up to 45 amps and only weigh in at five pounds! They are low-noise, and work great. I also like the MFJ-259B SWR analyzer that will check out any HF and VHF antenna system from 1.8 MHz to

170 MHz. Just hook up the coax, turn the meter on, and swing it through the bands, and see where you need to do some pruning or lengthening of the antenna elements to bring it into a perfect match.

And speaking of worldwide antennas, there's a great book out there on *Frequently Asked Questions About Wire Antenna Systems* by well-respected ham Jim Thompson W4THU. Jim and his wife run (and own) Radio Works (Portsmouth, VA; 757-484-0140) which specializes in wire antennas and baluns. We recently tried out his CAROLINA WINDOM on high frequency, and Mike and Sally Davis (K7ACM and KK7IO) swear by its operation over a traditional five-band trap vertical.

"When I switched from the vertical over to the Carolina Windom from Radio Works, I can now stay in touch with both long-range DX, as well as locally to my SkyWARN buddies," comments Sally Davis, an avid SkyWARN weather-watcher.

The expected explosion of ham radio recruitment has led to large telecommunication accessory companies coming up with products specifically for the amateur radio service. Well-known six-meter DXer Tom Glaze K4SUS, has an inexpensive (under \$20.00) VHF/UHF compact dipole with a small cable attachment to interchangeable connectors that works great for both classroom demonstrations, as well as in-the-field work. Screw on the specific connector type for your particular handheld, and you are on the air. It also works on land mobile, marine, and aircraft frequencies, too (Antenna World, Miami, FL; 305-471-9507).

OOPS — Here's something that's maybe NOT so great for the ham UHF operator, and that is those wireless weather stations that may be fun to look at, but noisy for the 70 cm band. The problem is where the weather stations transmit their wireless information back to the fancy LCD displays ... around 433 MHz. I recently discovered an irritating once-a-

E-Math Pro Windows version!

E-Math is the Essential Formula Tool for Engineers, Technicians, and Students.

Features

- Over 300 formulas
- Ability to rotate equations.
- Solve for any variable.
- Help for each equation.
- Win95, Win98, NT compatible

Formula Categories:

- (A) Fundamental DC Formulas
- (B) Fundamental AC Formulas
- (C) RL and RC Circuits
- (D) RLC Impedance Magnitude and Phase
- (E) L's, C's, R's and Conductors
- (F) Magnetics #1, Basic Equations
- (G) Magnetics #2, Losses
- (H) Magnetics #3, Design Equations
- (I) Waveshapes and Miscellaneous Power
- (J) Transmission Lines
- (K) Pulse Forming Networks
- (L) Buck and Boost Topologies
- (M) Flyback and Forward Converters
- (N) Half/Full Bridge and Push-Pull Topologies
- (O) Passive Filters
- (P) Active Filters
- (Q) Thermal Calculations
- (R) Semiconductors and Integrated Circuits
- (S) Radar, Antennas and Noise



E-Math Pro Windows v1.0
\$49.95

Bytech Services
www.bytechservices.com
US Toll-free: 1-888-422-7521
Voice/FAX (360) 422-7520

Dealer and Distributor
inquiries — YES



Bytech Services

Metric
Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886

www.metricsales.com

RENT • BUY • SELL
Yes, we will buy your surplus equipment!

Scopes, Meters, Analyzers, Power Supplies, Signal
Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu,
Wavetek, Keithley, and more

Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty

Save 30-90% • 5-Day Free Trial

minute data burst square on the weak signal 432.100 MHz frequency that would just about knock my ear-phones off when straining to listen to the distant Hawaiian radio beacon. I tracked it down to a water temperature floating sensor on a pool five houses down the street. This is about the extreme range of a Part 15 transmitter, but nonetheless, I had to convince my water-loving neighbor that they really wanted to send it back to the manufacturer for a different frequency because the frequency they were on would probably cause irreparable damage to their VCR library just a few feet away. They bought the warning, and a few weeks later the signal was nowhere to be found on UHF. I suppose those VCR tapes are now "interference free."

We know that the present ham operators with almost any class of license are still hot with their hobby — many going into the all-receive mode when going to ballgames, car races, airshows, or marine stadium events. The Optoelectronics R11 near-field receiver is one of MY favorites because it tunes from 30 MHz to 2,000 MHz and can lock onto a 5-watt 460 MHz frequency as far as 500 feet away in less than a second. Down on 150 MHz, it listens even further! Great stuff from the Opto gals and guys. Look at their web site (Optoelectronics web site www.optoelectronics.com).

I also tried out some of the scanners from AOR USA (Torrance, CA; 310-787-8615), and recently enjoyed scanning in England with the AR-8200 described last month, and now I'm working with their little tiny AR-16; and although it doesn't give me high-frequency scanning, it does a terrific job on the VHF and UHF bands. All the gang at AOR are active hams; and when the new rules hit, they promise me some new and exciting products that will really add to our popular amateur service.

FROZEN POOLS AND HOT OPPORTUNITIES

The pending Rulemaking has caused all of the ham radio written question pools to be frozen. This is good news for those of you preparing for Advanced class — the July 31st, 1999 cut-off date has been thrown out, so your present manual for Advanced and all of the other question pools from beginning to top remain


GORDON WEST HAS JUST ANNOUNCED A SIX-CASSETTE MORSE CODE HOME-STUDY COURSE SPECIFICALLY FOR PASSING 5 WPM AT ANY EXAMINATION SITE IN AND OUT OF THE COUNTRY. THE COST FOR SIX LONG-PLAY AUDIO CODE-LEARNING CASSETTES IS \$35.00 (INCLUDES POSTAGE) FROM GORDON WEST RADIO SCHOOL, 2414 COLLEGE DRIVE, COSTA MESA, CA 92626. CHECKS, CASH, OR MO, PLEASE.

unchanged.

Same thing for the 5 wpm code test — examiners are not permitted to make it any harder even though the applicant will gain additional worldwide privileges after the rules change sometime this winter. This is why I recommend hams with a Technician No-Code license bring in the six-tape code-learning course for anyone tone deaf to dits and dahs. I was in a good mood when I put this one together and, so far, everybody that gets through all six tapes has been 100 percent successful when they sit for the 5 wpm code test that will add to their Tech-license worldwide privileges in Europe right this minute, as well as

add to worldwide privileges here in the USA within the next six months. Do it now before the code test gets more complex!

It's going to be a great year for ham radio — everyone is positive with the restructuring rules, the equipment is continuing to stay priced within reach, features are up at steady prices, and the disappointment of bombing an exam at the test center will be way down when new hams will only need to learn half the questions to be able to get the Technician-class privileges. If you are a ham, stay tuned into the ham scene because plenty will be changing within days or weeks, or certainly months. **NV**

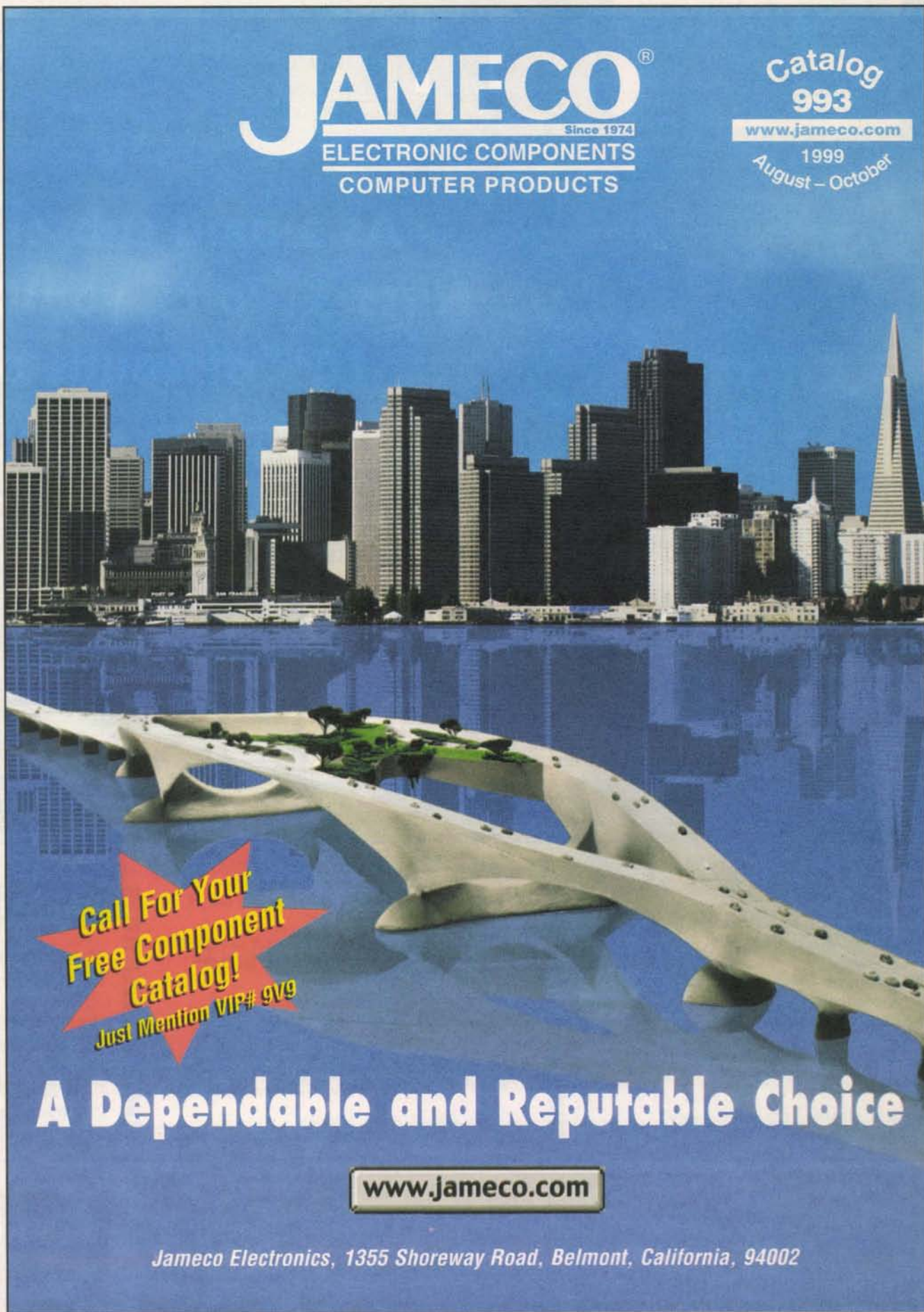

JAMECO[®]
Since 1974
**ELECTRONIC COMPONENTS
COMPUTER PRODUCTS**

**Catalog
993**
www.jameco.com
1999
August – October

**Call For Your
Free Component
Catalog!**
Just Mention VIP# 9V9

A Dependable and Reputable Choice

www.jameco.com

Jameco Electronics, 1355 Shoreway Road, Belmont, California, 94002

Build your electronics library at a price you can afford!! Order now from the Nuts & Volts Bookstore!!

September's Featured Titles

by Joseph J. Carr

SECRETS OF RF CIRCUIT DESIGN

\$29.95



From one of today's most respected electronics authors comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.

PRACTICAL ANTENNA HANDBOOK

\$49.95



The most popular book on antennas ever written, widely known as "the antenna builder's bible." This *Third Edition* is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.



\$34.95

"Programming and Customizing the BASIC Stamp Computer" by S. Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.



\$44.95

"Handbook of Radio and Wireless Technology" by S. Gibilisco

A comprehensive compendium on the entire field of radio and wireless technology.



\$39.95

"Encyclopedia of Electronic Circuits" Vol. 7 by R. Graff

An extensive library of 1,000 circuits from the bestselling, seven-volume "Encyclopedia of Electronic Circuits."



\$54.95

"Handbook of Microcontrollers" by M. Predko

This much-needed reference is the first to cover all the most common types of eight-bit microcontrollers.



\$39.95

"Circuit Troubleshooting Handbook" by J. Lenk

This handbook gives full descriptions of the operation of important circuits, and how each circuit's characteristics may figure in its failure or poor performance.



\$24.95

"How Electronic Things Work ... and What to Do When They Don't" by R. Goodman

Never again be flummoxed, flustered, or taken for a ride by a piece of electronic equipment with this fully illustrated, simple-to-use guide.



\$34.95

"Electronic Troubleshooting" by D. Tomal and N. Widmer

Troubleshoot and repair any type of electronics with this comprehensive guide.



\$39.95

"Programming and Customizing the 8051 Microcontroller" by M. Predko

This tutorial/disk package details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices.

BOOKS PUBLISHED BY MCGRAW HILL

OTHER AVAILABLE TITLES ...

"The Illustrated Dictionary of Electronics" by S. Gibilisco \$39.95

"The Robot Builder's Bonanza" by G. McComb \$18.95

"Programming and Customizing the PIC Microcontroller" by M. Predko \$34.95

"How Radio Signals Work" by J. Sinclair \$24.95

"Making Printed Circuit Boards" by J.L. Axelson \$22.95

"TAB Encyclopedia of Electronics for Technicians and Hobbyists" by S. Gibilisco \$69.50 (Hard Cover)

"How to Read Electronic Circuit Diagrams" by R.M. & Lawrence Brown \$19.95

"Build Your Own Test Equipment" by H.L. Davidson \$22.95

"Radio Receiver Projects You Can Build" by H.L. Davidson \$21.95

"Basic Electronics Theory" by D.T. Horn \$26.95

OTHER AVAILABLE TITLES ...

"Troubleshooting and Repairing Consumer Electronics Without a Schematic" by H.L. Davidson \$24.95

"Amateur Radio Encyclopedia" by S. Gibilisco \$50.00 (Hardcover Only)

"Ready-to-Build Telephone Enhancements" by D.T. Horn \$17.95

"The Benchtop Electronics Handbook: 260 Most Common Popular Electronics" by V. Veley \$65.00 (Cloth Cover)

ORDERING INFO

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 91719. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. ALL ORDERS MUST BE PREPAID.

Call 1-800-783-4624 today!
WE ACCEPT VISA AND MASTERCARD

POWERPOINTING YOUR PROJECTS

Part I

This article describes the use of Microsoft's PowerPoint for creating a personalized "palette" of schematic symbols and a "toolkit" for creating PC board drawings.

This member of Microsoft's Office suite is most commonly used for doing slides for business presentations, but I found that I could adapt it for electronic hobby applications; it offers a large repertoire of standard lines and shapes that can be combined to create schematic symbols, and its precise drawing features make it easy to create accurate, actual-size artwork for transfer to a PC board.

An added bonus is that, as a component of MS Office, it is already paid for. Also, it integrates perfectly with the other members of the suite — Word in particular — for situations in which I want to marry text and graphics.

This article describes the use of PowerPoint for creating a per-

sonalized "palette" of schematic symbols and a "toolkit" for creating PC board drawings. We will then go through the complete process of drawing a simple schematic for a two-chip oscillator circuit (suitable for use as a warning or alarm signal). Part II will describe the construction of a second palette and toolkit for creating component layouts and the artwork for a PC board.

A few cautions: First, I am presuming that you are familiar with the basic functions of PowerPoint for drawing lines and simple shapes (with and without the Snap To Grid feature), moving them around, re-sizing and grouping them, and adding text boxes within a slide that contains a drawing. If you have never used


by Steve Daniels

As an author and hobbyist, I need to create several drawings for every construction project, both for my own reference and to be able to share my ideas with others. For a typical project, I

need four drawings: a schematic; a component layout drawing; an etch pattern for making a PC board; and an "x-ray" drawing that shows both the component layout and the PC board traces.

While there are a number of specialized (and often expensive!) software packages available for doing technical drawing, I have long used Microsoft's PowerPoint.

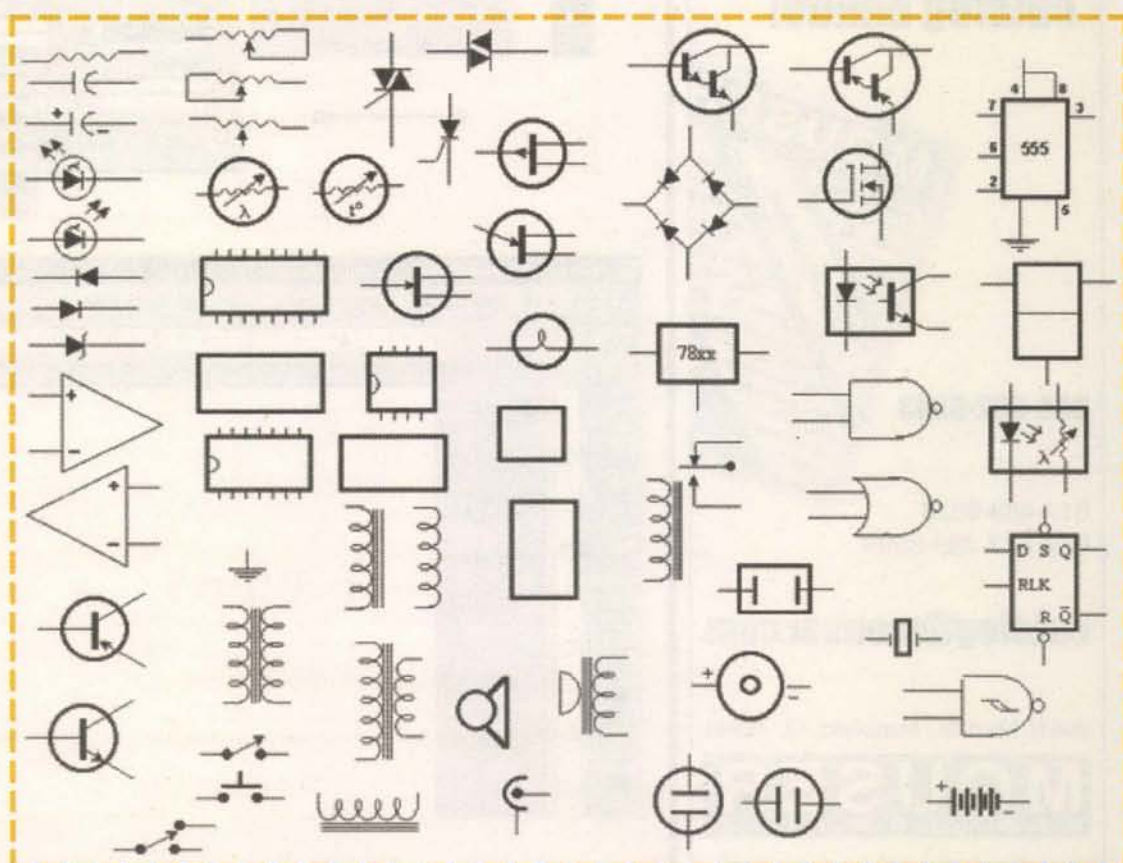This member of Microsoft's Office suite is most commonly used for doing slides for business presentations, but I found that I could adapt it for electronic hobby applications.



PICmicros & BASIC

PicBasic Compiler - \$99.95

PicBasic Pro Compiler - \$249.95

Now it's even easier to program the fast and powerful Microchip PICmicros. The PicBasic and PicBasic Pro Compilers convert your English-like BASIC programs to files that can be put directly into a PICmicro. True compilers for faster, longer programs. BASIC Stamp™ I/II* libraries. For mid-range PIC12C67x, 14Cxxx, 16C55x, 6xx, 7xx, 8x, 87x, 9xx and high-end 17Cxxx (PicBasic Pro only).

*BASIC Stamp is a registered trademark of Parallax Inc.

New! PIC-XI
Experimenter/
Lab Board

Assembled - \$199.95
Kit with parts - \$139.95
Bare PCB only - \$49.95



EPIC Plus PIC Programmer - \$59.95



Programs PIC12C5xx, 67x, 14Cxxx, 16C505, 55x, 6xx, 7xx, 8x, 87x and 9xx.

Optional ZIF adapters for DIP, SOIC, MQFP, PLCC.

Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

PICProto
Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds PICmicro, 5V reg, caps, oscillator, DB9-25, large proto area. \$8.95 - \$19.95




microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933
(719) 520-5323 (719) 520-1887 fax
<http://www.melabs.com>

Write in 107 on Reader Service Card.

www.mouser.com

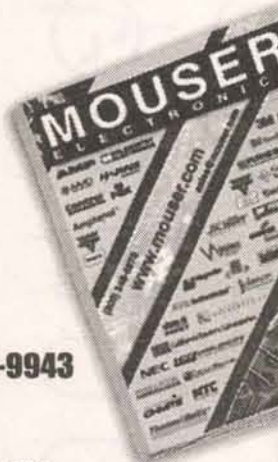Subscribe,
download, or view
catalog online!



800-992-9943

817-483-6828


Fax: 817-483-6899

catalog@mouser.com

958 N. Main St., Mansfield, TX 76063

MOUSER
ELECTRONICS

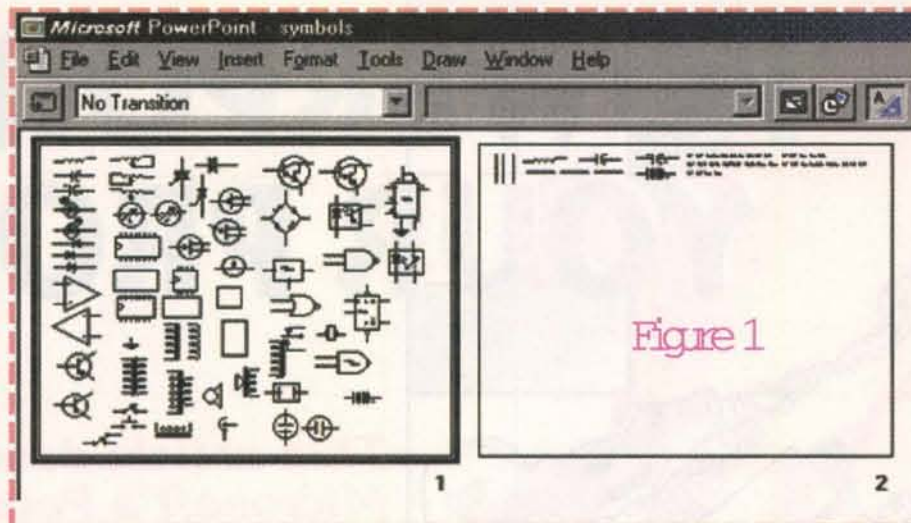POWERPOINTING • POWERPOINTING • POWERPOINTING



PowerPoint or have only limited experience with it as a drawing tool, I suggest that you go through one of the many tutorials or references available for this program before going further.

Second, all of my commands and menu designations apply to PowerPoint 7.0; if you have a different version, many of the commands will be in different places. That said, however, the general method described in this article will still work.

As far as hardware goes, a 15" monitor is bare minimum and a 17" or better is preferred for this application. Fortunately, the larger format is much cheaper than it once was and is practically standard equipment with new home systems.




Last, while I have gotten good results for hobby purposes, realize that PowerPoint isn't a CAD program and PC monitors aren't the most sophisticated of graphics displays. Most people will have to create the palette of symbols at high magnification — 200 percent or 400 percent — and then zoom down to 100 percent to have sufficient room on screen to create a schematic.

The re-scaling distorts a few lines in the display, but symbols will still print okay. Also, in my experience, complex figures will not always copy perfectly from palette to composition area and will need minor re-touching. If you can live with this, you'll be pleased with the printed results.

The Schematic Palette

Figure 1 shows two slides in Slide Sorter view. Slide 1 is the palette that contains several dozen symbols from which we can choose. Slide 2 is the "composition" area on which new schematics are drawn. For convenience's sake, a few very commonly-used symbols (resistor, capacitor, ground, etc.) and designators (R1, C1, etc.) are placed on the upper edge of slide 2.

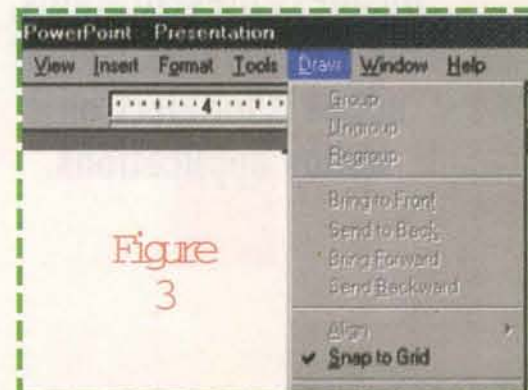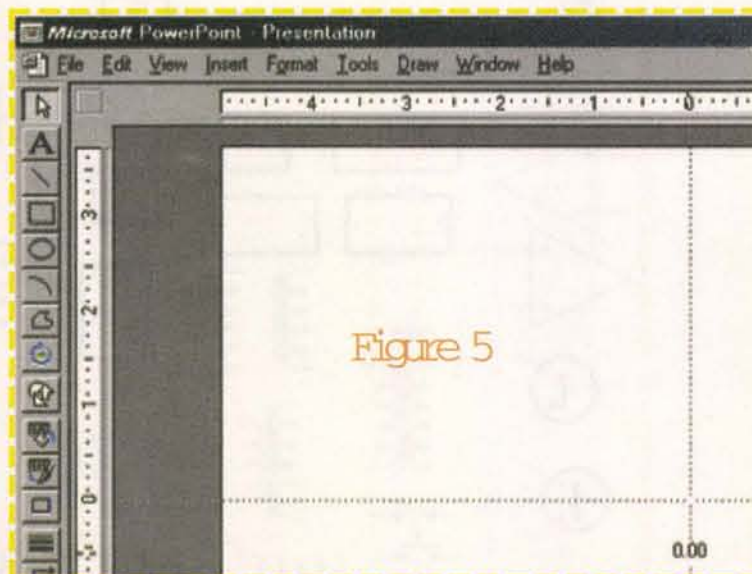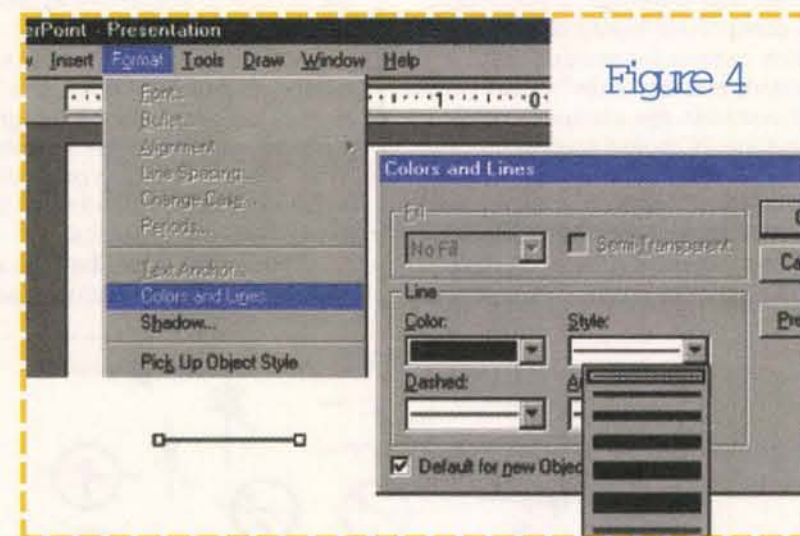To begin creating the palette, make sure that your display resolution is 600 x 800 pixels (for a



17" monitor) and open a new PowerPoint file. Create two slides in the usual way, and remove the placeholders that PowerPoint inserts by default. The slide orientation (set this in the File menu under Slide Setup, if necessary) should be Landscape; slide size 7.5 by 10 inches for an 8-1/2 by 11 sheet.

Drawing Our First Symbols

Refer to Figure 2. With the palette slide active, set PowerPoint's magnification to 400 percent in the View menu. We will be using PowerPoint's precise drawing features, so make sure that the Ruler and the Guides are checked in the View menu. Snap To Grid (set in the Draw menu, see Figure 3) should not be active for now. The line style (set in the Format menu, see Figure 4) should be at its thinnest setting, and the Default For New Objects box should be checked.


If you have never used PowerPoint's precise drawing features, now is a good time to learn. Having checked Guides in the View menu, you'll notice that the slide is bisected by two dotted guide lines (Figure 5). Move the mouse pointer so that the arrow touches the vertical guide, and then press and hold the left mouse button. The number 0.00 appears, which represents the present centered position of the vertical guide.

If you drag the mouse to the right or left (refer to Figure 6), you will notice that this number increases in increments of .01 inches. Also, an arrow points right if you are right of center and left if you are left of center. Try the same experiment with the horizontal guide; you'll find that it works similarly, but the guiding arrow points up or down. Now return both guides to 0.00. Let's




draw a resistor symbol (refer to Figure 7).

Activate Snap To Grid

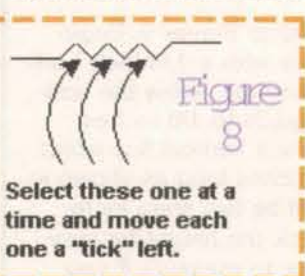Draw a line 1/4" long by the ruler, right on the horizontal guide (a). Move the vertical guide to .25" right and leave it there (b). Move the horizontal guide up one "snap" increment to .08" and, from the right end of the horizontal line, draw a line up and rightward toward the horizontal guide (c). The Snap To Grid feature will automat-



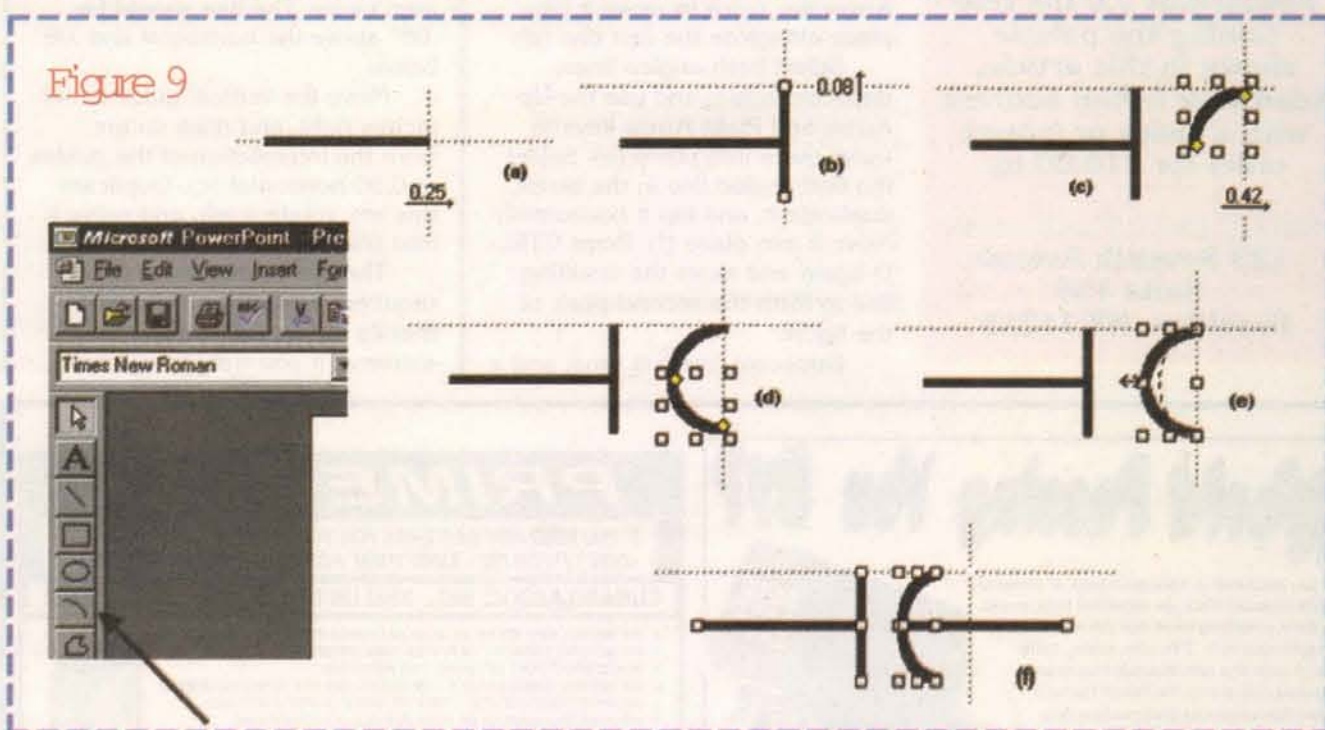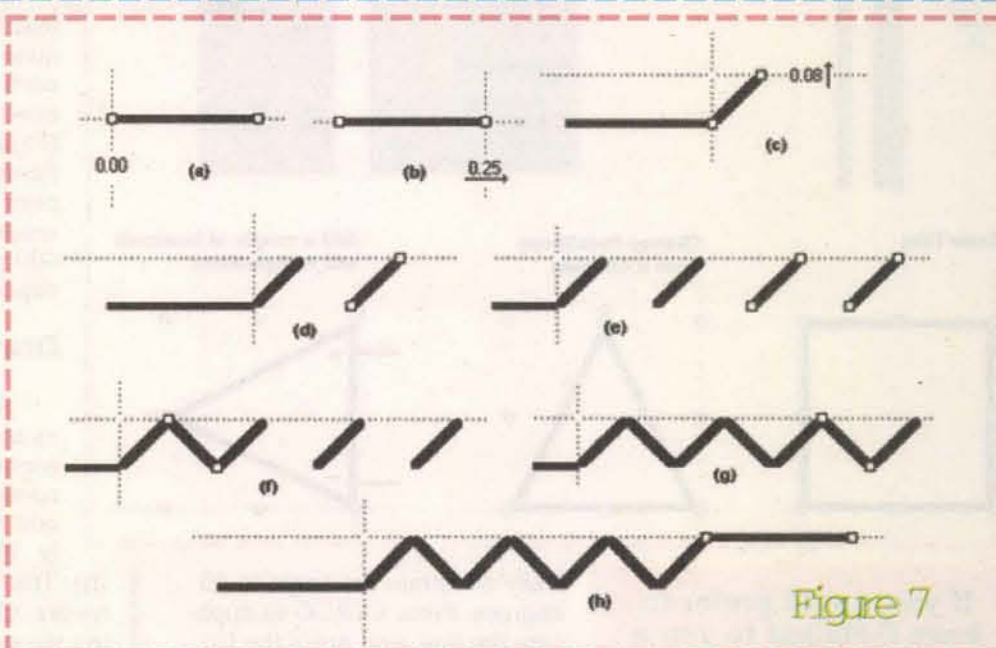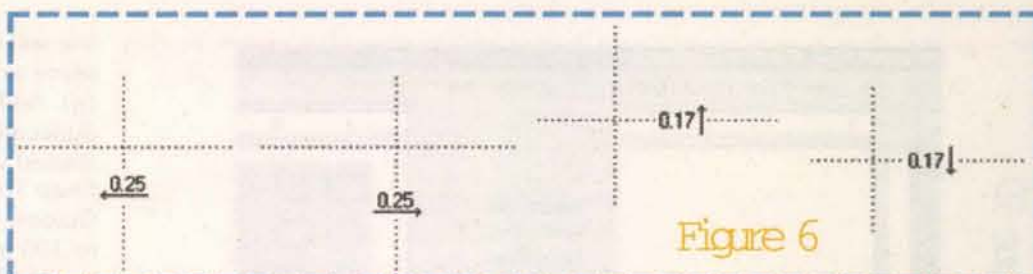Select these one at a time and move each one a "tick" left.





digital multimeters STANDARD MODELS

3 1/2 Digit Display (3/4" Digits)
Diode and Transistor Check
19 Position Rotary Range Switch
Voltage Range:

DC: 200mV-1000V
AC: 200V-750V

DC Current Range: 200uA-10A
Resistance Range: 200Ω-200KΩ
Requires 9V Battery (included)
4.96"(H)x2.76"(W)x0.94"(D)

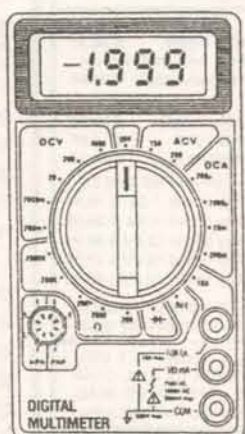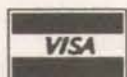

DT830B
No Continuity
Beep
\$7.49

DT830D
Continuity
Beep
\$8.69

DT830E
Continuity
Beep

Temperature
Measurement

Thermocouple
Included
\$11.97

Sales tax and shipping charges will be added to all orders. Prices subject to change without notice.
1A Sales-560 N. Moorpark Road, Suite 311-Thousand Oaks-CA-91361
888-651-9502, Fax 888-651-9503, www.1asales.com, 1asales@earthlink.net

Write in 110 on Reader Service Card.

DIGITAL SATELLITE TV REVOLUTION!

KNOWLEDGE is POWER!

- A clear explanation of all aspects of digital satellite TV
- Communication fundamentals and standards
- Digital compression, MPEG-2, DVB, error correction
- Uplink, satellite and receive system operation
- Internet operation and satellite delivery of data
- Installing fixed and tracking dishes
- Retrofitting older systems and mobile systems
- Conventional and IF distribution systems
- Troubleshooting and repair ... and much more ...

www.baylin.com
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$5 s/h to:

Baylin Publications, 1905 Mariposa, Boulder, CO 80302
MASTER, VISA & AMEX / COD orders accepted

FREE CATALOG - Satellite TV books, videos and software



486 pages, 8-1/2" x 11"



**JUST
PUBLISHED!**

Telephone: 303-449-4551
FAX: 303-939-8720

Write in 109 on Reader Service Card.

Nuts & Volts Magazine/SEPTEMBER 1999 51

Figure 10

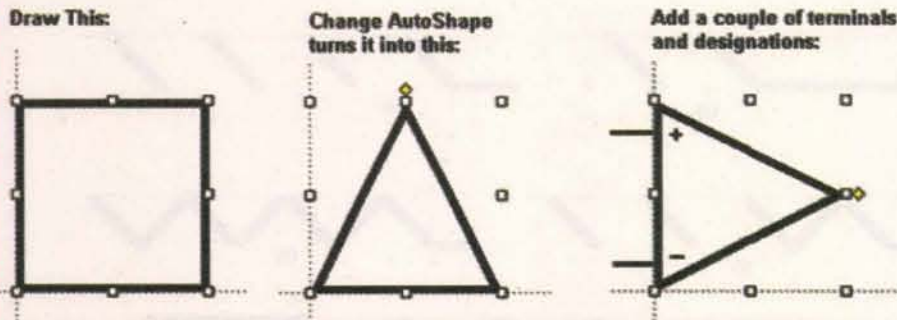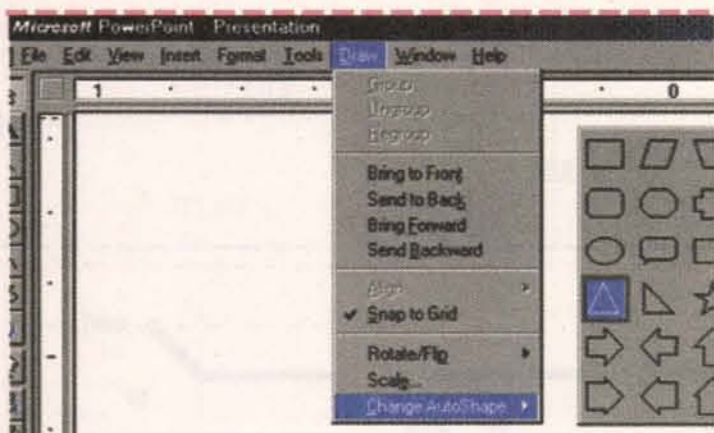

If you would prefer to have E-Mailed to you a PowerPoint 7.0 file containing the palette shown in this article, send your E-Mail address with a check or money order for \$10.00 to:

Small Bear Electronics
123 Seventh Avenue
Suite 156
Brooklyn, NY 11215

ically constrain the angle to 45 degrees. Press CTRL-D to duplicate the line, and press the Up Arrow key twice to move it into place alongside the first one (d).

Select both angled lines, duplicate again, and use the Up Arrow and Right Arrow keys to move them into place (e). Select the first angled line in the series, duplicate it, and flip it horizontally. Move it into place (f). Press CTRL-D again and move the resulting line to form the second peak of the figure.

Duplicate one last time, and a

line will appear in the correct place to form the third peak (g). Add the ending line by duplicating the one that you started with (h). Now turn off Snap To Grid, turn off the Guides, and reduce the Zoom to 100 percent.

You'll notice that the lines that make up the figure don't quite touch. I had to nudge each of the left-leaning lines exactly one "tick" further left (Figure 8), and I had a solid figure. Group all the lines and print the slide to see the result. Restore the zoom to 400 percent, and we'll do a capacitor.

Drawing A Capacitor

Refer to Figure 9. Begin as before with a 1/4 inch horizontal line (a). Raise the horizontal guide to .08 inches. and draw a vertical line exactly .16 inches long as shown in

(b). This will be two snap increments. Check the height by moving the guide to measure if you aren't sure. The line should be .08" above the horizontal and .08" below.

Move the vertical guide to .42 inches right, and draw an arc from the intersection of the guides to 0.00 horizontal (c). Duplicate this arc, rotate it left, and move it into place as shown (d).

Though we now have the required curved line, I thought that its arc was a little too extreme. If you want to correct

this as I did, first turn off Snap To Grid and group the two arcs together. If you now place the mouse pointer on the left-hand center "handle" of the arc (e), you'll find that the pointer becomes a two-headed arrow. Press and hold the left mouse button, and move it a little to the right to "squosh" the curve a little. Close up the distance between halves of the capacitor, add a right terminal, and you have the result shown in (f).

To finish this symbol, I moved it next to the resistor to compare it for size. It looked a little small, so I used the Scale function in the Draw menu to increase it to 125 percent of its original size. I then ungrouped, increased the length of the horizontal lines, and grouped everything together again.

I use lots of electrolytics, so I duplicated the capacitor symbol, added polarity markings, and put the result on the palette. The markings are in Arial 12 point bold, and they are separate, single-character text boxes in my version. I found that an underscore character looks better than a hyphen for the negative symbol. You can see my result in the overview of the palette.

How About An Op-amp?

Refer to Figure 10. To create the amplifier symbol, we need to draw a triangle. Unfortunately, this is one function that I know definitely operates differently in other versions of PowerPoint. Check your manual or the Help screens if you need to. In version 7:

Starting from zero horizontal and zero vertical, draw a square 3/4" by 3/4". From the Draw menu, select Change AutoShape and then select the isosceles triangle. Rotate the figure right and add two 1/4 inch long horizontal lines at .17 inches high and at .58 inches high. Turn off Snap To Grid, and add the plus and minus symbols as we did for the electrolytic capacitor. I used 10 point type for this rather than 12 point. Group everything together.

Move this figure next to the others and compare it for size. I scaled the whole thing up to 115 percent of its original size using the Scale function in the Draw menu.

I think you get the idea at this point. Each figure is an inch to an inch-and-a-half long, and as wide as needed for pleasing proportional appearance; use your judgment. A few observations that might help as you construct your own additions:

• I have noticed that a line or

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

- Examples Include:**
- Measuring Temperature
 - Using a Photocell to Detect Light Levels
 - Making a Waveform Generator
 - Constructing a Capacitance Meter
 - Motor Speed Control Using Back EMF
 - Interfacing and Controlling Stepper Motors
 - Scanning Keypads and Writing to LCD/LED Displays
 - Bus Interfacing an 8255 PPI
 - Using the Primer as an EPROM Programmer
 - DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.
11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: <http://www.emacinc.com>

1985 - 1998
OVER
12
YEARS
OF SERVICE

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM - SEND THEM FOR REBUILDING! - SAVE \$\$

CUNARD ASSOC. INC., 9343 US RT 220, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / EST. 1986
- WE SAVE YOU \$\$\$ MONEY \$\$\$




- NO JOB IS TOO LARGE OR TOO SMALL VOLUME DISCOUNTS AVAILABLE

GENERAL ELECTRIC	UNIDEN	RADIO SHACK
19A704850P(1200mAh) \$ 34.95	APX650 1050 \$ 29.95	HTX Packs \$ 29.95
19A704860P(1800mAh) \$ 39.95	1000 1010 1070 \$ 34.95	New 8.4V pack & chgr
PL19D429763(777)G1/3 \$ 37.95	1100 1200 Series \$ 36.95	1500mAh nimh \$ 34.95
19A705293P 344A4506P \$ 34.95	BP205 650mAh \$ 19.95	
	BP200 1500mAh \$ 24.95	KENWOOD
MAXON SA-1155 1160 \$ 39.95	SC150 1500mAh \$ 22.95	PB2 / KNB3 \$ 29.95
TAD 1450 1510 1520 \$ 21.95		PB21/21H \$ 14.95
	ICOM	PB25/H26 \$ 24.95
MOTOROLA	BP2 / BP3 / BP22 \$ 18.95	
P200 HT600 MT1000	BP5 / BP23 / 24 \$ 24.95	CORDLESS DRILLS
NTN 4585 4824 5414 \$ 37.95	BP7 / CM7 / BP8 \$ 32.95	Any brand 7.2V \$ 18.95
NTN 5447 5521 5545 \$ 37.95	BP180 / CM79 \$ 34.95	Any brand 9.6V \$ 29.95
NLN 5860 NTN 4327 \$ 39.95		Any brand 12.0V \$ 32.95
	YAesu	Any brand 14.4V \$ 37.95
MIDLAND	FNB 3 4 12 14 16 \$ 32.95	Any Brand 18.0V \$ 45.95
70-B10 B16 B19 B21 \$ 39.95	FNB19 21 26 27 38 \$ 32.95	
B25 B26 B32 B36 B60 \$ 39.95	FNB 10 1117 25 35 \$ 23.95	COMPUTER PACKS
		Send battery for quote.

FOR INFORMATION ABOUT YOUR REQUIREMENTS CONTACT US:
PHONE OR FAX : (814) 623-7000 E-MAIL TO: PRIMECELL@AOL.COM
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL
VISIT OUR WEB SITE <http://members.aol.com/primecell/primecell.htm>

BATTERY REBUILD SERVICE

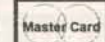MANY OTHERS AVAILABLE - WRITE OR CALL
FREE CATALOG
ADD \$ 4.50 SHIPPING & HANDLING PER ORDER



lines in a figure that I have built will sometimes get distorted when the figure is copied or rotated or the zoom is changed. No problem — just ungroup the figure, delete the affected line or lines, and re-draw. Don't try straightening lines that have been distorted by re-scaling.

Once you get a drawing that prints cleanly and displays reasonably well at the magnification you typically use for composition, you're set.

• If you need to put one shape inside another (as in the LEDs, for example), realize that the shape that surrounds the other(s) must either be sent to the back or have no fill.

• When you need to orient lines within a figure with respect to the center of the figure, use the guides. Take, for example, the photoresistor symbol. Figure 11 shows how I drew it.

• Snap to Grid is sometimes useful when you are constructing a complex symbol.

• Some complex symbols are drawn by combining standard shapes and hiding parts of them with another shape or shapes; my transformer and coils fall into this category. See Figure 12 for the how-I-did-it. If some figures of this sort display correctly but a part of the figure that should be white prints black, check your printer settings. Some printer drivers (like mine) have a "Print Black and White" checkbox that will override Color and Line settings in PowerPoint.

• You can get the Greek letter lambda (λ), which is used in the symbols of various electro-optical devices, in the following way:

Create a text box and type into it a lower-case letter "l." With this text box selected, click Format and then Font. Set the font type

to Symbol, select the font size you need, and then click OK. You will find that your "l" has become "λ," and you can move it to where you

want it. To rotate it as you see in my examples, select the box, and then either use the Rotate choice in the Draw menu or click the Free Rotate button.

• To get the degree symbol for the thermistor: Start the text box and type the lower-case "t." Make sure that the Num Lock key is active, hold down the Alt key, and type the sequence 0176 on the numeric key pad. The symbol will appear when you release the Alt key.

Now fill the palette with symbols of your own choice. You can use my examples to start and check the pages of this magazine for other ideas. Once you are satisfied with your palette, copy a

few of the figures that you expect to use most often across the top of the composition slide. I found that this leaves a maximum of working room for a drawing. Also create the designators R1-R10, C1-C10, etc., as individual text boxes lined up as you see in Figure 13. I found that having this available is a major time-saver over typing individual designations later.

Our First Schematic

As I mentioned earlier, I do my actual drawing at 100 percent. Also, I don't usually use Snap To Grid when

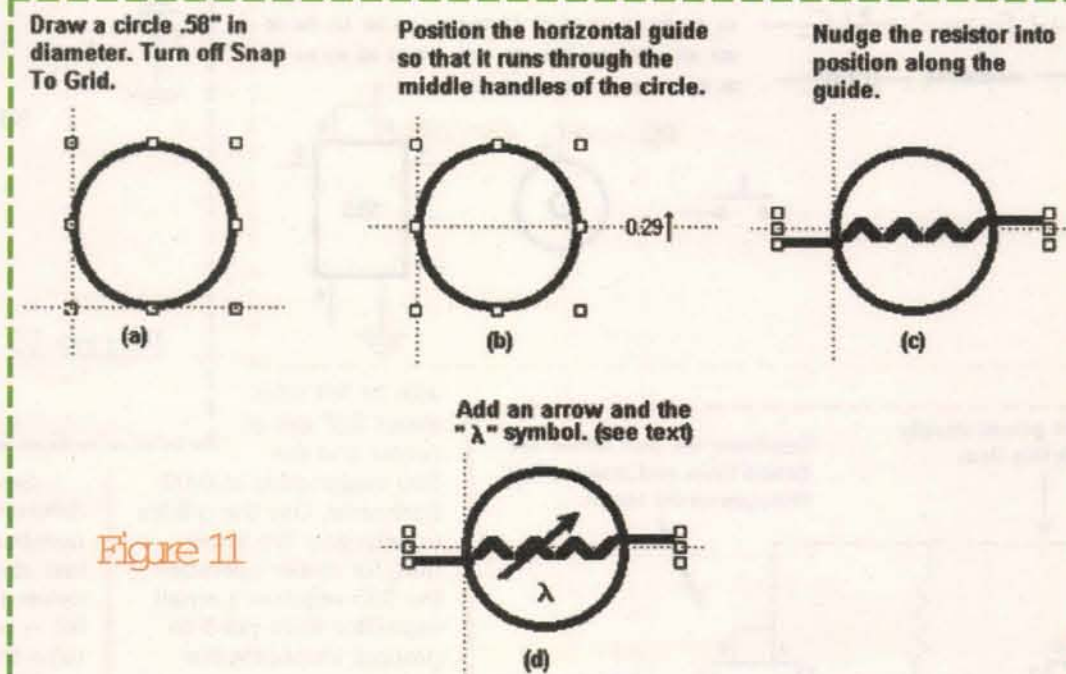


Figure 11

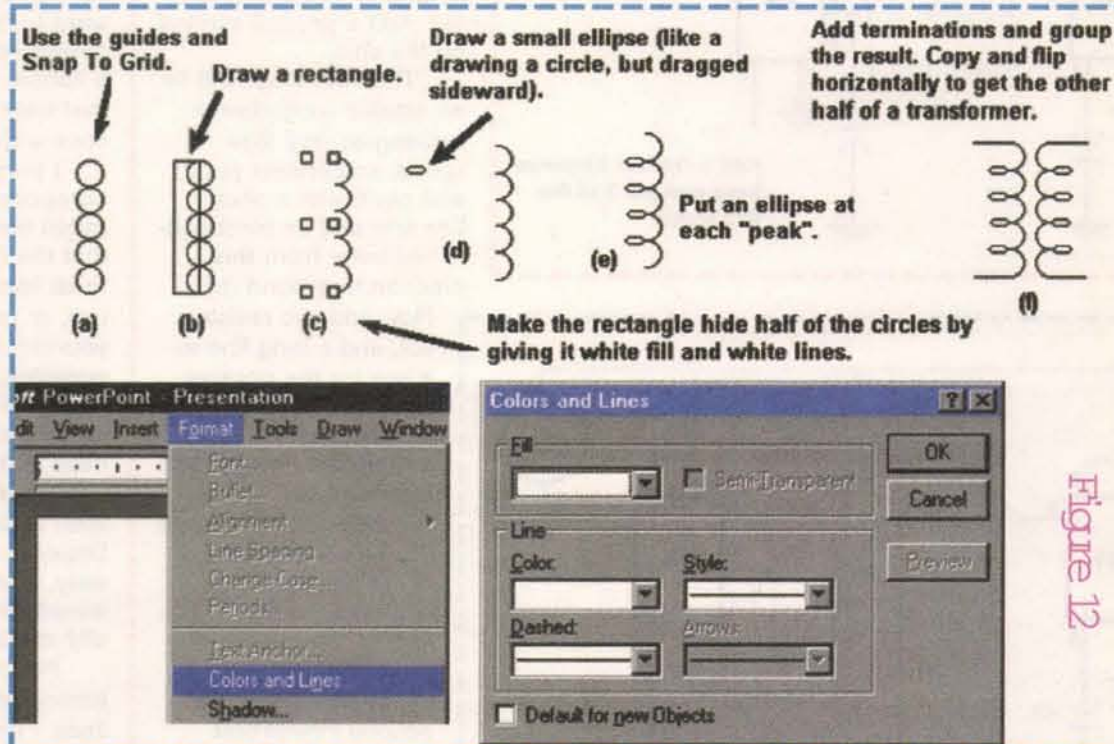


Figure 12

USB Relay Module

Model JSB-210

Controls 8 to 16 "form C" relays over the USB (Universal Serial Bus). Program the module with simple commands in any program language that supports USB Communications. Driver and sample code provided

J-Works, Inc

12328 Gladstone St., Unit 4
Sylmar, CA 91342
(818) 361-0787 Voice (818) 270-2413 Fax

Other Products

RS-485 Remote I/O
ISA Waveform Generator
RS-485 to DS-1820
RS-485 Temperature I/O
DS-1820 Probe

Visit our Web site for
Information on all our products
<http://www.j-works.com>
E-mail sales@j-works.com


LASERS & ACCESSORIES

HELIUM NEON LASERS

- ☒ Complete Systems
- ☒ Plasma Tubes
- ☒ Power Supplies

ACCESSORIES

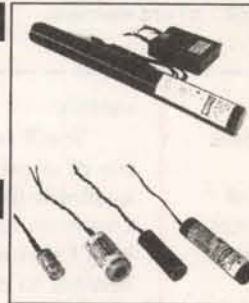- ☒ Optics
- ☒ Electro-Optics
- ☒ IR Viewers
- ☒ Books & More



MEREDITH
INSTRUMENTS

Phone: 602-934-9387 • Fax: 602-934-9482

DIODE LASERS

- ☒ Visible / IR
- ☒ Complete Modules
- ☒ Collimating Optics
- ☒ Drive Circuits

FREE CATALOG

WEB SITE:
www.mi-lasers.com

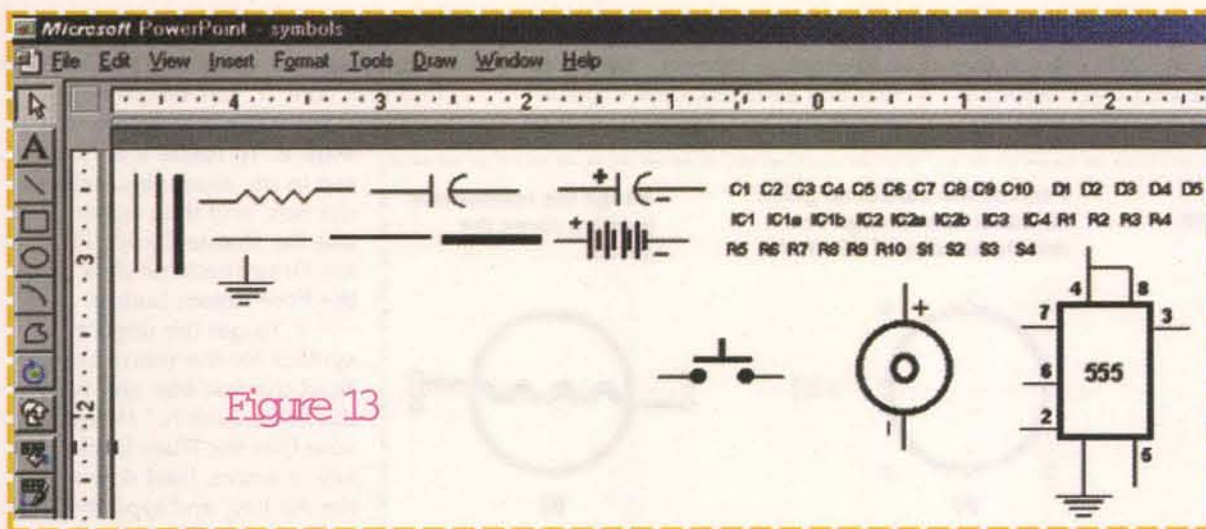


Figure 13

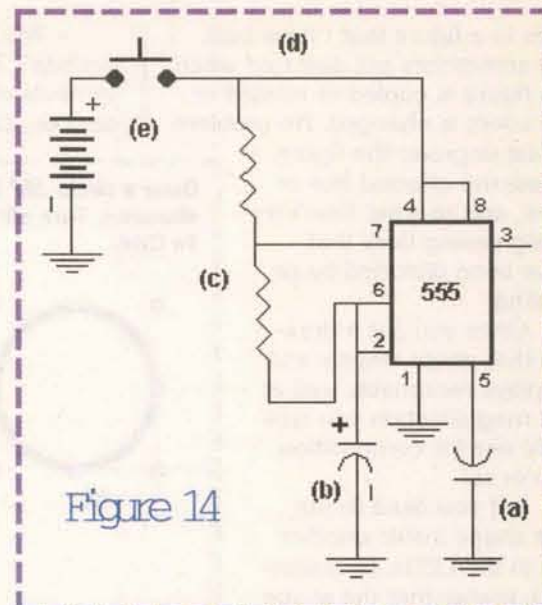


Figure 14

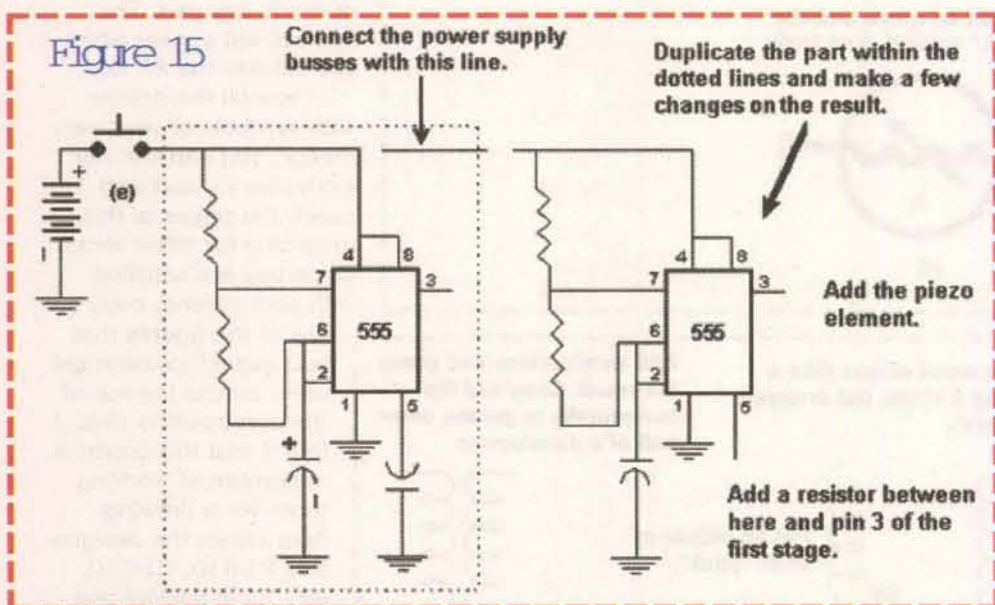


Figure 15

with its left edge about 2.5" left of center and the 555 designation at 0.00 horizontal. Use the guides to help you. We know that, for stable operation, the 555 requires a small capacitor from pin 5 to ground. Duplicate the capacitor symbol, rotate it, and move it into place (a). Add a ground symbol on the end.

This first stage will be an astable multivibrator running at very slow speed, so connect pin 2 and pin 6 with a short line and add an electrolytic capacitor from this junction to ground (b).

Now add two resistors (c), and a long line as a bus for the positive side of the power source (d). Add the switch, the battery, and a ground (e).

Now look at Figure 15. The second stage of our circuit is the same as the first except that it runs at a much higher frequency, so let's pull off a serious PowerPoint trick: Select all of the components in the first stage, group them, and then duplicate. Move this second stage into place. Ungroup the electrolytic in this stage, remove its polarity markings and regroup. Remove the capacitor from pin 5 and then connect the two stages with a resistor. The last bit of drawing is adding the piezo element. Pretty easy, Yah?

To finish up, see Figure 16. Do your designations by moving the appropriate component numbers into place, and then clean up any symbols that you're not using. Add the appropriate value to each designation. Done!

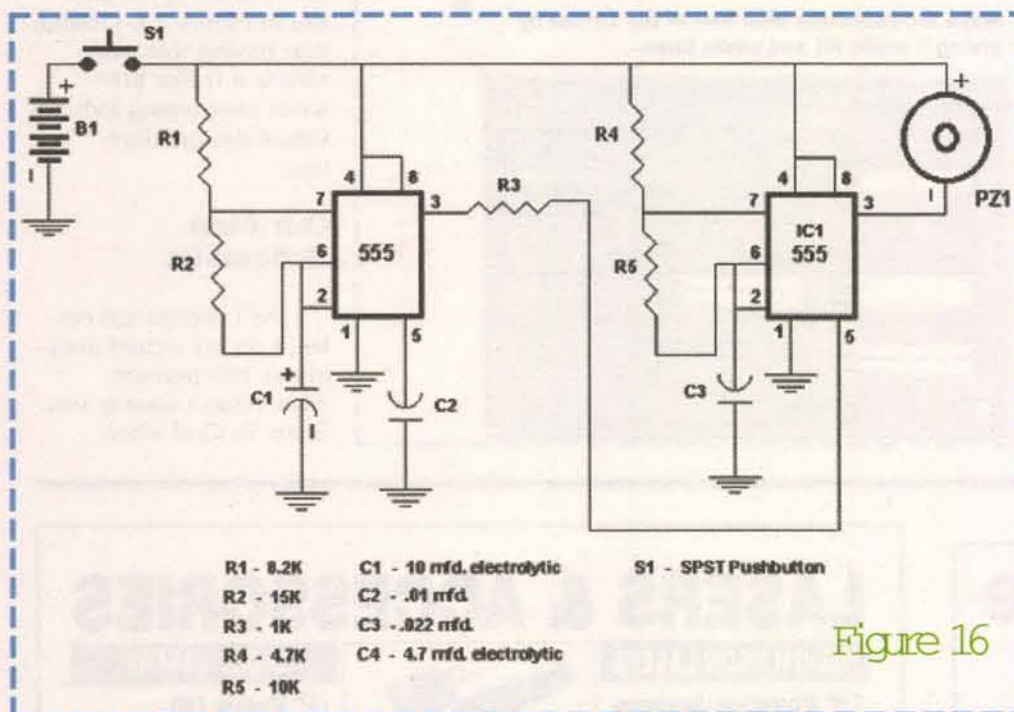


Figure 16

drawing a schematic. Set these parameters to start and see how they work for you.

Figure 13 shows the top of the composition slide, with a couple of additions; 555 timer chips are used a lot in a couple of generic circuits, so I preconfigured one on the palette. To begin, copy this figure to the composition slide along with a piezo element and a push button or toggle

switch.

You'll notice that I have a couple of short lines of various widths available in the same area as the common components. To draw a line, I sometimes find it more convenient to duplicate one of these (CTRL-D) and extend it if necessary than to go back to the Line Draw tool.

Figure 14 shows the drawing of the first stage. Locate the 555

Save this presentation under a different name, and delete slide number one. Be careful with this last step! You would not want to delete the palette from its original file — only from the file that contains the new schematic.

Now that you have done one schematic, I'm sure that you will want to try using these tools to develop other ideas. I will mention a couple of other "practicalities" that have come from my experience with them:

I purposely made the passive components a little larger than I might have, because I presumed that the typical drawing would most likely not extend more than two, or perhaps three, stages. If you are doing something more complex, you may want to scale down the "common" components on the composition slide, and perhaps some of the others that you copy there as well, before you start to draw. The PowerPoint Draw/Scale feature makes this easy, and any distortion that it introduces to your models is usually small and easily retouched.

My other comment relates to joining of overlapping component lines. I have noticed that when I connect, say, a terminal line of a capacitor to the line extending from a chip, the lines will sometimes appear to be completely merged on screen but will then print out just slightly out of alignment. I don't know exactly why this happens — it may have do with the fact that I am using this program in a way that its designers didn't foresee — but it's easy enough to deal with if the misalignment is a real problem. Just ungroup one of the figures that you are joining, remove one or the other of the offending lines and redraw as necessary.

Creating the palette is a good deal of work and it requires some skill with PowerPoint, but I think the results are well worth the effort. NV

ROBOTS WANTED: Dead or alive, whole or parts. Marvin (Iowa Precision), Gemini, RoPet, Hubot, RB5X, Newton SynPet, ComroTot, ELAMI, ITSABOX, HeathKit (HERO JR, 1, 2000, or Arm Trainer), Androbots (TOPO, BOB, Fred, and Androman), Rhino, Maxx Steele, Omnibots, etc. Also looking for robot prototypes, options, and literature, will pay cash. Please E-Mail rodoerr@bizserve.com Call 810-777-1313 or write to: Robert Doerr, 26308 Cubberness, St. Clair Shores, MI 48081.

www.futurerobots.com ROBOTICS for active security systems is now possible for the amateur electronic experimenter to design and build. Come and see the future of home robotics and read Lab Note 116 Design Concepts for Various Types of Guard Robots. Also other technical articles about active security robot and systems.


PLANS — KITS — SCHEMATICS

BUILD THE MENDOCINO MOTOR. This fascinating device is a solar powered, magnetically levitated motor. It will delight and amaze you and your friends. The 27 page plans book includes a list of parts suppliers. The motor uses readily available parts. Plans are \$15 plus \$2.50 S&H. Write to: St. Elmo's Fire, PO Box 141, Stow, MA 01775. E-Mail: tcv@gennad.com

200+ ELECTRONICS PROJECTS. Build for pleasure or make 100% (or more) profits reselling printed plans. \$1 (refundable) for catalog & dealer info. MATCO-A5, PO Box 509, ROSEVILLE, MI 48066-0509.



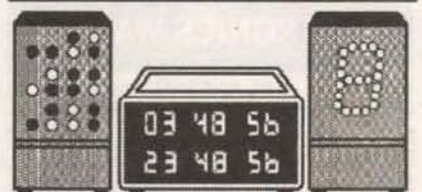CIRCUIT BOARDS. Low-cost, precision-made PC boards from your CAD program files (no photoplots required). Single and double-sided with contour routing. Ideal for RF/analog/digital prototypes. Full details at <http://www.pcbmilling.com> E-Mail: feedback@pcbmilling.com FAX: 703-818-0071.



TERRIFIC TIMEPIECES! LED binary clock. LED digital clocks, other kits! Free catalog! WPC, 805-339-0702. www.ElectronicsUSA.com


AWESOME KITS: Ion propulsion motor, solar robot, stepper driver, scrolling clock, and more! Catalog \$1. LNS Technologies, PO Box 67243, Scotts Valley, CA 95067. www.techkits.com

HEATHKIT COMPANY is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: 616-925-5899, 8-4 ET.

VOICE CHANGER: PCB with all board mounted components plus speaker. (Watch for our N&V article.) New price \$9.95 postpaid in US. MicroMethods, PO Box 909, Warrenton, OR 97146. 503-861-1765 jdennon@seasurf.com

MAKE YOUR OWN PHOTOVOLTAIC CELLS! Incredibly easy, cheap, compact, and versatile. Complete instructions. wclark@infoave.net

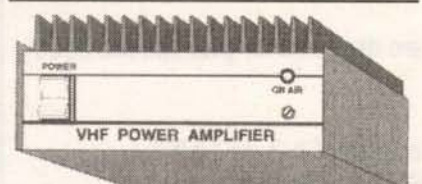PALM PILOT never replace batteries again. Simple modification charges batteries in cradle. For Palm Pilots up to IIX. \$10. Mark Lopez, 22689 Silver Dollar, Corona, CA 91719.



BROADCAST FARTHER! 75-110MHz amplifier connects to stereo transmitters. Produces 2-15 watts. Requires 50-150mW drive. Complete plans with part source and antenna information only \$14 + \$2 S&H. **Progressive Concepts**, PO Box 586, Streamwood, IL 60107. 630-736-9822.




ELECTRIC POWER METER STOPPER MAKES METER RUN SLOWER, STOP, OR EVEN REVERSE! COMPLETE PLANS \$10, SOLD FOR EDUCATIONAL PURPOSES ONLY. (VISA/MC/AMEX/COD) OPEN 24 HOURS! 407-654-9677 **BRINKER ENGINEERING LABS, USA.**

CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena. **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. www.tsc-global.com

PIC INSTRUMENTATION and monitor chips, kits, quick-build protoboards, telephone electronics, pocket testbench. Oricom Technologies, 303-449-6428. www.sni.net/~oricom

Don't miss a single issue! Have Nuts & Volts delivered right to your door every month for only \$19 per year. Call 1-800-783-4624

The Pocket Programmer

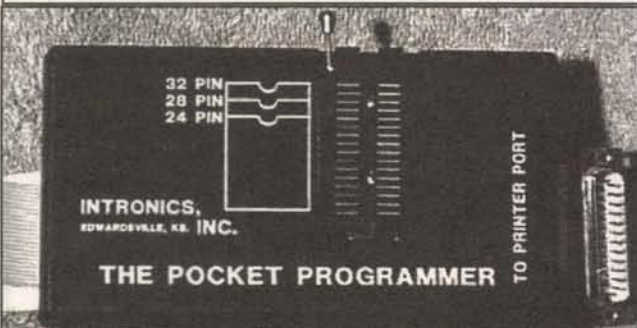

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8. Only \$129.95

Same Name, Address & Phone Number for 16 Years.... Now isn't that Amazing?

Intronic, Inc.
Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$5.00 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge / Amex

REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single, Black, \$8.00. **CANON BJC-600 (BC-201)** Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJL-481 & BJL-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240 (BC-05 Cart)** 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and **Apple Stylewriter 2400 Black 3-bottle kit** (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70 and Apple Stylewriter 2400** Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880 3-bottle kit** (for BJI-643B) \$19.00. **CANON BJC-800/820/880 3-bottle tri-color kit** (Cart #BJL-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049). Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00. **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **EPSON STYLUS COLOR 440 AND 640** Black refill kit. (S020187) 4 refills plus free vacuum bottle \$19.00. **EPSON STYLUS COLOR 440, 640, AND 740** (S020191) Color refill kit. 4 refills of each color \$24.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560**. Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C**. Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C**. (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark ExecJet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **Lexmark 3200, 5000, 5700, 7000, 7200, Optra 45 and Z51** (12A1970) 3 refills Black \$19.00. **Lexmark 3200, 6000, 5700, 7000, Optra 45 and Z51** (12A1980) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.

HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Inforunner \$8.00; Commodore MPS-801 \$5.00; MPS 803 \$5.00; Decwriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannisman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00; Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00. ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed. Order directly or send SASE for complete list.

Add \$4 per order shipping. CA residents add 7.75% sales tax. On ribbon orders over \$50 deduct 10% dis-

H.T. ORR Computer Supplies
249 Juanita Way, Placentia, CA 92870-2216
714-528-9822 • 800-377-2023 • FAX 714-993-6216
<http://www.extremeplay.com/occomp/orr.htm>

Write In 73 on Reader Service Card.

COMPUTER PARTS

Attention Dealers and Consultants

Scrambled data while flashing upgrade BIOS? Our BIOS repair service will correct any virus or flashing errors. Save the cost of a new BIOS chip, or worse yet, a new motherboard. **BIOS RECOVERY SERVICE \$25.00**

MEMORY UPGRADES

2Mx32 72-pin SIMM F/P	\$20
4Mx32 72-pin SIMM F/P	\$29
8Mx32 72-pin SIMM F/P	\$59
64MB SDRAM (PC100)	\$59
128MB SDRAM (PC100)	\$99
256MB SDRAM (PC-100)	\$245

CACHE

64Kx1-15ns 22-DIP.....	\$5.50
32Kx8-25/20/15ns 28-DIP.....	\$3/2/2.50
64Kx8-15ns 32-DIP.....	\$6
128Kx8-15/20ns 32-DIP narrow.....	\$12 & up
128Kx8-15/20/25ns 32-DIP wide.....	\$12 & up

CPU

Pentium II 400.....	\$199
Pentium II 333.....	\$188
Celeron 333 PGA.....	\$95

VIDEO

1MB KIT(2-256x16)2CAS SOJ/ZIP.....	\$18/35
1MB KIT(2-256x16) 2WE SOJ/ZIP.....	\$19/36

MISC.

IDEAL BIOS Enhancer Card. Break the 8.46GB barrier. Supports any IDE hard drive over 528MB up to 128MB. Works with any X86, Pentium, or PII System. \$29.95

PACKARD BELL UPGRADES

PRICES SUBJECT TO CHANGE WITHOUT NOTICE
TERMS: VISA/MC -- MIN. ORDER \$20 -- SHIPPING & HANDLING: \$7 MIN.
ORDER LINE: (800) 586-4199

LA PAZ ELECTRONICS INT'L
www.lapazusa.com
P.O. BOX 261095, San Diego CA 92196
TEL (858) 586-7610 FAX (858) 586-1482
e-mail: lapazusa@pobox.com

Write In 67 on Reader Service Card.

ACP's 93rd GIANT COMPUTER SWAP★MEET

Orange County's Original!

Be a Seller...for your space Call Mary

All Day Sunday 8am-2pm

Sept 26th

FREE Admission & Parking Shop 100's of Sellers

in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.

ACP SUPER★STORE

Since 1976

1310 E. Edinger
Santa Ana, CA
714-558-8813


MANUALS — SCHEMATICS WANTED

MINISCOPE #MS-15 by NonLinear Systems, 535 Stevens Ave., Solana Beach, CA 92075.

MISCELLANEOUS ELECTRONICS FOR SALE

NUCLEAR ELECTRONICS (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: oetech@newmexico.com <http://www.oetech.com>

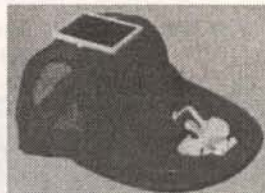CALL FOR a free electronics catalog or visit our web site at www.bgmicro.com/ B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 1-800-276-2206.



SOLAR-POWERED FAN HAT. Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

CABLE TV(MMDS) CONVERTER

Our converters are designed for your specific need

85 Ch Plain Converter, Ch-3, AFT/MFT
PG Lock, HRC/STD and Sleep Timer
Price: between \$29 - \$49

99 Ch Plain Converter, Ch-3, AFT/MFT
PG Lock, HRC/STD and Sleep Timer
Price: between \$49 - \$69

125 Ch Volume Converter, Ch-3/4 out
ACW/MFT, PG Lock, HRC/STD and Sleep Timer
Price: between \$59 - \$89

FREE BROCHURE
CALL (310)515-5085 or
FAX 1-800-579-5000

PCW Company



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call **1-800-626-7540**, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: info@anaheimwire.com

ELECTRONIC PARTS: LOW, LOW PRICES! Phone, fax, E-Mail for free flyer. Hoffman Industries, 853 Dundee Ave., Elgin, IL 60120. Ph: 847-622-8201, Fax: 847-622-8202, E-Mail: hoffind@aol.com Web site <http://hoffind.com>

FREE FLYER on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.

SOLAR ELECTRIC SUPPLIES: All manner of solar electricity available here. 64 watt panel, \$319. 120 watt panel, \$589. Flexible 5 watt, \$89. Controllers start at \$39.95. Inverters, shunts, racks, mounts, etc., solar roofing shingles. Visit www.planetarypower.com 1-877-SOLAR-PV.

PC CABLES: <http://www.pccables.com> connectors, RS232, IDC, SVHS, ribbon cable, DB9, DB15, loopback, null modem, jumpers, SCSI, screws, rails. Secure online catalog, ordering, browsing. 954-418-0817.

CNC SERVO control 3 axis PC based CNC servo control. Software features feed override, real-time position display editor, canned cycles, graphics, and block lookahead. 4 axis ISA card, \$650. CNC software, \$600. Complete systems with motors and amps also available. Call JRA at 248-637-9480 for more info.

MISCELLANEOUS ELECTRONICS WANTED

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

WANTED: AVIONICS test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

WANTED: TUBE HiFi/commercial amps, preamps, corner/horn speakers. Altec, Marantz, McIntosh, Western Electric, etc. 405-737-3312 fax 405-737-3355.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.



TZPC-175 Converters

\$39.00

20-lot



Centurion: CF-3000 (Brand New) True, 99-Channel


\$49.00

20-lot

THE BEST DEALER PRICING

- ✓ Call for other models
- ✓ One stop shop
- ✓ Same day shipping
- ✓ One full year warranty

Intek Electronic Systems
405-634-1535

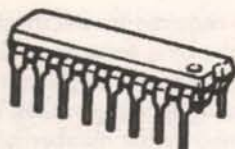

WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LA PALMA SEMICONDUCTOR, 714-523-8892 FAX 714-523-8898.

HIGHEST PRICES PAID: I will pay the following prices for Western Electric tubes: 211A/D/E new \$300, used \$175; 212A/D/E new \$750, used \$275; 274A/B (engraved base) new \$250, used \$200; 300B (engraved base) used \$550; 422A new \$50, used \$25; 437A new \$50, used \$25; and many more. Also buying Western Electric, and other audio tube and equipment literature. Call or send us your list. Toll free tel/fax: 1-888-715-8823. Don Singerhouse/Singerhouse Sound, LLC, PO Box 321, New Richmond, WI 54017. E-Mail: singtube@frontiernet.net

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

WANT USED or surplus DC motor controls or adjustable frequency AC drives, 1/2 HP and up. DC motors fractional to 3 HP. C. Woodruff, 5507 55th Ave. S., Seattle, WA 98118. Voice/Fax 206-723-8487.

WANTED: X-BAND radar equipment. Military, civilian, working or not, parts, TMs, etc. Box 10215, Pittsburgh, PA 15232.

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.,** 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronicsurplus.com

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

EDUCATION

RF OSCILLATOR DESIGN. Learn to design RF oscillators from a pro. Unique course for hobbyists, students, and engineers presents the knowhow of RF oscillator analysis, simulation and design with experiments. Requires AC/DC and some calculus. \$25 + \$5 S&H. RFLS, PO Box 9185, Gaithersburg, MD 20898-9185. Free information: E-Mail: rfls@worldnet.att.net phone 301-528-6671.

BUSINESS OPPORTUNITIES



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

REPAIRS - SERVICES

ENGINEERING CONSULTING. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05xx, HC11xx, and PIC families. Software design for IBM PC. XILINX and Altera FPGA design. In-house schematic capture and PWB. Hicks Electronic Design, PO Box 7366, Loveland, CO 80537-0366. Toll Free 1-888-849-6792 E-Mail: steve@hicksengineering.com website: www.hicksengineering.com

(E)EPROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

PC BOARDS REPAIRED. Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.

PC BOARD ASSEMBLY. Thru hole only. Small or large quantities OK. Call Network Sales. 616-683-0500.

CABLE CONVERTER REPAIR: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: **HIGHENG1@AOL.COM** ask for George.

WELD ALUMINUM WITH PROPANE! EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. http://www.dura-fix.com

PRINTED CIRCUIT design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. www.circuit-applied-tech.com call toll free 877-236-3223.

PLAYSTATION MOD chips. Works with all models up to 750x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

RADIO REPAIR! Reasonable charges. Jim Rupe, 998 Whipple, Grayland, WA 98547-0697. 360-267-4011. E-Mail: w7ddf@yahoo.com

Order Today! ONLY \$34.95

"PROGRAMMING AND CUSTOMIZING BASIC STAMP COMPUTERS"

by Scott Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off** the list price!!

(See ad on page 48 for ordering details and other titles currently available.)

ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS


Alitech 360D11, Frequency Syn., 01-2GHz	\$800	HP 86602A, RF Plug-In, 1300MHz	\$500
Alitech Type 32, Precision Attenuator, 0-100dB	\$300	HP 86603A, RF Plug-In, 2600MHz	\$800
Argosystems AS210, Frequency Calibration System	\$2,000	HP 8672A, Frequency Synthesizer, 2-18GHz	\$4,500
Austron 2100R, Loran-C Frequency Monitor	\$500	HP 8697A, RF Plug-In, 26.5-40GHz	\$250
Bird 4381, RF Power Analyst, Opt. 832	\$200	HP 8743A, Reflection Transmission Test Set	\$200
Boonton 82AD, Modulation Meter	\$450	HP 8743A/018, Reflection Transmission Test Set, 18GHz	\$300
Boonton 92BD, Digital RF Millivolt Meter	\$250	HP 8750A, Storage Normalizer, Includes Cable	\$250
Boonton 102B, Signal Generator, 45-520MHz	\$500	HP 8753B, Network Analyzer, Opt. 002,006,010	\$8,000
Boonton 518-A4, Q Standard	\$100	HP 8756A, Scalar Network Analyzer	\$1,500
Boonton 2500, DC Range Calibrator	\$250	HP 8901A, Modulation Analyzer	\$1,000
Boonton 4G, Power Meter Sensor, 01-26.5GHz	\$200	HP 8903B, Audio Analyzer, Opt. 001	\$2,000
Boonton 4200, Power Meter w/4G Sensor, Cable	\$600	HP 8920D, Dual-Mode Cellular Mobile Test System	\$6,500
Boonton 4220/51013, Power Meter with Sensor	\$800	Opt. 002,008,014	\$6,500
Boonton 4300, Power Meter, 2 Channel	\$1,200	HP E3617A, DC Power Supply, 0-40V, 1A	\$250
Bruehl & Kjaer 1612, Bandpass Filter	\$400	HP P486A, Power Sensor, 12.4-18GHz	\$100
Calif. Inst. 101T, AC Power Source	\$250	HP X486A, Power Sensor, 8.2-12.4GHz	\$100
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	Hughes 8010H, TWT Amplifier, 3-8GHz	\$1,000
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Hunttron 5100DS, Computer Controlled Troubleshooting System	\$1,200
EIP 578, Source Locking Microwave Counter, 26.5GHz	\$2,200	Keithley 192, Programmable DMM, 6.5 Digits, HP/IB	\$600
EIP 931, Microwave Source, 01-18.6GHz, Opt. 9320	\$6,000	Keithley 195A, Digital Multimeter	\$300
ESI 296, Auto LCR Meter	\$800	Keithley 614, Electrometer	\$700
Fluke 515A, Portable Calibrator	\$500	Krohn-Hite 3202, Filter, LP, HP, BP, Unused	\$350
Fluke 540B, Thermal Transfer Standard	\$1,000	Leeds & North 1091, Capacitor Decade, .001uF-1uF	\$150
Fluke 5450A, Programmable Resistance Calibrator	\$300	Micrometrical NSI-52640W, Noise Source, 26.5-40GHz	\$350
Fluke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$400	Micro Sciences ICT-101, IC Tester	\$300
Fluke 6080A/AN Frequency Syn., 5-1024MHz	\$250	Ming HT-21, Handy IC Tester	\$100
Fluke 8520A, Digital Multimeter	\$250	Narda 5082, High Directivity Bridge, 2-18GHz	\$300
Fluke 8922A, True RMS Voltmeter	\$200	Narda 5292 Directional Coupler, 1-18GHz	\$200
Fluke A55, Thermal Converter	\$400	Racal Dana 1515, Delay Pulse Generator	\$500
FTS 1150/001, Frequency Standard	\$700	Racal Dana 1992, Frequency Counter, High Stab.	\$500
General Microwave 478A, Peak Power Meter	\$400	Racal Dana 9082P, Signal Gen. 1.5-520MHz	\$400
General Radio 1557, Vibration Calibrator	\$700	Simco A300, Aerostat Anti-static	\$100
Gigatronics 600B-12, Frequency Synthesizer	\$1,000	Tek 134, Probe Amplifier for P6021 & P6022	\$100
Gigatronics 910, Frequency Synthesizer, 05-26GHz, Opt. 0306	\$8,000	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
Guideline 915AC, Transvolt Standard Cell	\$300	Tek 1502C, TDR	\$3,200
Guideline 9577, Precision DMM, 7.5 Digits	\$300	Tek 1503/0105, TDR, Scale in Meters	\$1,000
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 178, Linear IC Test Fixture, For 577	\$150
HP 1122A, Probe Power Supply	\$200	Tek 1730D, Digital Waveform Monitor	\$500
HP 11590A, Bias Network	\$250	Tek 242, Oscilloscope, 4-Channel, 100MHz, Cursors	\$1,200
HP 11604A, Universal Extension	\$100	Tek 2432, Scope, Digital, 300MHz, 4 Channel, HP/IB	\$2,000
HP 11605A, Flexible Arm	\$100	Tek 2445A, Scope, 150MHz, 4 Channel	\$1,200
HP 11638A, Calibration Kit, Type N	\$600	Tek 2445B, Scope, 150MHz, 4 Trace, HP/IB	\$1,500
HP 11665B, Modulator	\$250	Tek 2465, Scope, 300MHz, 4 Channel	\$1,500
HP 11713A, Attenuator Switch Driver	\$400	Tek 305DMM, Scope, 10MHz, Dual Trace, DMM, battery	\$500
HP 11869A, Adaptor for Plug-In 8350A/B	\$350	Tek 318, Logic Analyzer w/ports	\$500
HP 11970A, Harmonic Mixer, 26.5-40GHz	\$800	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 11970K, Harmonic Mixer, 18-26.5GHz	\$800	Tek 492, Spectrum Analyzer, Opt. 01/02	\$4,500
HP 11970Q, Harmonic Mixer, 33-50GHz	\$900	Tek 492/02, Spectrum Analyzer	\$4,000
HP 1600A, Logic Analyzer w/ports	\$400	Tek 492BP, Spectrum Analyzer	\$8,500
HP 1630D, Logic Analyzer w/ports	\$500	Tek 492P, Spectrum Analyzer, Opt. 01,02	\$5,000
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 576, Curve Tracer	\$1,800
HP 214B, Pulse Generator	\$1,000	Tek 604, XY Monitor	\$100
HP 33102A, Microwave Switch, 100MHz-18GHz	\$100	Tek 7D20, Programmable Digitizer PI	\$600
HP 3314A, Function Generator, Opt. 001	\$1,500	Tek 7S11, Sampling Unit w/S4 Head, DC-14GHz	\$800
HP 3325A, Function Generator	\$1,000	Tek AM503/A6302, Current Probe, Amp & Power Supply	\$800
HP 3325A/0102, Function Gen., Opt. 01/02	\$1,500	Tek DC503, Universal Counter Timer TM500	\$100
HP 33322H, Programmable Attenuator, DC-18GHz	\$250	Tek DC504, Counter/Timer TM500	\$100
HP 3336C, Synthesizer, Level Generator, Opt. 005	\$1,000	Tek DM502A, Autorangeing DMM	\$150
HP 339A, Distortion Analyzer	\$900	Tek FG501, Function Generator, 1MHz	\$100
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$200	Tek FG502, Function Generator, 1Hz-11MHz	\$250
HP 3403C, True RMS Voltmeter	\$200	Tek P6046, Differential Probe	\$300
HP 3456A, Digital Multimeter	\$600	Tek P6201, FET Probe Kit, 900MHz	\$400
HP 3468A, Multimeter, 5.5 Digits	\$400	Tek P6202A, FET Probe, 500MHz unused	\$300
HP 35689A, 5-Parameter Test Set for 3568A	\$1,400	Tek P6602, Temperature Probe for DM5110, DM511	\$150
HP 3582A, Spectrum Analyzer, 02-25.5KHz	\$1,800	Tek PG506, Scope Cal System w/FG501, SG503, New Style	\$1,500
HP 4140B, Picometer, DC Source	\$2,000	Tek PG508, Pulse Generator, 50MHz	\$300
HP 4274A, Multi-Frequency LCR Meter, Opt. 001,002,003	\$2,000	Tek PS503A, Dual Power Supply	\$150
HP/IB, includes Test Fixture	\$2,000	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 4342A, Q-Meter	\$1,000	Tek SG502, Sig. Gen. 5Hz-50KHz	\$200
HP 435B, Power Meter	\$350	Tek TDS410, Digitizing Oscilloscope, 150MHz	\$2,800
HP 436A/022, Power Meter, HP/IB	\$500	Tek TDS410A, Digitizing Scope, 200MHz, Opt. 13,1F	\$3,000
HP 5005B, Signature Multimeter	\$350	Tek TM503, 3 Slot Power Module	\$100
HP 5006A, Signature Analyzer	\$300	Tek WM490A, Waveguide Mixer, 26.5-40GHz	\$800
HP 5316A, Universal Counter, Opt. 004	\$200	Tek WM490K, Waveguide Mixer, 18-26.5GHz	\$800
HP 5334A/020, Universal Counter w/DVM	\$600	Texscan SSG2000, Freq. Syn., 100KHz-2GHz	\$1,800
HP 5335A/010, Frequency Counter	\$600	Ungar 4624, Solder, Desolder Station	\$250
HP 5335A/030, Frequency Counter, 1300MHz	\$900	Valhalla 2000, Auto Digital Watt-Ammeter	\$200
HP 5340A, Frequency Counter, 18GHz	\$600	Vu-Data 5110, Semiconductor Tester, In/out Circuit	\$150
HP 5340A, Frequency Counter w/Opt. 01/02/0211	\$900	Wavetek 178, 50MHz Programmable Waveform Syn.	\$1,000
HP 5342A, Microwave Counter	\$1,000	Wavetek 180, Sweep/Function Generator	\$200
HP 5345A, Frequency Counter, Opt. 012	\$400	Wavetek 185, Sweep Function Gen. .0001-5MHz	\$400
HP 5350A/010/002, Microwave Frequency Counter	\$2,000	Wavetek 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 54100D, Digital Scope, 1GHz	\$2,000	Wavetek 1910, XY Monitor, Dual Trace	\$400
HP 54200A, Digital Storage Scope	\$800	Wavetek 452, Filter, Dual Hi/Low, 1Hz-10KHz	\$450
HP 54601A, Digital Scope, 100MHz, 4 Channel	\$1,600	Wavetek 7530A, FFT Spectrum Analyzer 0-100KHz	\$500
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	Wavetek 907, Signal Generator, 7-11GHz	\$600
HP 577, Curve Tracer w/177 Test Fixture	\$1,000	Wavetek 955, Micro Source, 7.5-12.4GHz, AM, FM, Sweep	\$1,000
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Wiltron 560-7K50, RF Detector, 10MHz-40GHz	\$400
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,000	Wiltron 610D, Sweeper Mainframe	\$250
HP 8165A, Programmable Signal Source, Opt. 02/03	\$1,200	Wiltron 6213D, RF Plug-In, 10MHz-4.2GHz	\$400
HP 8350B, Sweep Oscillator Mainframe	\$2,000	Wiltron 6219D, RF Plug-In, 2-8GHz	\$200
HP 83540A, RF Plug-In, 2-8.4GHz	\$1,200	Wiltron 6223D, RF Plug-In, 4-12.4GHz	\$250
HP 83545A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wiltron 6229D, RF Plug-In, 7.9-18.5GHz	\$300
HP 8410C/8412B, Network Analyzer w/8411A/Opt. 18, 18GHz	\$800	Wiltron 62FF75, VSWR Bridge, 10-1000MHz	\$150
HP 8411A, Frequency Converters	\$250	Wiltron 6NFS0, Autotester, 1-1500MHz, for 640	\$100
HP 8414A, Polar Display	\$100	Wiltron 7B50, Detector, 1-1500MHz, for 640	\$100
HP 8444A, Tracking Generator	\$650		
HP 8445B, Spectrum Anz., Automatic Pre-Selector	\$300		
HP 8447E, Amplifier, 1-1300MHz, Gain 22dB	\$600		
HP 8501A, Storage Normalizer, w/cable	\$800		
HP 85033C, 3.5mm Calibration Kit	\$1,000		
HP 8505A, Network Anz., w/8501A & 8503A, Opt. 05	\$4,000		
HP 85021B, Directional Bridge, 10MHz-26.5GHz	\$1,200		
HP 8557A, Spectrum Analyzer, .01-350MHz	\$800		
HP 8558B, Spectrum Analyzer, 1-1500MHz	\$1,300		
HP 8559A, Spectrum Analyzer, .01-21GHz	\$2,000		
HP 8559A/853A, Spectrum Analyzer, Digital, .01-21GHz	\$3,000		
HP 8565A, Spectrum Analyzer, .01-22GHz, Opt. 100	\$3,000		
HP 8569A, Spectrum Analyzer, 10MHz-22GHz	\$5,000		
HP 86220A, RF Plug-In, 10-1300MHz	\$500		
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400		
HP 86260A, RF Plug-In, 12.4-18GHz	\$400		
HP 86290A, RF Plug-In, 2-18GHz	\$1,200		
HP 86290B, RF Plug-In, 2-18GHz	\$1,400		
HP 8643A, Synthesized Frequency Generator	\$6,000		
HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500		
HP 86601A, RF Plug-In, 110MHz	\$300		

MONTHLY CLEARANCE SALE

HP 3325A PROGRAMMABLE FREQUENCY SYNTHESIZER, .001Hz-21MHz, 11 DIGIT DISPLAY, HP/IB PROGRAMMABLE, OUTPUT 1mV-10V INTO 50Ω. \$795

PHELPS INSTRUMENTS

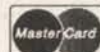2631 Hillside Ave., Norco, CA 91760
909-279-7347 • FAX 909-279-7323



ELECTRONICS Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:

TJBYERS@aol.com

TJBYERS@juno.com

or by snail mail at

Nuts & Volts Magazine,
430 Princeland Ct.,
Corona, CA 91719.

What's Up:


Another look at surplus Variacs and high-power switching regulator ICs. Looking at and understanding old ICs. Theory on sodium-vapor lamps and antennas. Computer keyboards, game ports, and streaming tape backup.

Using 400-Hz Variac

Q - I was scrounging through a local military surplus warehouse here in Utah and ran across a small Variac manufactured by General Radio. The box said 120 volts at 2 amps, so I took one home hoping to construct a small variable AC power supply. However, inside the box was a note that said "350 cycles minimum." I tried (briefly) hooking it up to the AC mains in my house — but it got real hot real fast. This Variac was obviously used in an aircraft of some sort, but I need to find a way to use it on the ground. Any ideas?

Garry Iman
via Internet

A - This is a 400-Hz Variac made specifically for WWII planes like the B-29. But I doubt many of them ever flew. Most were used on the ground to bench test and repair the avionics. The power source was probably a gasoline generator or dynamotor. Generally, you can wire two 400-Hz transformers together in series and they will work off 60 Hz without running hot. The problem with wiring a Variac this way is that you can't get the full voltage range from one dial. One dial will vary the output from 0 volts to 1/2 AC and the other will output a voltage from 1/2 AC to full AC. Depending on how you plan to use the Variac, this could be an annoyance or an advantage. Here's how to connect them.

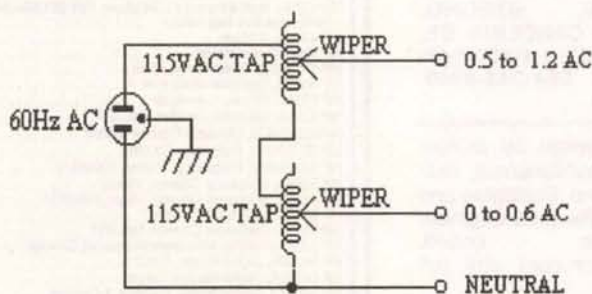

Lightning Observing ... Revisited

Q - In the Feb. '99 issue, there was an article describing an apparatus described by Joe Carr that's used for lightning observing. I'd like to know more about the theory of its operation and some practical details regarding construction. For example:

1. Why is the coil shielded?
2. My scope (10M inputs) can easily read 15 mV. How much amplification of the signal from the coil is needed?
3. How is the output voltage affected by the size and shape of the coil?
4. The X and Y inputs to my scope share a common ground. Can't I just ground one wire from each coil and amplify the signals from the other two wires?
5. Why does using the Z input remove the directional ambiguity?

Dan North
via Internet


A - The metal shield is required to electrically and magnetically isolate the coils from each other. Without it, the antenna appears as a single-turn of wire that has no value in detecting lightning strikes. Their voltage output is determined by the number of turns; the more numerous the turns, the higher the output voltage. The shape of the coil (round or square) isn't important; the size is — the bigger the better. You can ground one lead from each loop, but it decreases sensitivity and, if the coils are reversed, can null out the signal altogether. A differential amp is more sensitive and provides maximum isolation. The gain of the amplifier depends on several factors, including the number of coil turns, distance from the storm, and the sensitivity of your scope. Basically, you'll have to play with these values. The reason the Z-input provides directionality is because of the cardioid pattern of the antenna. Check out *The Radio Amateur Antenna Handbook*, available from Amazon books (<http://www.amazon.com>), for more details on antenna theory.

Alphanumeric LED Display Pinouts Needed

Q - I'm hoping you can help me with two different numeric readout semiconductor devices that I have. The first one is made by Texas Instruments and is labeled TIL311. The second is made by Hewlett-Packard and says hpHDSP-A903. This is a small green (5/16 inch), seven-segment, 10-pin DIP package. It also has a decimal point to the right side of the digit, which the TI chip lacks. I bought them at a local hamfest, but I have no pinout information. Can you help me with this?

Jeff Ulich
via Internet

A - The first, the Texas Instrument TIL311 chip, is easy because it's still in production and sells for about \$10.00. It's a 14-pin DIP package that contains a four-bit latch, decoder, driver, and 4 x 7 LED matrix display. The data sheet is located at <http://www.ti.com/sc/docs/products/analog/til311.html>. (BTW, this chip really has two notches on top and one on the bottom.) The second chip was a little harder, but easily found at http://ftp.hp.com/pub/access/hp/COMP/led_displays/hdsp335x.pdf. According to HP, this display comes in four dazzling colors: AlGaAs red, high-efficiency red (HER), yellow, and green.

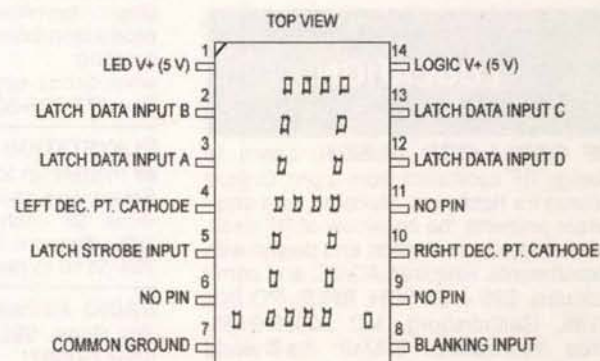

This TR-3 Isn't a Triumph, It's Travan

Q - I have two Colorado T-1000 tape backup drives that I use on a regular basis. A friend of mine recently gave me several TR-3 tapes to use. However, my tape drives use TR-1 tapes. I've looked at the two tapes and can't see any differences except for the labeling. My question: Is it possible to use the higher capacity tapes in my drives? I also have friends that have TR-1 tapes that they would like to use on their T-3000 drives. Could this also work if they were reformatted?

Bob Drought
via Internet

A - There is a slight difference between these two tape cartridges, even though they might look the same on the outside. First, there's a physical notch that

tells the drive that it's a TR-3 and not a TR-1 cartridge. The technology is called Travan (before Travan it was called QIC, as in QIC-80) and it's now migrated to the NS-20 level (20GB), none of which are interchangeable. Second, we're talking two different languages here, like English and Chinese. It's hard to translate between the two because they're totally unrelated. In other words, there's no way your T-1000 can understand a TR-3 cartridge. It can't even reformat it to work in your drive. However, a TR-3 drive can read your TR-1 cartridge, but not talk (write) to it. So your T-3000 friends are out of luck, too, when it comes to using TR-1 cartridges. Let's do an analogy. Today we have high-resolution digital TV with the same dilemma — it's slightly backward compatible with my B&W TV, but my TV isn't forward compatible. Any day now, they will pull the plug on my B&W and I'll have to invest in a color digital TV. Same thing is going to happen with the TR-1 and maybe TR-3. For now enjoy, but realize it's a dead-end solution that sounded good at the time. Check into read/write CDs as a replacement. They're getting cheaper by the minute and are a lot faster.

Dualing Game Ports

Q. Is there a way to connect an A-B box to my computer's 15-pin serial (game) port so that I can use my joystick on "A" and my Nascar wheel control on port "B"? If this is possible, where can I order this kind of A-B box? The one that I ordered has 15 pins alright, but they are in three rows and not the two rows that I need.

**D.E. Wright
via Internet**

A. Actually, there are two game ports on your PC, which means you don't need an A-B switch. What you do need, however, is a dual game port adapter board like the DPGI from Jameco (1-800-831-4242; <http://www.jameco.com>) — catalog number 105515. The price is \$12.95 — about the same as for an A-B switcher. Better yet, you don't have to switch between

the devices; you can use both at the same time in the same game with a buddy. The A-B box that you have is for VGA video so that you can switch between two monitors.

Shakey Sodium Lamp

Q. The high-power sodium light pole I have is 10 years old and, for the last two years, it has developed a puzzling quirk. It goes off then comes right back on — well kinda. Actually, the light goes down to a dull glow, then the lamp comes right back on. It doesn't go out all the way. It looks very much like the light reduction you get with an incandescent bulb when a heavy load, like a motor, starts up. I've tried replacing the bulb, ballast capacitor, photocontroller, FET driver, and have even switched it over to the other side of the 220VAC line. Still it happens. The strangest part is that it's sporadic. It can stay on for long periods of time between all this. Any clues?

**Lawrence Dunlap
Bethany, IL**

A. What you describe sounds like an interruption of power to the lamp. Sodium vapor lamps fall into a category of lighting called High Intensity Discharge, or HID, which includes mercury vapor and metal halide lamps. Basically, an arc is struck, usually using an inductive kick from a ballast transformer, and the gas begins to grow hot. The hotter it gets, the brighter the light. This can take anywhere from 3 to 15 minutes, depending on the chemistry and geometry of the lamp. If power to the lamp is lost, even for a moment, the arc goes out. Once the arc is extinguished, the gas has to cool before the spark can be reignited because it can't cross the gap due to the higher internal pressure. This can take anywhere from one-half minute for low-pressure sodium types to over seven minutes for high-pressure versions. Typically, it's a wait of a minute or two. During this time, the hot gas is still glowing while the pressure drops. This is the glow that you see. What can cause this you ask? What's

High-Power/Low-Voltage Switching Regulator

Q. The switching regulator article (Switching Voltage Regulator Basics) in the May '99 issue was great. But the examples you provided don't meet my requirements. The LM2577-12 cited has a low start-up voltage limit of 3.5 volts. What I need is a switching regulator that can output 10 volts at 1.5 amps working off a single 3-volt lithium battery. Do you know of any suitable chips?


**Jim Halbert
via Internet**

A. Well, it wasn't easy because of your power requirements, but I found a chip that will work.

The MAX1771 from Maxim (1-800-998-8800; <http://www.maxim-ic.com>) can deliver 12 volts at 2 amps from a 3-volt input. You can purchase this chip from QuestLink (<http://www.questlink.com>) for under \$5.00. The clincher is that you have to use an external pass transistor, which increases the part count and ups the construction cost. Maxim also sells an evaluation kit for this chip. Here's the schematic of the evaluation kit.

In this circuit, the MAX1771 is preset for 12 volts output, but that's easily adjusted via a voltage divider formed by R2 and R3. For a 10-volt output, R3 would be in the range of 150K and R2 would be about 30K. The formula is on the schematic. Don't forget to add C6 if R2 is installed. The 1260.pdf data sheet (available from the Maxim web site) shows the PC board artwork for this evaluation circuit.

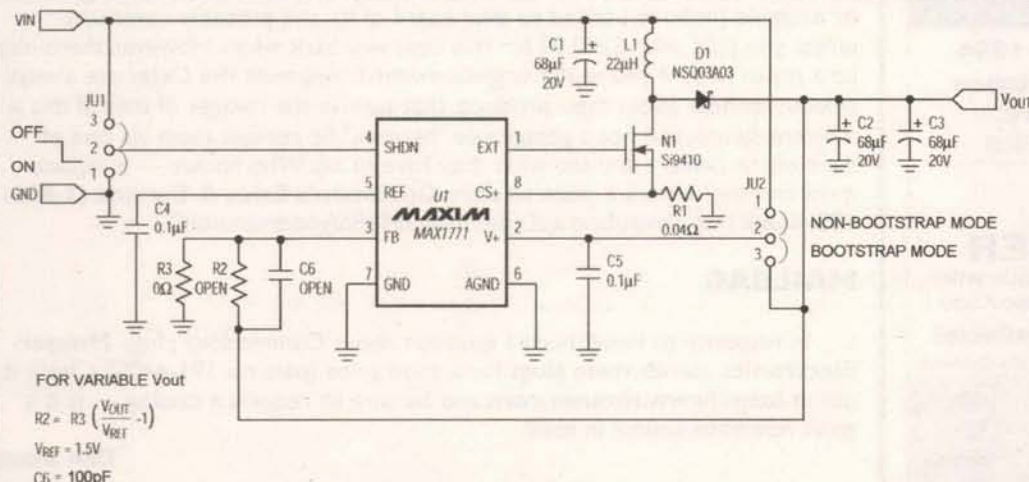BTW, I seriously doubt you'll get 15 watts ($P = IE = 10V \times 1.5A = 15W$) from a single lithium battery. You might want to consider alkaline batteries; the start-up voltage of the MAX1771 is 2 volts, well within their lifetime voltage range.



D.T.M.F. DECODER

For interconnect and remote control applications

**Model
NC401**

The Model NC401 is a micro-miniature DTMF decoder, designed for selective control of local or remote applications. Measuring .80"Wx1.37"Lx.23"H, the NC401 combines three distinct, multi-addressing decoders offering multiple user-configurable functions. All programmed features are stored in non-volatile E2PROM memory and are easily programmed by means of a conventional DTMF encoder or the Model NC500 Universal/P.C. programmer. This highly engineered decoder is ideal for portable radio applications having limited space for accessories. The NC401 comes complete with micro-miniature 14 pin header and 12" color coded cable assembly.

\$59.95

Nor-fax Doc. #5545

VOICE SECURITY ENCRYPTION

**Model
NC802**

The Model NC802 is a miniature voice scrambler designed to provide intermediate level security for two-way radio voice communication systems and is a perfect, cost-effective solution to entry-level voice scrambling as a defense against unauthorized or casual listeners. The NC802 provides eight user selectable carrier codes commonly used by other manufacturers and interfaces easily to most radios with near transparency to the user.

\$59.95

Nor-fax Doc. #5759

For Detailed Specifications or Product Catalog call our 24-Hour NorFax retrieval system at 530-477-8403 or on our Web Site at www.norcommcorp.com



800-874-8663

15385 Carrie Drive
Grass Valley, CA 95949 USA

puzzling about this scenario is that it worked flawlessly for eight years, so let me polish off my crystal ball and take a guess. First, the power company may be causing power glitches as it changes its load level from station to station and line to line. Second, the ballast could be bad. This generally happens when a lamp nears the end of life but isn't replaced before it damages the transformer (this is a common problem with fluorescent fixtures). My guess is that the FET itself is getting close to the end of its life. The life of most power semiconductors is about eight years. Another reason may be due to changes in the footing of the lamp. Some lamps can't be moved, tilted or vibrated during operation. If so, the spark goes out, and the above recovery sequence goes into effect. I hope this helps.


(Note: Mr. Dunlap responded and said the problem was a bad FET. Thanks for the feedback, Lawrence.)

Old Keyboards


Q - I was given an old IBM keyboard that has 10 function keys which are lined up in a 5-by-2 pattern on the left side of the keyboard. The interface is a six-pin telephone style plug. I'm wondering if it's possible to find or build a converter to use this keyboard with a PC/XT, AT, or PS/2 style computer?

A - This keyboard was made to plug into a DEC AT-compatible computer, and can be modified to work with an AT or PS/2 PC. The two outer wires of your six-pin connector are the power leads, and the inner two are the clock and data. I don't remember the colors (this is 1986 technology and I long ago gave away my DEC PC keyboard), but red should be +5V, black GND, and yellow data — but don't quote me. Anyway, here are the new pinouts.

PC AT 5-PIN DIN

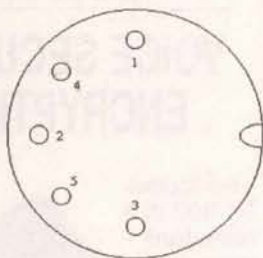

PS/2 6-PIN MINI DIN

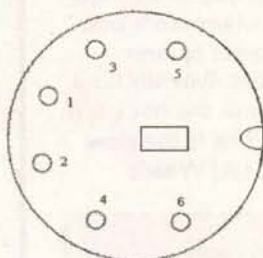

PC AT 5-Pin DIN	Function	PS/2 6-Pin Mini DIN	Function
1	CLK	1	DATA
2	DATA	2	---
3	RESET	3	GND
4	GND	4	+5V
5	+5V	5	CLK
		6	---

However, this keyboard may not work with all PCs. The polarity of the data signal is inverted between the PS/2 and the AT keyboards. Some motherboards

Flush Rush Flow Meter


Q - I need a device that can be installed in a commode water supply line that will detect when water is flowing. It has to be capable of sending the signal over an interface wire of about 150 feet and set off an alarm after a predetermined time.

Edwin Spencer
Burns, TN

A - This is an interesting question because it poses a score of solutions. You can break the water line and insert a pressure sensor, or you can insert a flow sensor that uses a switch, paddlewheel, or propeller to detect water flow. But both

force you to know something about plumbing. A better solution is a microphone flow sensor, like the one below.

The nice thing about this design is that you don't have to break the water line. When water flows through the pipe, it makes noise which the microphone picks up and outputs to the op amp. This, in turn, triggers the 555 timer. If the water flow doesn't stop before the timer times out, the alarm screams. To keep the microphone from triggering the timer everytime somebody walks past the bathroom, I've included a high-pass filter with a cut-off frequency of about 10 kHz so that only the sound of gushing water — not thump-thump footprints — will trigger the timer.

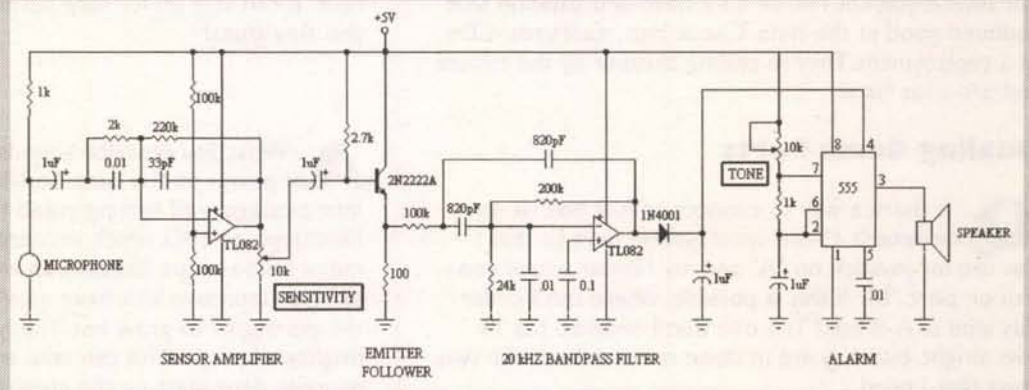

can take either keyboard, some cannot. BTW, not all keyboards that have the function keys on the left follow this formula. Before IBM introduced the AT the keyboard data flow pattern was different and may not be compatible with your current PC.

Understanding ICs By The Numbers

Q - I'm in need of a part for the wife's kitchen appliance. The microcontroller chip is dead, due to voltage surges caused by the brushes of the motor (cheap engineering at work again). Here are the markings on the chip.

Oster 1981
A7570-12
Mexico B
0110-1 (version number)
8529

Harry Shipley
via Internet

A - I'm glad you gave me the model date and IC code numbers, because they say a lot. First, it tells me this is probably an Osterizer blender by the 1981 date. Oster has since been acquired by Sunbeam and has branched out to more low-tech endeavors, like hair clippers and quality toasters. The date code, 8529, is the date the A7570-12 part was made, which is the 29th week of 1985. Mexico B means it was assembled in Mexico, plant B (wherever that is), sometime after that date. The version code probably isn't important; it simply tells you which firmware code is imbedded in the microcontroller's ROM. Now what does all this gain you? It means that a replacement chip is no longer listed or available (nobody I talked to ever heard of it), and probably never was unless you paid over \$200.00 for this item way back when. However, there may be a ray of hope if you're the original owner. Companies like Oster are always anxious to hear about their products that survive the ravages of time. If this is a recent failure, and not a garage sale "bargain," I'd contact them via one of their repair centers and see what they have to say. Who knows — a replacement blender? Here's a place to start: **Goodman's Sales & Service (1-888-333-4660; <http://members.aol.com/miami33186/goodman.html>)**.

MAILBAG

In response to Frank Nally's question about Commodore plugs, **Mouser Electronics** carries these plugs for a good price (part no. 171-4405). Check it out at <http://www.mouser.com> and be sure to request a catalog — it is a great reference source in itself.

Dan Jones
via Internet

SOLUTIONS TO YOUR CABLING NEEDS

Cat.5 -- Enhanced Cat.5 -- USB -- IEEE1284 / 488 / 1394
Firewire -- High-End Monitor -- Manual & Auto Switches
Apple -- Custom Cables -- Premise Wiring -- more!
HUGE SELECTION OF SCSI CABLES & ADAPTERS

TAKE 10% OFF!
THRU THE MONTH OF OCTOBER

(YOU MUST MENTION THIS AD. OFFER GOOD ON ALL ITEMS EXCEPT BULK WIRE & CUSTOM WORK. DISCOUNT DOES NOT APPLY TO SHIPPING/HANDLING/COD.)

Order Online 24 hrs./day. Reseller & Qty. Discounts Available!

No minimum order, same day shipping on most orders, A+ and CET technician available to answer your questions.

	Northwest Cable & Connector Co.	
	www.nwcable.com	
	Phone: (360) 754-3606 Fax: (360) 754-0825	

CALL TOLL FREE

(800) 292-7711
Orders Only

Se Habla Español

C&S SALES

Excellence in Service

**CALL OR WRITE
FOR OUR
FREE**

**64 PAGE CATALOG!
(800) 445-3201**

Digital Multimeters

Elenco Model M-1740



\$39.95

- 11 Functions:
- Freq. to 20MHz
- Cap. to 20µF
- AC/DC Voltage
- AC/DC Current
- Beeper
- Diode Test
- Transistor Test
- Meets UL-1244 safety specs.

Model M-2760 - \$24.95
(9 functions)

Elenco Model LCR-1810



\$99.95

- Capacitance .1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

Fluke 87III



\$299

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

Series II (limited qty.)
\$289

Generators and Counters

Elenco Sweep Function Generator with built-in frequency counter Model GF-8036



\$225

This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.

20MHz Sweep / Function Generator with Frequency Counter Model 4040

\$399



- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

BK PRECISION

10MHz Model 4017 **\$309**
5MHz Model 4011 **\$239**

Elenco Handheld Universal Counter 10Hz - 2.8GHz Model F-2800



\$99

- Sensitivity:**
- <1.5mV @ 100MHz
 - <5mV @ 200MHz
 - <5mV @ 1GHz
 - <100mV @ 2.8GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

B&K Frequency Counter Model BK-1875



1Hz - 2.8GHz
3 Channels
\$189

Sensitivity:

- <0.8mV @ 100MHz
- <6mV @ 300MHz
- <7mV @ 1GHz
- <100mV @ 3GHz

Ultra sensitive synchronous detector bargraph and RF strength.

Elenco RF Generator with Counter (100kHz - 150kHz) Model SG-9500



Features internal AM mod. of 1kHz, RF output 100mV - 35MHz. Audio output 1kHz @ 1V RMS. SG-9000 (analog, w/o counter) \$119.95

Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300



\$175

Features built-in 150MHz frequency counter, low distortion and sine/square waves. SG-9200 (w/o counter) \$119.95

Elenco Oscilloscopes

Free Dust Cover and 2 Probes



S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$995

DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$995
DS-603	60MHz/20Ms/s Analog/Digital	\$1295

Four Functions in One

Elenco Model MX-9300



\$459.95

Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply - 0-30V @ 3A, 15V @ 1A, 5V @ 2A

Elenco Educational Kits

Model AR-2N6K



2 Meter / 6 Meter
Amateur Radio Kit
\$34.95

Model AM/FM-108K



Transistor
Radio Kit
\$29.95



Model AK-700
Pulse/Tone
Telephone Kit
\$15.95

Model AK-870



Radio Control Car Kit
• Solderless
• 7 Functions
• Radio Control
Included
\$24.95



Model M-1005K
Digital Multimeter Kit
• 18 Ranges
• 3 1/2 Digit LCD
• Transistor Test
• Diode Test
\$19.95



Model XP-720K
Power Supply Kit
• 1.5VDC - 15VDC @ 1A
• -1.5VDC - -15VDC
• 5VDC @ 3A
• 6.3VAC @ 1A and
12.5VAC center
tapped @ 1A
\$54.95



Model XK-150
Digital / Analog
Trainer
\$89.95



Model EP-50
Electronic
Playground and
Learning Center
\$19.95

Tekk Radios

Pro-Sport FRS Two-Way Radio Model PRO-SPORT+

- 14 Channels
- Battery Monitor
- Key Lockout
- Monitor Button
- Lightweight
- Palm Sized
- Large LCD Display
- Removable Belt Clip
- Removable Antenna
- Two Radio Call Tones
- Busy Channel Lockout
- Accessory Connector
- Highly Water Resistant

\$79 each
or
\$149.95
Set of 2

Talk up to
2 miles!



PRO SPORT Model
\$109.95 set of 2

Miscellaneous

Elenco Technician Tool Kit Model TK-1500

28 tools plus a DMM
contained in a large
flexible tool case with
a handle ideal for
everyone on the go.



Elenco Quad Power Supply Model XP-581



\$89.95
4 Fully Regulated DC Power
Supplies in One Unit
4 DC voltages: 3 Fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A

Dual-Display LCR Meter w/ Stat Functions B&K Model 878



\$219.95
Auto/manual range
Many features
with Q factor
High Accuracy

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax

SEE US ON THE WEB

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710
<http://www.cs-sales.com>



15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Build a Photo-Electric Counter

If you want to know how many people or things pass a certain point, a counter is used. Counters are used on production lines, at public events, and at store entrances, among other applications.

This construction project describes a digital counter that counts up to 999 each time a light source is interrupted. A special feature allows you to "cascade" another unit, so you can count up to 999,999.

by Fred Blechman

Basically, there are three types of counters: mechanical, electric, and electronic. Some counters are variations and combinations of each of these basic types.

Mechanical counters can be triggered manually, such as the digital counter held in a user's hand, where a button is pressed for each count. This advances the units-counting numbered drum one count each time. As the ones-count digit drum completes a rotation, it advances the 10s-count digit. Similarly, the 100s-count is advanced when the 10s-count completes each rotation, and so forth, up to the maximum number of counter digits. Some mechanical counters operate by direct gearing, such as the odometer on your car, which advances based on tire rotation.


Electric counters are really just mechanical counters that are triggered by switches such as on

extended use. A sensitivity adjustment allows use in various light conditions, and the count can be reset or stopped at any time.

If your need is for more than a count of 999, an "overflow" pulse is provided for clocking additional digits. For example, you can easily cascade additional photo-electric counters for three additional digits each, as described later.

Circuit Description

Figure 1 shows the schematic of the photo-electric counter. The circuit basically consists of three seven-segment LED displays controlled by a counting circuit composed of two integrated circuits (IC2 and IC3) which are triggered by IC1. Figures 2, 3, and 4 show the pinouts of IC1, IC2, and IC3, respectively.

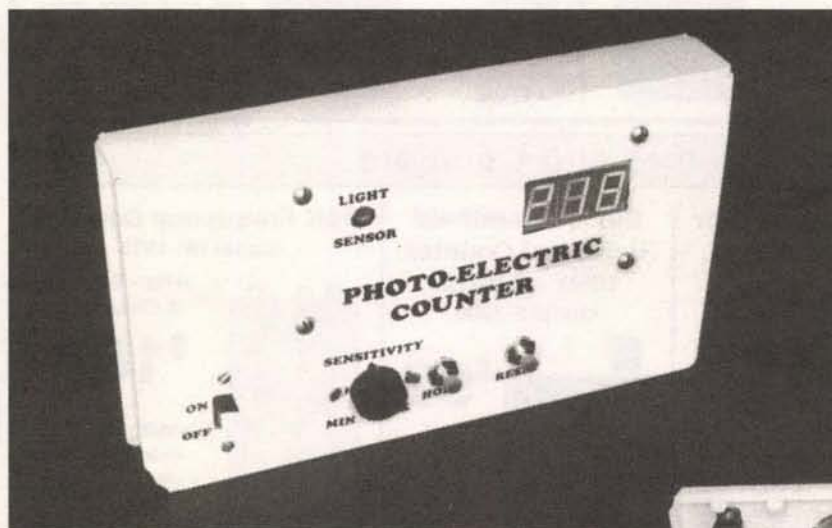

The Photo-Electric Counter can be built into a standard VHS video cassette box with all the controls and light sensor mounted on the cover.

mats or turnstiles. The switches operate solenoids to advance the digits on the linked rotating drums. Because both mechanical and electric counters are essentially mechanical in operation, they are noisy, subject to failure from wear, and limited in their counting speed.


True electronic counters, on the other hand, are completely silent, and have no moving parts to wear out. They use lighted digits to display the count, and can operate at high speed. While some electronic counters use switches to trigger their counting, the construction project we will describe here uses the interruption of light as its count trigger.

Description

The "Photo-Electric Counter," available in kit form for under \$25.00, has a three-digit display that counts to 999 before resetting to 000. It uses three integrated circuits to detect and count the interruption of light on a photocell, and shows the total count on three red LED seven-segment digital displays. This counter can be used in business, industry, and security applications to count just about anything, from cartons on a conveyer belt, or copies on a printer, to people moving through a doorway. You can make money building these counters and selling them to stores and companies.

The photo-electric counter (really, a Photo-ElecTRONIC Counter) is completely silent, has no moving parts (except "Hold" and "Reset" switches), and can count at very high speed. We even used it to count the speed of a four-bladed fan by counting the fan blades interrupting a light beam in a given time; try to do THAT with a mechanical or electric counter!

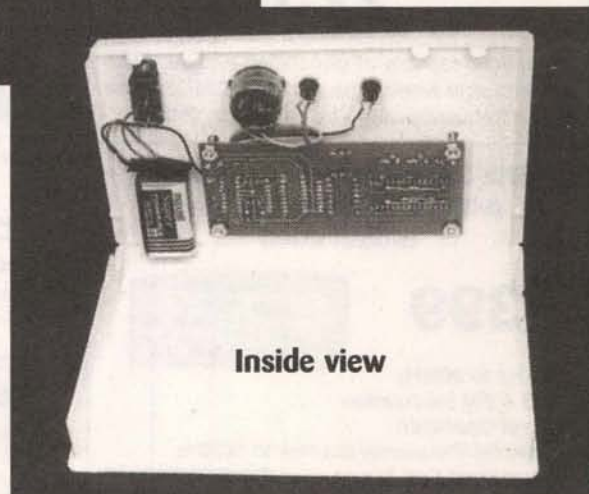The photo-electric counter can be powered by a regular nine-volt battery for occasional or short-duration use, or a DC wall-plug transformer for



Inside view

Only one section of IC1, a CD4093B quad two-input Schmitt Trigger, is used. This is a NAND circuit, where the output is the opposite of BOTH inputs. That is, if BOTH inputs are LOW, the output is HIGH, and if BOTH inputs are HIGH, the output is LOW.

This is a Schmitt-Trigger device, so change of state is triggered when BOTH inputs increase SOMEWHAT ABOVE one-half the supply voltage, or decrease SOMEWHAT BELOW one-half the supply voltage. The difference between trigger points (almost two volts with a nine-volt supply) is called "hysteresis," and reduces false response to noisy or slowly changing input voltage levels.

The two inputs, pins 1 and 2, are connected together to a voltage divider at the junction of photocell P1 and resistor R2. Since the photocell has a supply voltage at its top, and R2 is connected through potentiometer R1 to circuit ground, the voltage at the IC1 input depends on the resistance of P1 and the setting of R1.

When little or no light falls on the photocell, it has a very high resistance of several hundred thousand ohms. Since this is considerably higher than the sum of R1+R2, the input to IC1 is at a LOW voltage, so the output of IC1 is HIGH. However, as light falls on P1, its resistance drops drastically, down to

less than 100 ohms in strong light. This causes the voltage at the input to IC1 to increase. When the input to IC1 reaches somewhat above one-half the supply voltage, its output at pin 3 suddenly changes state to LOW.

Potentiometer R1 lets you set the light sensitivity of the trigger point; the higher the resistance setting of R1, the less the resistance of P1 must drop to trigger IC1, and therefore the greater light sensitivity.

The negative-going voltage at output pin 3 of IC1 acts a CLOCK pulse to pin 12 of IC2, an MC14553B three-digit BCD counter. This IC is an amazing device. It not only counts upward in BCD ("Binary Coded Decimal") — that is, a four-digit code from 0 to 9 decimal — but it enables the output of this binary code for three digits, one at a time, each for a short duration, using "time multiplexing."

To explain further, if neither push-button switch S1 or S2 is closed, pins 13 and 11 of IC2 are held LOW by resistors R3 and R4. This allows IC2 to accept clock pulses. With each incoming pulse, internal counters create the BCD code for each of three digital displays: DS1, DS2, and DS3. As an example, if the total clock count was 319 decimal, then the IC2 internal count for DS1 (units) would be BCD 1001 (9), DS2 (10s) BCD would be 0001 (1), and DS3 (100s) BCD would be 0011 (3). (If you don't follow this, don't worry about it, but you may want to brush up on the binary counting system.)

This four-digit binary count for EACH digit is

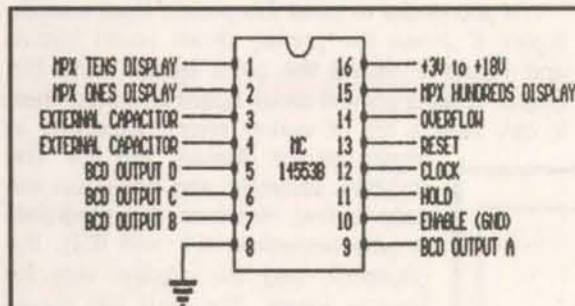


Figure 3: IC2 — MC14553B Three-Digit BCD Counter.

enabled at pins 9, 7, 6, and 5 (called A, B, C, and D in Figure 1), but only for an instant — about 2.5 milliseconds. Why? Because an internal oscillator switches between the three digital BCD codes at a speed dependent upon capacitor C1, which is connected between pins 3 and 4 of IC2.

With a value of about .001 mF for C1, the IC2 oscillator runs at about 400 cycles per second, changing output state to LOW at pins 2, 1, and 15 in that order. As we'll see later, this multiplexing sets the number to be shown on each of the three digital displays at any instant, although they all appear to be on at the same time. When the count exceeds decimal 999, an overflow pulse appears at pin 14 (normally LOW, goes HIGH), which can act as a trigger to another counter, thus allowing higher counts. More on this later.

When switch S1 is closed, this puts a HIGH on pin 13 — the RESET pin of IC2 — and the internal counters are returned to 000. When switch S2 is pressed, this puts a HIGH on pin 11, the HOLD pin of IC2, and counting stops. Unfortunately, since this switch is not "debounced," some jump in the

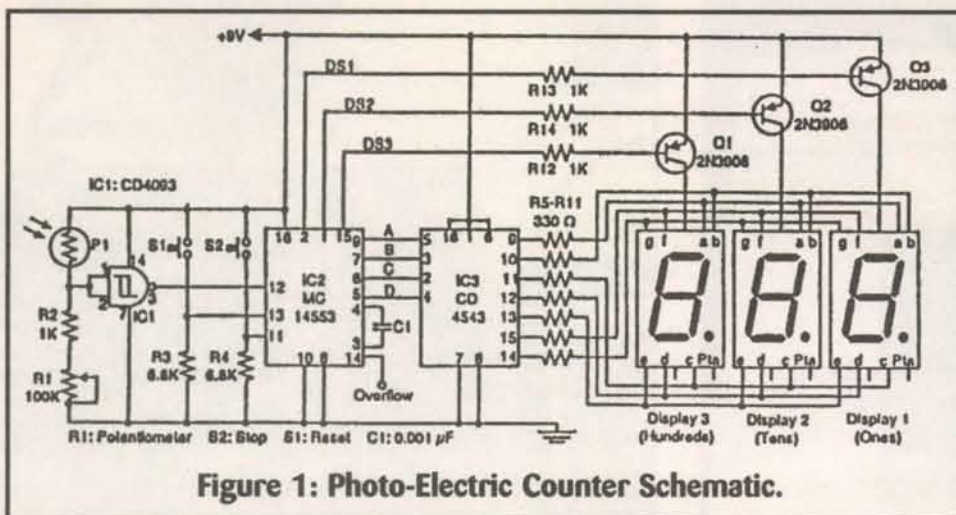


Figure 1: Photo-Electric Counter Schematic.

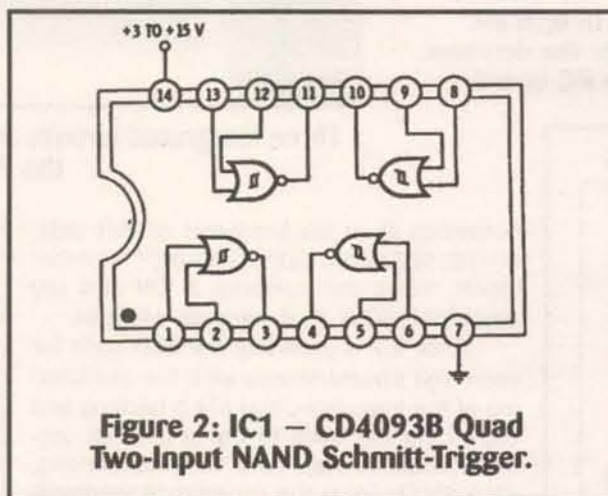


Figure 2: IC1 — CD4093B Quad Two-Input NAND Schmitt-Trigger.

counting may be observed when this push-button switch is pressed. (Preventing this would require additional connections to the other NAND circuits of IC1, and a double-throw switch in place of S2.)

The BCD outputs are multiplexed to IC3, a CD4543B BCD to seven-segment latch/decoder/driver, another amazing chip. As each incoming BCD code is input from IC2 to pins 5, 3, 2, and 4 of IC3, internally the BCD code is latched and interpreted to determine which segments of each seven-segment display should be lighted.

Each display has segments designated A to G, as shown in Figure 5. These digital displays need to have power to light their segments. They are common anode displays, which means the common to each segment LED is positive voltage, and each segment is looking for a ground (LOW) to light. The positive voltage is supplied to each display through separate 2N3906 PNP silicon transistors,

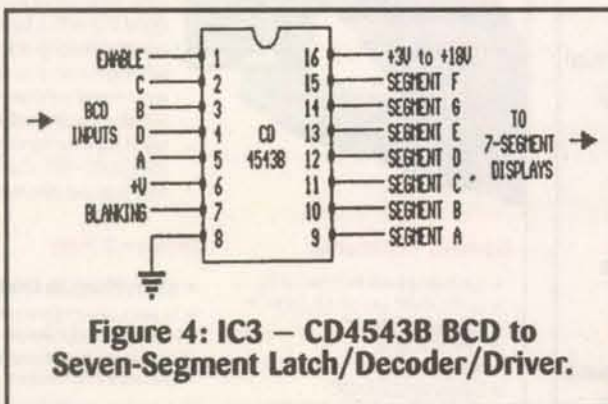


Figure 4: IC3 — CD4543B BCD to Seven-Segment Latch/Decoder/Driver.

Q1, Q2, and Q3.

In this circuit, these transistors all have positive voltage applied to their emitters, but they will not conduct current unless there is a lower voltage (negative bias) on their base. Looking at Figure 1, we see that pins 2, 1, and 15 of IC2 each go to the base of one of the transistors. When these pins are HIGH, the associated transistor is OFF.

However, as previously discussed, each of

Great Books for Hobbyists, Students, Engineers . . .

Simple, Low-Cost Electronics Projects

by Fred Blechman

Learn electronics with Fred Blechman's exciting new book. Begin with simple designs and progress to more sophisticated projects. Each project comes with a complete discussion of circuit theory and parts list, as well as information on troubleshooting and testing. Build voltmeters and multimeters, inductance and semiconductor testers, variable frequency audio oscillators, a photoelectric counter, and much more!

1-878707-46-9/224 pages/\$19.95

Controlling the World with Your PC

by Paul Bergsman

PC Disk Included! Connect your computer to the real world and make it do useful work like controlling stepper motors, turning appliances on and off, or monitoring fluid levels. PC disk contains software files in ready-to-use form.

1-878707-15-9/208 pages/\$35.00

The Forrest Mims Engineer's Notebook

by Forrest Mims III

This revised edition of Forrest's classic book includes hundreds of useful circuits built from integrated circuits and other parts available from convenient sources.

1-878707-03-5/156 pages/\$19.95

The Integrated Circuit Hobbyist's Handbook


by Thomas R. Powers

Covers the major types of integrated circuit devices—linear, TTL, and CMOS—and provides complete details and theory about their operation. Contains lots of useful application circuits—an essential reference for every hobbyist. 1-878707-12-4/256 pages/\$19.95


Order on the Web!
For these and other great books on electronics, visit:
www.LLH-Publishing.com

or
call 1-800-247-6553 to use a major credit card, or send check or money order to:

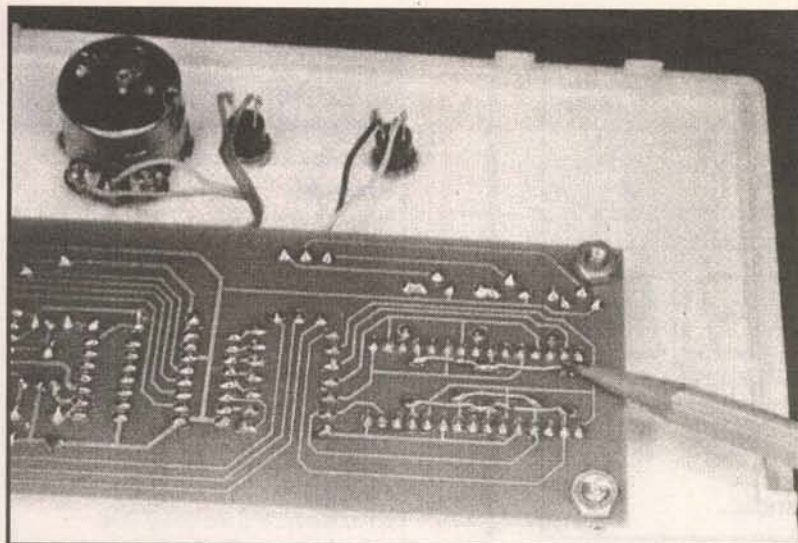LLH
Technology Publishing
3578 Old Rail Road
Eagle Rock, VA 24085



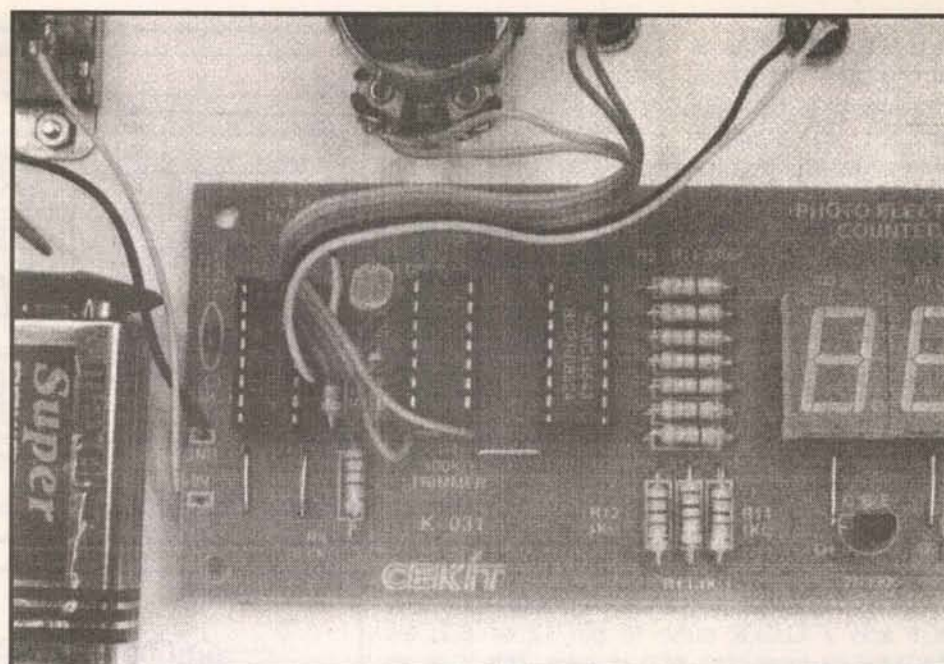Five jumpers are needed for the displays to operate properly. If you don't put these jumpers under the displays, they may be put on the etched side of the PC board.



Three integrated circuits and a photocell are the brains and trigger of the Photo-Electric Counter.

DISPLAY PINOUTS

- 1 - CATHODE E
- 2 - CATHODE D
- 3 - COMMON ANODE
- 4 - CATHODE C
- 5 - CATHODE D.P.
- 6 - CATHODE B
- 7 - CATHODE A
- 8 - COMMON ANODE
- 9 - CATHODE F
- 10 - CATHODE G

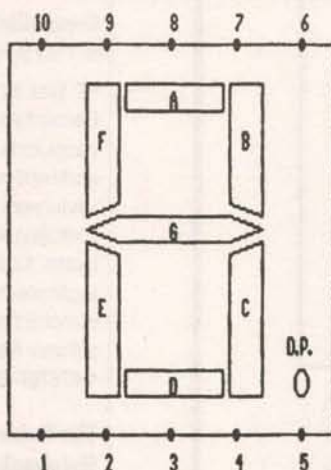


Figure 5:
Common-anode
seven-segment
displays.

these pins goes LOW when they are cycled by the IC2 internal oscillator during the time multiplexing process. As each pin goes LOW, it switches the associated transistor ON, allowing it to conduct

current to all of the segments of that digit, IF THE SEGMENT SEES GROUND! In other words, when the transistor is ON and any segment is LOW, that segment will light.

Since IC2 is providing the BCD code for each digit simultaneously with the multiplexing of the transistors, and IC3 is latching and converting this code to the seven-digit segment code in step with the multiplexing, each display lights the appropriate segments for the decimal digit to be shown as its associated transistor is turned ON. The sequence is Display 1, Display 2, Display 3.

Resistors R5 to R11 are used to limit the current to each display segment. Because of multiplexing, each segment is lighted only about one-third of the total time, but the transition between digits is so fast that the eye does not see any flickering. Later, under "Troubleshooting," we'll show how to slow down the multiplexing frequency for closer observation

of this action. This all may seem confusing on first reading. Read it again, referring primarily to Figure 1, and it should make more sense. However, the circuit works even if you DON'T understand it!

Assembly

If you purchase the \$24.95 kit indicated in the Parts List, all the parts you need — especially the "hard-to-find" parts — are supplied, and an etched and drilled silk-screened printed circuit board is included. This makes assembly a less-than-one-hour job. Also included with the kit are sockets for the three integrated circuits, a nine-volt battery snap, wire for jumpers, and solder, as well as assembly instructions.

If you desire to build this project from scratch, Figure 6 shows the printed circuit board layout, and Figure 7 shows the parts layout using this board. While a printed circuit board is not required, it can save a lot of wiring errors, especially in regard to the displays and ICs. The resistors, switches, and transistors are easy to find. However, the integrated circuits (especially IC2 and IC3), the photocell, and the displays may be hard to locate. The Parts List shows possible sources.

Use care in assembly regarding parts placement and soldering. Many of the pins are only one-tenth of an inch apart, so be careful to avoid unintentional solder bridges. NOTE: Be sure to install all 11 jumpers shown silk screened on the PC board, including five UNDER the displays!

We didn't notice that these jumpers were needed until AFTER the displays were soldered to the board, so we had to figure out where they went and then soldered them on the back (printed circuit side) of the PC board!

When wiring to the potentiometer, R1, you only need to connect to two of the three terminals, since R1 acts as a variable resistor in this circuit. One wire goes to the center terminal. Holding the potentiometer with the back facing you and the terminals at the bottom, connect the other wire to the right terminal. This will give your light maximum sensitivity when the potentiometer shaft — looking from the front — is rotated fully clockwise.

When Visiting Disney World And Sea World...
Come To The World Of Electronic Surplus!

SKYCRAFT

PARTS & SURPLUS, INC.
ORLANDO, FLORIDA

Located At The Intersection Of I-4
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial
And Government Electronic Surplus Including:

- ★ WIRE
- ★ SWITCHES
- ★ RESISTORS
- ★ TRANSISTORS
- ★ TRANSFORMERS
- ★ TEST EQUIPMENT
- ★ NI-CAD BATTERIES
- ★ COAX
- ★ RELAYS
- ★ HARDWARE
- ★ CAPACITORS
- ★ PANEL METERS
- ★ CIRCUIT BOARDS
- ★ INTEGRATED CIRCUITS

★★★★★★★★

We Buy Surplus
Electronic Parts —
FAX your list.

www.skycraftsurplus.com

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186

HOURS:

Monday - Friday 8:30-6:00
Saturday 8:30-5:00



BIG POWER LOW COST



Dominos are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominos are true plug-and-go control.

Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware clock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**

740 Florida Central Pkwy., Longwood, FL 32750
(407) 262-0066



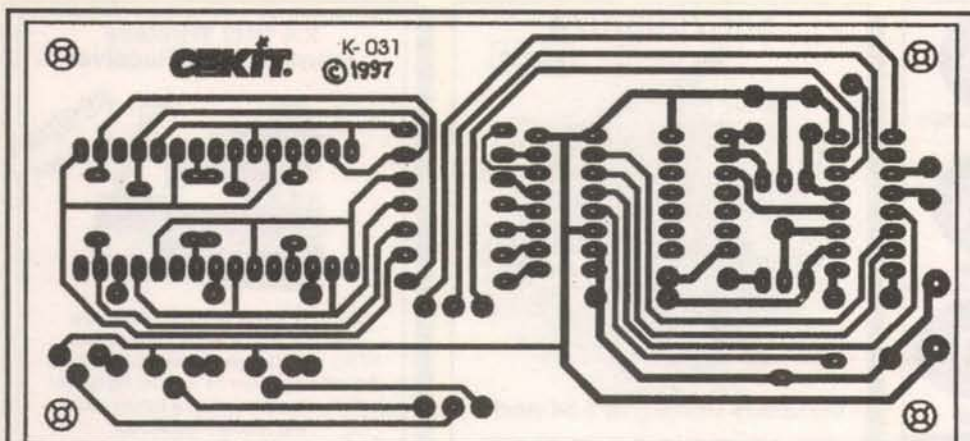


Figure 6: Printed Circuit Board Layout.

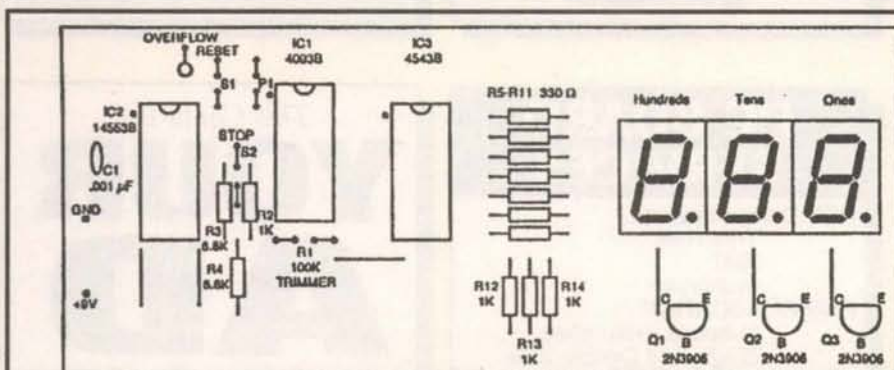


Figure 7: Parts Layout.

Packaging

We decided to assemble the printed circuit board into a white plastic VHS video cassette tape case, as shown in the photos. We decided to mount everything on the inside of the case lid. We cut a rectangular hole for the displays, used four mounting screws to hold the PC board in place, and mounted the two switches and the potentiometer. The battery is held in position with double-sided tape.

The battery draws considerable current (about 55 milliamperes at nine volts), so we added a simple slide switch to turn it OFF when not in use. This was more convenient than opening the case and unsnapping the battery connector.

You may prefer to power the counter externally, and this works fine. We found it worked well down to five volts (using only 20 milliamperes), and a regulated power supply was not required. A standard six- or nine-volt DC wallplug type of power supply worked fine.

Testing the Counter

There's nothing much to testing the counter. Connect the battery or external power and all three digits should light, showing "0" for each digit. This tests all the LED segments except the center bar, G.

Dim the lights, or go in a closet, and use a flashlight for testing. The digits should increase one count each time the light shines on the photocell. Note that counting occurs NOT when the light beam is broken, but when the beam strikes the photocell again. It is easy to verify this. Shine a flashlight beam on the photocell, then cover the photocell with your finger (no count), and then uncover the photocell so the beam shines on it again (up one count).

The potentiometer has a definite effect on the counter's light sensitivity. Turn it clockwise to MAX sensitivity for a weak light source, counterclockwise to MIN for a strong light source. Watch the digits until they advance reliably after each resumption of the light path after interruption.

High ambient light can make counting unreliable since the photocell is very sensitive. It is best to

use a light source aimed directly at the photocell. If ambient light remains too high, and interruption of the light source does not trigger a count when the interruption is removed, extend a one-inch long black tube over the photocell to shield it from external ambient light.

The HOLD button may cause the digits to advance several counts whenever it is pressed. This is most common when the photocell is in complete darkness, or when the sensitivity control is turned to minimum sensitivity with some light on the photocell. This effect can be used to advance the digits manually to test all digit segments. The RESET button returns all digits to zero.

More Digits?

As mentioned earlier, an overflow condition (the next count after 999) causes pin 14 of IC3 to go HIGH. If this pin is connected to pins 2 and 3 of IC1 of an identical photo-electric counter using a common power supply, this will allow you to count up to three additional digits (999,999). The first three digits will be the added counter. Since the added counter ALSO has an overflow, you can add three MORE digits in the same manner with a third photo-electric counter, for a total count of 999,999,999!

Troubleshooting

Suppose, when you add power, none of the digits light! Check the wiring to the switches and potentiometer to see that you don't have them mixed up. Careful as we were, this happened to us! We moved the wires to the right place and some display segments lighted, but others didn't. This is when we dis-

Parts List and Sources

C1 - .001 mF 50V ceramic disk capacitor
DISP1, DISP2, DISP3 - Common-anode seven-segment .56-inch high red LED display (NTE3078)
IC1 - CD4093B Quad Two-Input NAND Schmitt-Trigger (NTE4093B)
IC2 - MC14553B Three-Digit BCD Counter (NTE4553B)
IC3 - CD4543B BCD to Seven-Segment Latch/Decoder/Driver (NTE 4543B)
P1 - Photocell (RadioShack 276-1657; five styles/\$2.29)
Q1, Q2, Q3 - 2N3906 PNP silicon transistor
R1 - 100K linear potentiometer
R2, R12, R13, R14 - 1K 1/4-watt resistor
R3, R4 - 6.8K 1/4-watt resistor
R5 to R11 - 330 ohm 1/4-watt resistor
S1, S2 - Normally open push-button switch
Miscellaneous: Etched/drilled/silk screened printed circuit board, jumper wires, nine-volt battery snap, one 14-pin IC socket, two 16-pin IC sockets, solder.

ALL of the above parts are included in the "CEKIT #K-Q31 Photo-Electric Counter Kit" available from **Centerpoint Electronics, Inc.**, 5421 Lincoln Avenue, Unit A6, Cypress, CA 90360, (800) 422-1100. The price is \$24.95 plus \$7.95 shipping, and 7.75% sales tax for California residents.

Centerpoint offers many other kits. See their web page on the Internet at www.shopsite.com/kits/. This particular kit is shown at www.cpcare.com/prod85.html.

The parts listed above as NTE are available from **NTE Electronics, Inc.** Call (800) 631-1520 for local distributor, price, and delivery.

covered — by tracing circuit paths on the PC board, and referring to the display pinouts shown in Figure 5 — that we had omitted five jumpers that should have been put in place under the displays.

Of course, other things can go wrong. Be sure the transistors and ICs are oriented properly, and that the right values of resistors are where they should be. Voltage and ohmmeter checks can be useful. An oscilloscope can be used to see the multiplexing action on pins 2, 1, or 15 of IC2.

If any of the displays are not lighted, check the path from IC2 pins 2, 1, and 15 through transistors Q3, Q2 and Q1 to see if the multiplexing signal is switching between displays. To slow this action down so you can see the switching of each display, temporarily put a .22 mF capacitor across C1. If you use a 1 mF capacitor across C1, you can see each display light separately for several seconds.

If any segment does not light for ALL three displays, trace the path for that segment back through its current dropping 330-ohm resistor to the proper output pin of IC3. Look for poor solder joints or solder bridges. Generally speaking, unless badly handled or treated, the ICs, transistors, or displays are most likely NOT at fault. **NV**

Mr. NiCd

SEPT. 1999 SUPER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:			
FNB-40xh 51m-NMH	7.2v	650mAh	\$41.95
FNB-47xh (NMH)	7.2v	1800mAh	\$49.95
FNB-41xh (5w NMH)	9.6v	1000mAh	\$49.95
For YAESU FT-51R / 41R / 11R:			
FNB-38 pack (5w)	9.6v	700mAh	\$39.95
For YAESU FT-530 / 416 / 816 / 76 / 26:			
FNB-26 pack (NMH)	7.2v	1500mAh	\$32.95
FNB-27S (5w NMH)	12.0v	1000mAh	\$45.95
For YAESU FT-411 / 470 / 73 / 33 / 23:			
FNB-11 pack (5w)	12.0v	600mAh	\$24.95
FBA-10 6-Cell AA case			\$14.95
Packs for ALINCO DJ-580 / 582 / 180 radios:			
EBP-20ns pack	7.2v	1500mAh	\$29.95
EBP-22nh pk (5w)	12.0v	1000mAh	\$36.95
EDH-11 6-Cell AA case			\$14.95
For ICOM IC-21A / T22-42A / W31-32A / T7A:			
BP-180xh pk (NMH)	7.2v	1000mAh	\$39.95
BP-173 pack (5w)	9.6v	700mAh	\$49.95
For ICOM IC-W21A / 2GXAT / V21AT: (Black or Grey)			
BP-132s (5w NMH)	12.0v	1500mAh	\$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:			
BP-83 pack	7.2v	600mAh	\$23.95
For ICOM 02AT etc & Radio Shack HTX-202 / 404:			
BP-8h pack	8.4v	1400mAh	\$32.95
BP-202s pack (HTX-202)	7.2v	1400mAh	\$29.95
For KENWOOD TH-79A / 42A / 22A:			
PB-32xh pack (NMH)	6.0v	1000mAh	\$29.95
PB-34xh pack (5w NMH)	9.6v	1000mAh	\$39.95
For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:			
PB-13 (original size)	7.2v	700mAh	\$26.95
PB-6x (NMH w/cho plug)	7.2v	1200mAh	\$34.95

Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express
Call 608-831-3443 / Fax 608-831-1082
Mr. NiCd - E. H. Yost & Company
 2211-D Parview Road, Middleton, WI 53562
CALL OR WRITE FOR OUR FREE CATALOG!
 Cellular / Laptop / Videocam / Commercial / Aviation packs too!
 E-mail: ehyost@midplains.net



GPS Design Kit — \$379

The design kit SGM5600KS is a complete and immediately usable means of evaluating the SIGEM GPS receiver module and high performance GPS antenna, which are included in the kit. Software running on the GPS receiver module communicates to a user supplied computer via NMEA 0183 formatted messages. Advanced PC software provides map integration and a demonstration of tracking. Provision has been made for DGPS inputs.

SIGEM Inc.
50 Hines Road
Kanata, Ontario
Canada K2K 2M5
Tel: (613) 271-1601 (Can)
(541) 923-3733 (USA)
Fax: (613) 271-1996

SIGEM

Web: www.sigem.ca
Email: info@sigem.ca

PCBs

PER SQIN
\$100.00 SETUP
WE SPECIALIZE IN SINGLE SIDED, 1 OZ, PC75

9¢

PCB LAYOUT

PER COMPONENT PIN \$100.00 MINIMUM

59¢

ENGINEERING DIAGRAMS


PER COMPONENT PIN \$100.00 MINIMUM

39¢

V&V MACH. & EQUIP., INC. (HOUSTON, TX OFFICE)
PH (281) 397-8101 FAX (281) 397-6220
MARKETING TECH. S.A. (MEXICO/PLANT)
PH 011 (525) 361-3351 FAX 011 (525) 361-5996

SBC2000-074

RS-232

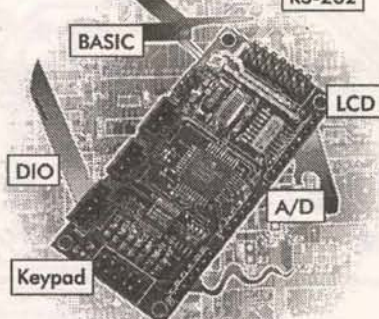


Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800
www.sbc2000.com

Vesta Technology, Inc.

2.4 GHz Wireless Transmitter & Receiver

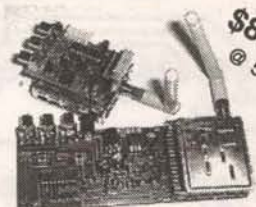

\$89/pair
@ 50 pcs

2.4 GHz ~ 2.48 GHz User Selectable
Over 700' Range and 4 Chl Auto-scan
NTSC, PAL, Composite video B/W or Color
2 Audio Inputs may be used for digital data
Customizations including battery packs
and Special Frequencies

Matco Inc.

(800)440-0299 or (800)719-9605
www.mat-co.com

Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.



RING-IT! TELCO SIMULATOR
• Single Line (two RJ-11 Jacks)
• LED Display
• DTMF Operation
• Automatic Ring-up Mode
• \$325 (\$149 kit available)

PARTY-LINE TELCO SIMULATOR

• Six Extensions
• Caller-ID (Name/Nbr)
• Distinctive Ringing
• \$425 (\$199.95 kit avail)



Digital Products
COMPANY

134 Windstar Circle
Folsom, CA 95630 USA
Tel: 916-985-7219
Fax: 916-985-8460

<http://www.digitalproductsco.com>

LCD Terminal \$99



Re-Programmable
LCD 240 x 64 EL Backlit
RS-232 Port
1200 Baud Modem
8051 Compatible Microcontroller
192k Low Power Static Memory
Infrared Transmitter
Nicol Battery Pack
QWERTY Keyboard
FM SCA Data Receiver

Junkware.com

<http://www.junkware.com>

PC BOARD SERVICES

PCB Design Layout

Thru Hole

SMT

Multilayer

PCB FABRICATION

In-house Prototypes

Single and Double Side

Plate Thru Hole

ASSEMBLY

Thru Hole

Small Project Specialists

Serving Engineers and Hobbyists
for 16 Years

MIDLAND TECHNOLOGIES

800-726-8871 Voice

406-586-0300 FAX

This Could Be

YOUR AD

Read by thousands of
electronics consumers.

For information, write or call:
Nuts & Volts Magazine
430 Princeland Ct., Corona, CA 91719

(909) 371-8497

FAX (909) 371-3052

GPS Units

Trimble Placer 400 \$79.95

6 Chan. & Magnet Mt. Ant.

Trimble SVEeSix \$89.95

6 Chan w/ Diff. & Mag. Mt. Ant.

Rockwell MicroTracker LP \$89.95

5 Chan., Module w / Differential

& Mag. Mt. Ant.

ACE GPS Mag. Mt. Antenna \$54.95

Call for Software Packages

Communications Surplus

713-526-8000 or 1-877-878-6GPS(477)
lshaefer@flash.net Fax to 713-522-6309

New!

ActiveWire™USB Simple USB Interface



- Internet Browser Script-able
- 24 MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel I/O
- Expandable add-on boards
- New firmware and scripts available from website

\$59 plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph(650) 493-8700 fx(650) 493-2200

QUALITY KITS

#1 Source for Electronic Kits

Great selection of Hi-Fi AUDIO Kits,
PSUs, Transmitters, Oscilloscopes,
PIC Programmers, and much more.

Toll Free Order Line:

1-888-464-5487

Secure On-Line Ordering

www.qkits.com

Call 613-544-6333 for free catalog

North American Kit Distributor

49 McMichael St., Kingston, ON

K7M 1M8, CANADA

Aviation Components Corp.

28 Hunting Hills Drive
Landenberg, PA 19350

We buy and sell:

- Relays
- Switches
- RF Components
- All MIL-SPEC
- Electro-Mechanical Devices
- Resistors
- Circuit Breakers
- Semiconductors
- ICs

Home Office (sales)

610-255-3761 • FAX 610-255-3548

Morrisville Office (purchasing)

215-295-3507 • FAX 215-295-8633


E-Mail: aviationcomp@earthlink.net

For more info check out our website:

<http://home.earthlink.net/~aviationcomp/>


Program PICs in Basic Complete kit to get started!

\$115.95

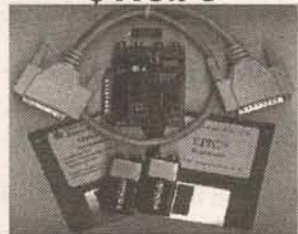

Includes:
Compiler, Programmer, PIC, Cable & Batteries

ORDER

 

Electronic Products

(248) 515-4264 Fax: (413) 825-0377

www.elproducts.com

NEED BATTERIES!!
batterystore.com

TNR Technical, Inc.
301 Central Park Drive
Sanford, FL 32771
1-800-346-0601

Plans-Kits Unlimited

PLANS KITS PARTS OVER 120,000 PLANS

LASERS MASERS EMP TESLA
RAIL & COIL GUNS JAMMERS
ULTRASONICS HIGH VOLTAGE
PLASMA & ION GUNS HERF
MIND CONTROL NUCLEAR
PHREAKING BIO-ELECTRONIC

IF WE DON'T HAVE IT, WE'LL GET IT.

<http://www.plans-kits.com>

AD SPECIAL!!! RUBY & SAPPHIRE SURPLUS RODS
FOR HIGH POWER CUTTING LASERS. 1/8" D X 3" L.
FLAT ENDS, MATTE FINISHED, SURPLUS MILITARY.
\$12.00+\$15/H EA. CHECKS, CASH, MONEY ORDER.

PLANS-KITS UNLIMITED: (BASE FOR CATALOG)
1839-D WEST VISTA WAY #515, VISTA CA 92083

GREAT
FOR TEST FIXTURE
BUILDING



LAB-1
(1.5" x 2.0" x 0.75")

FREE!

PHONE, FAX, WRITE
OR E-MAIL WITH YOUR
MAILING ADDRESS
MUST MENTION
OFFER "LAB 199"

PRE-PUNCHED END PANELS
ALSO AVAILABLE
8 BOX SIZES
25 PRE-PUNCHED
END PANELS

ALSO IN STOCK AT:
JENSEN TOOLS: 800-436-1194
MCM ELECTRONICS: 800-543-4330
TECH AMERICA: 800-442-7271

ALL ALUMINUM CONSTRUCTION LOW COST
OFFER GOOD ONLY IN THE 48 STATES, ENDS DECEMBER 30, 1999. LIMIT ONE
REQUEST PER CUSTOMER. MAILED 1ST CLASS, ALLOW 1-2 WEEKS FOR DELIVERY



ORDERS 800-634-3457 • FAX 800-551-2749
OFFICE 702-565-3400 • FAX 702-565-4828
www.sescom.com • info@sescom.com

SES.COM, INC. 2100 WARD DR. HENDERSON, NV 89015
SES.COM, INC. is not responsible for inadvertent typographical errors
and prices and specifications are subject to change without notice.

CIRCUIT CHEM, INC.

PROTOTYPE TO PRODUCTION

S/SIDED: 5-days, 10 Pcs.	\$275.00
D/SIDED: 5-days, 5 Pcs.	\$300.00
D/SIDED: 5-days, 10 Pcs.	\$350.00
4-LAYERS: 5-days, 5 Pcs.	\$750.00
4-LAYERS: 7-days, 10 Pcs.	\$850.00
6-LAYERS: 5-days, 5 Pcs.	\$950.00
6-LAYERS: 7-days, 10 Pcs.	\$1,175.00
(Up to 30 sq. inch each, includes Tooling)	

SERVICES - UL Approved


SMOBC, LP1 mask & Legend
Photoplotting, Electrical Testing
Thru hole/SMT, Gold/Nickel Plating
Routing and Scored Panel, Instant Quotes

PH: (888) 427-2920, Fax (847) 427-1949

E-Mail: cir1920@aol.com

LOWEST COST & FAST DELIVERY

VIDEO PRODUCTS

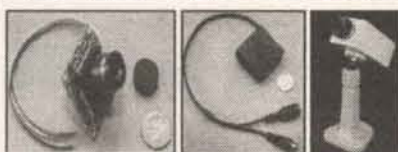

CNL-100 \$49 **BX-120-P \$59** **SX-800 \$79**

- 430 TV Lines Resolution
- 9-14 VDC Operation
- Infrared Sensitive
- SX-800 has Audio Output
- A-300 Camera Enclosure also available

MATCO, INC.

Schaumburg, IL
1-800-719-9605 • 1-847-619-0852 FAX
E-Mail - info@mat-co.com
Website - www.mat-co.com

10&14 Hour Telephone

Recorders Starting at \$69



Times based on a 180 tape
14 Hour \$89+S/H
120 Tape included!
Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!
Printed catalog \$3 (free with order)

Visit our Online Catalog
www.mscelectronics.com

MSC Electronics

PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925

No Checks • US & Canada Only



EPS

EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
2732A	27C4096	28F020	8755
27C32	574000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C622
27C512-90	27C010	8744	GAL16V8
			GAL22V10
			MEMORY
			D-RAMS
			SIMM

STATIC RAM

HM628128 8255

62256 8254

6264 80C31

6116

- Many more parts in stock
- All major brands
- All guaranteed

E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822

WE BUY EXCESS INVENTORY



FREE SAMPLE COPY!

ANTIQUE RADIO CLASSIFIED

Antique Radio's Leading Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)

6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23

Carlisle, MA 01741

Call: 978-371-0512 - Fax: 978-371-7129

Web: www.antiqueradio.com

TOGGLE SWITCHES - All sizes and types Commercial Quality

FULL SIZE TOGGLE SW. 1/2" DIA.				PRICE
TYPE	MODEL	RATING	LEAD	100-1000
SPST	D125	6A/125V	6" wire	.77 .67
SPST	D128	4A/125V	Solder	.57 .47
DPDT	D126	5A/125V	Solder	.77 .67
DPDT	D127	10A/125V	Solder	1.17 1.06
on-off-on				
5A/250V				
Screw				
MINIATURE TOGGLE SWITCHES 1/4" DIA.				
SPST	D131	6A/125V	Solder	.57 .47
SPDT	D132	6A/125V	Solder	.61 .51
SPDT	D129	6A/125V	Solder	.77 .67
mom-off-mom				
SPDT	D134	3A/250V	Solder	.77 .67
on-off-on				
SPDT	D133	6A/125V	Solder	.77 .67
DPDT	D135	6A/125V	Solder	.92 .82
on-off-on				
DPDT	D130	6A/125V	Solder	.92 .82
mom-off-mom				
3A/250V				
MOMENTARY PUSHBUTTON SWITCHES 1/4" DIA.				
SPST Nor Open DM1	3A/125V	Solder	.32	.27
SPST Nor Close DM2	3A/125V	Solder	.32	.27
ANY ORDERS LESS THAN 100, ADD 20¢ EACH				
LEDs Red, Yellow, Green — \$12.00/100 \$10.00/1,000				

DEMAR ELECTRONICS

P.O. Box 7215, Algonquin, IL 60102

Toll Free 877-655-6433

Fax 847-854-4434

CABLE BOXES

CUT MANUFACTURING COST!
WE ACCEPT SMALL ORDERS TOO.


SHEET METAL

20 GAUGE

SILK SCREEN

PRINTED

WITH YOUR CO. NAME

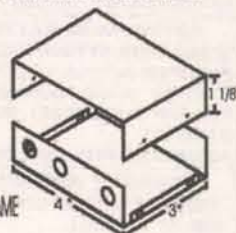

ALSO PCB, SMT, PROTOTYPES, ASSEMBLY, PLASTIC MOLDS, INJECTION MOLDING.

USA Office: V&V Mach. & Equipment, Inc.

Ph: (281) 397-8101, Fax: (281) 397-6220.

Mexico Plant: Marketing Tech.

Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

COVERT CATALOG2000

BRAND NEW!

The Latest, Up-to-date, Hands-on Supplier and Source Guide for:

- Electronic surveillance equipment
- Covert video cameras and transmitters
- Counter measures gear
- Entry supplies
- Electronic tracking systems
- Computer surveillance and remote viewing

Equipment, exact addresses and ordering info from 15 countries!! 220 pages - \$39.95

Il 3555 S El Camino Real, San Mateo, CA 94403

Phone 650-513-5549 • fax 650-728-0525 or

www.intelligence.to (no "dot com")

ASSEMBLY & ENGINEERING

Producible designs since 1970

Contract Engineering

Embedded Microprocessors
PCB Layout and Packaging Design
Analog Including RF to 1 GHz
Instrumentation
A/D and D/A

Contract Assembly

High-Speed Fuji Surface Mount
Through hole
Turn-key or Kit
Run sizes one through thousands
Test and burn-in available

Bilocon Corp.

800-736-5927

425-353-2276

www.bilocon.com

Stereo Microscopes for Large PC boards



- 9 in. arm for Large boards
- 10X & 30X
- Dust cover
- Eye guards
- 5 year warranty

ST 231P - \$395.00



jlittle@netwizards.

3580 Haven Ave. Redwood City, CA 94063

650/367-8320 Fax 365-5845

CONTROL • MEASURE • INPUT


MODEL 40-\$109

- RS-232 Interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports



MODEL 100-\$279

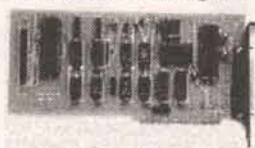- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK

PRAIRIE DU SAC, WI 53578

TEL: (608) 643-8599 • FAX: (608) 643-6754

dmdsystems.com

[electronic test & mfg]

[test]

[measurement]

[rf/microwave]

[specialized equipment]

[computers]



DMD SYSTEMS RECOVERY, INC.

602 305-8485

fax 602 305 8490 • email info@dmdsystems.com

ASTRO TOO

Surplus/Electronics Equipment

Web Site: AstroToo.Com

E-Mail: Astro@AstroToo.Com

2854 Sarno Road
Melbourne, FL 32935

(407) 253-3371
Fax: (407) 727-1546

When visiting Central Florida,
come see us!
I-95, Exit 72

SOLAR ELECTRICITY

All manner of photovoltaics and solar electronics available here.

www.planetarypower.com

120 Watts Panel
\$589

64 Watts Panel
\$319

P.V. Power Corp.

Inverters, Controllers, Racks,
Meters, Shunts, Fans, Pumps

(877) SOLAR PV

softwarecloseouts.com

DOS - Windows - Win95
UNIX - MAC - Upgrades
Secure on-line ordering

softwarecloseouts.com

Corel Office 7 \$29
Norton Anti-Virus 2 \$5
Windows WGP 3.11 \$39
Office 4.2upg \$39

Up to 85% off titles by Symantec!

softwarecloseouts.com

New Arrivals Weekly!
Hard-to-find a specialty ...
We buy your surplus software.

softwarecloseouts.com

Doctor GB card / Xchanger for Professional Game Developers

Doctor GB card is a Gameboy compatible ROM emulator FlashROM cartridge. It has built-in SRAM and supports MBC1, MBC2 and MBC5 standard.



GameBoy

The advanced design of the Doctor GB card and Doctor GB Xchanger makes it easy for programmers and coders to burn a ROM file to the Doctor GB card. To transfer data into the Doctor GB card, the only requirements are the Doctor GB Xchanger, PC and our customized software. No need for expensive and difficult to use EEPROM burners.

www.UpstateGames.com

E-mail: sales@upstategames.com Fax: (716) 442-7223

P.O. Box 40184 Rochester, NY 14604 U.S.A.

Power Quality Inc. 800-255-5545
Fax: 520-344-8847

Heavy Duty Surge Suppressor
Plug Strips, 6 outlet, circuit breaker,
Case of 25 in individual boxes...\$50/case

HP Power Supplies, HP6260B
current is 0-50A,\$100

UPS, 250va to 3 kva, functional and
nonfunctionalPlease call

Power Conditioners, Onac, TLC,
Teal, Sola, various sizesPlease call

BMI, Dranetz, and RPM
Power Quality Monitors Please call

www.powerqualityinc.com

SURPLUS SALE

1,000,000 WALL TRANSFORMERS



3VDC/100MA CX099 \$0.75
6VDC/100MA CS039 \$1.45
9VDC/100MA CR314 \$1.45
12VDC/200MA CS033 \$0.99
13.5VAC/400MA... CR574 \$1.29
24VDC/500MA CR174 \$3.40

Min 1000/type - Call for other types

SURPLUS TRADERS
PO Box 276,
Albany, VT 05440
Tel: (01) 514-739-9328
Fax: (01) 514-345-8303
<http://www.73.com/vt>

FREE CATALOG!

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAM'S DATA I/O ICE TECHNOLOGY HILO
SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



FROM MAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX
629 ICE TECH MICROV 795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUPA/R
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUPA/R
509 EETOOLS MEGAMAX4 49 EPROM 1G TO 512K
369 XELTEK SUPERPRO II 69 EPROM 1G TO 1MEG
409 XELTEK SUPERPRO II P 99 EPROM 4G TO 1MEG
249 XELTEK SUPERPRO L 199 EPROM 16G TO 1 MEG
165 XELTEK ROMMASTER II 89 EPROM 1G TO 8MEG
479 MOD-MCT-EMUPA 129 EPROM 4G TO 8MEG
739 STAG ORBIT-32 250 EPROM 8G TO 8MEG

LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

General Device Instruments
Sales 916-393-1655 Fax 916-392-4949
Web www.generaldevice.com E-Mail icdevice@best.com

Electronics Kits connect directly to your stamp or microprocessor




MicroClock II kit (assembled)
▲ Real Time Clock with backup
▲ keeps accurate time and date
▲ \$24.95+ ship/handling

RHT7 kit (assembled)
▲ Relative Humidity &
▲ Temperature Sensor
▲ \$64.95+ ship/handling

Visit our Webpage for more! See the AT6 Digital Inclinometer kit!

Technology Electronics, Ltd.
Phone: 937-438-4683 Fax: 937-438-5934
www.technologykit.com kits@technologykit.com

Serial Port Problems ???

No heavy, aging serial protocol analyzer available? Use **Serial** to turn your PC into a test tool for asynchronous serial communications. **Serial** uses your PC serial ports to capture data, control and time stamps to give you what's needed to develop or debug your serial communications.

- Captures Data & Control lines
- Contextual Help
- Autobaud Detect
- Block Transmit
- Millisecond Timing
- Trigger Strings
- Extensive Manual
- Full Duplex Monitoring

Serial with manual US\$99.00
Full Duplex monitor cable US\$40.00

Allison Technology Corporation
2006 Finney Valley Rd., Rosenberg, TX 77471
800-980-9806 or 281-239-8500, Fax: 281-239-8006
<http://www.atcweb.com> atc@accesscomm.net

JUNE SPECIAL SAVE \$10.00

SHIELDED LOOP RECEIVER
30M, 40M KITS W/ ANTENNA.
VERY SENSITIVE. HAS HIGH IMMUNITY TO QRN & LOCAL AM BROADCAST.. \$92.50 PP

12/14V PULSE BATTERY TESTER
(LEAD ACID). ATTACH THE BATTERY & PUSH THE BUTTON TO DETERMINE IF THE BATTERY NEEDS RECHARGING. A MUST FOR THE GLIDER SET, BOATERS, ETC.
BASIC KIT \$55.50 PP
ASSEMBLED WITH ENCLOSURE \$106.50 PP

MARCONI ANTENNA 700W 50 Ω
THE BEST "LITTLE" LOW BAND ANTENNA
80M: 67' OVERALL \$47.45 PP
160M: 130' OVERALL \$54.45 PP
CODE PRACTICE OSCILLATOR... \$23.45 PP

SEND FOR FREE CATALOG
1-800 JADE PRO (523-3776)
www.jadeprod.com/
email: jadepro@jadeprod.com
JADE PRODUCTS E. HAMPSTEAD NH 03826-0368

CABLE SECRETS!!!

This ad has been **CENSORED!**

Want to know why?
Visit us at <http://www.worldwyde.com>

- Find out how "Test" Devices work
- Installation of "Test" Devices
- Descrambling Methods Explained
- Detailed Construction of "Test" Devices

Includes plans and source code

Complete source code \$79.95
Code for individual boxes \$29.95

DSS SECRETS - Vol. 2

Instructions on programming DSS access cards. This is the most current information on the market! Includes software, plans, and hardware sources. Book & CD-ROM.
Get this before they censor it too!!
DSS Secrets Vol. 2 \$49.95

VISA • MasterCard • American Express
To order, call Worldwyde • 1-800-773-6698
21365 Randall Street • Farmington Hills, MI 48336
Visit us on the web at www.worldwyde.com

Build Your Electronics Library At A Price You Can Afford!

Check out the **HOT DEALS** at the **Nuts & Volts Bookstore!!**
(See ad page 48.)

As a paid subscriber, you'll get 10% off the listed price!!

TV 85 PJ & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE
VOICE 1-800-473-0506
FAX 1-800-488-0525

FOSS WAREHOUSE DISTRIBUTORS
285 Schenck St.
N. Tonawanda, NY 14120
www.fossw.com

CUSTOM PLASTIC PARTS

- MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.
- MOLD DESIGN AND BUILDING.
- PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.
- VERY COMPETITIVE ON HIGH LABOR PARTS.




We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA. Office: V&V Mach. And Equip. Inc.
Tel. (218) 397-8101, Fax. (218) 397-8220.
Please send blue prints or samples to:
Marketing Tech. S.A. • Alamo 93, 4. Piso • Sta. Monica, Tlal. • Eco. De Mexico 54040 • Tel. 011 (525) 38* - 3351.
Fax. 011 (525) 361-5996. AT "N" VICTOR M. MENDOZA
e-mail: marktech@infosel.net.mx

PCB's in Minutes From LaserPrint!*

8 1/2" x 11" Sheets

* Or Photocopier Use household iron to apply.

Press n Peel

PnP BLUE or PnP WET

For High Precision Professional PCB Layouts

1. LaserPrint
2. Iron-On
3. Soak-Off w/ Water
4. Etch

Adds an Extra Layer of Resist for Super Fine Lines on Std. Clad Bds

20Sh\$30/40Sh\$50/100Sh\$100 Blue/Wet (No Mix)
Sample Pack 5 Shets Blue + 5 Shets Wet \$20
VISA/MC/PO/CH/MO \$4.58 - 2nd Day Mail

Techniks Inc. P.O. Box 463 Ringoes NJ 08551 (908)788-8249
100% Money Back Guarantee-Dealer Inquiries Invited

Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to 4,000 feet, at up to 1 MEGA-BPS, full or half duplex, up to 32 units on one serial link, with 31 jumper options for flexible configuration, LED indicators.

COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

R.E. SMITH
(513) 874-4796
4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011
www.rs485.com

Continued from page 10

REQUESTED HIGH "TEC" REFRIGERATOR SOURCES FOR THE TEC DEVICE

After receiving several inquiries about where author Kenton Chun purchased his TEC device from for the August '99 article, we asked Kenton to put together a list of sources.

Dear Nuts & Volts:

Here are some surplus dealers known to carry Peltier modules. If you need one or two modules to experiment with — these outfits may be easier to buy them from than from the manufacturers. But don't be surprised if you can buy new modules from a manufacturer for the same or even lower prices than from the surplus outfits.

All Electronics, 1-800-826-5432, FAX 818-781-2653. E-Mail: allcorp@allcorp.com, Web: <http://www.allcorp.com>. Fall 1996 catalog 596 shows two 127-couple devices. One is 1.18" square for \$17.00. The other is 1.57" square for \$26.00. No minimum order. Takes charge cards.

Alltronics, 408-943-9773, FAX 408-943-9776. E-Mail: ejohnson@alltronics.com, Web: <http://www.alltronics.com>. Catalog 961 shows a 1.1875" square unit for \$24.95 and a 1.56" unit for \$34.95. Specs are not listed.

American Science & Surplus, Skokie, IL; 847-982-0870, FAX 1-800-934-0722. Catalog 100 dated 1/97 shows two units, 3-12VDC, #22627 1.17" sq. x 0.12" thick \$25.00, #89143 1.56" sq. x 0.15" thick \$35.00.

Gateway Electronics, 8123 Page Blvd., St. Louis, MO 63130; 1-800-669-5810, 314-427-6116, FAX 314-427-3147 (10/97). Web:

<http://www.gatewayelec.com>. Web site shows 127-couple modules, documentation included. Small module \$20.00 (approximately 1.17" x 1.17" x .12"). Large module \$29.50 (approximately 1.56" x 1.56" x .15").

Javanco, Nashville, TN; 615-244-4444, FAX 615-244-4446. E-Mail: javanco@javanco.com. Web: <http://www.javanco.com>. Web site catalog lists a 71-couple unit, 8V, 3.4A, 59C Temp differential, 18W, for \$16.95.

Marlin P. Jones, Lake Park, FL; 1-800-652-6733. Web: <http://www.mpja.com>. Catalog 1996 shows a 71-couple, 8V, 3.4A unit for \$16.95.

Shreve Systems, 1200 Marshall St., Shreveport, LA 71101. 1-800-227-3971, Fax 318-424-9771. Web: www.shrevesystems.com. 1-3/16" x 1-3/16", \$10.00 each or three for \$25.00.

Kenton Chun

Whether you play with robots, model planes, or boats, there are motors inside which supply the muscles and habits that make them go. Choosing the right motor for your project, though, can be a daunting experience. Motors that provide locomotion aren't the same as those that move robotic arms or pilot a plane.

Basically, controller motors come in three flavors: servos, steppers, and encoders.

Last month, I did an in-depth study of servos. In that article, you discovered that servos are actuators — motors that move robotic elbows and grippers — whereas stepper

electromagnet, where it stops. By properly sequencing the polarity of the electromagnets, we can make the rotor spin — one step at a time. Hence the name, stepper motor. The speed at which this sequencing takes place controls the speed of the rotor. The stepper motor type — bipolar or unipolar — is determined by the way the coils are wired together.

Before the advent of high-power ICs, the unipolar stepper motor almost exclusively dominated the stepper motor market because of its simpler controller electronics. Today, that scenario has changed, and bipolar stepper motors are all the rage for several reasons. That's not to say that unipolar steppers are out of the running, because they're not. They

are every bit as popular as ever. But bipolar motors have several advantages over unipolar, and are gaining ground. Table 1 shows how they compare.

Bipolar Stepper Motors

Bipolar stepper motors are so named because of the way the electromagnetic stator polarities are sequenced. The stators are wired according to Figure 2, where coils A and B are in series, and coils C and D are in series.

Basically, there are three ways to spin the rotor: One-Phase-On (full-wave), two phase, and half step. All three modes use the wiring configuration shown in Figure 2.

Which one works best in your robotic or R/C project? Here's everything you need to know. This month: Bipolar stepper motors.

Full-Wave Step

In the One-Phase-On (full-wave)

Servos, Steppers, and Optical Encoders — Part 2

by TJ Byers

motors are free-spinning, like car engines. This month, we look at bipolar stepper motors — the movers and shakers of robotics and R/C.

Stepper Motors

Stepper motors are often used in robotics and R/C models to provide locomotion for the device. Stepper motors are preferred over standard hobby motors because they can be precisely controlled. The speed and torque of a hobby motor is directly proportional to the applied voltage — the higher the voltage, the faster it spins and the more power it can deliver.

Stepper motors, on the other hand, are digitally controlled. The speed and power is proportional to a digital input code. Stepper motors are used in applications where precise torque and motor speed control are required, as in:

- Robotics locomotion
- R/C aircraft/boat propeller speed
- X/Y positioning
- Tool feed for lathe and milling machines
- Disk drives

There are two basic types of stepper motors: permanent magnet and variable reluctance. Permanent magnet motors are further divided into bipolar and unipolar types. Both permanent-magnet motor types consist of a rotating magnet, attached to a rotor shaft, surrounded by a circle of stator coils (Figure 1).

When a coil is energized by running current through it, it creates an electromagnet in that particular stator pole. This causes the permanent magnet to spin and align with the

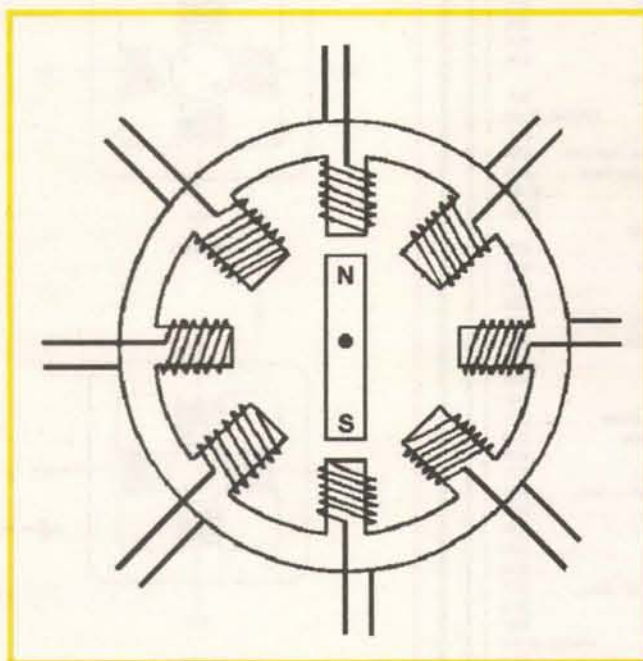


Figure 1. Permanent-magnet stepper motors consist of a rotating magnet surrounded by a circle of stator coils.

mode, current initially flows through coils A and B, which are wound in such a way that the top stator is polarized south and the bottom stator is polarized north. The rotor magnet aligns itself with the south pole up and the north pole down (Figure 3). Coils C and D are disconnected — or off. This is Phase 1.

In the next phase (Phase 2), A and B are turned off, and C and D are energized to create a north pole on the right and a south pole on the left, causing the rotor magnet to rotate clockwise by 90 degrees.


Phase 3: C and D are turned off, and voltage is applied to the A and B coils — in the opposite polarity of Phase 1. This forces the magnet to rotate another 90 degrees clockwise. Notice that the rotor magnet is now facing the opposite direction of Phase 1. The next, and final step (Phase 4), is to disconnect A and B, and energize C and D with an opposite voltage. The sequence then repeats itself with Phase 1.

Two-Phase Step

In the Two-Phase mode (sometimes called the Normal mode), both the AB and CD coils are energized at the same time. While the number of steps are the same as for one-phase-on — four per rotation — the angle of the rotor magnet is at the corners of the compass rather than the up-down orientation outlined above. This mode produces the highest torque — obviously, because you have twice the current flowing through the motor. The sequence is as follows (Figure 4).

Positive voltage is applied to both the AB and CD coils, which polarizes both of their upper-right stators north. Without a clear loca-

Figure 2. In bipolar stepper motors, the stators are wired so that coils A and B are in series, and coils C and D are in series.

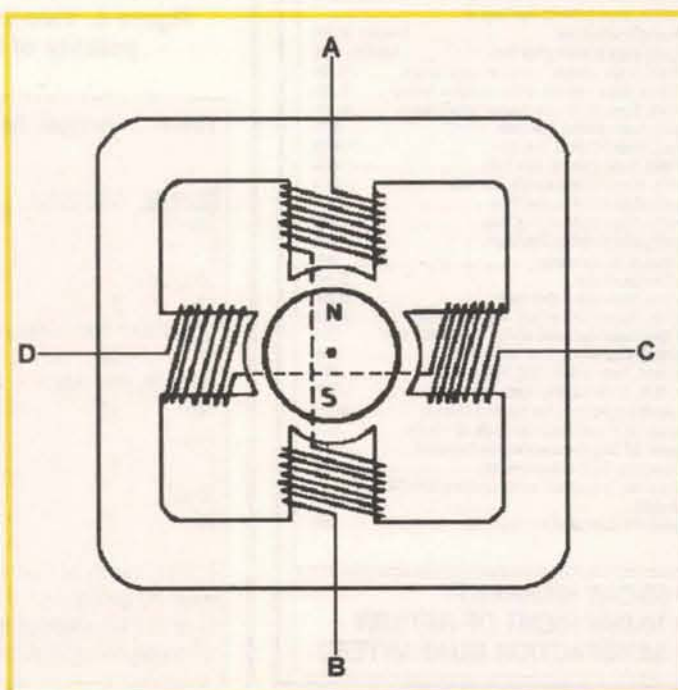

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
QUICKLY ... AT REASONABLE PRICES.

EIP 545, Microwave Counter 18GHz.....	\$500
EIP 931, Microwave Source, .01-18GHz, Opt. 9320.....	\$4,500
Fluke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fluke 3330B, Constant Current/Voltage Calibrator.....	\$325
Fluke 5100B, Multifunction Calibrator, Opt. 03/05.....	\$2,800
Fluke 5100B, Multifunction Calibrator.....	\$2,700
Fluke 5200A, Programmable AC Calibrator.....	\$1,000
Fluke 5215A, Precision Power Amp.....	\$800
Fluke 6070A, Synthesized RF Signal Generator.....	\$1,400
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8520A, DMM 5-1/2 Digit.....	\$275
Fluke 9010A, Micro System Troubleshooter.....	\$375
General Radio 1658, Digibridge.....	\$475
Gigatronix 6061A, Synthesized Signal Generator.....	\$2,200
HP 141T, Spectrum Analyzer Mainframe.....	\$475
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,000
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8556A, 20Hz-300KHz.....	\$1,100
HP 141T, Spectrum Analyzer w/8552B/8556A, 1KHz-1.2GHz.....	\$1,700
HP 141T, Spectrum Analyzer w/8552B/8556A, 10MHz-18GHz.....	\$1,900
HP 214A, Pulse Generator, .08V-100V.....	\$200
HP 334A, Distortion Analyzer.....	\$275
HP 339A, Distortion Analyzer w/Low Distortion Oscillator.....	\$950
HP 400EL, AC Voltmeter, 10Hz-10MHz.....	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V.....	\$175

HP 6294A, Power Supply, 0-60V @ 1A (metered).....	\$275
New in box w/manual.....	\$275
HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$175
HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$275
HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$400
HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator.....	\$1,000
HP 8180A, Programmable Pulse Generator, 50MHz, Opt. 001.....	\$850
HP 8180A, Programmable Pulse Generator, 50MHz, Opt. 001/020.....	\$1,000
HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$950
HP 8443A, Tracking Generator, 1KHz-110MHz.....	\$275
HP 8445B, Auto Preset, 1.8-18GHz.....	\$275
HP 8445B, Auto Preset, 1.8-18GHz Opt. 002/003.....	\$375
HP 8601A, Sweeper Generator, 1-110MHz.....	\$400
HP 8614A, Signal Generator, 800-2400MHz, AM/FM Leveled.....	\$300
HP 8616A, Signal Generator UHF, 1.8-4.5GHz, +10-126dB, AM/FM.....	\$300
HP 8620C, Frame w/8622B Sweeper .01-2.4GHz.....	\$1,150
HP 8624D, RF Plug-in, 5.9-9.0GHz.....	\$225
HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003.....	\$1,800
HP 8640B, Signal Generator, 5-512MHz, Opt. 001 or 003.....	\$700
HP 8656A, Synthesized Signal Generator, 100KHz-990MHz.....	\$1,400
HP 8743A, Reflection Test Set, 2-12.4GHz.....	\$200
HP 8901A, Modulation Analyzer Opt. 010.....	\$875
HP 58303A, D/A Converter.....	\$125
Keppco ATE15-50M, Power Supply, 0-15V @ 50A (metered).....	\$500
Keppco JQE 36-15MVPT, Power Supply, 0-36 @ 15A (metered).....	\$275
Keppco JQE 36-3MVPT, Power Supply, 0-36 @ 3A (metered).....	\$175
Krohn-Hite 3202R, Dual Channel Tunable Filter, 20Hz-2MHz, High Pass, Low Pass Band Reject.....	\$200
National Instruments GPIB-100A, Bus Extender.....	\$175
PG506A, Calibration Generator Plug-in.....	\$500
Power Designs 2K-10 HV PS 1-2000V@10MA.....	\$375
Racal Dana 1991, Counter/Timer, 2 Channel.....	\$275
Racal Dana 1992, Counter/Timer, 1GHz.....	\$375
Rockland 1022F, Dual HiLo Filter.....	\$125
Rockland 5100, Synthesizer, DC-2MHz, .001 Hz Resolution.....	\$325
Sencore CM2000, Computer Analyzer.....	SPECIAL \$1,400
Sencore LC102, Capacitor/Inductor Analyzer.....	\$950
Sencore SC61, Scope (100MHz) w/New Probes, Dual Trace.....	\$750
Sencore SC61, Scope (100MHz) w/Probes, Dual Trace.....	\$400
Sencore TVA92, TV Video Analyzer.....	\$1,100
Sencore VG91, Universal Video Generator.....	\$1,200
Sorenson DCR-80-5A, Power Supply, 80V @ 5A (metered).....	\$375
Tek 7514, Plug-in Sampling Plug-in, DC-1GHz.....	\$425
Tek AM501, Plug-in Op Amp.....	\$175
Tek AM502, Plug-in Differential Amp.....	\$225
Tek DC503, Plug-in Counter Universal, 100MHz.....	\$150
Tek DC509, Plug-in Counter, 135MHz, UNUSED.....	\$375
Tek DM502, Plug-in DMM.....	\$125
Tek DM502A, Plug-in DMM.....	\$125
Tek DM502, Plug-in DMM, 4-1/2 Digit.....	\$150
Tek FG504, Plug-in Function Generator, .001-40MHz.....	\$375
Tek PG501, Plug-in Pulse Generator, 5Hz-50MHz.....	\$175
Tek PS501-1, Plug-in Power Supply.....	\$150
Tek PS503A, Plug-in Power Supply Triple.....	\$175
Tek OIG-502, Plug-in Optical Impulse Generator (unused).....	\$500
Tek T922, Scope (15MHz), Dual Trace, nice.....	\$175
Tek TMS503, Power Module, 3 Slot.....	\$125
Tek TMS504, Power Module, 4 Slot.....	\$150
Tek TMS506, Power Module, 6 Slot.....	\$200
Tek TR503, Plug-in Tracking Generator, 100KHz-1.8GHz.....	\$575
Tek 2213, Scope (60MHz), Dual Trace.....	\$375
Tek 2215, Scope (60MHz) Dual Trace.....	\$450
Tek 2230, Scope (100MHz) Digital Storage.....	SPECIAL \$1,800
Tek 2235, Scope (100MHz) Dual Trace.....	\$650
Tek 2236, Scope (100MHz) w/Counter/Timer/DMM.....	\$850
Tek 2246, Scope (100MHz) 4-Channel Cursor RO.....	SPECIAL \$1,200
Tek 2247A, Scope (100MHz) Dual Trace w/Counter/Timer/Volmeter.....	SPECIAL \$1,400
Tek 2336, Scope (100MHz) Dual Trace.....	SPECIAL \$625
Tek 2445, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,100
Tek 2445A, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 2465, Scope (300MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 453, Scope (60MHz), Dual Trace.....	\$175
Tek 465, Scope (100MHz), Dual Trace.....	\$425
Tek 465B, Scope (100MHz), Dual Trace.....	\$475
Tek 466, Scope (100MHz storage), Dual Trace.....	\$575
Tek 475, Scope (200MHz), Dual Trace.....	\$475
Tek 475A, Scope (250MHz), Dual Trace.....	\$625
Tek 485, Scope (350MHz), Dual Trace.....	\$700
Tek 520A, NTSC Vectorscope.....	\$400
Tek 576, Curve Tracer.....	\$1,900
Tek 7104, Scope (1GHz), Dual Trace.....	\$1,200
Tek 7104, Scope (1GHz) w/7A29, 7A29, 7B10 & 7B15.....	\$2,200
Tek 7844, Scope (dual beam) w/7A24, 7A26, 7B80 & 7B87.....	\$750
Tek 7904, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$750
Tek 7904A, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$825
Tek 7904A, Scope (500MHz) Frame.....	\$425
Vahlia 2724A, Program. Res. Standard w/Manual.....	\$1,800
Wavetek 145, Pulse/Function Generator .0001-20MHz.....	\$300
Wavetek 157, Programmable Waveform Synthesizer.....	\$425
Wavetek 1855, CATV Sweep/Transmitter.....	\$750
Wavetek 288, Synthesized Function Generator, 20Hz-20MHz (unused).....	\$800
Wavetek 442, Dual HiLo Filter, 1Hz-10KHz.....	\$400

TURN IDLE TEST EQUIPMENT
— INTO CASH —
CALL OR FAX FOR QUOTATION

HP 415E, SWR Meter.....	\$100
HP 432A, Power Meter w/Cable/847B, .01-18GHz Sensor.....	\$350
HP 436A, Power Meter w/8481H Sensor/Cable.....	\$1,200
HP 436A, Power Meter, Opt. 002/009/022 w/8481H Sensor/Cable.....	\$1,400
HP 651B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 652B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator.....	\$195
HP 1630D, Logic Analyzer w/pods.....	\$550
HP 1630G, Logic Analyzer w/pods.....	\$650
HP 3312A, Function Generator, 1Hz-13MHz.....	\$490
HP 3314A, Function Generator, Opt. 001.....	\$1,500
HP 3325A, Programmable Frequency Synthesizer 1Hz-32MHz.....	\$950
HP 3330B, Automatic Synthesizer, 20Hz-13MHz.....	\$295
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V.....	\$125
HP 3408A, RF Voltmeter, 50uV-3V, 1.2GHz.....	\$200
HP 3455A, DMM 5-1/2 Digit.....	\$250
HP 3456A, DMM 6-1/2 Digit.....	\$525
HP 3468A, DMM 4-1/2 Digit, AC/Battery, 5 Function.....	\$175
HP 3488A, Switch Control.....	\$450
HP 3551A, Portable Transmission Test Set.....	\$550
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz.....	\$500
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, LED Readout.....	\$850
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, Mechanical.....	\$500
HP 3582A, Spectrum Analyzer, .02-25.5KHz.....	\$1,800
HP 3585A, Spectrum Analyzer, 20Hz-40MHz.....	\$3,900
HP 3702B, IF/BF Receiver w/3705 DfL Phase Detector.....	\$475
HP 3770A, Amplitude/Delay Distortion Analyzer.....	\$300
HP 3779B, Primary MPX Analyzer.....	\$500
HP 3781B, Pattern Generator.....	\$250
HP 4275A, LCZ Meter.....	\$2,400
HP 5314A, Counter, 100MHz, Opt. 002, w/Manual, Nice!.....	\$175
HP 5314A, Counter, 10MHz, Opt. 001 (Icaro), Nice!.....	\$175
HP 5315B, Counter, 100MHz, Opt. 001, w/Manual, Nice!.....	\$275
HP 5315B, Counter, 1GHz, Opt. 001/003, w/Manual.....	\$425
HP 5316A, Counter, 100MHz, GPIB.....	\$350
HP 5328A, Counter, 100MHz w/DVMOpt. 021.....	\$200
HP 5328A, Counter, 500MHz.....	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven.....	\$500
HP 5340A, Counter, 18GHz (nice).....	\$600
HP 5345A, Counter, 500MHz.....	\$450
HP 5345A, Counter, 500MHz, HP-IB.....	\$650
HP 54111D, Color Scope, 500MHz, Logic Triggering, (1GIGASAMPLE/SEC) Digitizing.....	\$2,800
HP 54600A, Scope, 100MHz, Digital Storage w/54657A.....	\$1,400
HP 6101A, Power Supply, 0-20V @ 1A.....	\$125
HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A.....	\$150
HP 6112A, Power Supply, 40V @ .5A (metered).....	\$150
HP 6116A, Power Supply, 0-100V @ 200MA.....	\$150
HP 6202B, Power Supply, 40V @ .75A (metered).....	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered).....	\$150
HP 6205B, Power Supply (dual), 0-40V @ .3A, 0-20V @ .8A (metered).....	\$175
HP 6206B, Power Supply, 0-80V @ 1A (metered).....	\$200
HP 6212A, Power Supply, CV/CC, 0-100V @ 100MA.....	\$125
HP 6213A, Power Supply, CV/CC, 0-10V @ 1A.....	\$75
HP 6217A, Power Supply, CV/CC, 0-50V @ 200MA.....	\$100
HP 6218A, Power Supply, CV/CC, 0-50V @ 200MA.....	\$125
HP 6227B, Dual Tracking PS 0-25V @ 2A.....	\$375
HP 6260B, Power Supply, 10V @ 100A (metered).....	\$300
HP 6264B, Power Supply, 0-20V @ 20A.....	\$225
HP 6265B, Power Supply, 40V @ 3A (metered).....	\$200
HP 6266A, Power Supply, 40V @ 6A (metered).....	\$200
HP 6266B, Power Supply, 0-40V @ 5A.....	\$275
HP 6289A, Power Supply, 0-40V @ 1.5A (metered).....	\$175

• 60-DAY WARRANTY
• 10-DAY RIGHT OF RETURN
• SATISFACTION GUARANTEED

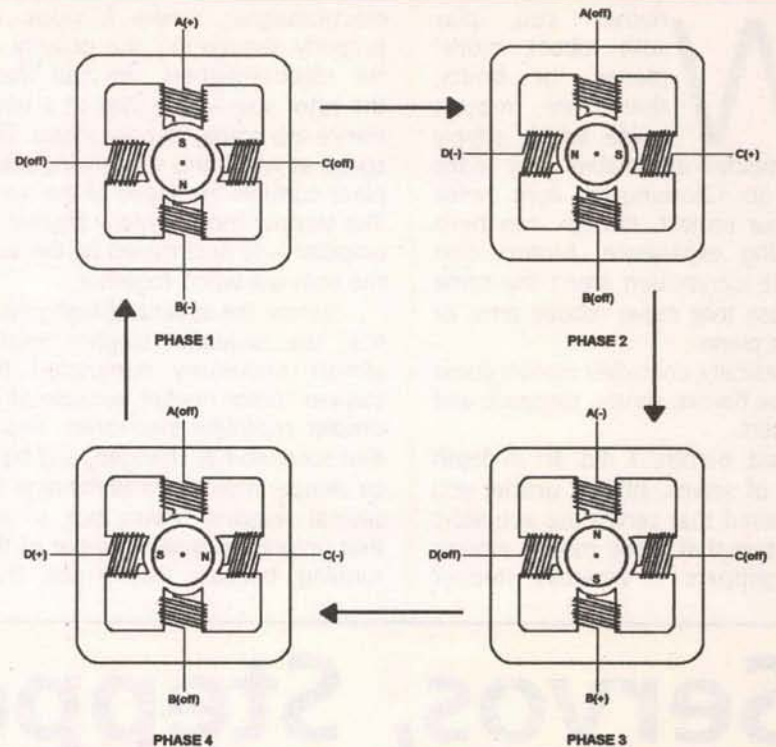


Figure 3. Full-Wave bipolar stepper motors work by reversing the polarity of the drive voltage across alternate stator coils.

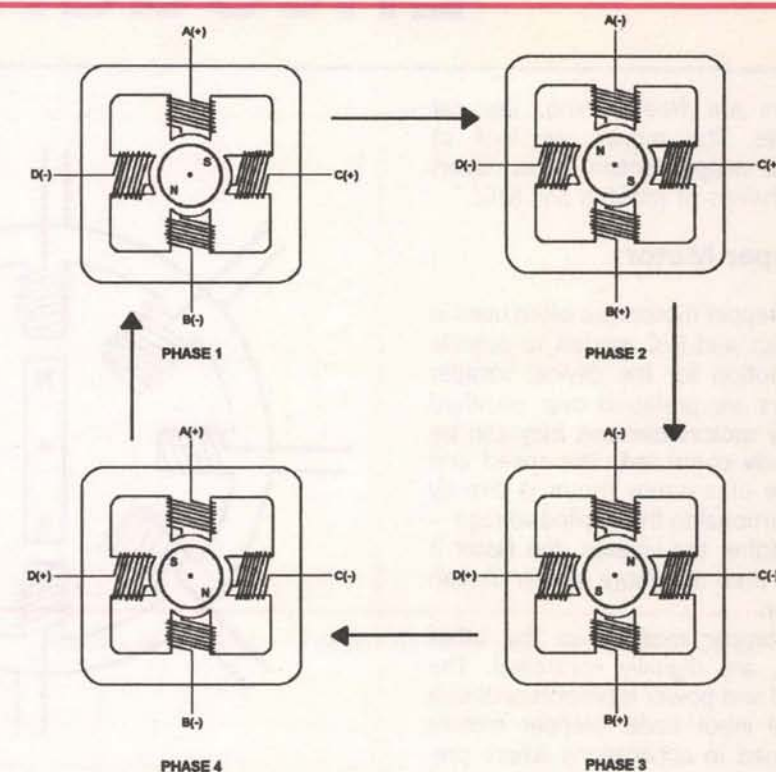


Figure 4. Two-Step bipolar stepper motors work by reversing the polarity of the drive voltage across adjacent stator coils.

Table 1. Stepper Motor Comparison

	Bipolar	Unipolar	Variable Reluctance
Speed			
5	5	10	
Torque			
10	5	4	
Controller complexity			
5	10	10	
Position stability			
10	10	3	
Price			
7	5	10	
Total	37	35	37

The numbers are on a scale of 1 to 10, with 10 being best. For example, the bipolar (10) stepper has twice the torque of a unipolar (5) stepper motor.

tion to lock onto, the rotor magnet seeks out a middle ground, which is halfway between the poles. This is Phase 1. The A and B coils now reverse polarity (Phase 2), which forces the rotor magnet clockwise to 4:30 o'clock. Phase 3 reverses the C and D coil polarity, and we end up at Phase 1 with the next voltage polarity reversal.

Half-Step Operation

While the Two-Phase stepping mode provides a huge gain in torque, it still lacks resolution. Like the Full-Wave mode, the best you can do is control the motor in increments of 90 degrees.

For many applications, this is too

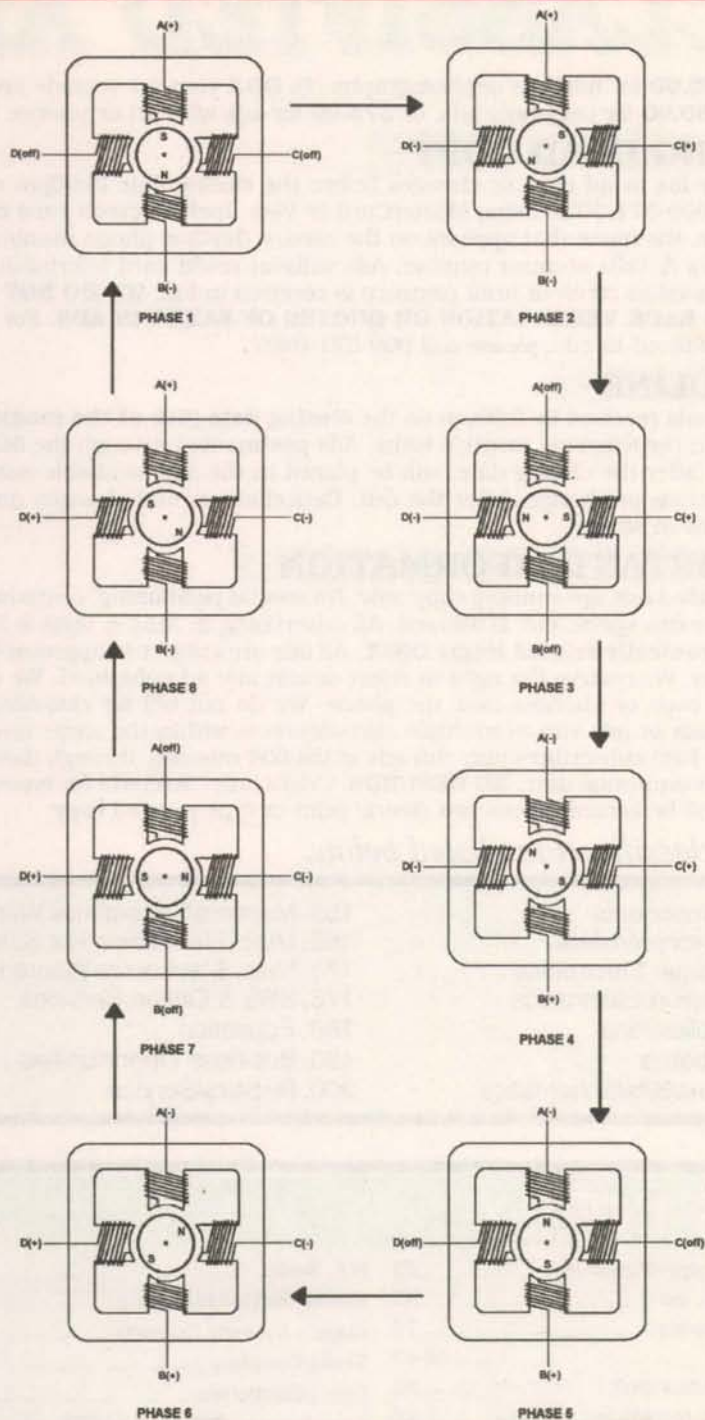


Figure 5. Half-step operation provides the highest resolution.

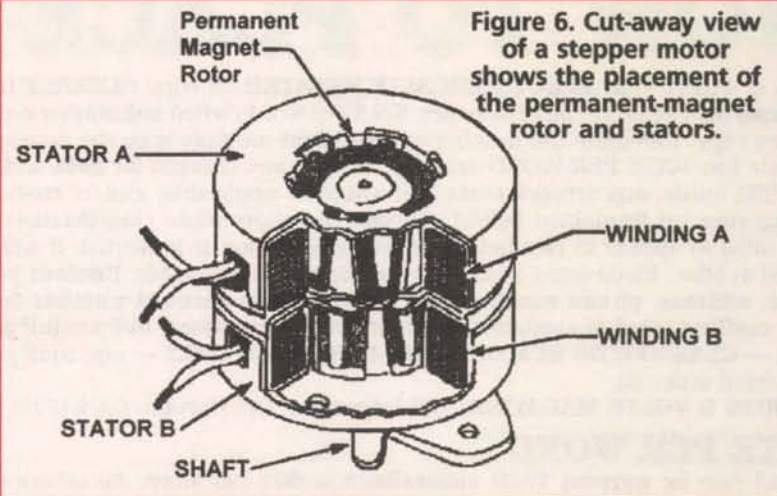


Figure 6. Cut-away view of a stepper motor shows the placement of the permanent-magnet rotor and stators.

coarse. What we need is a way to increase the number of steps per revolution. Enter the Half-Step controller. Basically, Half-Step operation is a combination of Full-Wave and Two-Phase. It goes like this (Figure 5).

Phase 1: Coils A and B are energized, coils C and D are off. The rotor magnet points to 12:00 o'clock. Phase 2: Coils AB and CD are energized at the same time. The rotor magnet points to 1:30 o'clock. Phase 3: Coils C and D are energized, coils A and B are off. The rotor magnet points to 3:00 o'clock.

Phase 4: Coils A and B reverse polarity. The rotor magnet points to 4:30 o'clock. Phase 5: Coils A and B are energized for opposite polarity of Phase 1, coils C and D are off. The rotor magnet points to 6:00 o'clock.

Well, you get the pattern. Using this method, the number of steps per

revolution is increased from four to eight.

Of course, these examples were selected for the sake of argument only. Real world stepper motors have far more steps per revolution—typically in increments of 7.5 and 15 degrees, with some steppers having a resolution as high as 0.9 degrees per step.

The number of steps is determined by the construction of the motor, which has more than four stator poles (Figure 6). The principle of operation and drive sequences remain the same, though.

Coming Next Month

That's all the room I have for this month. Next month, I'll describe the electronics needed to make these motors spin. Stay tuned, there's a lot more to come. **NV**

Table 2. Permanent-magnet stepper motor operating modes.

Operating Mode	Comments
One-Phase-On (full-wave)	Easy to implement, lowest torque
Two-Phase (normal)	Easy to implement, highest torque
Half-Step	Highest resolution, medium torque

A DEGREE ON A DISK!

Electro Science Applications Inc.

EM FORMULARY

File Formulas Conversions Data Search Tables Windows Help

- 500+ formulas and simulations
- Unit conversions and data tables
- Physical constants
- Electronics, communications, radar
- Antennas, filters, optics
- Physics, math, space science
- Practical and educational

Self-contained and intuitive, you'll be up and running in minutes. Fast menu and hyper-linked access to equations and data. Current version 1.7 works with Windows 3.1, 95, or 98.

ELECTRO SCIENCE APPLICATIONS, INC.
P.O. BOX 11158, TORRANCE, CA 90510

To order, call (310) 539-2422 or E-Mail esa@earthlink.net
Send \$29.95 check or money order (CA residents add 8.25% sales tax).
Foreign orders add appropriate shipping charge.

Electronic and RF design services also available.
Visit us at <http://www.esap.com>

Write in 152 on Reader Service Card.

Weeder Technologies

ON-LINE
CATALOG

www.weedtech.com

Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

Voice/Fax 850-863-5723

Stackable RS-232 Kits

Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32**

Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49**

Home Automation (X-10) - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. **\$39**

Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ASCII character string. Example: *12/31 08:45 850-863-5723 Weeder, Terry <CR>. Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$35**

Touch-Tone Input - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. **\$34**

IR Remote Control Receiver

Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. **\$32**

Telephone Call Restrictors

Two modes of operation: either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.

Block out selected outgoing calls. Bypass at any time using your password. **\$35**

Block out selected incoming calls. Calls identified using Caller ID data. **\$46**

Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49**

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$55**

HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for **bold** and/or **CAPPED** words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 91719.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your **Nuts & Volts** account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

ADVERTISER'S INDEX

1A Sales	51	DMD Systems Recovery, Inc.	67	LLH Technology Publishing	63	R.E. Smith	68
Abacom Technologies	86	Earth Computer Technologies	39	Lynxmotion, Inc.	45	Resources Un-Ltd.	17
ABC Electronics	80	EDS	86	M2L Electronics	79	Roger's Systems Specialist	77
ACP Super Store	56	E.H. Yost & Co.	65	Matco, Inc.	66-67	Saelig Company	29
ActiveWire, Inc.	66	Electro Mavin	15	Meredith Instruments	53	Sam's Electronics	80
Alfa Electronics	33	Electro Science Applications, Inc.	71	Metric Equipment Sales, Inc.	46	Scott Edwards Electronics, Inc.	84
All Electronics Corporation	41	Electro Tool, Inc.	35	microEngineering Labs	50	Seabird Technical	67
Allison Technology Corporation	68, 85	Electronic Goldmine	34	Micromint	64	Sescom, Inc.	66
Alltech Electronics	31	Electronic Products	66	Midland Technologies	66	Shreve Systems	8
Alltronics	22	EMAC, Inc.	52	Milestone Products	33	SiGEM	66
AM Research, Inc.	25	EPS	67	Miller Engineering	83	Skycraft Parts & Surplus, Inc.	64
Andromeda Research	45	Equipment Management Technology	44	Modern Communications	34	softwarecloseouts.com	67
Antique Radio Classified	67	ExpressPCB	12	Mouser Electronics	50	Square 1 Electronics	35
AST Global Electronics	70	Foss Warehouse Distributors	68	Mr. NiCd	65	SuperCircuits	15
Astro Too	67	Gateway Electronics, Inc.	20	MSC Electronics	67	Surplus Traders	68
Aviation Components Corp.	66	General Device Instruments	68	MVS	13	Techniks, Inc.	68
BasiConcepts, Inc.	75	Gibraltar Trade Center, Inc.	32	Netcom	11	Technological Arts	90
Baylin Publications	51	Halted Specialties Co.	3	Norcomm	59	Technology Electronics, Ltd.	68
Bilocon Corp.	67	Howard Electronic Instruments, Inc.	36	Northwest Cable & Connector Co.	60	Telulex, Inc.	30
Black Feather Electronics	82	H.T. Orr Computer Supplies	55	Optoelectronics	4	Test Equipment Plus	32
Brigar Electronics	14	Information Unlimited	24	OS Systems	76	The RF Connection	75
Bytech Services	46	Inkjet Southwest	19	Parallax, Inc.	Back Cover	Timeless Products	42
C & S Sales, Inc.	61	Intek Electronic Systems	56	PARAMAX, INC.	81	Timeline, Inc.	37
C and H Sales Company	42	Intelligence	67	Patco Service, Inc.	90	TNR Technical, Inc.	66
Circuit Chem, Inc.	67	Intersoft	82	PCW, Inc.	56	Unicorn Electronics	85
Circuit Etching Technics	25	Intronics, Inc.	55	Phelps Instruments	57	Upstate Games	67
Circuit Specialists, Inc.	94	Jade Products, Inc.	68	Pioneer Hill Software	84	USI Corp.	35
Communications Surplus	66	Jameco Electronics	47	Plans-Kits Unlimited	66	V&V Mach. & Equipment, Inc.	66-68
Consumertronics	39	Jam RF	74	Polaris Industries	7	Vesta Technology, Inc.	66
Convergent, Inc.	83	Jason Ranheim	12	Power Quality, Inc.	68	Visitect, Inc.	23
Corporate Systems Center	2, 95	Junkware.com	66	Prairie Digital, Inc.	67	Weeder Technologies	71
Cunard Associates	52	J-Works, Inc.	53	Pulsar, Inc.	14	Western Test Systems	26-27
Davilyn Corp.	37	La Paz Electronics Int'l.	55	P.V. Power Corp.	67	Wholesale Cable	44
DeMar Electronics	67	Lemon-Pladd, Inc.	79	Quality Kits	66	Worldwyde	68
Digital Products Company	66	Lemos International Co., Inc.	31	R & S Surplus	40		
Direct Factory Supply, Inc.	74	Linear Systems	13	Ramsey Electronics, Inc.	38		

AMATEUR RADIO & TV

Alltronics	22
Astro Too	67
Communications Surplus	66
Convergent, Inc.	83
Gateway Electronics, Inc.	20
Intersoft	82
Jade Products, Inc.	68
Lemos International Co., Inc.	31
Matco, Inc.	66-67
Norcomm	59
Ramsey Electronics, Inc.	38
The RF Connection	75

ASSEMBLY SERVICES

Bilocon Corp.	67
---------------	----

BATTERIES/CHARGERS

1A Sales	51
Cunard Associates	52
E.H. Yost & Co.	65
Jade Products, Inc.	68
Mr. NiCd	65
Power Quality, Inc.	68
TNR Technical, Inc.	66

BUSINESS OPPORTUNITIES

Intek Electronic Systems	56
--------------------------	----

BUYING ELECTRONIC SURPLUS

ABC Electronics	80
Alltech Electronics	31
Aviation Components Corp.	66
Black Feather Electronics	82
C and H Sales Company	42
Earth Computer Technologies	39
EPS	67
Equipment Management Technology	44
Intek Electronic Systems	56
Metric Equipment Sales, Inc.	46
Roger's Systems Specialist	77
Skycraft Parts & Surplus, Inc.	64
Timeline, Inc.	74

CABLE TV

Direct Factory Supply, Inc.	74
Foss Warehouse Distributors	68
Milestone Products	33
Modern Communications	34
PCW, Inc.	56
Sam's Electronics	80
Timeless Products	42
Wholesale Cable	44
Worldwyde	68

CB/SCANNERS

USI Corp.	35
-----------	----

CCD CAMERAS/VIDEO

Black Feather Electronics	82
Circuit Specialists, Inc.	94
Matco, Inc.	66-67
MSC Electronics	67
Polaris Industries	7
Ramsey Electronics, Inc.	38
Resources Un-Ltd.	17
Seabird Technical	67
SuperCircuits	15
Timeline, Inc.	74
USI Corp.	35

COMPONENTS

1A Sales	51
Aviation Components Corp.	66
BasiConcepts, Inc.	75
Circuit Etching Technics	25
Communications Surplus	66
Convergent, Inc.	83
Electronic Goldmine	34
Electronic Products	66
EPS	67
Jameco Electronics	47
La Paz Electronics Intl.	55
Linear Systems	13
OS Systems	76
Pulsar, Inc.	14
SiGEM	66
Skycraft Parts & Surplus, Inc.	64
Unicom Electronics	85
Visitec, Inc.	23

COMPUTER

Hardware	
ACP Super Store	56
ActiveWire, Inc.	66
Allison Technology Corp.	68, 85
Alltech Electronics	31

AM Research, Inc.	25
Bytech Services	46
Consumertronics	39
Corporate Systems Center	2, 95
DMD Systems Recovery, Inc.	67
Earth Computer Technologies	39
Electro Mavin	15
General Device Instruments	68
Gibraltar Trade Center, Inc.	32
Halted Specialties Co.	3
Jameco Electronics	47
Jason Ranheim	12
La Paz Electronics Intl.	55
Northwest Cable & Connector Co.	60
Roger's Systems Specialist	77
Shreve Systems	8
Techniks, Inc.	68
Upstate Games	67

Software

AM Research, Inc.	25
Bytech Services	46
Electro Science Applications, Inc.	71
Gibraltar Trade Center, Inc.	32
Pioneer Hill Software	84
softwarecloseouts.com	67

Microcontrollers / I/O Boards

AM Research, Inc.	25
BasiConcepts, Inc.	75
Bytech Services	46
Convergent, Inc.	83
EMAC, Inc.	52
Jameco Electronics	47
Junkware.com	66
La Paz Electronics Intl.	55
Lemon-Pladd, Inc.	79
Micromint	64
MVS	13
OS Systems	76
Parallax, Inc.	Back Cover
PARAMAX, INC.	81
Prairie Digital, Inc.	67
R.E. Smith	68
Scott Edwards Electronics, Inc.	84
Square 1 Electronics	35
Technological Arts	90
Vesta Technology, Inc.	66

Printers/Printer Supplies

H.T. Orr Computer Supplies	55
Inkjet Southwest	19

DESIGN/ENGINEERING SERVICES

Electro Science Applications, Inc.	71
ExpressPCB	12
Midland Technologies	66
Plans-Kits Unlimited	66
Prairie Digital, Inc.	67
Pulsar, Inc.	14
V&V Mach. & Equipment, Inc.	66-68

EDUCATION

BasiConcepts, Inc.	75
Electro Science Applications, Inc.	71
EMAC, Inc.	52

EVENTS/SHOWS

ACP Super Store	56
Gibraltar Trade Center, Inc.	32

KITS

Alltronics	22
C & S Sales, Inc.	61
Digital Products Company	66
Earth Computer Technologies	39
Electronic Goldmine	34
Electronic Products	66
EMAC, Inc.	52
Gateway Electronics, Inc.	20
Information Unlimited	24
Inkjet Southwest	19
Jade Products, Inc.	68
Lemon-Pladd, Inc.	79
Miller Engineering	83
Plans-Kits Unlimited	66
Quality Kits	66
Ramsey Electronics, Inc.	38
Scott Edwards Electronics, Inc.	84
SiGEM	66
Technology Electronics, Ltd.	68
USI Corp.	35
Weeder Technologies	71

LASERS

Information Unlimited	24
Meredith Instruments	53
Resources Un-Ltd.	17
Unicom Electronics	85

MISC./SURPLUS

1A Sales	51
All Electronics Corporation	41
Alltech Electronics	31
Aviation Components Corp.	66
Black Feather Electronics	82
Brigar Electronics	14

FIND
what you need ...
FAST
BY PRODUCT
OR
CATEGORY

C and H Sales Company	42
Circuit Chem, Inc.	67
Communications Surplus	66
Consumertronics	39
DeMar Electronics	67
Electronic Goldmine	34
EPS	67
Equipment Management Technology	44
Halted Specialties Co.	3
Jam RF	74
Linear Systems	13
Power Quality, Inc.	68
Resources Un-Ltd.	17
Shreve Systems	8
Skycraft Parts & Surplus, Inc.	64
Surplus Traders	68
Timeline, Inc.	74
Unicom Electronics	85
Visitec, Inc.	23
Weeder Technologies	71

PROGRAMMERS

Andromeda Research	45
Electronic Products	66
General Device Instruments	68
Intronics, Inc.	55
Jason Ranheim	12
M2L Electronics	79
microEngineering Labs	50
Upstate Games	67

PUBLICATIONS

Antique Radio Classified	67
Consumertronics	39
Intelligence	67
LLH Technology Publishing	63
Mouser Electronics	50
Netcom	11
Plans-Kits Unlimited	66
Square 1 Electronics	35

RF TRANSMITTERS/RECEIVERS

Abacom Technologies	86
---------------------	----

ROBOTICS

Astro Too	67
Lemos International Co., Inc.	31
Lynxmotion, Inc.	45
OS Systems	76
PARAMAX, INC.	81
SuperCircuits	15

SATELLITE

Baylin Publications	51
Milestone Products	33
SiGEM	66
Worldwyde	68

SECURITY

Information Unlimited	24
Intelligence	67
Intersoft	82
Lemos International Co., Inc.	31
Matco, Inc.	66-67
MSC Electronics	67
Norcomm	59

Polaris Industries	7
SuperCircuits	15
Visitec, Inc.	23

SOLAR EQUIPMENT

P.V. Power Corp.	67
------------------	----

STEPPER MOTORS

Alltronics	22
PARAMAX, INC.	81

TELEPHONE

Digital Products Company	66
Telulex, Inc.	30
Weeder Technologies	71

TEST EQUIPMENT

ABC Electronics	80
Alfa Electronics	33
Allison Technology Corp.	68, 85
AST Global Electronics	70
Astro Too	67
C & S Sales, Inc.	61
C and H Sales Company	42
Circuit Specialists, Inc.	94
Davilyn Corp.	37
Digital Products Company	66
DMD Systems Recovery, Inc.	67
EDS	86
Electro Tool, Inc.	35
Equipment Management Technology	44
Howard Electronic Instruments, Inc.	36
Intronics, Inc.	55
J-Works, Inc.	53
Metric Equipment Sales, Inc.	46
Optoelectronics	4
Phelps Instruments	57
Pioneer Hill Software	84
Power Quality, Inc.	68
Prairie Digital, Inc.	67
R & S Surplus	40
Saelig Company	29
Seabird Technical	67
Sescom, Inc.	66
Telulex, Inc.	30
Test Equipment Plus	32
Western Test Systems	26-27

TOOLS

C & S Sales, Inc.	61
Electro Tool, Inc.	35
Howard Electronic Instruments, Inc.	36
Lemon-Pladd, Inc.	79
Patco Service, Inc.	90
The RF Connection	75

WIRE/CABLE & CONNECTORS

Northwest Cable & Connector Co.	60
Roger's Systems Specialist	77
The RF Connection	75

Open Channel

Dealing With Instrument Problems

My problem was that I relied on the ground connection in the AC power cords of the instruments. After all, it seems to make sense, doesn't it? The third-wire ("green") inside the power cord is connected to ground in the AC outlet and to the chassis in the equipment.

One time many years ago (so long ago that I had hair), I had a particular problem working on a sensitive piece of medical-scientific instrumentation. It was a microvolt level high gain amplifier used for amplifying biopotentials. I was trying to balance the common mode adjustment ratio (CMRR), but kept getting odd results. It would be in balance and then not so well balanced, and seemed to change while I was watching it. Sometimes, it seemed like a random thing ... the CMRR adjustment would just pop out of adjustment. Darned disconcerting, but there was a solution.

The main problem was that the grounding of the instruments being used was defective. Figure 1 shows the basic set-up, but with correct grounding. To make a CMRR adjustment on a differential amplifier (one would not make such an adjustment on a single-ended or unbalanced amplifier), it is necessary to tie both inputs together, and connect them to the output of a signal generator. This is done because the CMRR is the ratio of the differential gain to the common mode gain, and common mode signals are those which affect both inputs equally.

The signal generator output is set to some convenient high level (e.g., 100 mV, 500 mV, or 1 volt), and then null the output signal on an AC voltmeter or oscilloscope. The procedure is repeated several times at increasingly sensitive settings of the meter or 'scope input channel until no further improvement is possible.

My problem (stupid me!) was that I relied on the ground connection in the

AC power cords of the instruments. After all, it seems to make sense, doesn't it? The third-wire ("green") inside the power cord is connected to ground in the AC outlet and to the chassis in the equipment. The problem is noise on the ground line and ground loops. As the AC loading changes, the amount of leakage current flowing in the ground line also changes. Because the amplifier was so sensitive, these tiny little ground loop currents gave rise to non-common mode signal voltages that were right in the range the amplifier wanted to see.

Drat! Actually, I knew better. The reason why the manufacturers of the medical equipment and the bench instruments I used to make the adjustment provide chassis ground terminals on the front panels (sometimes rear panels) is to help dummies like me. The ground scheme shown in Figure 1 is a "star ground." The attribute of interest here is that the chassis grounds and signal commons of all instruments — including the amplifier under test — are grounded to a single point. Make the ground wire as heavy and as short as possible.

The lesson of star grounding also should apply to operation of an instrumentation system. I've seen medical and scientific researchers plagued by noise and other problems that were easily avoidable. Sometimes, when you

connect a group of very good instruments together improperly, grounding problems make them behave poor collectively.

Preamp Goes a Long Way

One physiologist I worked with was using a small strain gauge sensor to measure the contractions of a guinea pig heart. The sensor was calibrated in force units of one to two grams maximum. What? You say grams as mass not force? In that instrument the gram-force unit was used, i.e., the force of gravity on a mass of one gram (about 960 dynes). The innards of the sensor was a set of piezoresistive strain gauges in a classical Wheatstone bridge. It has a sensitivity of 20 $\mu\text{V/gm-force}$. The typical deflection was about 0.2 gm-force, so the output voltage was typically about 4 μV .

The good doctor was taking the 4 μV output of the sensor through a pair of shielded cables to the differential input of a high gain oscilloscope. Actually, the amplifier was the normal two channel oscilloscope vertical amplifiers, and he used it in the A-B mode, simulating (but not exactly) differential operation. The CMRR was atrocious, and he was showing a large 60-Hz hum on the output trace. He asked us to fix the problem.

My solution was to build a simple DC differential preamplifier from an

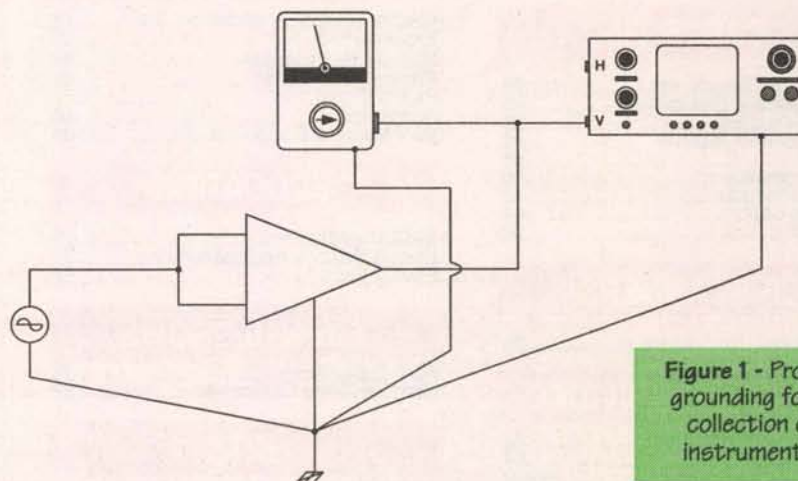


Figure 1 - Proper grounding for a collection of instruments.

FASTER THAN MOTOROLA

Two-way radio jamming equipment 800/900MHz. Stop illegal surveillance. **Pager jammers 900MHz.** Stop pagers from going off during school or church service. **Cellular phone jammers.** Stop cellars from going off during school or church service. **PCS jamming, PCS phones.** **Lojack/teletrack/boomerang.** Stop illegal tracing/anti-surveillance. **Cordless phone jammers 49MHz/900MHz • Radar jammers Xband • Nextel jammers • Car alarm jammer • CB radio jammer • Garage door jammer • RC radio jammers • AM/FM radio • HF/VHF/UHF radios • 1/8000MHz jamming equipment.**

This equipment is designed for anti-surveillance customers: embassies, schools, churches, governments, law enforcement.

IF YOU DON'T SEE WHAT YOU WANT, WE WILL BUILD IT FOR YOU!!

We sell only to specific organizations or for export. Anyone implying illegal activity will be denied assistance and will be reported to law enforcement.

Jam RF • 954-561-8128 or www.jamrf.com

www.nutsvolts.com

CABLE TV CONVERTERS


	5 lot	10 lot	20 lot	100+
►Viewstar MXC - 2020 85 CH Plain Converter PG Lock HRC/STD SleepTimer	\$45.	\$40.	\$35.	\$30.
►Century CTC - 3000 99 CH Plain Converter PG Lock HRC/STD SleepTimer	\$50.	\$45.	\$40.	\$35.
►Wireless Video Senders Transmits Aud/Vid to any TV	\$20.	\$18.	\$15.	\$13.
►REM -100 Magnavox 3 in 1 Univ. Remote control	\$ 6.	\$ 5.30	\$ 4.75	\$ 4.

All converters are factory new with remote control. Call us today for all your cable accessory needs.

DIRECT FACTORY SUPPLY, INC.
1-888-748-0946

E-MAIL YOUR REQUESTS TO: DIRFACSUP@AOL.COM (No Descrambler Sales)

Figure 2 - EMI proofing an instrumentation amplifier.

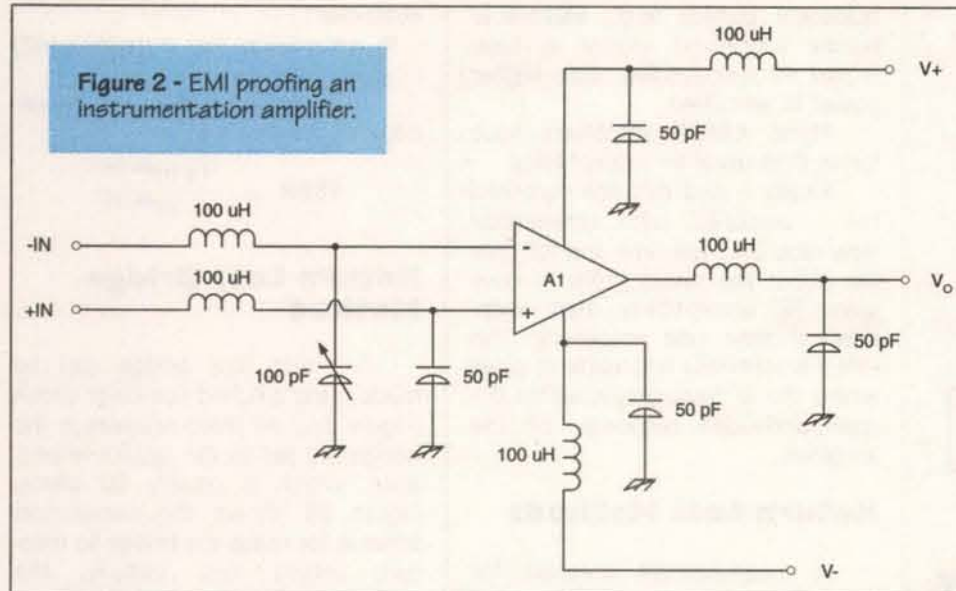

op-amp. With a gain of X200, it boosted the 4 μ V output of the sensor to about 800 μ V. Still small, but good enough. With the preamplifier mounted right on the sensor body (through a common connector), the signal could be sent single-ended through shielded cable to the oscilloscope ... and the 60 Hz disappeared.

A couple weeks after I solved the problem (for about \$50.00 in parts and shop labor), the scientist called me and asked for a technical description. I typed up about a half page and gave him a hand drawn schematic. He then asked me for "... a bit more ... maybe four or five pages." Hmmmm ... how do you cram half a page worth of text into four or five pages?

Well, you spend a lot of time talking about basic op-amp theory. About a year later, he handed me a pile of reprints "... from our article." It seems that "we" had published a technical note in a physiology journal. I protested that it was too simple, and most hobbyists could easily do that chore for him. His reply: "... but most physiologists couldn't ... they would've spent \$1,900.00 for the correct preamplifier from a scientific supply house ... and I didn't have the money in my grant."

Power Line Noise

In the same medical center, we once flunked the entire freshman class of medical students on their physiology exam. Also failed were all of the basic sciences (i.e., PhD) students and allied health students (e.g., nurse anesthesia, nurse practitioner, physicians assistant). Those people are about "up-to-here" with stress their first year in medical school so the profs hoped that the results would not get out until we solved the problem. It turned out to be power line noise.

In those days, computing was mainframe computing. The examination was taken on "mark sense" optical scanner paper. You know the stuff ... "use a No. 2 pencil and completely blacken the desired box." In

our case, the optical scanner was connected to a keypunch machine. To younger readers: A keypunch was a noisy, clunky machine that looked like a typewriter on steroids that punched the holes in old-fashioned computer cards. The cards were then taken to the computer center for processing overnight. When the computer print-out paper was returned, the grades were recorded (manually!) and the paper posted for all to see.

The problem came to light when one of the engineers I worked with noticed that one column on the computer card had all digits punched out. There is no EBCDIC code that has all digits punched out in a single column. The problem was traced to high-voltage power line transients arising from loading shifting switching gear in the basement. It seems that the local power company gave the university a two-percent break on the electric bill if they installed equipment that would periodically balance the load between the three phases (which makes for more efficient operation). Unfortunately, the triac switches tossed huge (>2KV) transients that averaged 50 to 100 microseconds.

The solution to the problem (we couldn't rewire the building or turn off the load switchers) was to place a

Topaz isolation transformer between the power line and the optical scanner and keypunch machine. These transformers are specially designed to snuff power line noise (today, we might use a computer surge suppressor for many such applications).

We then found that the noise was the basis for a lot of problems. For example, the electron microscope guy had been attempting to find a "vibration problem" in his equipment (it didn't help that the subway ran right beneath our building foundation ... so he was tuned in on "vibration problems"). Adding an isolation transformer to his equipment cured the little glitches that were showing up in the pictures he took.

Still another guy was almost comical. He was a hematology researcher, i.e., he knew more about human blood than anyone else. He had a high-priced microscope that had a special light source. It was a glass tube that had been evacuated, and then refilled with a special combination of rare gases that each gave off a different color light when ionized. There were about a half dozen electrodes on the tube that each had to see a different voltage.

The poor guy had to spend 45 minutes anytime he wanted to use the microscope balancing the voltages on these interactive electrodes ... it was a touchy thing, I suspect. Once in awhile, usually (as Murphy's law dictates) when he could ill afford the time, a power line transient would commutate the tube, extinguishing the light. After cursing and yelling at his Graduate Research Assistant (GRA), he would spend another half hour to 45 minutes re-doing the job. When we gave him an isolation transformer, it solved both his technical problem and the GRA's blood pressure problem.

EMI Problems

A large number of scientific



The RF Connection
213 North Frederick Ave.
Suite 11NV
Gaithersburg, MD USA
20877

<http://www.therfc.com/>

Complete Selection of MIL-Spec Coax, RF Connectors and Relays

UG-21B/U N Male for RG-213/214\$5.00
UG-21D/U N Male for RG-213/214\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913\$6.00 Pins Only\$1.50
UG-21D/9913\$4.00 Extra Gasket\$75

Amphenol 83-1SP-1050 PL-259\$0.90
UG-176/U Reducer RG-59/8X .25 or 5/\$1.00
UG-175/U Reducer RG-58/58A .25 or 5/\$1.00
Silver Teflon PL-259/Gold Pin\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F, 9913 with High Density PE Foam dielectric, stranded center cond. and Duobond III Jacket80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket Intro Price\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female\$2.50
8 Pin Mike Male Panel\$2.50
13 Pin DIN for Kenwood\$2.75
8 Pin DIN for Icom\$1.00
8 Pin DIN for Kenwood\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/869-3680

Write in 29 on Reader Service Card.

2 Great Books by Joseph Carr



SECRETS OF RF CIRCUIT DESIGN

From one of today's most respected electronics authors comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.

PRACTICAL ANTENNA HANDBOOK

PRACTICAL ANTENNA HANDBOOK

The most popular book on antennas ever written, widely known as "the antenna builder's bible."

\$49.95

This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.

As a paid subscriber to Nuts & Volts, you'll receive 10% off the list price!!

(See ad on page 48 for ordering details and other titles currently available.)

Explore Fuzzy Logic

with the AL220 device and

Fuzzy Logic Applications Expert (FAE) Development System.

The AL220 Device is a complete Single Chip Fuzzy Logic microcontroller which contains 4 analog inputs and 4 analog outputs. It was voted the most innovative product of 1994 by EDN magazine. Now it is available with a complete PC based development system, programmer, and real time hardware Emulator for hobbyist as well as professionals! Check out our web site at www.BasiConcepts.com for free data sheets, application notes, and additional product information.

Order	Description	Price Each
AL220	18 Pin Dip AL220 Device	\$12
FAE	FAE Dev System for Win 95/98 on CD	\$65
Hobby Pack	AL220, FAE, and Printer Port Programmer	\$95
Professional Pack	AL220, FAE, Programmer, and Real Time Hardware Emulator System	\$495

BasiConcepts, Inc. 312 W. First St. Suite 201, Sanford, FL 32771
Tel: (407)322-5608 Fax: (407)322-5609 Email: info@BasiConcepts.com


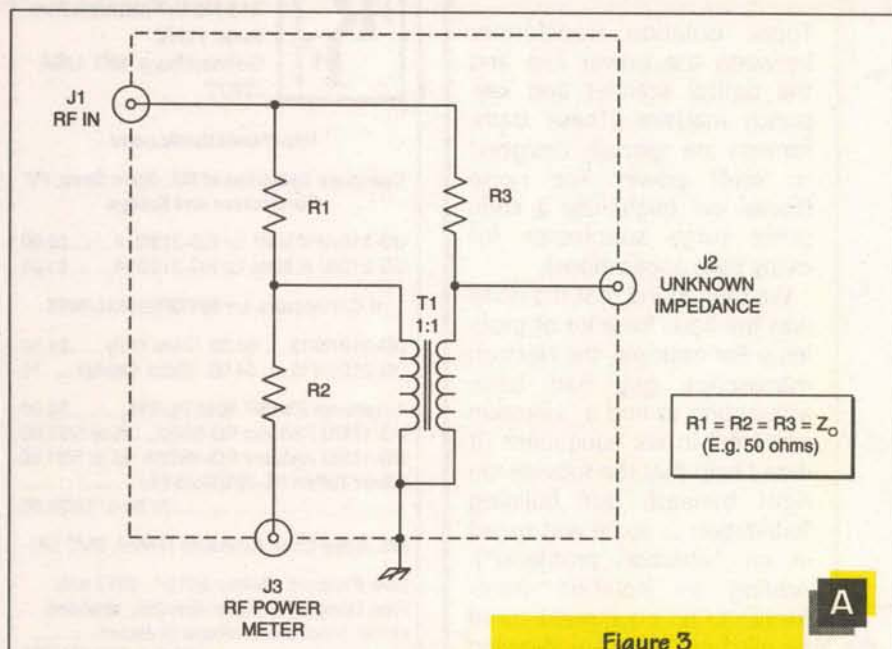


Figure 3
A) Return loss bridge;
B) using the bridge.

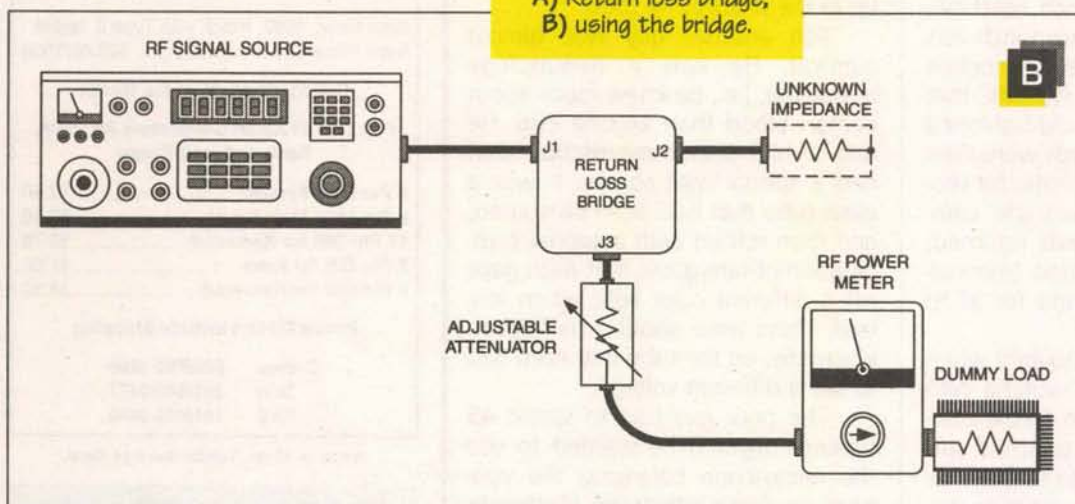

instruments use differential amplifiers in the front-end. Figure 2 shows some of the things one can do to protect these amplifiers against electromagnetic interference (EMI). The inductors and capacitors form L-section low-pass filters. Each consists of a 100 μ H inductor and a 50 pF capacitor. The capacitors should be placed as close to the pins of the IC amplifier as possible. Note that one of the input line filters contains a variable capacitor. This is a trimmer capacitor and is used to balance the circuit for minimum output voltage offset when an interfering RF signal

is applied to the inputs.

A friend of mine in the semiconductor industry provided the circuit in Figure 2, along with some advice on circuit design features that help reduce the susceptibility of the amplifier to electromagnetic interference.

First, if the internal circuits of an amplifier are biased close to one end of their ranges, then EMI susceptibility is increased. The solution is to select circuits in which the transistors are biased in the middle of their ranges. There is less likelihood of the circuit being driven into nonlinearity.

Second, IC amplifiers with low

quiescent current (e.g., low-power bipolar amplifiers) appear to have higher RF susceptibility than higher power IC amplifiers.

Third, CMOS amplifiers have lower than usual RF susceptibility.

Finally — and this one surprised me — amplifiers with symmetrical slew rates (i.e., rise time and fall time are about the same) seem to have lower RF susceptibility than asymmetrical slew rate amplifiers. This effect is especially noticeable in cases where the RF frequency is within the gain-bandwidth response of the amplifier.

Return Loss Methods

A measurement method for transmission lines that is not used as often as VSWR measurements is return loss. Return loss is the comparison of the forward and reflected signals, as expressed in decibels (dB). It compares an unknown impedance with a known impedance, and then reports the degree of mismatch or match in both phase and magnitude. When the match is perfect, then the return loss is infinite and, when all of the forward

power is reflected (as in a shorted or open load), the return loss is minimized ($P_r = P_f$). In addition, the same method is used for characterizing filters and other load-sensitive circuits.

Power Meter Method

The definition of return loss is given by:

$$\text{Return Loss} = 10 \log \left[\frac{P_f}{P_r} \right] \text{ dB}$$

This equation suggests a simple method for measuring return loss: Compare the forward and reflected power using a directional RF wattmeter. The actual return loss of the load is the indicated return loss less twice the known transmission line loss (when return loss is measured at the transmitter end of the line).

Return loss can also be used to determine reflection coefficient and VSWR. We can write the return loss expression as:

$$\text{Return Loss} = 20 \log |\Gamma|$$

To determine reflection coefficient, we need only solve for Γ :

$$|\Gamma| = 10^{(RL/20)}$$

Where:

Γ is the voltage reflection

coefficient

RL is the return loss in decibels (dB)

To determine VSWR from knowledge of the return loss:

$$\text{VSWR} = \frac{1 + 10^{(RL/20)}}{1 - 10^{(RL/20)}}$$

Return Loss Bridge Method

A return loss bridge can be made using a hybrid combiner circuit (Figure 3A). All three resistors in the bridge are set to the system impedance, which is usually 50 ohms. Figure 3B shows the connection scheme for using the bridge to measure return loss. Initially, the unknown impedance is not connected to the UNKNOWN IMPEDANCE port (J2) of the return loss bridge. An RF signal source is tuned to the frequency at which the measurement is made.

The signal source might be a signal generator, a special high power source, or a transmitter. The idea is to get enough RF power to the RF power meter so that small levels of reflected signal power can be measured on the selected meter. A step attenuator is in the line between the RF POWER METER port (J3) of the bridge and the RF watt-meter. Set the power level from the source so that a relatively large amount of attenuation is required to bring the watt-meter to some value in the upper half of its scale.

With the unknown impedance disconnected, measure the RF power appearing at the RF POWER METER port (J3). Once this value is recorded, connect the unknown load impedance (which might be an antenna) and again measure the RF power. When measuring this reflected power, it may prove necessary to adjust the step attenuator to get a good reading. The value of the attenuation must be accounted when making this measurement.

An equal deflection method could also be used in this measurement. Set the attenuator to a high value that produces a reading at a recognizable point on the meter (e.g., a calibration point, full-scale, or some other repeatable point). Note the amount of attenuation required. Connect the unknown impedance to J2 on the bridge, and the power indication on the meter will drop. Adjust the attenuator until the meter again reads the same value as before. The difference in the settings of the attenuator required to make the two readings is the return loss. **NV**


Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJJ@AOL.COM.

UNI-MICRO™

Super-Small-Low Power

The NEW UNI-MICRO series of modules provides a complete ready to use single board computer on a 1.75" X 1.5" module with large amount of non-volatile flash based memory. Expanded capabilities, multiple serial busses, in-circuit programming, including first time programming and a very low power consumption of 58 mA, makes this series of modules perfect for instrumentation, monitoring and control applications.

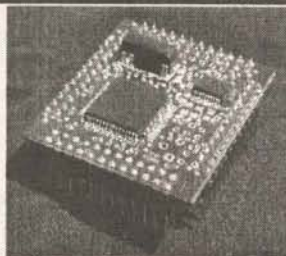

Microcontroller Design Made Simple

Small • 80C51 code compatible • 256 x 8 ram • 2K x 8 Battery backed sram with automatic power switching • 128K x 8 Flash memory • Parallel or serially programmable • 32K x 8 Flash memory • 3 16 bit timers • One 8 channel 10 bit A/D converter • Two 8 bit PWM outputs • One full duplex UART • 16 Mhz speed • 3000 gates flash CPLD • IIC serial bus • JTAG bus • 54 configurable I/O pins • RS232 driver on board • Voltage regulator on board • Power-on reset • Program security • Very low development costs • Assembly, C, Basic programmable.

\$59

OS Systems

908-979-1885 <http://www.ossystems.net>
1464 Route 57th, Port Murray, NJ 07865

Events CALENDAR

Continued from page 20

MO - ST. LOUIS - Hamfest. St. Louis ARC & Gateway to Ham Radio Club, Steve Welton WB0IUN, 314-638-4959. E-Mail: slw@partyline.net
OH - MARION - Hamfest. Marion ARC, Karen Eckard N8KE, 740-499-3565. E-Mail: meeker@gte.net
OH - MASSILLON - Hamfest. Stark County Fairgrounds. Talk-in: 147.18+ & 442.85. Massillon ARC, Don Wade W8DEA, 330-497-7232. E-Mail: marc.hamclub@juno.com

NOVEMBER 1999

NOVEMBER 6

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In. 619-561-0052
FL - SORRENTO - Hamfest. East Lake Chamber of Commerce Bldg. VE Exams. Talk-in: 147.255. Lake ARA, John Wentz W8HFK, 352-728-2615. E-Mail: capias@gate.com Chuck Crittenden KE4EXM, 352-669-2075
IN - FORT WAYNE - Hamfest & State Conv. Allen County War Memorial Coliseum Expo Center. Sat: 9am-4pm, Sun: 9am-3pm. Talk-in: 146.88-. ACARTS, 219-484-1314. Web: http://www.pipeline.com/~dagagnon/
KY - HAZARD - Hamfest. Kentucky Mountains ARC, John Farler K4AVX, 606-436-5354. E-Mail: jfarler@mis.net Web: http://www.geocities.com/SiliconValley/2564/kmarc.ht
NH - MANCHESTER - Hamfest. St. John Church. IRS, Paul K1LLX 603-432-1538. E-Mail: K1LLX@juno.com
SC - MYRTLE BEACH - Beachfest '99. Old Myrtle Beach Air Force Base. 7am-2pm. Talk-in: 147.120 +600. Grand Strand ARC, Jim Wood KF4CJE, 843-238-0800. E-Mail: kf4cje@juno.com Web: http://www.w4gs.org

NOVEMBER 6-7

GA - LAWRENCEVILLE - Hamfest. Gwinnett County Fairgrounds. Talk-in: 145.45- (PL 107.2), 444.25+ (PL131.8), 146.76- (PL 107.2). Allford Memorial RC, Hotline: 770-410-3989. E-Mail: hamfest@totrbs.radio.org
TX - ODESSA - Hamfest. West Texas ARC, Robert Jordan N5RKN, 915-335-7980. E-Mail: n5rkn@apex2000.net Web: http://www.wt5arc.org Web: http://nonprofit.apex2000.net/hamfest/

NOVEMBER 7

KY - HAZARD - Swapfest. Hazard High School
MI - ST. JOSEPH - Hamfest. Blossomland ARA, Duane Durlinger KX8D, 616-982-0404. E-Mail: comdac@comdac.com Web: http://www.comdac.com/bara
WI - KAUKAUNA - Hamfest. Starlight Club. VE testing. Talk-in: 146.52 simplex. Fox Cities ARC, Chad Pennings N9PRC, 920-993-0485. E-Mail: n9prc@kb9byq.ampr.org Web: http://www.w9zl.ampr.org

NOVEMBER 13

AL - MONTGOMERY - Hamfest. Garrett Coliseum, South AL State Fairgrounds, Federal Dr. 9am-3pm. FCC exams. Talk-in: 146.24/84, W4AP. Montgomery ARC, Phil Salley K4OZN, 334-272-7980 after 5pm CST. E-Mail: wb4ozn@worldnet.att.net Web: http://jschool.troy.edu/~w4ap/
CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves
NM - SOCORRO - Hamfest. Socorro ARA, Al Braun AC5BX, 505-835-3456. E-Mail: ac5bx@juno.com Web: http://www.ees.nmt.edu/sara/homepage.html

NOVEMBER 13-14

IN - FORT WAYNE - IN State ARRL Convention & Hamfest. Allen County AR Technical Society, Doug Jones N9NNT & Jim Boyer KB9IH, 219-484-3317. E-Mail: djones223@aol.com Web: http://www.pipeline.com/~dagagnon/

NOVEMBER 14

NY - FARMINGDALE - Hamfest. Radio Central ARC, Neil Heft KC2KY, 516-737-0019. E-Mail: nheft@ibm.net Web: http://www.li.net/~n2mdq

NOVEMBER 19-20

MS - OCEAN SPRINGS - Hamfest. St. Martin Community Center. Fri: 5-9pm, Sat: 8am-2pm. VEC testing Sat: 11am. Talk-in: N5OS 145.11-. West Jackson County ARC, Phil Hunsberger W9NZ, 228-872-1499. Stan Hecker N5SP, 228-875-0222

NOVEMBER 20

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In. 619-561-0052
CO - GOLDEN - Hamfest. Jefferson County Fairgrounds, 15200 W. 6th Ave. 8am-2pm. VE testing. Talk-in: 144.62/145.22. Rocky Mountain

Radio League, Inc., Ron Rose N0MQJ, 303-985-8692. E-Mail: n0mqj@arrl.net
MA - NEWTONVILLE - Auction. Masonic Hall, second floor, 460 Newtonville Ave. 11am-4pm. WARA/1200 RC, Eliot Mayer W1MJ, 617-484-1089. E-Mail: W1MJ@amsat.org Web: http://our.world.compuserve.com/homepages/emayer/auct
OH - GEORGETOWN - Hamfest. Grant ARC, Gordon Neal W8YQW, 513-379-1659. E-Mail: wb8yqw@juno.com Web: http://www.qsl.net/~n1djs

NOVEMBER 20-21

FL - TAMPA - Suncoast Hamfest, FL State ARRL Convention. State Fairgrounds, Expo Hall. Florida Gulf Coast Amateur Radio Council, Jean Endicott KC4KZU, 727-525-5178. E-Mail:

swaps@fgarc.org Web: http://www.fgarc.org

NOVEMBER 27

NC - GREENSBORO - Hamfest. Greensboro Coliseum Special Events Center. GGH, 336-851-1676. Web: http://www.sabwc.com/gsohamfest

NOVEMBER 28

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813
NY - PATCHOGUE - Hamfest. Mid-Island ARC, Mike Grant N2OX, 516-736-9126. E-Mail: globalcm@erols.com Web: http://www.qsl.net/mid-islandarc/hamfest.html

DECEMBER 1999

DECEMBER 4

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In. 619-561-0052
GA - CLAXTON - Hamfest. Claxton ARES, John Perkins W4HYU, 912-739-4589. E-Mail: w4hyu@juno.com
LA - MINDEN - Hamfest. Minden ARA, Lowell A. "Dusty" Collins KB5WFE, 318-371-0636. E-Mail: dustyc@microgear.net Web: http://www.microgear.net/gwinford/mara.htm

DECEMBER 5

IN - GREENFIELD - Hamfest. Greenfield Central High School Pavilion, N. Broadway St. Talk-in: 145.330, 444.725. Hancock ARC, Tom Donaldson N9LFU, 317-326-3168


Roger's Systems Specialist

24895 Avenue Rockefeller
 Valencia California 91355



"We Have Great Connections"

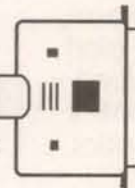Computer • Telecommunications
 Network • Audio • Video



www.rogerssystems.com

Category 5 Patch Cable

TE-038-L5	3ft. Straight Patch	\$1 ⁷⁵
TE-068-L5	7 ft. Straight Patch	\$2 ⁰⁰
TE-128-L5	14ft. Straight Patch	\$4 ⁰⁰
TE-258-L5	25ft. Straight Patch	\$5 ⁰⁰
TE-358-L5	35ft. Straight Patch	\$7 ⁰⁰
TE-508-L5	50 ft. Straight Patch	\$10 ⁰⁰
TE-758-L5	75ft. Straight Patch	\$17 ⁰⁰
TE-108-L5	100 ft. Straight Patch	\$20 ⁰⁰



USB Cables

CC-USB-6	6ft. USB "A" to "A" M/M	\$5 ⁰⁰
CC-USB-AB6	6ft. USB "A" to "B" M/M	\$5 ⁰⁰
CC-USB-PP	6ft. USB to IEEE Printer Cable	\$29 ⁰⁰
CC-USB-AB10	10ft.USB "A" to "B" M/M	\$6 ⁰⁰
CC-USB-AB15	15ft.USB "A" to "B" M/M	\$8 ⁰⁰
CC-USB-X10	10ft. USB Extension	\$6 ⁰⁰




USB Accessories

CC-USB-8	USB (2) to 2x8 pin w/ Bracket	\$5 ⁰⁰
CC-USB-9	USB (2) to 2x5 pin w/ Bracket	\$5 ⁰⁰
USB-PCI	USB x2 PCI Add on Card	\$27 ⁰⁰
USB-KB-104	USB 104-Key Kybrd Win98/PS2	\$24 ⁰⁰
USB-MOUSE	3-Button USB Mouse 4200dpi	\$12 ⁰⁰
USB-CAM	C-IT USB Cam w/ Software	\$69 ⁰⁰



Network Cards

NT-TBT-10	10-Base 16Bit ISA Slot Card	\$12 ⁰⁰
NT-TBT-100	10/100 32-Bit PCI Slot	\$19 ⁰⁰
NT-TBT-200	10-Base 32-Bit PCI Slot	\$12 ⁰⁰
NT-TBT-3C905B	3COM 3C905B-TX 10/100 PCI	\$62 ⁰⁰
NT-8460B	INTEL Pro+ 10/100 Express	\$55 ⁰⁰

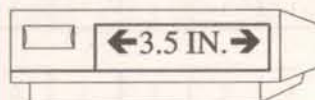

External SCSI Case

TM-CASE-HDS \$15⁰⁰

Limited to stock on hand

50 Pin centronics pass through connector
 Push button I.D. setting, On/Off switch
 Internal Fan, 50P Ribbon, 30watt Power Supply



Acer



KEYBOARD & MOUSE

KB-449	Acer PS/2 Win. Keyboard	\$8 ⁰⁰
TM-290-PS	Acer PS/2 2-button 6pin din	\$5 ⁰⁰

COMBO
 BOTH FOR \$12⁰⁰




Acer



cat. no. TM-177

ACER AMPLIFIED SPEAKER SET W/
 CABLES & POWER SUPPLY

Patch Panels

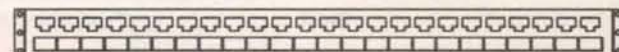

PP-24P-5	24 Port Cat5 Patch Panel	\$59 ⁰⁰
PP-48P-5	48 Port Cat5 Patch Panel	\$99 ⁰⁰
PP-12P-5	12 Port Cat5 Patch Panel	\$42 ⁰⁰
PP-64P-5	64 Port Cat5 Patch Panel	\$255 ⁰⁰

All Category 5 568B Wiring

- \$20.00 min. order required
- Add \$4.50 shipping for prepaid orders
- Prices subject to change without notice
- All major credit cards accepted
- Special offers only valid on items in stock
- California residents add tax
- Call for quantity discounts
- No out of state checks accepted

800-366-0579 661-295-5577 Fax 661-295-8777

AMATEUR ROBOTICS

NOTEBOOK

by Robert Nansel

This has been one long summer. I didn't discover until just before leaving on vacation that the code listings for my June column were omitted. Those of you who wrote to find out about TestA.asm, TestB.asm, and TestAB.asm will be glad to know you can download them from the MacRobotics website (www.MacRobotics.com).

I still don't have the I2C code for Breadbot working yet, though I do have a better appreciation of the amount of work it will take.

I just keep telling myself this multimaster I2C network idea is just too cool not to work, that it will ultimately simplify things, and I'll be able to build even cooler robots as a result.

Right now, though, it's

made hash of all my scheduled projects. It seems a good idea to talk about my motivations for going through all this grief. First, some background.

Why Multimaster?

Life is pretty simple with single-processor robots — until you try to make them do anything modestly interesting or useful in anything like real time. With more complicated tasks, you quickly find out that mobile robots are inherently multi-tasking creatures that must juggle dozens of functions at once in order to do the job.

The controller must regulate motor speeds, process sensor data, and make high-level decisions on what to do next. Single-processor code that does all this tends to be complex — buggy spaghetti code that breaks when even minor changes are made to it.

One way to deal with this complexity is to factor out the separate

functions, write code modules to handle each function, and then run each module as a separate process within a realtime operating system (RTOS). Depending on the RTOS and the robot, this may be the best approach provided the processor has enough horse power to handle the task-switching overhead.

Another way to approach the complexity problem (the one I've chosen) is to use separate, loosely-coupled processors to handle the individual modules. This has the advantage that you can completely isolate the behavior of each module from all the others.

Adding new modules won't directly affect the execution time of other modules, and you can use specialized processors tailored for certain tasks.

A disadvantage is that each processor must devote resources to interprocessor communications. Also, a module may depend on data that must come from another processor (and the sending/receiving delays that entails), and the sys-

tem can be more complicated to develop code for and to debug.

Multiprocessor systems can be hard to program because defining exactly how the processors should interact with each other is not trivial.

The simplest multiprocessor system is a processor and coprocessor combination where the coprocessor performs well-defined operations in response to commands or data from the main processor and returns data to the processor indicating the results of the operations and the status of the coprocessor.

An MPU with a separate math coprocessor chip is an example of this type of system. A much simpler example is the microcontroller in every PC keyboard.

The defining characteristics of such coprocessors are they use dedicated ports to interface to the host processor, the interface protocol is point-to-point, and the protocol is very simple, typically involving simple hardware handshaking.

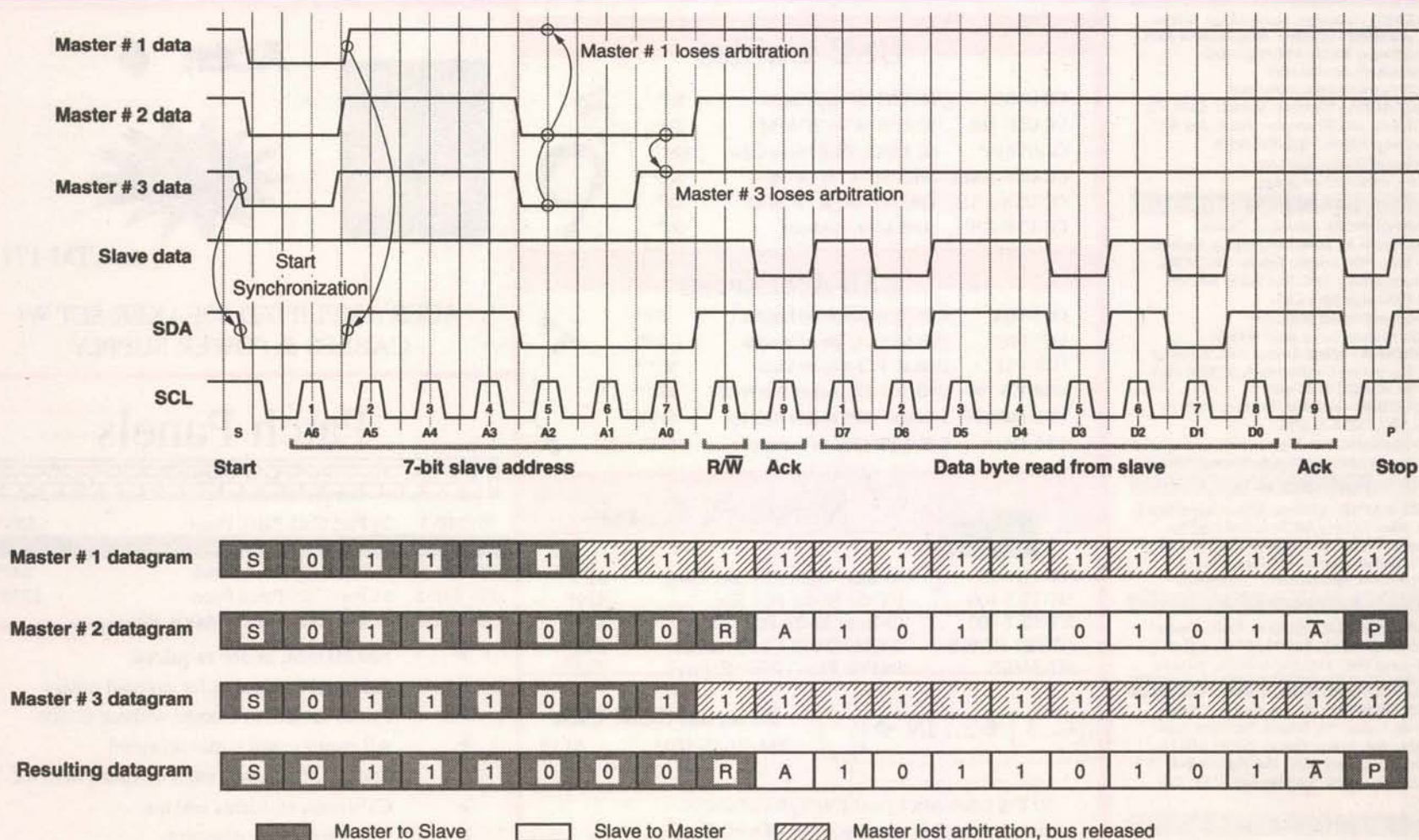


Figure 1: I2C Bus Multimaster Arbitration

Ties that Bind

Such tightly-coupled systems require the developer to know intimately the code and hardware of every processor in the system. Establishing the logical connection between the data one processor provides and another processor consumes is called binding.

In general, binding can occur at any stage in a system's development from initial design — early binding — to field configuration — late binding. Because processor/coprocessor architectures require very early binding, adding additional coprocessors always means a substantial code rewrite.

But what if you want a system that allows arbitrary expansion without rewriting code every time you add a new coprocessor module? Any early-binding system won't get you there unless you program it to handle every possible coprocessor add-on that you or others might devise; an unlikely prospect.

This applies to any tightly-coupled multiprocessing scheme regardless of the interface technology and is a direct consequence of early binding. In essence, early binding requires every module to know too much about every other module.

Publish and Subscribe

If early binding won't do the job, what about late binding? Late binding doesn't entirely remove the need for modules to know — or at least assume — details about each other, but it does reduce the amount and specificity of knowledge required. Such data hiding is highly desirable for systems where modules from different developers will be combined.

The ideal is a peer-to-peer network architecture where each processor is treated equally. It's not enough, however, for a module to conform to the interface protocol, to know how to send data to and receive data from the network. It must also know the logical interpretation of the data.

tation of the data.

In the case where every module is developed by different people, this can be a very difficult job indeed unless there are some data conventions agreed upon ahead of time. First, you need the idea of a network variable, a data abstraction similar to data types in structured programming languages; one node provides the value of the network variable and one or more nodes can use that value in their operation.

Implementing such network variables requires a common set of predefined procedures in each module for defining and initializing network variables, for binding data sources with data destinations, and for transparently propagating the

values of network variables across the network. Along the way, it's handy to come up with a set of predefined network variable types ("PNVT," pronounced "pinvit") which any module knows how to interpret.

Any module with data another module needs "publishes" that data in the form of assignments to PNVTs, and any module that requires information from outside itself must "subscribe" to the relevant PNVTs. Neither the publisher nor the subscriber needs to know very much about each other, only what PNVTs they have in common.

If there are no modules subscribing to a certain PNVT, then the module that would otherwise publish that PNVT could decide — in

Figure 2: I2C Clock Stretching

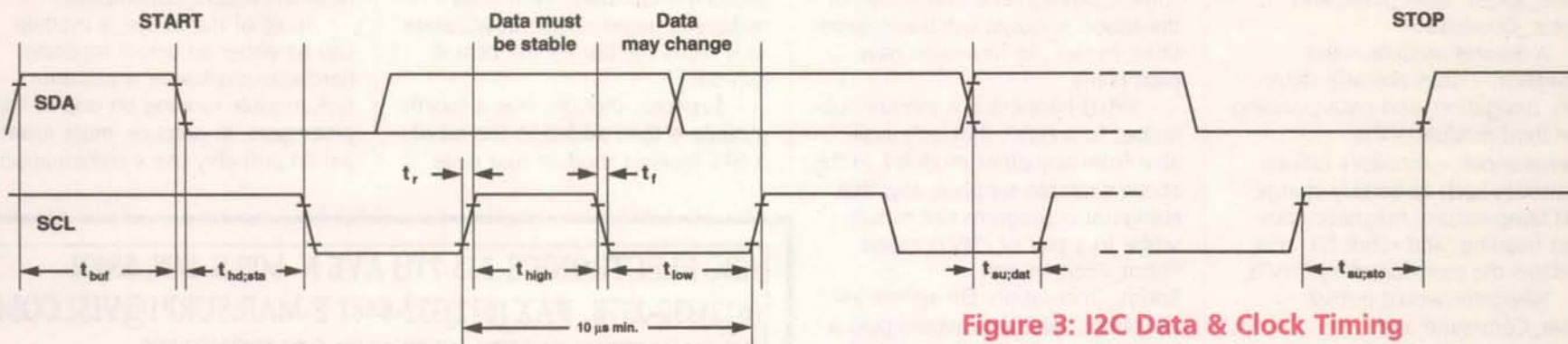
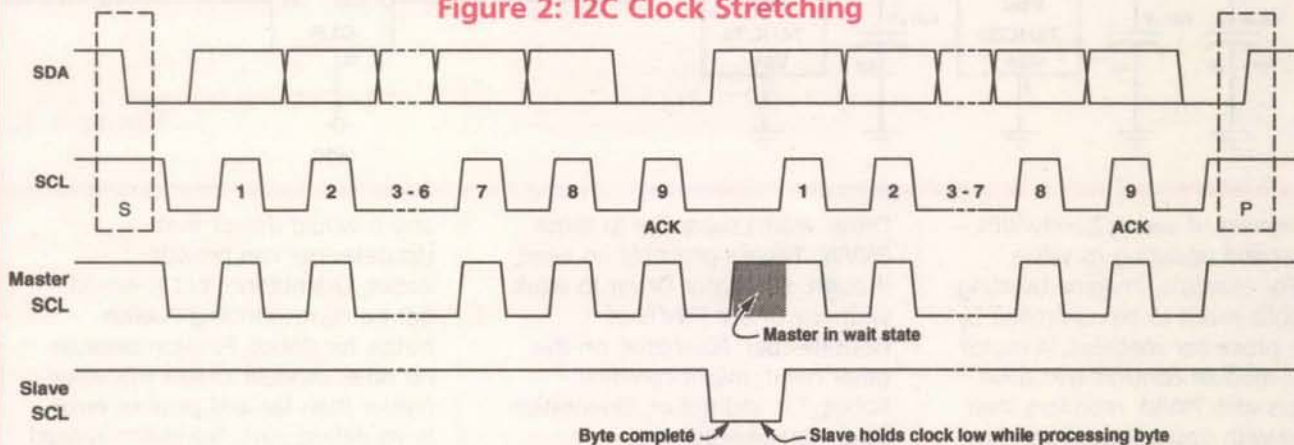


Figure 3: I2C Data & Clock Timing

WIDGETS

Sensors to RS232, 422 or 485

Starting at \$199

PRESSURE
THERMOCOUPLE
RTD
VOLTAGE
CURRENT
MOTION
GASES
RH
And more

Each system comes complete with one sensor, 10, 12 or 14 bit resolution w/ 7 extra channels of A/D, 30k of remote data storage, power supply, serial cable and WINLP-Lite data acquisition software (trending, storing and display)

1-888-597-3588

(530) 647-2028

LEMON-PLADD INC. FAX (530) 647 8951
PO BOX 1683 POLLOCK PINES CA. 95726
WWW.LEMONPLADD.COM

Write in 140 on Reader Service Card.

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200


- Correct implementation of manufacturer specified algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.

Available Adapters

EP-PIC (16C5x, 61, 62x, 71, 84)	\$49.95
EP-PIC84 (16C62-5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (88HC11 E/A)	\$59.95
EP-11D (88HC711D3)	\$39.95
EP-16 (16bit EPROMs)	\$49.95
EP-28 (286E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (ICT22v10, 18v8)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

M²L Electronics

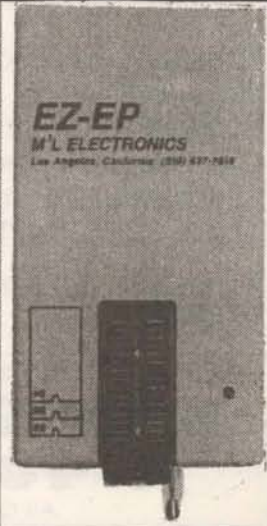970/259-0555
Fax: 970/259-0777
250 CR 218
Durango, CO 81301
CO orders please add 7% sales tax.
<http://www.m2l.com>



Write in 139 on Reader Service Card.

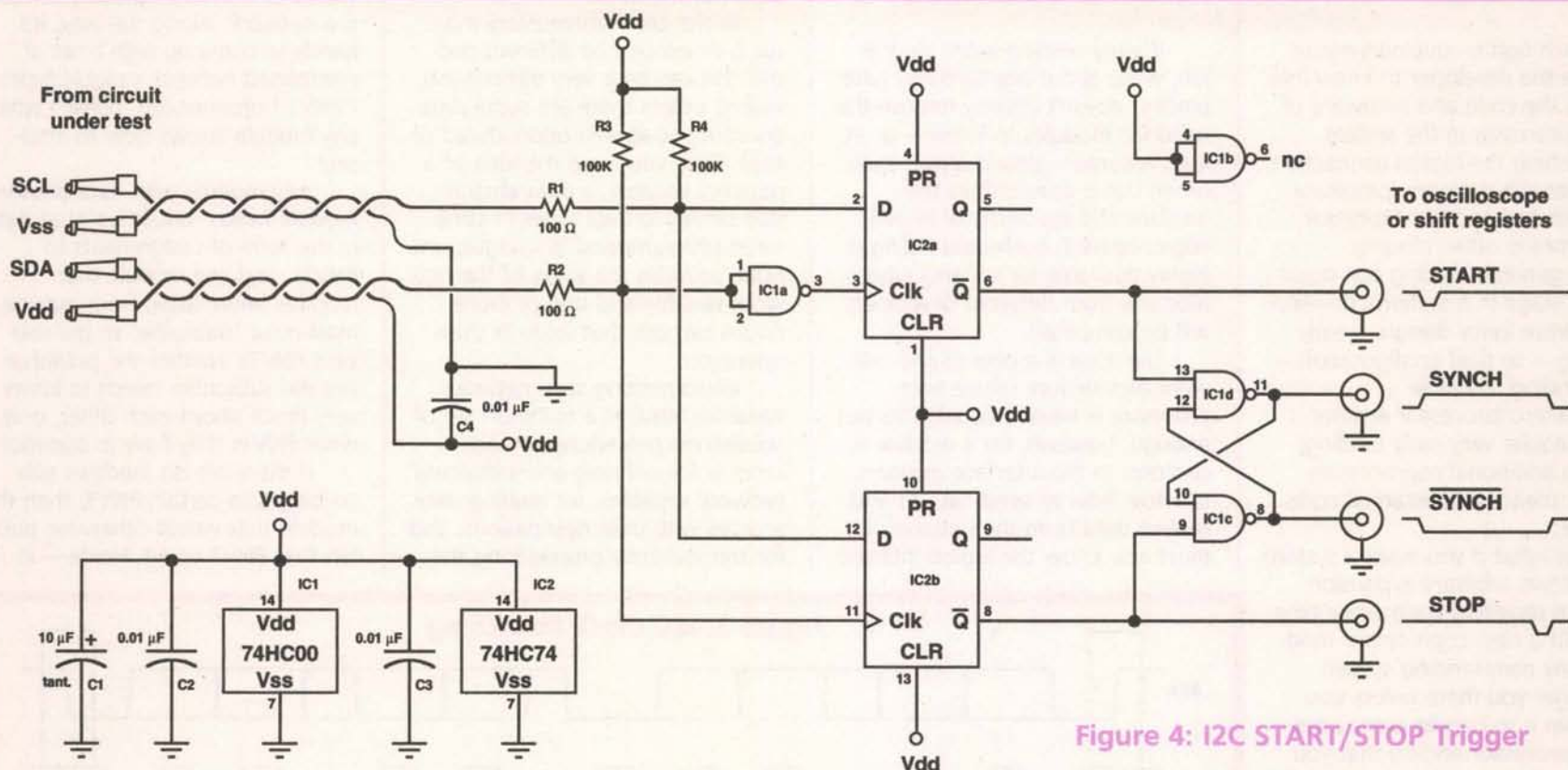


Figure 4: I2C START/STOP Trigger

the interest of saving bandwidth — to suspend updating its value.

For example, imagine building a mobile robot to be controlled by three processor modules. A motor driver module controls two drive motors with PWM, monitors their speed with optical encoders, measures the motor currents, and periodically updates three PNVTs: Drive_Speed, Steer_Rate, and Motor_Overload.

A second module — the Navigator — does obstacle detection, navigation, and path planning. The third module — the Housekeeper — monitors various quantities such as battery charge and temperature, magnetic compass heading, and robot tilt, and updates the corresponding PNVTs.

Navigator would publish Drive_Command and Steer_Command PNVTs and Motor

Driver would subscribe to those PNVTs. There's probably no need, though, for Motor Driver to work with any of the PNVTs of Housekeeper. Navigator, on the other hand, might combine Robot_Tilt and Robot_Orientation from Housekeeper with Drive_Speed and Steer_Rate from Motor Driver to dead reckon the current position and orientation of the robot. It would use these quantities, in turn, to formulate new path plans.

What happens if a module subscribes to a PNVT that isn't available from any other module? In the above example suppose, say, that Navigator is programmed to subscribe to a pair of PNVTs called Robot_Position and Robot_Orientation. On system initialization, Navigator would post a Subscribe notice for these PNVTs,

and it would detect that Housekeeper can provide Robot_Orientation, but it would get no corresponding Publish notice for Robot_Position because no other module knows this value. Rather than fail and post an error to its debug port, Navigator instead falls back on the dead reckoning algorithm mentioned above. The position it calculates with dead reckoning might not be as accurate as it could be, but it's the best it can do.

Suppose, though, that a fourth module is then added to the robot, a GPS receiver module that does

nothing but publish Robot_Position. When GPS initializes and posts a Publish Robot_Position PNVT, Navigator would detect this and switch to getting Robot_Position directly from GPS. Likewise, if a gyrocompass module were added, Navigator might choose to subscribe to Gyro's Robot_Orientation PNVT instead of the one derived from the magnetic compass.

In all of the above, a module can be either an actual separate hardware module or a real-time task module running on one of the processors. In practice, most robots would probably use a combination

Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145 Regal w/Remote	\$45	\$40	\$35
BC4535 86 Channel	\$38	\$35	\$30
Oak Sigma 99 Channel	\$30	\$28	\$25
75 Channel Converter	\$45	\$40	\$35
Zenith ST1600 w/Remote	\$18	\$18	\$18
Panasonic Converters Model-175 (550MHz)	\$75	\$70	\$65
Panasonic Converters Model-175 (550MHz)	\$65	\$55	\$45

Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!

SAM'S ELECTRONICS
1-405-631-1856

All Cable Equipment is unmodified.

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 54501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4355A TRANS. IMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 54200A 50MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$850.00
HP 5370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC. ANALYZER	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG.O-SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP 8558B/181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7B80 400MHZ TIME BASE	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7B92A 500MHZ DUAL TIME BASE	\$125.00
HP 1740A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7S12 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A. POWER SUPPLY OPT.J01	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6643A 45VDC-4.3A POWER SUPPLY OPT.J03	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

of the two module types. In defining a Publish and Subscribe network variable architecture, it's important for future flexibility to make sure that Publish and Subscribe work the same between tasks running on the same processor and tasks running on separate processors communicating over a network interface.

For the time being, though, I want to concentrate on implementing PNV Publish and Subscribe in a networked multiprocessor environment. Because I2C is low-cost and has clearly defined multimaster capabilities, it lends itself well to this project.

Multimaster I2C

Very few systems I've seen actually exploit the full multimaster capabilities of I2C — most I2C systems consist of a single master and a small number of slaves. You can find example code for lots of single-master I2C systems on the web, but I've yet to see a complete multimaster implementation. Multimaster mode is quite a bit more complicated to figure out and program, but the rewards of multimaster mode are compelling. So, how exactly does it work?

Figure 1 shows three masters attempting to access the I2C bus simultaneously. With most bus systems, this would spell disaster without some sort of arbitration mechanism built in to sort out which master would actually get to use the bus.

By its nature, I2C automatically takes care of most of this by mandating open-drain drivers for each node connected to the bus. After asserting a valid START condition, any node can output a logical one or a zero during each bit time but, if it outputs a one, it must always look at the SDA line afterward to make sure that SDA actually does go high.

If it does, all is well, and the node may continue sending data bits (I say "data," but what the bits represent in the datagram is of no consequence; address or data, it doesn't matter, they are treated equally).

If, however, the SDA line is low when a node has just output a logic high — and there's been enough time for the line to be pulled high (this can take as long as a microsecond) — then the node must stop sending data on the bus because it has just lost arbitration with another node.

The first time I read about I2C bus arbitration, I couldn't understand how it could be possible for two or more nodes to try to transmit at the same time without the

data of all of them getting corrupted. The key to understanding how it works is that arbitration takes place sequentially as each bit is placed on the bus. Any number of nodes can output high levels on SDA, but if just one node outputs a low, that is the level SDA will take.

For every bit sent, therefore, a transmitting node is obliged to check that the level of SDA matches the level the node sent. For a low level it should always match (unless there is a short circuit somewhere) but, for a high level, it will only match if no other node is sending a low level.

Table 1: I2C Bus Specifications

PARAMETER	SYMBOL	Min	Max	UNIT
SCL clock frequency	f_{scl}	0	100	kHz
Bus free time between START and STOP	t_{buf}	4.7	—	μs
Hold time START condition	$t_{hd;sta}$	4.0	—	μs
LOW period of SCL	t_{low}	4.7	—	μs
HIGH period of SCL	t_{high}	4.0	—	μs
Data set-up time	$t_{su;dat}$	250	—	ns
Rise time for SDA and SCL	t_r	—	1000	ns
Fall time for SDA and SCL	t_f	—	300	ns
Set-up time for STOP	$t_{su;sto}$	4.0	—	μs
Capacitive load for each bus line	C_b	—	400	pF

And the Winner is ...

Let's tie all this together by following the bit arbitration process as it unfolds in Figure 1. Three masters are attempting to access the bus: Master #1 wants to send binary 0111100 in the address field of its datagram; Master #2 wants to send 0111000; and Master #3 wants to send 0111001. Note that Master #3 asserts START a smidgen before the other two, and the time of the falling edge of SDA is thus determined by Master #3.

The first bit sent is the MSB of the seven-bit address, which is zero for all three masters. The next bit is

a one, again the same for all three masters. Notice Master #1 is the last to release SDA to assert logic one in this example, so it determines the time of the rising edge of SDA. Bits 3 and 4 (A4 and A3) are also ones for all three masters. None of the masters are aware that any other master is trying to use the bus because the bits sent so far have been identical when SCL goes high.

With bit 5, though, the situation is different. Master #1 wants to send a one, but the other two are sending zeros. Since the SDA line is open drain with only a passive pullup resistor, a zero output


ADDRESSABLE STEPPER MOTOR CONTROLLER

Part Number: JWP1X-1A

\$199.95

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data throughput rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

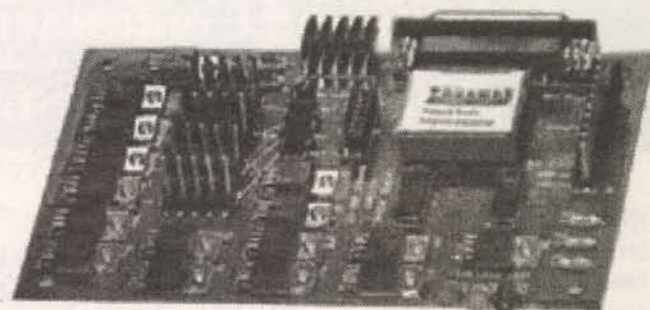Also available at:
FORD ELECTRONICS, INC
(714) 521 - 8080



PARAMAX INC.
(800) 473 - 8080

Come and visit us on the internet at:
www.paramax.net

by a node always overrides a one output by any other node.

After Master #1 asserts one, it therefore detects that the SDA line doesn't go high, and it must abort its transmission by leaving its SDA output high for the rest of the datagram.

The same thing happens to Master #3 when the seventh bit (A0) is sent, leaving Master #2 in sole control of the bus. If all three masters had been sending the exact same address, then arbitration would continue to the ninth bit, R/W. If Master #3 intended to write data to the addressed slave and the others intended to read, then Master #3 would win the arbitration because it sends a zero during the R/W bit time to indicate a write operation, while the others would send one.

What if all three masters were to attempt a write operation to the same slave? Simple. Arbitration would continue for each bit of the data byte until one master or another sends a one when the others send a zero. And what if the byte they are sending is identical? None of the masters would ever know that it wasn't the only one transmitting, right? Even in this unlikely case, everything still works out fine because the data value each of them wanted to send is what the slave receives. Neat, huh?

Clock Stretching

So far, I haven't said anything about the clock line, SCL. SCL is always generated by the master on an I2C bus, but in a multimaster system, there can be more than one master attempting to transmit at once, and each is generating its own clock. How does this affect the bus?

First, remember that SCL must be driven with open-drain drivers, just like SDA. As above for SDA, the time of the falling edge of SCL

is determined by the first master to pull SCL low, but the rising edge is determined by the last master to release SCL. In this way, the slowest master determines the period of time that SCL stays low, while the fastest master determines the period that SCL stays high. But that's not all.

In some circumstances, a slave can hold SCL low, too. Figure 2 shows a slave pulling SCL low right after receiving a byte from a master. The slave holds SCL low until it has finished processing the byte just received from the master.

After the master releases SCL, it detects that the line is still low and is obliged to go into a wait state until the slave releases SCL. This mechanism can be used by any node, master or slave, to ensure no transmission goes faster than the node can follow. The maximum clock rate for standard-mode I2C is 100 kHz. In practice, though, the bus only goes as fast as the slowest node on the network.

Trigger Happy

There are a lot of subtleties in the I2C system. Writing a software-only multimaster compatible master is exacting but not difficult because the data timings are all quite relaxed (see Figure 3 and Table 1). Software slaves, however, are another story. At first glance, it seems that to catch a START condition at full speed, a slave must sample the SCL and SDA lines at least twice every 4.7 microseconds during the bus free condition; this is less than 12 processor cycles for a 10 MHz PIC16F84. I don't yet know how to write a program that does this while doing any other useful work, such as generating control pulses for servos.

I'm taking things by stages, therefore, and the first stage is to write multimaster-aware code for a master. As part of debugging, I

need to be able to look at the waveform my code generates to check timing relationships. The problem, however, is how to get my scope to reliably trigger at the right place on the waveform; I2C waveforms are complex and offer no convenient trigger signatures to trigger on with a simple analog 'scope. Figure 4 shows a circuit I built that solves this problem.

Since a START is defined as SDA going low while SCL remains high, all that is necessary is to use SDA to clock the state of SCL into a D-type flip-flop. You want to clock on the negative-going edge of SDA, but since the 74HC74 dual D flip-flop clocks on positive-going edges, you must invert SDA. The STOP condition is detected with the second D flip-flop in the HC74; no inversion of SDA is needed since the STOP condition is defined as SDA going positive while SCL is high.

I used one gate of a quad 74HC00 NAND to do the inversion for the START detector, and two more NAND gates to form a simple SR flip-flop. The pulse lengths of the active-low START and STOP outputs depend on the data pattern being transmitted. The SYNCH pulse output (and its inverted version), however, will always be the same length as the I2C datagram itself, regardless of the data pattern being transmitted.

I provide all four signals on BNC connectors for maximum flexibility. I can directly hook any one of them up to the external trigger input of my 'scope. All my software has to do is send the same datagram often enough that I can see the datagram on the scope without flicker. The circuit could also be used with shift registers and latches to directly capture datagrams if you don't have an oscilloscope, or if you want to capture one-shot events.

The circuit draws its power from the circuit under test and was

built on a RadioShack protoboard (#275-150). The test probes are clip-ons, also from RadioShack. As the I2C spec calls for, I twisted SCL with Vss (ground) and SDA with Vdd (power) to reduce noise pick-up. C4 decouples Vss right at the point where the wires leave the circuit board, and C1 through C3 decouple the ICs.

I also included 100-ohm resistors to protect the inputs from voltage transients and weak 100K pullup resistors to ensure valid logic levels when nothing is connected to SDA or SCL. Layout isn't critical, but do keep all test leads shorter than 12 inches.

Once I have this code running right, then I'll tackle the harder problem of the slave code.

Two Tiny Teeth

Whew! The weather has started to cool to tolerable levels around here, and my son Yonatan finally cut his first two teeth. There was a while last month when I wasn't sure either event would ever happen. Then, too, I also got my Linux box up and running, almost as excruciating a process for me as teething was for Yonatan. Definitely a five-beer project, and I'll tell you all about that and more next time. **NV**

As always, if you have suggestions for improving Breadbot, or if you've built a Breadbot, or if you have questions or comments about amateur robotics topics, you can reach me at:

Robert Nansel
69 S. Fremont Ave. #2
Pittsburgh, PA 15202
E-Mail: bnansel@nauticom.net

Identify and Control with Radio Frequency IDentification

Tags/Transponders, Antennas, Reader/Decoders

RFID for access control, factory automation, timing, animal feeding, ticketing, vehicle identification, inventory control, datalogging, pallet tracking, personnel security, asset management, ...

Development kit
US\$ 179.00


Since 1991

INTERSOFT

1840 Lockmill Rd, Estill Springs TN 37330, USA

Tel: 1-931-967-8643 Fax: 1-931-967-5069

<http://www.cafes.net/intersoft>

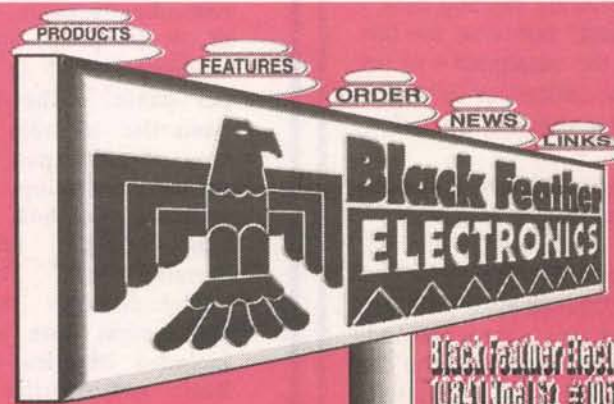

Black Feather Electronics
10841 Noel St. #103
Los Alamitos, Ca. 90720

DIRECT DIAL: 714/236-1778 FAX: 714/236-1778 E-MAIL: bjkred@juno.com

WWW.BLKFEATHER.COM

WE BUY EXCESS/SURPLUS ELECTRONIC SUPPLIES

Continued from page 68

Dear Nuts & Volts:

There are worse things than not getting the answers requested in a Tech Forum question — that is getting incorrect information. Chris from Bieber, CA provided multiple incorrect answers to two different questions.

In the answer to question #7994, in the US standard television system, the number of total scan lines is 525, not 480. Depending on the exact number of lines devoted to retrace blanking, vertical synchronization, test signals, closed captioning, etc., the actual number of visible scan lines range from 483 to 487.

The 480 lines that Chris refers to is actually the number of visible vertical pixels in the VGA computer screen and has no relationship to a television signal. This is the first error in providing incorrect information. All video cameras used in a US television system would have 525 scan lines. Exactly one-half of these lines are scanned in approximately 1/30 of a second with an interlaced set scanned in the next 1/30 of a second.

The basic question in television camera specification is the vertical lines of resolution in the horizontal axis. In the conventional manner, this is defined as the total number of alternate black and white vertical lines that can be resolved by the eye in the central 3/4 of the width of the screen. This is usually performed by viewing a standard test target having resolution wedges with varying the density as it would be too cumbersome to count the lines individually.

A good black and white tube camera (with a high quality black and white monitor) would be expected to have a resolution of around 600 lines. Color systems have a resolution generally in the range of 330 to 450 lines. Moderately priced CMOS or CCD cameras generally do not have this resolution.

The number reported in the advertisements should report resolution in this manner — equivalent to the number of vertical black and white lines in a width equal to the height of the screen. It is unknown if any of them actually do. The comment by Chris about a 410 line camera having less information than a 480 line system is totally incorrect.

The CMOS cameras have another characteristic — the actual number of image capturing pixels in both the horizontal and vertical dimensions. A camera actually having a resolution of 410 lines as specified above would have 547 pixels horizontally and 410 vertically for a total of approximately 224,000. This assumes an optical system with no defects. Most cameras advertised in *Nuts & Volts* do not specify the number of pixels in either axis.

The unit of illuminance is the lux which is defined as the illumination provided by an incident intensity of one lumen per square meter. The illuminance provided by a full moon is approximately 0.3 lux. The ability of a camera to see an object with this illuminance depends on the reflectivity of the object, the color of the object, and the spectral sensitivity of the camera.

It is unknown to me what is the spectral response of these cameras although all of the black and white CMOS cameras do have some sensitivity in the infrared range. The statement of .3 lux being equal to 0.3 candle per cubic meter of space is total gibberish. Lower lux numbers do indicate that the camera will provide some kind of a picture at lower light intensity.

The dimension usually given in millimeters (mm) is the focal length of the lens, not the width. Lower numbers indicate a wider view while higher numbers indicate a narrower view (more telephoto). However, the f number of the lens

must also be taken into consideration in order to maintain the lux sensitivity. The f number is the ratio of the focal length to the diameter. As the focal length of the lens increases, so must the diameter for the same sensitivity. Also, longer focal length lenses generally must be adjusted for correct focus while the wide angle lenses (under say 4mm) generally are in focus from relatively close in to infinity.

In the answer to question #7992, the first sentence is double talk — impedance is a function of the winding and frequency, not an inherent characteristic, but altering the frequency will not necessarily overheat the windings unless the frequency is made much too low.

What is true is that the normal single phase induction motor will not work correctly due to the failure of the eddy current induction in the rotor at low frequencies. Note, however, that many modern locomotives are now using AC synchronous motors with a DC excited rotor and variable frequency stator drive for wide speed control.

A so called "universal motor" such as that used in most portable electric tools will work even down to DC. These motors have the rotor connected in series with the stator through a commutator and brushes. A variable width, fixed frequency pulsed waveform will nicely control these motors. See how a variable speed drill works. If your motor has brushes, give the light dimmer (or drill motor speed control) a try.

An induction motor will not behave so nicely. As the voltage is lowered, the motor speed will fall but the torque will fall off faster, the back EMF will fall off, the current will rise, and the motor will stall. These motors are essentially designed to run at a constant speed with a designed voltage and do not behave well at drastically lowered voltage.

A Variac® does not consist of transformers that move in relationship to each other but is rather an autotransformer (with only one core and winding) and a movable sliding tap. It is like the AC equivalent of a potentiometer except that the output voltage can be greater than the input with the proper configuration of winding and taps.


In any event, there is no way a Variac could maintain a totally constant current while lowering the voltage even if this would control the motor speed in the desired manner.

I would hope that some of the responses from readers would

Go Wireless!


Its easy for just \$9.95 ea.

Digital Input, RF Output

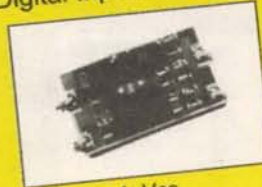

Pin 1: Vcc
Pin 2: Gnd
Pin 3: Digital In
Pin 4: Antenna

Antenna Input, Digital Output

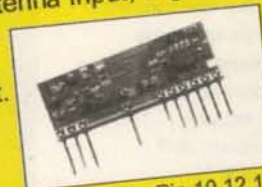

Pin 1: RF Vcc
Pin 2,7: RF Gnd
Pin 3: Antenna
Pin 4,5,6,8,9: NC
Pin 10,12,15: Digital Vcc
Pin 11: Digital GND
Pin 13: Audio testpoint
Pin 14: Digital Out

Transmits 150 ft.
2K Baud

Great for use in:
• Home Automation
• Remote Controls

• Remote Sensors
• Signal Presence
• much much more!



CONVERGENT INC.

1-888-577-7285, 716 River Crest, Leander, TX 78641
www.convergentinc.com/radio

have some reality and accuracy check before publication. These answers were unbelievable. I think that I have seen some questionable answers from the same Chris before. If this is true, I suggest that you check his qualifications before publishing his answers. I am a retired Electronics Engineer with extensive analog, video, and RF experience and have been a licensed radio amateur since 1953. While my new home is under construction at the present time, I do not have any convenient E-Mail or Internet access, so I must rely on the snail mail.

John E. Lemmer
Willits, CA

Dear Nuts & Volts:

I'm sorry to have to inform you that virtually everything in the answer published to question #7992 in your Aug. '99 issue, is misleading or plain wrong.

A variac is an autotransformer, but everything else said about it is incorrect. It is totally unsuited for speed controlling a single-phase motor, as is a light dimmer. Speed controlling a single-phase AC motor is possible, but so difficult that it is rarely done. That is why treadmills are made with DC motors. I would have suggested that the questioner look for a treadmill motor, and, ideally, a matching controller.

Robert Via Internet


LIGHT WORKS USA™

By Miller Engineering

Electroluminescence
Experimenters Kit!

\$22.95 plus \$3.00 S&H

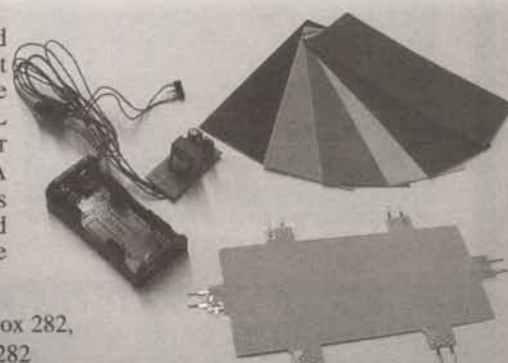This exciting kit is designed just for the experimenter! Kit includes one 1.7" x 3.75" white EL lamp that makes up to 6 EL lamps. Ready to run power supply that runs on two AAA batteries. Six color overlays and complete instructions and ideas on using this space age marvel.



Send To: Miller Engineering, P.O. Box 282,
New Canaan, CT 06840-0282

Tel. 203-595-0619 Visa & Mastercard accepted. Personal checks must clear first. www.microstru.com

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

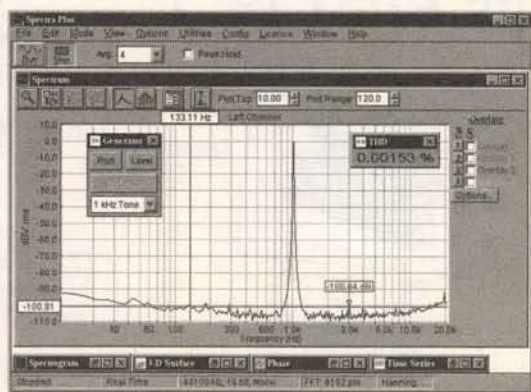- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only – not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.

Spectra Plus
FFT Spectral Analysis System

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

Write in 81 on Reader Service Card.

Serial in, graphics out. Almost too easy.

These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at www.seetron.com. All models are in stock for immediate delivery.

G12032
120x32-pixel LCD
SQX-120L **\$99.00**

Same size as 2x16 text LCD
Editable font(s) in 4 sizes
Up to 6 screens in EEPROM
Easy terminal protocol



(3.2 x 1.4 in.)



(3.7 x 2.8 in.)

G12864
128x64-pixel LCD
\$199.00 BGX-128L-1

Large, sharp LCD
Editable font(s)
Up to 14 screens in flash
Separate text, graphics layers
DB9 connector built in
AC adapter jack built in
Easy terminal protocol

www.seetron.com

Scott Edwards Electronics, Inc. ph 520-459-4802 fx 520-459-0623 nrv@seetron.com

Write in 82 on Reader Service Card.

TECH FORUM

Continued from page 31

Fifteen inch VGA monitors are a dime a dozen nowadays and it would probably be easier to buy a new or refurbished one. But, if you still want to make a cable, I have included the pin-outs for EGA and VGA (which is also the same for SVGA and all types of Ultra VGA).

The CGA pin-outs are the same as the EGA with a few exceptions. Pin 2 is also Ground, pin 7 is not used, and pin 6 is Intensity.

EGA pin-outs:

PIN	SIGNAL
1	Ground
2	Secondary Red
3	Red
4	Green
5	Blue
6	Secondary Green
7	Intensity
8	Secondary Blue/
9	Mono Video
	Horizontal Sync
	Vertical Sync

VGA pin-outs

PIN	SIGNAL
1	Red
2	Green
3	Blue
4	Monitor ID Bit 2
5	Digital Ground
6	Red Analog Ground
7	Green Analog Ground
8	Blue Analog Ground
9	not used
10	Sync Return (GND)
11	Monitor ID Bit 0
12	Monitor ID Bit 1
13	Horizontal Sync
14	Vertical Sync
15	not used

Chris
via Internet

ANSWER TO #8999 - AUG. 1999

I need information on how to hook up a "Rustrak" model 288 strip chart recorder. A current address for this company would be helpful, too.

Richard can contact the compa-

ANSWERS TO #7997 - JULY 1999

I have an 800 number on which I would like to deliver a three-minute message to callers, with a hang up at the end. The machine would not accept any incoming messages. Any ideas?

#1 Most answering machines can be set to "Answer Only" which will cause the machine just to play an outgoing message and then hang up. You may, however, have to do some shopping around to find an answering machine which allows you to record a three minute outgoing message.

Most machines limit the outgoing message to a minute or less. If you are expecting lots of calls to be made to your 800 number, I recom-

ANSWERS TO #8992 - AUG. 1999

I have an IBM Thinkpad computer. The hard drive is missing and I cannot get into CMOS. How I can tell it that it has no hard drive and boot on a floppy?

Also, where can I find a hard drive?

#1 I enter my IBM Thinkpad boot sequence control by pressing and holding F1 while turning on power. This should get you to "Easy Setup" where you can select the "Start Up" control section.

Ed Bell
Colchester, VT

#2 Depends on the model of your Thinkpad, but the hard drive should be a 2.5 inch drive. They can be found on the Internet or from a supplier such as "MegaHaus" 1-800-786-1153.

You should also then go to IBM's tech support on the Internet and download the set up for your Thinkpad (www.pc.ibm.com/us/thinkpad/index.html).

I bought a Thinkpad at the Dayton Hamvention and had to do the same as you need to do.

Bob Boehm
Cincinnati, OH

ny at Gulton Rustrak, 1015 E. Chapman Ave., Fullerton, CA 92831. 714-879-6385.

Bob Morrisette
via Internet

ANSWER TO #89918 - AUG. 1999

I have a Dentron linear amplifier that is no longer in production. I fixed the problem that caused arcing between the plates of the variable capacitor, but they keep arcing. I tried to file them smooth, but they still arc, so I tried looking for another variable capacitor, to no avail.

Perhaps the variable capacitor is not the problem. Your antenna or another part of the matching network may have failed, causing a large mismatch. The large mismatch

mend that you consider only tapeless digital answering machines for more dependability.

John W. McMichael
via Internet

#2 I recommend that you use a digital announcer. These tapeless telephone message repeaters are available from several sources. Here are two possible units:

1. Racom Products, Inc., Model 900L, www.racominc.com, 1-800-722-6664.

2. Viking Electronics, Model DVA-3003, www.VikingElectronics.com 715-386-8861.

Thomas Black
Folsom, CA

TECH FORUM

would create the high voltages that cause the arcs. Check all the components, and then try out the amplifier with a dummy load. You might also clean everything.

Variable capacitors are pretty simple, so I would expect you could repair one as long as the bearings were still intact. A file is a bit crude and will not leave a smooth surface, so you might touch things up with fine sandpaper, but the file or the sandpaper will wreck any silver plating.

The capacitor should not be so close to the breakdown voltage that a little roughness matters. That's why I suspect other problems.

Gerald Roylance
Mountain View, CA

ANSWER TO #89913 - AUG. 1999

Is there a way to connect a phone hand-set to a computer to take the place of the microphone and speakers when making an Internet call?

Most telephones use carbon microphone elements, so you will need to build a circuit to power the carbon element, however, most of the really "cheap" phones and many "electronic" phones (the type used with electronic KSUs or PBXs) use a dynamic microphone and speaker. I used a cheap handset that had a dynamic mic and speaker for my computer phone.

The connection is a narrow RJ-11, the mic connection is the two

outside pins and the speaker is the two inside pins. That equates to pins 1 and 4 to the mic and pins 2 and 3 to the speaker, polarity is not important and pins 3 and 4 may be connected together if you need mic-speaker-ground.

Bob Boehm
Cincinnati, OH

ANSWER TO #8997 - AUG. 1999

I have scrapped out several loads of computer boards for the gold in them.

I was told that there is a place that buys the programmable chips and reuses them.

Here are two companies that recycle ICs on a large scale:

Fox Electronics

686 North King Rd.
San Jose, CA 95133-1709
(408) 929-4369
(408) 929-4373 fax
<http://www.foxelectronics.com>

Krueger Company

1544 W. Mineral Rd.
Tempe, AZ 85283
(800) 245-2235
(602) 820-5330
(602) 820-1707 fax

They pay a bit more than scrap value, but don't set your expectations too high.

David DiGiacomo
San Francisco, CA

ANSWERS TO #7999 - JULY 1999

I changed out the video head on my VHS VCR. The picture had horizontal noise lines. This resulted in a picture that was normal on the bottom third of the screen. The top two-thirds of the picture was half-washed, blurry, with about 20 snake-like waves moving up the screen.

What is the cause and remedy to this problem?

#1 There are many factors that stop a VCR head from operating properly. Physical alignment of the mounting springs, worn bearings in the motor, magnetized head, belts slippage in the capstan wheel causing a timing error, and the list goes on.

There are many things that you can do to fix these problems from degaussing the head to checking the bearings that support the head. But the list is long and these checks may or may not fix the problem simply because the head may be physically worn out [missing some chrome plating].

Your best bet is to purchase a service booklet for any brand VCR and go down the list as instructed and learn as you go.

What you have to consider most when working on a VCR these days is the complete replacement price of the VCR versus the total repair price.

Unfortunately, the manufacturer wants you to buy a complete new unit and thus they price their parts way out of proportion so that you will buy a complete unit rather than fix the old.

Chris Bieber, CA

#2 Before changing the video head, I hope you checked the following:

1. The tape itself. 2. Clean heads first. 3. Check video cables for breaks from TV to VCR. 4. Check VCR jacks and TV jacks.

If you did, you should next check connection to video head to circuit board making sure you connected the heads properly so there are no shorts.

With troubleshooting, always check from the outside first. Check the obvious first and the difficult last. If the connection is okay, next check the tracking system, because more than likely it will need an adjustment if the heads were bad. Check the drive tire or belt tire for slipping, inspect for wear. Check tape guide, brake, and capstan.


If tracking is all okay, check board with voltmeter. You may need to get a manual for this. This procedure is to find the problem.

Mike Clemente
Mays Landing, NJ

Digital Storage Oscilloscopes From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

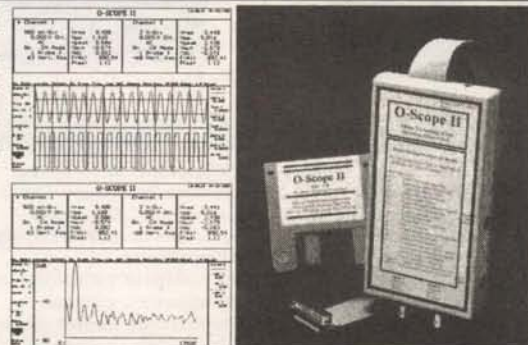O-Scope Ip \$189.
O-Scope II \$349.
Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit.

Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems ???
Check out Serial !! Our lowcost serial channel analyzer only \$99.00.

Allison Technology Corporation

2006 Finney Vallet Rd., TX. 77471 U.S.A.

800-980-9806 or 281-239-8500

<http://www.atcweb.com> atc@accesscomm.net

Celebrating our 17th Year Of Service !!

COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

ITEM	1-9	10-24	25+
LSLENS Lens Assembly	24.99	23.74	21.37

DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

ITEM	1-9	10-24	25+
DT100K	24.99	23.74	21.37

ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

ITEM	1-9	10-24	25+
S81102	1.99	1.89	1.70

EPROMS

ITEM	1-9	10-24	25+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

Popular I.C.'s

ITEM	1-9	10-24	25+
7400	.39	.37	.33
74LS00	.19	.18	.16
4017	.29	.28	.25
7805T	.33	.31	.28
7812T	.33	.31	.28
LM317T	.49	.47	.42
LM386N-1	.33	.31	.28
NE555N	.24	.23	.21
LM741N	.24	.23	.21
NE5532N	.55	.52	.47
68HC705C8P	8.99	8.54	7.69
8749	17.99	17.09	15.38
62256LP-10	2.79	2.65	2.39
2816	2.79	2.65	2.39

FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

ITEM	1-9	10-24	25+
K30	15.99	15.19	13.67

What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vises
- Resistors
- Capacitors
- Connectors
- Trimpots
- Kits
- Vices
- LED's
- Transistors
- And more!

GADGETEER'S GOLDMINE

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

• By Gordon McComb

ITEM	1-9	10-24	25+
TB3360	24.99	23.74	21.37

- Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882
- Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$5 charge) • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
- We Carry A Complete Line Of Electronic Components • Email - unielec@aol.com


Visit us on the web ! www.unielec.com

Unicorn Electronics

1142 State Route 18
Aliquippa, PA 15001

FREE SHIPPING!! on pre-paid orders

RF Data Modules

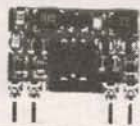

AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10



AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95



FM TRANSCEIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCEIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

Transceiver..... RTcom-4xx..... \$247.90
Transmitter..... RTcomTx-4xx..... \$ 87.15
Receiver..... RTcomRx-4xx..... \$105.52



ABACOM
TECHNOLOGIES



Tel: (416)236-3858
Fax: (416)236-8866
www.abacom-tech.com
abacomtech@compuserve.com

Newsbytes

Continued from page 16

Laurinburg, North Carolina.

<http://www.rostra.com>
910-276-4853 Voice
910-276-1354 Fax

DEVRY INSTITUTES AWARD SCHOLARSHIPS TO COMPETITION WINNERS

As part of an ongoing effort to address the shortage of qualified technicians in the consumer electronics (CE) industry, the DeVry Institute is continuing its support of the Skills USA Championships, Electronics Applications Competition. Kevin Boswell and Jeff See, the first-place winners of this year's championship held in Kansas City, MO on July 1, 1999, each received a \$30,000.00 scholarship donated by DeVry.

"We are happy to be involved with Skills USA and with similar industry efforts because we see the shortage of technically qualified workers as a very serious problem," explains Ellen Derwin, manager of outreach services for DeVry. "Awarding scholarships is a way for us to encourage students to get the education necessary to pursue a high-paying and exciting career in technology."

The Consumer Electronics Manufacturers Association (CEMA) sponsors the annual competition in an effort to attract and foster talented technicians. "The CE industry relies heavily on skilled technicians," said Don Hatton, vice president, CEMA Technical Education and Services. "Skills USA and the DeVry scholarships provide contest winners an opportunity to develop their skills through education."

A long-time supporter of the competition, DeVry has donated nearly \$250,000.00 in scholarships to the contest winners during the last four years, and has made continuing education a possibility for many students who may not have had the opportunity.

"The scholarship to DeVry has really helped me get training that I would not have otherwise received," explained 1998 Skills USA Championships winner, Jeff See. See, who is currently studying at the Kansas City campus of DeVry Institutes and hopes to work in the research and development department of a major electronics firm, would not have been able to attend DeVry if he had not won the scholarship. "I can't begin to think of what else I could be doing," said See. "I would probably end up making a lot less doing something I didn't like."

The Skills USA Championships are held annually to recognize the achievements of vocational students and to encourage them to strive for excellence and pride in their chosen occupations. Working against the clock and each other, the contestants prove their expertise in job skills for occupations such as electronics, technical drafting, precision machining, medical assisting, and culinary arts.

The Electronics Applications competition consists of five troubleshooting sections, a soldering/desoldering section, and a written exam. The exercises are designed to simulate real-world conditions and emphasize the quality, efficiency, and safety of the competitor's work.

The DeVry Institutes, founded in 1931 by Dr. Herman DeVry, have a combined enrollment of more than 33,000 full- and part-time students and 16 campuses, making it one of the largest private higher-education systems in North America. DeVry offers several associate's and bachelor's degree programs and provides curricula in electronics, computer information systems, business, telecommunications management, accounting, and technical management.

CEMA is a sector of the Electronics Industries Alliance (EIA), the 75-year-old Arlington, VA based trade organization representing all facets of electronics manufacturing. CEMA represents more than 500 US manufacturers of audio, video, accessories, mobile electronics, communication, information technology, and multimedia products that are sold through consumer channels.

CEMA also sponsors and manages the International CES — Your Source for Workstyle and Lifestyle TechnologySM. All profits from CES are re-invested into industry services, including technical training and education, product promotion, engineering standards development, market research, and governmental and legal affairs support. As the first major technology event of the new millennium, the 2000 International CES is the launch pad for 21st century technology.

UPCOMING EVENTS

Digital Hollywood
September 27-30, 1999;
Los Angeles, CA


DTV Summit, held in conjunction with Digital Hollywood
September 28, 1999;
Los Angeles, CA

EIA/CEMA Fall Conference
October 24-28, 1999;
Palm Springs, CA

The 2000 International CES — Your Source for Workstyle and Lifestyle TechnologySM

January 6-9, 2000; Las Vegas, NV
Digital Hollywood at CES
January 6-8, 2000; Las Vegas, NV

Don't be stupid.

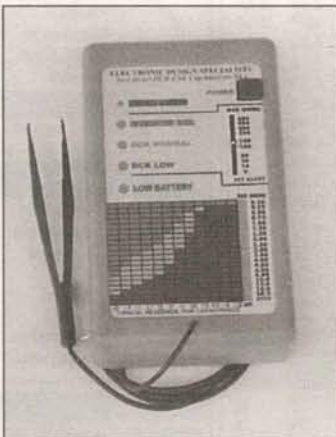

Smart techs know that to be productive you need to find defective components quickly. Maybe that's why 37 TV stations, General Motors, Matsushita Industrial, Sears Service, Pioneer Electronics, Panasonic Authorized Service, and thousands more independent service technicians have chosen the **CapAnalyzer 88** over all of the other capacitor checkers. Check www.eds-inc.com/88users.html for actual **CapAnalyzer** users' comments as they compare their **CapAnalyzer** to the "wizards" and "z-meters" they already own. They all prefer the **CapAnalyzer 88** because it

does what you expect it to do: check electrolytic capacitors, in-circuit, with 100% accuracy. Period. No unsoldering to check out-of-circuit, no mistaking a shorted or leaky cap as good, as other "ESR" meters do, no guessing about whether a value is good or bad. With our exclusive three-color chart right on the front panel, auto-discharge, multi-beep alert, and one-handed tweezer test probe, even your pet monkey could find defective caps in that problem TV, monitor or VCR in a few seconds. 55% of sales of **CapAnalyzers** are from recommendations by other **CapAnalyzer** owners, and 9% of sales are from previous customers buying a second unit. So get smart and buy one for yourself. It's only \$179. With our exclusive 60-day satisfaction-or-money-back guarantee, you risk nothing. Your only problem will be running out of work as you take care of all of those "dogs" that you've been sitting on. We're EDS. We make test equipment designed to make you money. Available at your distributor now. 561-487-6103

www.eds-inc.com

by Walt Noon

Outfitting Your "Mad" Scientist's Lair!

Graphics by
Matthew Roddy

This Halloween
is your time
to **cackle**,
throw back the
curtains, and
reveal wild
arcs of
electricity
surging through
your **house!**

Well, unless I miss my guess, that time of year is coming again. The time of year when it's possible to let the real "mad scientist" in you out, and not worry about the neighbors having you committed. A time when you can let your technical skills place you where you really belong; not behind a computer screen or over some smoky perf board, but in the electrical wizard's role!

This year is your time to cackle, throw back the curtains, and reveal wild arcs of electricity surging through your house!

Even though you find yourself in a burned lab coat, even though your hair may be standing on end, and even as you go wild with laughter, with two simple words with which

you CAN'T be blamed! Repeat after me: "Happy Halloween!"

That's right, it's the perfect excuse to build that wonderful gadget you've always wanted to — a Tesla Coil!

I warn you now, these coils are dangerous. Not so much because they produce large electrical arcs in open air (that when properly handled are remarkably safe), but because these devices can be so exciting to build that they can become an **OBSESSION**. You may well be at risk for continuing your mad scientist activities beyond ...

Remember — using your Tesla Coil this Halloween will produce one other type of magic, one that it has for more than 100 years ...

While the parents may jump out of their socks, the children will light up with delight and interest!

You and I can smile knowing that we may have just added some future "mad scientists" to our ranks!

The Tesla Coil

The coil featured in this article is a classic, and a real performer for its size! In fact, though the secondary coil stands at just 12" high and 3" in diameter, it will easily produce 70,000-volt sparks arcing 4" even with a LOW POWER input transformer (such as an automotive coil or equivalent).

You can step the power up considerably with a larger input transformer and produce as much as 250,000 volts! At these voltages, sparks are thick, brilliant, and noisy, and discharges of half a foot are possible. Sparks of this order are suitable for terrifying the staunchest of trick-or-treaters.

When operating, many special effects are possible: The coil will light a florescent light bulb held in your hand with no wires attached! It will drive plasma displays, and cause other florescent or tube lights in the room to flicker.

If you're REALLY of the mad scientist variety, the arc can be taken to a metal object held in an outstretched hand. (This coil is high frequency, and will exhibit the "skin" effect in which the electricity can travel over your skin without shocking you. However, you MUST read the safety tips for doing this later in the article.)

Though you are free to build the coil "as is," I'd like to briefly go over each component and give you some design philosophy. Significant increases in output and efficiency can be had with some thought on your part. And, that's what these coils are all about!

Important Sources

Later in the article, I'll give some sources for parts, and my web address where you can download free design software for altering the dimensions of your coil and even trying out your own designs on screen before building them!

How it Works

There are only five basic components in simple Tesla coil design (see the schematic in Figure 1). These are: the line transformer, capacitor, spark gap, primary, and secondary windings.

You'll notice that in the design we're using there are also a pair of radio frequency chokes and a second spark gap for safety. (The second spark gap is not absolutely necessary for operation, in fact, many coil designers leave it out. However, it can be important for coil longevity. The secondary gap protects your line transformer.)

Most of the components of the coil can be made by hand. I'll give you a brief description of each part, what it does in the circuit, and what options are available.

The Line Transformer

The line transformer boosts the voltage from your wall current to between 2,000 and 10,000 volts depending on the transformer you decide to use (2,000 volts is about as low as you can go and still have a useful spark). Things don't really pick up with this coil until you get to around 6,000 volts on your line transformer.

Many Tesla builders feel that the size of the secondary coil and type of discharge terminal are the keys to a big spark, but even with some of the interesting trade-offs you can make in design, you can't escape the fact that you can't get more out than you put in, so, this is where you can make the biggest difference.

A neon sign transformer rated at 9,000 volts or better and around 30 milliamps is ideal. Neon transformers are nice because they can be dead-shortened without damage, though, transients in a Tesla circuit can still harm them over time. The more power you draw from your neon transformer, the less efficient it becomes. This can cost you a little at the output side as well, and is why some Tesla purists steer away from neon transformers.

People often use oil furnace ignition trans-

formers with similar ratings, and even automotive coil type transformers (see details on this at the end of the article).

The automotive coil is nice because it's cheap and the sparks are safe, yet still impressive and entertaining. I often operate my coil for extended periods of experimentation with an auto coil type set-up. In a darkened room, the blue corona glow and subtle steamers of electricity are beautiful to watch. However — for special effects — your coil's output will be modest if you use an auto coil as compared to a neon transformer.

New neon transformers are relatively expensive, however, by poking around the Internet and Tesla groups (mentioned later), you can find some real bargains. Big Tesla systems use distribution transformers (as seen on your local telephone pole) which produce 17,000 volts or more, but you'll need a whole new design for that!

The Jacob's Ladder!

Before we go on, I should describe a quick stunt with a neon transformer that could be "must-have" equipment for your Halloween's lair.

Figure 2 shows a neon sign transformer. Connected to the transformer are two metal rods angled close together at the base and then slanting apart. (I usually use welding rods.)

This is a classic "Jacob's Ladder" in which a spark will form at the narrow point and rise with a loud crackle to the top and then repeat.

This is a simple, mesmerizing effect. Just make sure your transformer is grounded, and keep people clear of this somewhat dangerous spark. (The metal rods can be placed inside a large plexy tube for safety.)

The High Voltage Capacitor

The high voltage from the line transformer is

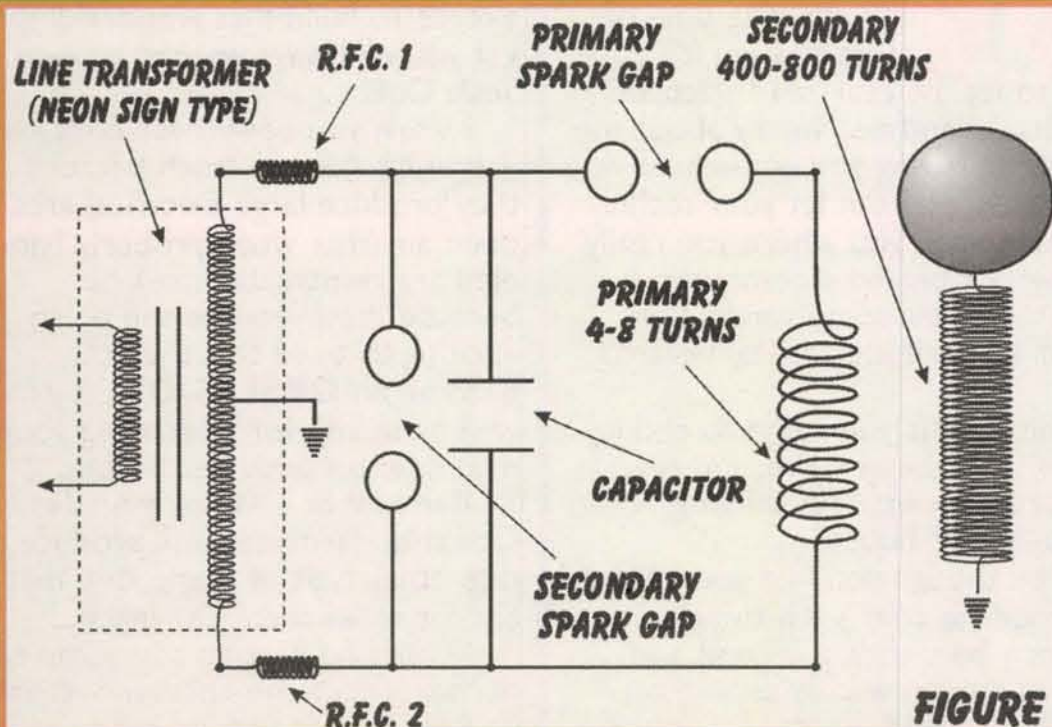
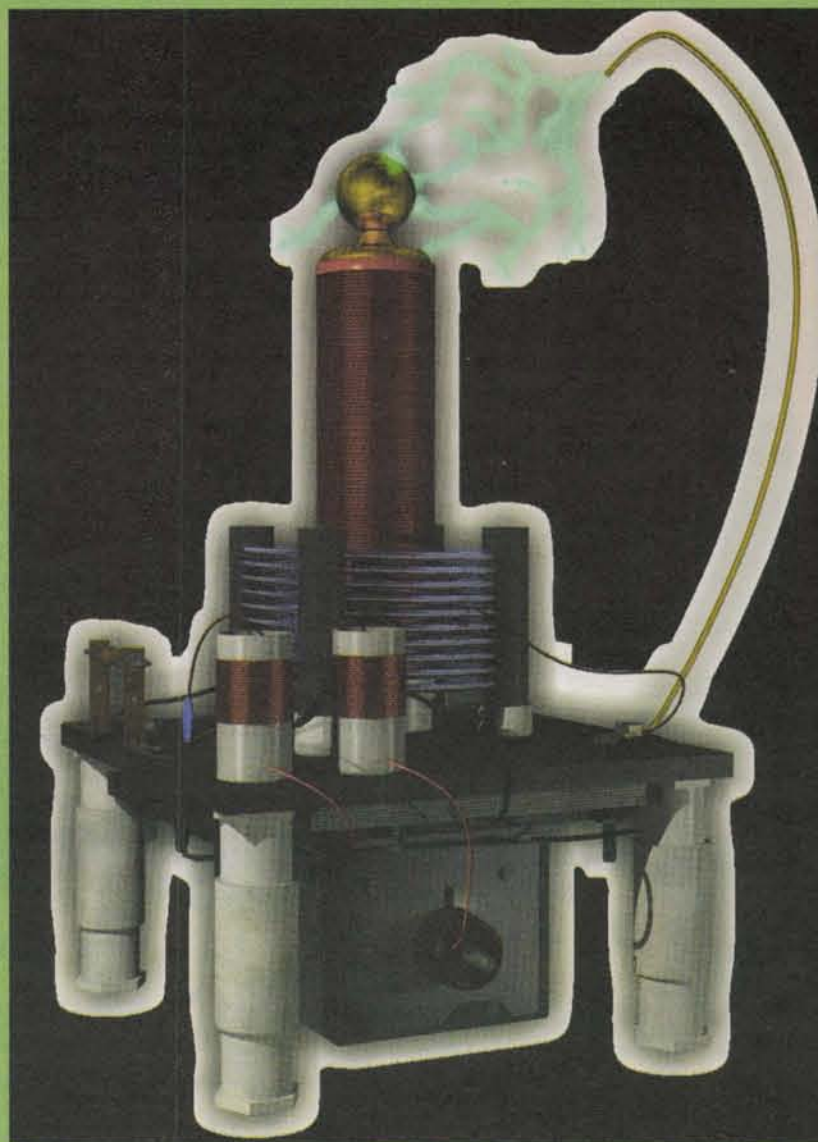


FIGURE 1

needed to supply enough energy to the capacitor so that it can "kick" out pulses at a very high speed (600 kHz is common) and not be depleted. The idea is that as a charge builds up in your capacitor, it eventually becomes large enough to arc across the spark gap.

For this coil, we'll assemble a capacitor rated at .0052 uF and at least 15,000 volts.

Commercial caps of this voltage are the best, but tend to be expensive. So, most builders create their own. See Figure 3A for a simple capacitor plan. (Figure 3B shows an exploded view.)

The capacitor is made by alternating five sheets of .032" polystyrene and four sheets of 10" square metal. Note in the "top view" that each metal plate does not go all the way across the polystyrene.

Copper or aluminum foil can be glued down and used for the plates. I personally use thin sheets of aluminum such as those used to patch the roof.

To keep my capacitor together, I glue it and sandwich it between two pieces of wood mounted under the coil.

Other configurations of this capacitor are possible so that its size and dimensions can be changed to fit your coil's housing. Other home-made high voltage capacitors are also possible using everything from rolled plates in PVC and oil to beer bottles. Handy calculations for all these caps are provided in the free software.

The Spark Gap

The spark gap acts as a high voltage switch (Figure 4). When energy in the capacitor is sufficiently high, it arcs across the gap and supplies power to the Tesla primary winding. This partially depletes the capacitor and thereby quenches itself, restarting the cycle.

The spark gap shown is the simplest, and works well. It's made from two bolts and two rounded screw-on caps. By threading the bolts back and forth, you can adjust the gap. The ideal gap for this coil should be around one millimeter; however, changing the gap will get wildly different results and I encourage you to do so!

The spark gap is a key place where coil efficiency can be improved. The faster the spark is quenched after firing, the better the Tesla secondary will oscillate! (A sloppy spark will cancel out some of the secondary coil's output.)

To quench the spark, many experimenters apply a blast of air from a compressor across the gap to literally blow out the spark. Others use a "multi gap" spark gap by having several points the spark must leap to in crossing the gap(s). I have heard of exotic spark gaps inside of vacuum chambers that increase efficiency by 50%!

I usually just use a gap as shown and it works quite well. Due to the heat and damage that an arc can do to a steel bolt head over time, I often make a trip to the welding store and use Tungsten welding rods instead of steel bolt heads.

The Primary Coil

The primary coil is just a few turns of heavy gauge wire. I like RadioShack's catalog #15-035.

Since this wire is bare, you will be able to tune your coil by sliding a wire along it until a point is found where the coil fires most efficiently.

To get nice even circles, I first wrapped the heavy gauge wire around a cylinder, then removed it and threaded it through the PVC posts seen in the photos.

In the photo, you'll also notice I had 12 turns of wire. This was simply for experimental purposes as I was playing with a wide variety of components. The coil was "tuned" with less than six windings, so I suggest you limit your primary to 6-1/2 or so

windings. The spacing between each winding was approximately 2/16 of an inch.

The Secondary Coil

In my mind, this is where much of the magic happens!

Unlike a conventional transformer, a Tesla coil's output is not only related to the ratio of turns in the primary and secondary windings. In fact, the primary coil acts as a tuned radio transmitter, and the secondary a tuned radio receiver. When the high frequency wave emanating from the primary strikes the secondary — if they are properly in tune — the secondary will begin to oscillate powerfully.

This has been described to be like the effect of a child on a swing. If the child is pushed at just the right moment, the swing will gain in amplitude. If pushed at the wrong time, however, the swing will be deadened. (This is why quenching the gap and good tuning on the primary are so important.)

The secondary coil is simply a long winding of wire (typically 500 turns) wound tightly on a cylindrical form.

PVC is typically used, or very dry cardboard tubing with a few coats of shellac. Actually, the thinner and more electrically inert your form can be, the better. Many Tesla purists have attempted (and some succeeded) to wind a coil and remove the form altogether.

In the Tesla coil shown, I used a very thin butyrate tube from a local plastics store. It consists of 424 windings of #24 enameled wire tightly wound along a tube three inches in diameter and 12 inches long.

The top of the coil will have high energies so, the last few windings at the top are spaced slightly apart and can optionally be covered with a little corona dope. This prevents arcing between coils which can damage your secondary.

To protect the windings, I gave the coil several thick coats of epoxy, rotating it while the epoxy cured for an even finish. Shellac or varnish can also be used.

Odds and Ends


For a top discharge terminal, I used a smooth brass doorknob. All rough edges were coated with corona dope. An optimal discharge terminal should be at least the same diameter as your secondary coil, so I fell a little short here, but it worked well. Using a torroid-shaped top terminal instead of a sphere can make a dramatic improvement, as well. For the radio frequency chokes, I simply used 21 turns of #18 enameled wire on a common 1-1/2 inch diameter PVC tube.

Final Assembly

Assembly is straightforward from the schematic in Figure 1, and components are placed as shown in Figure 5. I used simple PVC pipes with end caps, and screwed the end caps to the board. This included the Tesla secondary coil for which I found a three-inch end cap to seat it in.

The primary coil should have at least 2-1/2 inches of spacing between it and the secondary coil all the way around. Electrical strikes from the primary to the secondary can damage a coil over time. A ground rod should be attached to allow sparks to have a place to fly. It can be connected

FIGURE 2

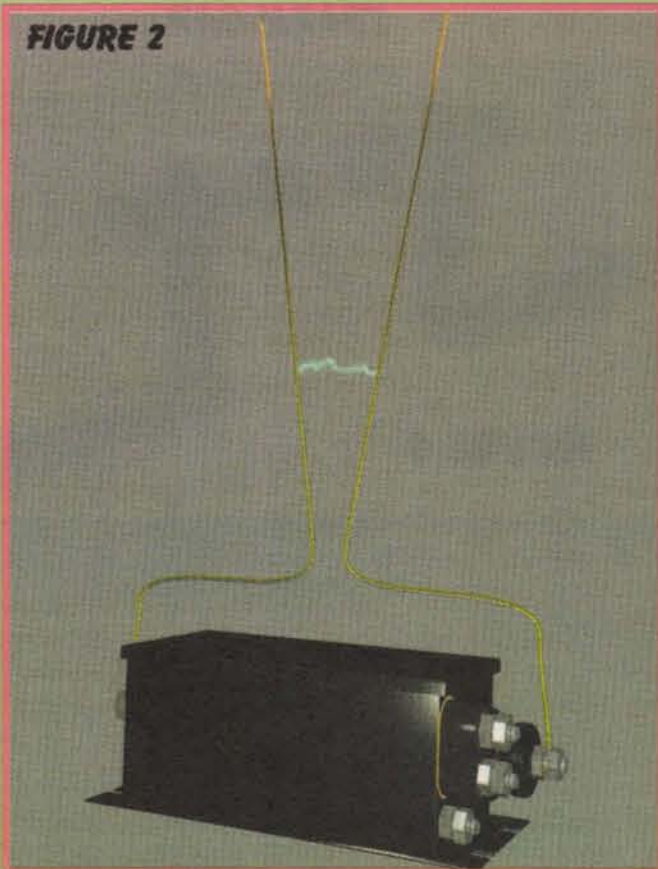

HOMEMADE CAPACITOR

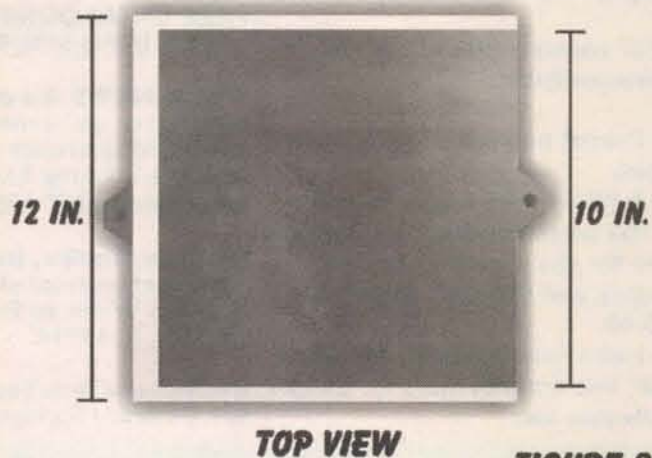


FIGURE 3A



FIGURE 3B

SPARK GAP



FIGURE 4

to the wire leading from RFC 2 to the primary. It can be bent in, to around four inches from the top discharge terminal.

If using a neon transformer, it is very good electrical practice to run your neon transformer from a variac (one rated at five amps would suffice) so that you can do low voltage testing, and control the output of your coil. A variac is simply a variable transformer that connects between the wall and your transformer and allows you to control power output. Several *Nuts & Volts* vendors advertise them, or look around the net to pick one up for less than \$50.00.

Firing it up!

Now the fun begins! Your coil is complete except for tuning, which is easy to do. One of the

wires attached to your primary coil should be movable. Often an alligator clip is used. Attach this wire about 5-1/2 turns away from the other wire attached to your primary. Briefly run the coil and observe the spark length and character.

By moving this wire along your primary coil, you'll find a sweet spot where "spark" is at a maximum. This — and playing with spark gap distance — is all that is required to get the effect you want.

Tip: In the schematic, the bottom of the secondary coil is shown grounded. You can increase spark length by instead attaching this wire to the wire connecting RFC 2 and the primary. However, this makes the spark *dangerous*.

Let the Experiments Begin!

The stunts that can be pulled with your Tesla coil are endless. The simplest and most fun for this Halloween might be to hold a florescent tube in your hand and have it light with no wires when passed near the coil which is blasting away! You can create a stunning "electric chair" with sparks flying from the coil

behind you while your victim's scream!

If you are using a low input coil like an auto coil or equivalent driver, sparks of four inches can be taken to the hand painlessly! Remember that you should have metal thimbles on your fingers or be holding some metal object since the sparks themselves can be warm.

Remember good electrical practice when doing any high power work. Tesla wore thick rubber sole shoes, and kept one hand in his pocket!

If you get the Tesla bug, many serious and bizarre experiments are possible from wireless power transmission, to passing a million volts safely through a person! I have even read accounts of temporarily, painlessly scrambling a person's nervous system.

If you visit the web page soon, I'll set up a mailing list for *Nuts & Volts* readers to keep you informed of upcoming Tesla events.

So, let's get winding our coils, and give our neighborhood friends a REAL shock this Halloween! **NV**

My address is:

walt@noonco.com

The web address for free Tesla software and info from me will be:

<http://www.noonco.com/tesla>

For construction of the article, I have available:

- Precut polystyrene, \$1.25 per sheet.
- A "Wire Kit" which includes all the wires needed, including the wire for the primary, the secondary, and the RFC chokes for \$25.00.
- I also have a few of the "auto coil" line transformers for \$34.00 while they last.

For those who don't have access to the web, I'll be happy to send out a sheet of sources with more Tesla info and experiments to anyone who writes by E-Mail.

FREE CATALOGS/FURTHER TESLA INFO SOURCES

TCBA NEWS is a practical newsletter on homemade coils published quarterly by Harry Goldman, 3 Amy Lane, Queensbury, NY 12804.

Lindsay Books, Inc., has many Tesla and unusual electrical reprints. Write to P.O. Box 538, Bradley, IL 60915.

International Tesla Society, P.O. Box 636, Colorado Springs, CO 80931.

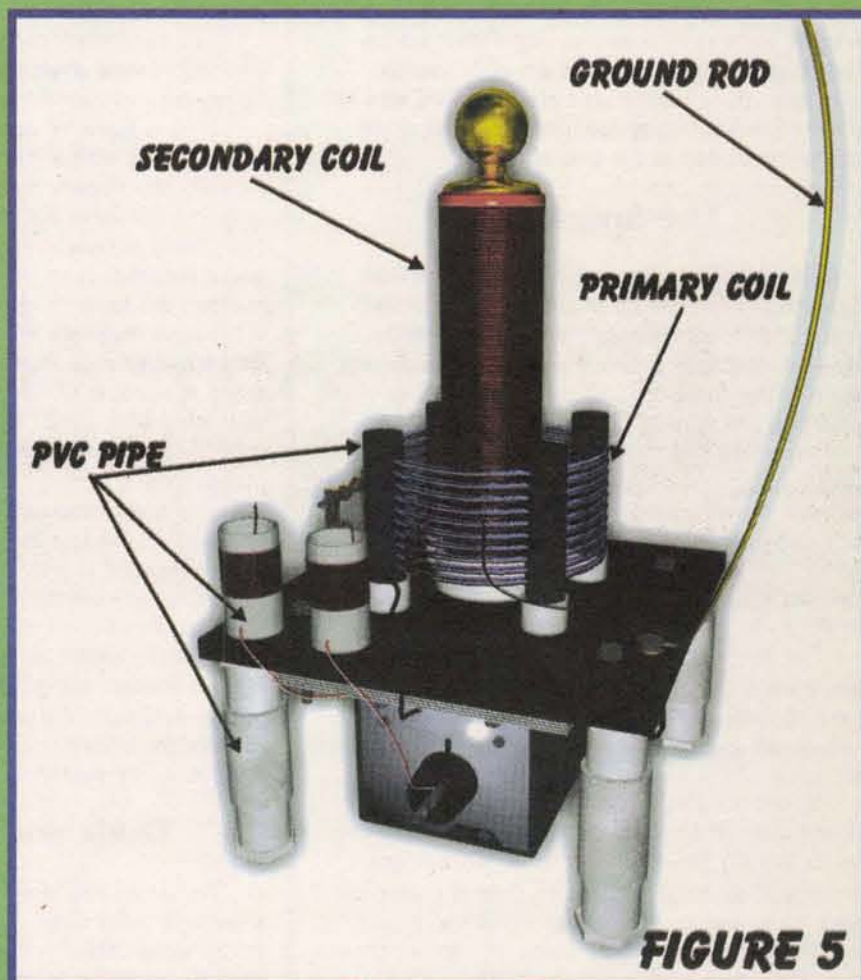


FIGURE 5

Your shrinking options are expanding!

MicroCore-11™

- tiny 2" x 2" 68HC11 module
 - RS232, 5V regulator, 8MHz crystal
 - 32K SRAM plus 8K or 32K EEPROM
 - plugs into your breadboard like a DIP
- 8K Starter Package #MC11SP8K.....\$75*
32K Starter Package #MC11SP32K...\$89*


* plus shipping & handling
Visa*MasterCard*Discover*Amex

Technological Arts

Phone: (416) 963-8996

Fax: (416) 963-9179

www.technologicalarts.com

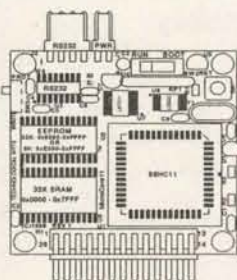

Model PTS-10
\$55



LIFETIME WIRE STRIPPER, a breakthrough in wire stripping technology. Extremely fast tool will strip PVC insulation #14 to #30 AWG from solid, stranded or shielded wires. High quality strip is achieved by patented stripping element (.008" thick) which thermally cuts the insulation all the way to the conductor without nicks. Five year test, with over 2 million stripped wires, using the same element, speaks for itself. The stripper has won a —

"FIVE STAR PRODUCT OF THE MONTH"

award in DESIGNFAX magazine. Strippers for TFE, KAPTON, KYNAR, SILICONE RUBBER, etc. and rechargeable, battery powered strippers also available.

PATCO Service, Inc., 2515 Glencoe Rd., Baltimore, MD 21234
(410) 444-4010 Fax (410) 254-9566

Wireless pet-containment breakthrough

Computerized collar creates world's first radio-controlled dog?

Small U.S. company develops technology that uses radio waves and a microprocessor on your dog's collar to replace expensive fencing, cruel chains and leashes...keeping your dog safe and free!

by Guy Yeadon

Some of the hottest products in recent years have been electronic pet containment systems. Unfortunately, they require wires that have to be buried in your yard to create a boundary and communicate with the dog's collar. This makes them a nightmare to install and subject to damage from lawnmowers, shovels... even other dogs! One of the

major manufacturers in the industry, Radio Systems Corporation, asked its team of engineers, "How can we eliminate the wires?" That's how Instant Fence was born.

Smart collar. Instant Fence gives you the ability to set up a safe and secure area for your pet to play, without the time and expense of conventional fences. Most fences can cost thousands of dollars and can affect the appearance of your property. In many new neighborhoods, they aren't even allowed. Electronic fences that use wires and special collars can cost nearly as much to have professionally installed, usually well over a thousand dollars. Instant Fence is a revolutionary new concept that is clearly the best value in pet containment.

Safe, secure and totally portable. This is the safest, most

secure fence you can buy for your pet. It is far superior to alternative containment methods, because there are no wires to bury and because the pet cannot "run through" the warning zone. When the collar picks up the signal from a buried wire, a stubborn or poorly trained dog can learn to break out. With Instant Fence, there is no "other side" to

run to, since the only safe area lies inside the containment circle. Compared to conventional fences, which dogs can jump over or dig under...Instant Fence is unbeatable.

What's more, it's totally portable. You simply unplug it and take it with you to your new house, while visiting friends or even while traveling. No more ties, cages or boarding costs—your pet can enjoy vacations as much as you.

The humane solution. Instant Fence will provide greater happiness and freedom for you and your pet. No more cages, dog runs or tie-outs. No more waiting for you to go for a walk on a leash. Your dog will be able to run and play throughout the yard.

Easy installation, simple training. Instant Fence emits a radio signal that extends up to 90 feet from the transmitter. While the signal area forms a circle, you can adjust it to keep your pet in your yard. While your dog may not be able to roam every square inch of your property, it can have over a third of an acre in which to play. The system has a variety of safety features to protect your dog. Patented coding in the software

prevents any accidental electric pulse in the event of a power shortage. The boundary area remains stable, never fluctuating with disturbances within the signal area. If your pet is poorly trained and gets out of the containment area for over 30 seconds, the correction pulses will cease and the receiver will revert to a beep. Training is simple

Computerized collar receives signal from the transmitter in your home



- As the signal diminishes, the collar will emit a warning
- If your dog leaves the safe zone, the collar will administer a correction
- The system resets when your dog returns to the safe zone



Instant Fence's breakthrough design took 3 years and \$2 million of research to develop...



• **Wireless.** No more digging up your yard to bury wires. Just plug it in.



• **Affordable.** Costs significantly less than other containment options.



• **Totally portable.** Take it with you wherever you go.



• **Safe & Secure.** Keep your dog in your yard—safe and out of trouble.

• **Hidden barrier.** Without fences, posts or wires, only your dog will know it's there.

Instant Fence includes everything you need:

- Transmitter with AC adapter
- Receiver collar and batteries
- Boundary flags
- Training manual and video



Installs in seconds—just plug it in!

and a video is included to walk you through the process. Once you have adjusted the signal to the desired strength, mark the boundary by placing the small training flags at the edge of the signal area. The training takes only minutes a day, and dogs generally learn their boundary within a few weeks. After thirty days, you can begin to remove the flags gradually.

It's risk-free...and only Comtrad has it. Why wait to take advantage of this breakthrough technology? Instant Fence comes with a one-year limited warranty from Radio Systems, and it's backed by Comtrad's exclusive risk-free guarantee. Try it for yourself, and if you are not satisfied, simply return it within 90 days for a full "No Questions Asked" refund.

Exclusive limited time offer! Order today and get a factory-direct discount on Instant Fence.

Instant Fence:

Three credit card payments of . . . \$99.95 \$19 S&H

Please mention promotional code 5821-15987.

For fastest service, call toll-free 24 hours a day

800-992-2966



To order by mail, send check or money order for the total amount including S&H. To charge it to your credit card, enclose your account number and expiration date. Virginia residents only—please add 4.5% sales tax.




comtrad industries

2820 Waterford Lake Dr., Suite 102
Midlothian, Virginia 23112

Instant Fence—Breakthrough Engineering and Design



The Instant Fence Transmitter emits a radio signal around your home, so all you do is plug it in somewhere inconspicuous. Your dog wears a lightweight receiver collar that picks up the signal—up to 90 feet from the transmitter. As long as the receiver is in range, your dog is free to run and play. When it approaches the boundary of the signal area, the dog will hear a warning beep. If the dog continues, it receives a light static energy pulse, which is startling but not harmful. After only a little training, your dog will learn the boundaries of the system. The system is totally adjustable for smaller areas.

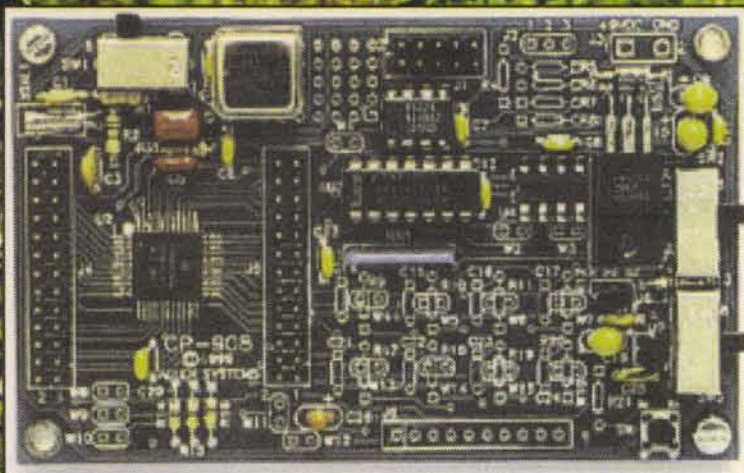

CP-908

The CP-908 is a single board computer based on the 68HC908 microcontroller. The 68HC908 is a member of the 68HC08 family and has 20K of on-chip Flash for program storage. A variety of control-related resources are also integrated into the chip. These include an eight-channel, eight-bit A/D converter, eight keypad interrupt inputs, eight general-purpose I/O lines, built-in monitor ROM, SCI (asynchronous)

serial port, SPI (synchronous) serial port, timer interface module, and 512 bytes of RAM.

A unique feature of the 68HC908 is that its Flash memory is "in-system" programmable. Because user software can erase, write, and read the Flash, it can be programmed in the standard user mode. However, a special "monitor mode" is

also available on the 68HC908. This mode allows the user to perform various low-level operations on the 68HC908 without executing user code.

The CP-908 is priced at \$149.00. For more information, contact:

ALLEN SYSTEMS
2346 BRANDON RD., DEPT. NV
COLUMBUS, OH 43221
614-488-7122
E-MAIL: allensys@aol.com
WEB: <http://members.aol.com/allensys>

RX5000

Precision Navigation, Inc. introduces the first radar/laser detector with a built-in digital compass, the RX5000 for use in autos, RVs, and SUVs.

The RX5000 brings together state-of-the-art technologies in one small six-ounce unit designed to provide all types of drivers with the most accurate radar/laser/safety and compass combination on the market today.

Ideal for long-distance drivers who find themselves in new cities, the RX5000 not only alerts the user to all bands of radar, 360 degrees of laser protection and VG-2, it also functions as a safety device informing drivers of road hazards such as approaching emergency vehicles, roadwork, and upcoming train crossings with an illuminated eight-digit text display.

The digital compass displays directional information with numeric digits and cardinal points. Its magnetic distortion detection and correction elements means it operates without the worry of interference from outside metal sources like traditional compasses.

Designed to be very user-friendly, the sleek profile of the 4-1/2" x 3" metal-finish unit mounts easily to any windshield with suction cups and is powered by a 12-volt cord that plugs into the car lighter. The easy-to-read display has four city modes, brightness and volume controls, a mute button, and can withstand operating temperatures from -14 degrees to 158 degrees.

The RX5000 can be purchased at specialty retailers and from catalogs at a suggested retail price of \$199.00.

For more information, contact:

PRECISION NAVIGATION, INC.
5550 SKYLANE BLVD., STE. E, DEPT. NV
SANTA ROSA, CA 95403
707-566-2260 FAX: 707-566-2261
E-MAIL: csherer@precisionnav.com
WEB: www.precisionnav.com



New Product News

SEPTEMBER DRAWING
HOSTED BY

MCM Electronics
(see page 17, Aug. issue)

Tenma
Full Function DMM
with temperature function

List Price \$79.95

July Prize Winners:

James W. Hayes
of Lake Placid, FL
Tom Davies
of McMinnville, OR

Check us out on the web!
<http://www.nutsvolts.com>

If you do not wish to order a subscription, but would like to be entered in our drawing, simply **send or E-Mail** your name, address, and telephone number, to NUTS & VOLTS, 430 Princeland Court, Corona, CA 91719, drawing@nutsvolts.com. No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

As a current, paid subscriber, you will be automatically entered each month in our drawing.

To Subscribe - Just fill in and mail the enclosed subscription card or call our toll free order line at (800) 783-4624 with a Visa or MasterCard.

You Win with Nuts & Volts

Subscribe today and be
automatically entered in
our *new* MONTHLY PRIZE
DRAWING!!!



SPECIAL BONUS: NETCOM (page 11)
WILL FURNISH PRIZES MONTHLY!!

Contributors ...

Parallax (back cover) • **Corporate Systems Center**
(pages 2, 95) • **HSC (page 3)** • **Resources Unlimited**
(page 17) • **Timeline, Inc. (page 37)**

• **Alltronics (page 22)** • **Electro Mavin (page 15)**

• **All Electronics (page 41)** • **Roger's Systems Specialist**
(page 77) • **Electronic Goldmine (page 34)**

• **MCM Electronics (page 17, Aug. issue)**

• **Velleman (page 59, Aug. issue)** • **Seabird Technical (page 67)**

New Product News



MULTI-SENSOR VEHICLE COMPASS


Designed to give drivers a variety of essential trip information, the V5000 Series multi-sensor vehicle compasses integrate state-of-the-art sensor technology to

provide directional readouts, the inside temperature of the car, automatic trip timer, digital clock, outside temperatures, black-ice warnings, altimeter readings, trip logs, and "SMART" sensor features such as an auto shut-off when the car is not in use after 10 minutes, magnetic distortion detection, and correction elements that tell when the compass reading may be affected by an outside source, and a multiple trip log that stores and records time and temperature information, as well as the time traveled, for up to three trips.

Prices for the V5000 Series range from \$79.95 to \$129.95 and can be purchased at specialty retailers and from catalogs.

For more information, contact:

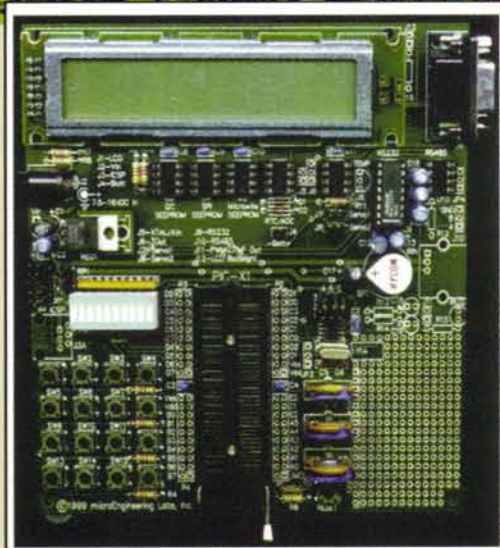PRECISION NAVIGATION, INC.
5550 SKYLANE BLVD., STE. E, DEPT. NV
SANTA ROSA, CA 95403
707-566-2260 FAX: 707-566-2261
E-MAIL: csheer@precisionnav.com
WEB: www.precisionnav.com



PICMICRO EXPERIMENTER/LAB BOARD

The new PIC-X1 is microEngineering Labs first pre-assembled experimenters platform for the Microchip Technology PICmicro microcontrollers. While our PICProto boards allow you to create your own projects with a minimum of hassle, the PIC-X1 goes one step further. It provides an assembled testbed containing most of the circuitry commonly used with PICmicros.

The PIC-X1 contains the circuitry required by the PICmicro to operate: five-volt power supply, oscillator, reset circuit, as well as additional application circuits. The crystal controlled oscillator includes jumpers to set the speed between 4 MHz and 20 MHz.

Application circuits include a switch matrix, potentiometers, LEDs, LCD module, serial EEPROMs, real-time clock, temperature sensors, servo connectors, RS232 interface, RS485 interface, IR interface, and


speaker. A prototyping area is also included in case we missed your favorite circuit.

All of the PICmicro I/O pins are brought out to headers next to a 40-pin ZIF socket. This allows connection to off-board circuits, as well as allowing on-board circuits to be connected to other PICmicro pins, if desired. The PIC-X1 is designed to work with 40-pin PICmicros, but may be jumpered to work with smaller devices.

The PIC-X1 is available in either bare PCB, kit, or assembled form. A parts list and schematic along with PicBasic Pro example programs, are included.

For more information, contact:

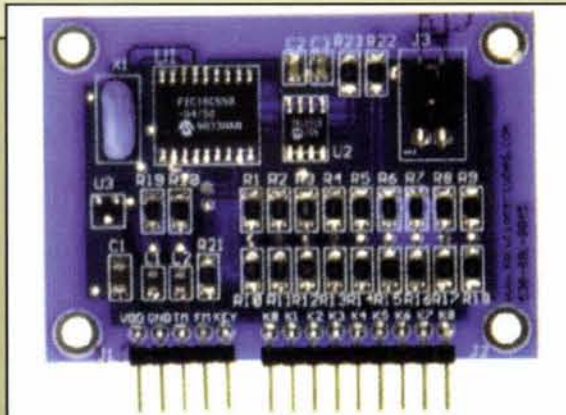MICROENGINEERING LABS, INC.
P.O. BOX 7532, DEPT. NV
COLORADO SPRINGS, CO 80933
719-520-5323 FAX: 719-520-1867
E-MAIL: info@melabs.com
WEB: <http://www.melabs.com>



MEMKEY

The MEMKey is a fully programmable keypad encoder. Using a jumper, the MEMKey supports either a simple serial communication protocol or the standard PC/AT communication protocol. In either communication mode, it can decode key matrices of up to four columns by five rows. The rows and columns can be programmed to match the row-column configuration of any off-the-shelf keypad.

The value returned by the MEMKey can be pro-



IC-2800H DUAL BAND

icom's new IC-2800H has a unique full color LCD display with user-selectable modes and video capabilities. With durable construction, installation flexibility, a bandscope function, 9600 bps packet, independent tuning controls, convenient memory editing, and much more. The IC-2800H offers advanced functions, convenient features, and superior performance.

The IC-2800H has a 3" TFT color LCD remote control head that gives a wide angle viewing for flexibility and all-around usability. The high visibility screen offers a wealth of information: scope, S meter, memory names, scan condition, and more.

With optional and/or third-party equipment, preview real-time VCR or digital camera images, monitor TV broadcasts with a TV tuner, display GPS maps, and more.

The IC-2800H transmits 50 watts on 144-148 MHz, and 35 watts on 430-450 MHz.

A tuning dial, AF gain, squelch level control, and four function control switches are available for each band.

For more information, contact:

ICOM AMERICA, INC.
2380 116TH AVE. N.E., DEPT. NV
BELLEVUE, WA 98004
425-454-8155 FAX: 425-454-1509
WEB: www.icomamerica.com

Showcase your New Products here! Send all press releases or information/photos to:

Nuts & Volts Magazine
New Product News
430 Princland Court,
Corona, CA 91719
or E-Mail to
newproducts@nutsvolts.com

grammed to any standard value. In addition, the debounce time and typematic rate are fully programmable. All programmable values are stored in non-volatile memory so they are saved when power is off.

When operating with the serial protocol, the MEMKey communicates at 2400 baud, 8N1, LSB first, asynchronous. This can be either a one-wire or a two-wire interface.

In addition, there are 64 bytes of EEPROM memory which is made available to the user as scratch pad space.

The MEMKey's small size and connection scheme allow the device to be inserted directly into circuit boards for production runs, or into breadboards for easy prototyping.

Complete data sheets and application notes are available.

The MEMKey comes in a 1.6" x 2.25" SIP module, and sells for \$36.00 (quantity 1).

For more information, contact:

SOLUTIONS CUBED
3029 ESPLANADE STE. F, DEPT. NV
CHICO, CA 95973
530-891-8045 FAX: 530-891-1643
E-MAIL: lon@solutions-cubed.com
WEB: www.solutions-cubed.com

Fantastic DMM Offer!

Don't let this price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch. **Rubber Boot Included!**
 Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity
 Overrange Indication: 3 Least Significant Digits Blank
 Temperature for Guaranteed Accuracy: 23°C ±5°C RH<75%
 Temperature Ranges:
 Operating: 0°C to 40°C (32°F to 104°F)
 Storage: -10°C to 50°C (14°F to 122°F)
 Power: 9V Alkaline or Carbon-Zinc Battery (NEDA 1604)
 Low Battery Indication: BAT on Left of LCD Display
 Dimensions: 188mm(L) x 87mm(W) x 33mm thick
 Net Weight: 400g **Get All the Specs From Our Web Site**

**ONLY \$19****2GHz RF Field Strength Analyzer**

- Frequency Range: 100KHz to 2.060MHz
- Narrow Band FM (NFM), Wide Band FM (WFM), AM and Single Side Band (SSB) Modulated Signals May Be Measured
- PLL Tuning System for Precise Frequency Measurement and Tuning
- LED Backlight LCD (192x192 dots)
- Built-In Frequency Counter
- Hand-Held and Battery Operated
- All Functions are Menu Selected
- RS232C for PC Interface and Printer

ONLY \$1529

#3201

See the web site for details

Removable Hard Drive Rack

For IDE/Ultra DMA Hard Drives

We Sold Over 14,000 in 1998!

This product can be used with any 3-1/2 IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI). **Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.**

**RH-10C-IDE****ONLY \$14.95 any qty.****new! Removable Hard Drive Rack with Auto Door And Cooling Fan**

- Auto door on the outer frame
- ABS material of outer frame, High efficiency cooling fan
- Worldwide patent pulling function handle
- CE Approved
- Coating iron bottom cover
- For IDE interface
- For 1" high 3.5" HDD
- Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.



#MR-27

Details at www.web-tronics.com

ONLY \$18.95 any qty.**Auto-Temp Solder Station with Ceramic Element**

- With Ceramic Heating Element for More Accurate Temp Adjustment
- 3 Conductor Grounded Power Cord
- 250°C-480°C (470°F-900°F)
- Fast Heating Feature

SR-976

Extra Tip Options Available. See Web!

For More Info See www.web-tronics.com

ONLY \$39

CTRL - D to bookmark this site

www.web-tronics.com

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

In Business Since 1971

Circuit Specialists Inc.**CCD B&W Board Cameras**

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web



VM1030PA-B
30mmx30mmx25mm,
Pinhole lens with
audio, 12V
\$49.00
any qty.



VMCB21
44mmx38.5mmx28mm
with 6 infra-red
LEDs, 12V
\$49.00
any qty.



VM1035A
42mmx42mmx25mm
Standard lens with
audio, 12V with back
light compensation
\$59.00
any qty.



VM1030A
30mmx30mmx26mm
Standard lens with
audio, 12V
\$49.00
any qty.



VM1036A
32mmx32mmx25mm
Standard lens with audio,
12V, reverse mirror
image feature
\$59.00
any qty.

COLOR CCD Mini Board Cameras

- Low Power Consumption
- 1 Lux Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation
- Internal Synchronization
- 12Volts
- 400 TV Lines



VM3011-A
45mmx40mmx24mm
Standard lens
with audio,
single board
\$99.00
any qty.



VM3010PA
33mmx33mmx18mm
Pinhole lens
with audio
\$129.00
any qty.



VM3010-A
33mmx33mmx32mm
Standard lens
with audio
\$129.00
any qty.

Detailed Specs on the Web

Bullet CCD Cameras**B&W and Color**

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-In Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)



VMBLT3025W
Digital Color, Weatherproof
20mm(D)x83mm(L)
\$189.00
any qty.



VMBLT1020W
B&W Weatherproof
21mm(D)x58.5mm(L)
\$79.00
any qty.



VMBLT1020A
B&W with audio
21mm(D)x55mm(L)
\$69.00
any qty.

Detailed Specs on the Web

new! Mini CCDs (B/W & Color)**Sensational NEW Design for Small Observation Cameras. Smaller and Better!**

- Ultra Miniature Design
- Black & White Versions Only 25mm x 25mm
- Color Versions Only 32mm x 32mm
- Available in Standard Lens or Pinhole Lens
- All Include Audio
- All Include Pre-Wired Cable Harness for Audio, Video & Power
- 12V Regulated Power Supply Required (120mA typical power consumption)
- 0.1 LUX Rating (B/W), 1 LUX (color)
- CCD Area Image Sensor for Long Camera Life
- Back Light Compensation Circuit
- Built-In Electronic Auto Iris Lens



VMPS-718A
25mmx25mmx30mm,
B/W CCD with standard
lens, pre-wired cabling
for video/audio, 12V DC
Power Input
\$69.00
5 or more



VMCW-H11A
32mmx32mmx30mm,
Color CCD with
standard lens, pre-
wired cabling for video/
audio, 12V DC Power
\$149.00 \$139.00
5 or more



VMCW-H12A
32mmx32mmx19mm,
Color CCD with
pinhole lens, pre-wired
cabling for video/audio,
12V DC Power Input
\$149.00 \$139.00
5 or more

Detailed Specs on the Web



VMPS-250A
25mmx25mmx15mm,
B/W CCD with pinhole
lens, pre-wired cabling
for video/audio, 12V DC
Power Input
\$69.00 \$59.00
5 or more

Our Most Sophisticated DMM We Sold Over 700 Last Year!

- True RMS Mode
- 10MHz Frequency Counter
- Time Mode with Alarm, Clock, and Stop Watch
- Dual Display
- 10 Location Memory
- Min, Max, Avg and Relative Mode
- Decibel Measurement
- Cap and Ind. Measurement
- Temperature Mode (C/F)
- K Type Temperature Probe Included
- Pulse Signal for Logic & Audible Test
- Continuity/Diode Test
- Logic Test
- Auto Power OFF/"Keep ON" Mode
- Fused 20A Input with Warning Buzzer
- Back Light
- Data Hold/Run Mode
- Safety Design UL1244 & VDE-0411
- Protective Holster
- Silicon Test Leads

**NOW ONLY \$129**

Reg. \$169

More Details on our Web Site

PROTEK 506**Protek****Series 6500 Deluxe 20MHz/40MHz/60MHz/100MHz Dual-Trace Oscilloscopes**

- Alternate Trigger
- Internal Sync Separator Circuit
- Alt-Mag Sweep
- Delay Sweep (6510)

LATEST DESIGNS!

#6502 - 20MHz
\$289

#6504 - 40MHz
\$569

#6506 - 60MHz
\$689

#6510 - 100MHz
\$799

Part No.	6510	6506	6504	6502
Bandwidth	100MHz	60MHz	40MHz	20MHz
Vert. Sensitivity	1mV/Div to 5V/Div	1mV/Div to 5V/Div	1mV/Div to 5V/Div	1mV/Div to 5V/Div
Max Sweep Rate	2nS/Div to 0.2S/Div	0.1µS/Div to 0.2S/Div	0.1µS/Div to 0.2S/Div	0.2µS/Div to 0.5S/Div
Delay Sweep	YES	YES	YES	YES
Vert. Mode Trig.	YES	YES	YES	YES
Cursor Readout	NO	NO	NO	NO
CRT Volts	12KV	10KV	10KV	2KV

new! 3000 Series Digital R/O Bench Power Supplies

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. The dual output versions can be used in both serial voltage and parallel current configurations to double maximum outputs. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.


Line Regulation: $2 \times 10^{-4} + 1 \text{ma}$
 LED Accuracy: Voltage $\pm 1\% + 2$ digits
 Current $\pm 1.5\% + 2$ digits
 Wave Line Noise: $\leq 1 \text{mVrms}$
 Dimensions: 291mm x 158mm x 136mm (CSI3003 & CSI3010)
 365mm x 265mm x 164mm (CSI3003-3 & 3005-53)



CSI3003: 0-30V/0-3amp Digital R/O Bench PS, $1 \times 10^{-4} + 5 \text{mV}$ Load Regulation	\$99.00 5/\$89.00
CSI3010: 0-30V/0-10amp Digital R/O Bench PS, $1 \times 10^{-4} + 30 \text{mV}$ Load Regulation	\$149.00 5/\$139.00
CSI3003-3: Triple Output $2 \times (0-30 \text{V}/0-3 \text{amp}) + 5 \text{V}$, 3amp Fixed, $1 \times 10^{-4} + 5 \text{mV}$ Load Regulation	\$239.00 5/\$219.00
CSI3005-3: Triple Output, $2 \times (0-30 \text{V}/0-5 \text{amp}) + 5 \text{V}$, 3amp Fixed, $1 \times 10^{-4} + 25 \text{mV}$ Load Regulation	\$269.00 5/\$249.00

3000 Series Supplies Will Become Available Approximately September 15, 1999. Orders Are Being Taken Now.

MONSTER 47GB SCSI DRIVE

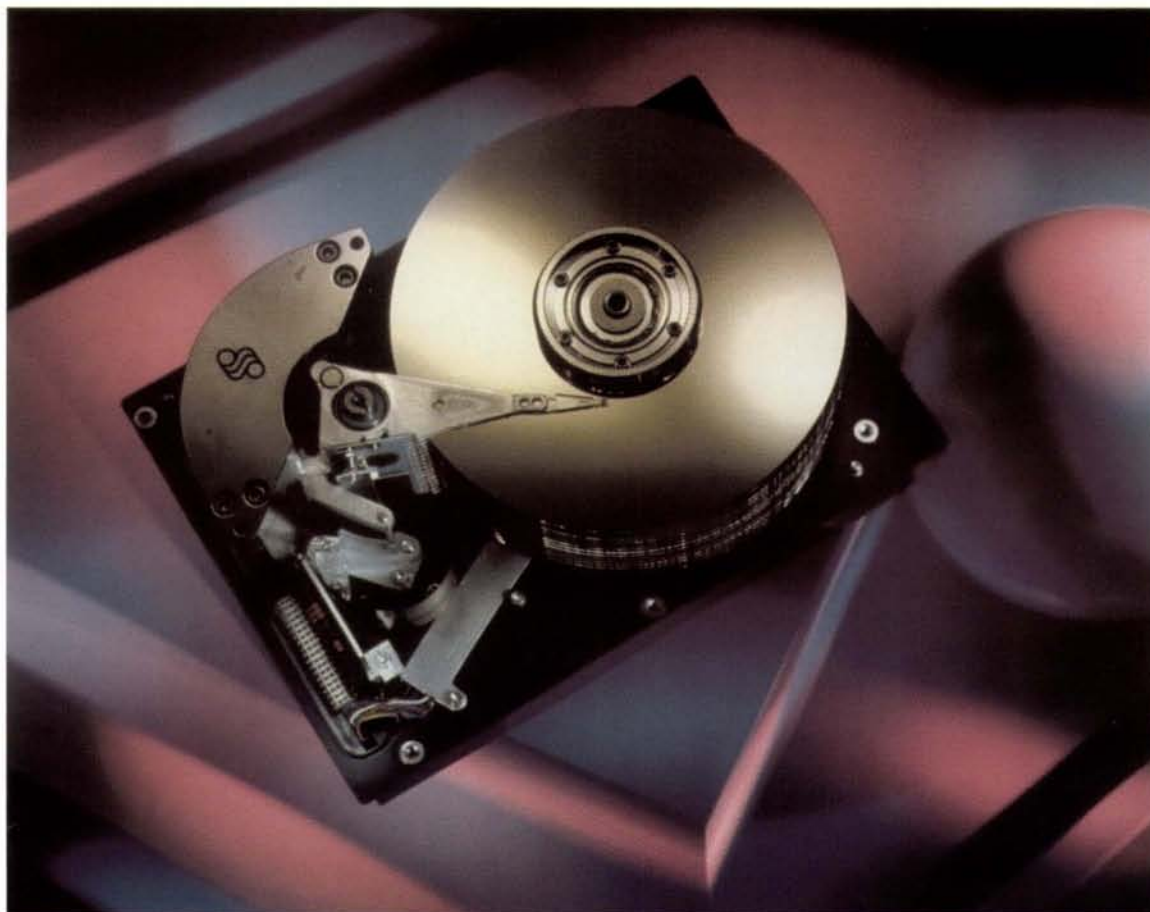

\$895!

**FREE SCSI ENCLOSURE
408 330-5523**

Open Windows instantly. Process huge graphic and database files with ease. Make your file server scream with speed.

The 47GB Seagate Elite is the drive you need for serious performance. It features 14 disks and 28 heads for blazing performance 3.5" drives can't touch. The Ultra Wide interface makes installation a snap. A 4MB cache buffer accelerates data transfers.

A special volume purchase brings you brand new drives at low, low PC prices. Shop around. Compare price. No one else can match this deal.

Buy just one drive and build the ultimate workstation. Or add several to take advantage of NT RAID performance. Let us custom-build your multi-drive disk array at no extra charge. Redundant rack-mount trays stack to build arrays bigger than 1,000GB per rack!

Get the speed you need and the reliability you deserve. Get rock solid Seagate quality backed by a warranty of up to six years! Call now! Try your 47GB monster drive risk-free.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.SCSIDRIVES.COM

Seagate ST446452W drives are PC, Mac, SGI, and Sun compatible. 5 1/4" Elite drives are sold only in OEM enclosures and disk array trays. CSC carries low-cost, top-quality PCI controllers and SCSI accessories. If you haven't already upgraded to SCSI, call us for help. No-risk guarantee refunds your entire purchase price (less shipping) if you're not completely satisfied within 15 days. Call for your free catalog of hard drives, duplication equipment, and accessories.

SXTech ToolKit

#45180

Introductory Offer
Expires 9/30/99


\$149

+ shipping

(CA residents add 7.25% sales tax)



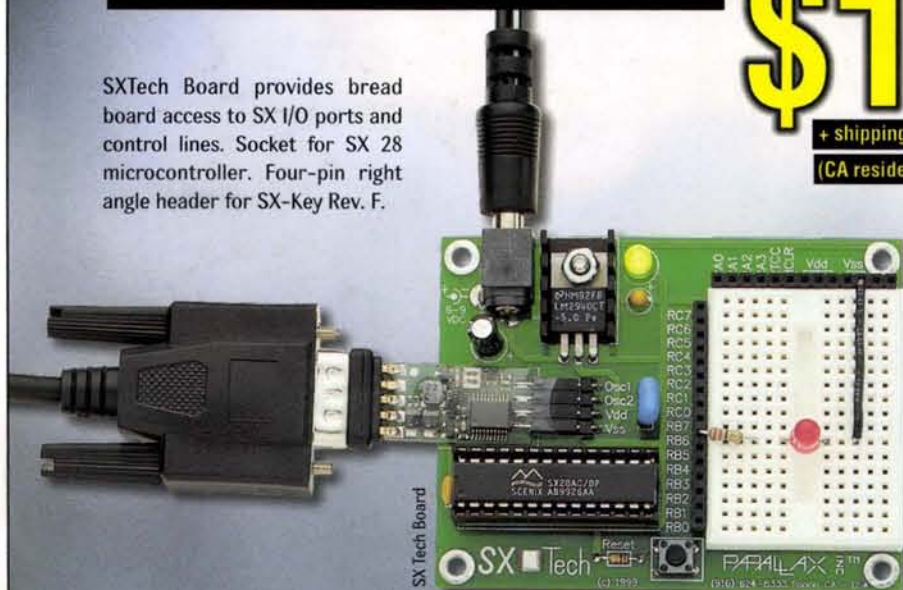SXTech Board provides bread board access to SX I/O ports and control lines. Socket for SX 28 microcontroller. Four-pin right angle header for SX-Key Rev. F.



From the first SX tool manufacturer!
Download free SX-Key software and manual from <http://www.sxtech.com>



\$149 SX Tech Tool Kit - #45180

Complete assembler, programmer and debugger for SX development includes the new SX-Key Rev. F. The SX-Key programs SX chips in-system and performs in-circuit source-level debugging. User programmable clock operates at any frequency between 400 kHz and 100 MHz. Complete Win95/98/NT4 compatibility. New \$149 SX-Tech tool kit includes:

- SX-Key Rev. F. Programmer
- SX-Tech Board
- Two (2) SX 28AC/DP "A" 50 MIPS microcontrollers
- One (1) Murata 50 MHz resonator
- Printed Manual
- CD-ROM, power supply and serial cable (#45181- NO power supply)

New 50 MIPS SX Microcontrollers have arrived at Parallax!

We've received our first shipment of the new 'A' series Scenix Semiconductor microcontrollers. These chips program quickly (10 ms per location) and offer a wider voltage operating range (2.5V to 5.5V). Available separately or in the new SX Tech Tool Kit.


To celebrate the arrival of the new "A" SX28AC/DP we're offering them at \$4.25 each (qty. 1-25). Just order stock code #SX28AC/DP. Need a couple more 50 MHz resonators? Order #250-05060 at \$1.50 each! Getting started with the SX has never been so inexpensive and easy!

Check <http://www.sxtech.com> for the \$99 SX Tech University Tool Kit!

CONTACT PARALLAX BY:

E-mail: sxtech@parallaxinc.com Web: <http://www.sxtech.com>
Toll free in U.S.: (888) 512-1024

PARALLAX

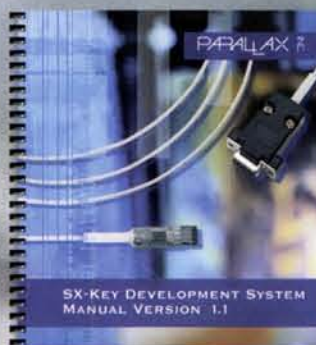

SX-Key manual

SXTech.com

The Parallax logo is a registered trademark of Parallax, Inc. SX-Key is a trademark of Parallax, Inc. SX is a trademark of Scenix Semiconductor.

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
430 PRINCELAND COURT
CORONA, CA 91719

ADDRESS SERVICE REQUESTED